



The  
University  
Of  
Sheffield.

**Data Provided: Smith Chart (4 copies)**

**DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING**

**Autumn Semester 2006-2007 (2 hours)**

**High Speed Electronic Circuit Design 6**

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1.
  - a. List, with the aid of diagrams, three types of transmission lines used to carry RF or microwave signals. List typical applications of each type. (4)
  - b. Explain briefly the difference between a lumped and distributed representation of a circuit element. (4)
  - c. A load impedance of  $Z_L = 80 + j20\Omega$  is to be matched to a  $100\Omega$  source using a lossless transmission line of characteristic impedance  $Z_0$  and length  $\ell$ . Find the required  $Z_0$  (real) and  $\ell$ . (6)
  - d. A load impedance of  $Z_L = 75 - j50\Omega$  is connected to a lossless transmission line with a 30cm length and  $Z_0 = 50\Omega$  at a frequency of 500MHz. Find the input impedance, the impedance and the reflection coefficient at 10cm away from the load. (6)
2.
  - a. Explain briefly how to calculate reflections on a lossy transmission line using the Smith chart. (4)
  - b. An unknown load impedance is connected to a  $0.1\lambda$  long  $50\Omega$  lossless transmission line. The VSWR and phase of the reflection coefficient measured at the input of the line are 4 and  $-20^\circ$  respectively. Determine the input and load impedances by using the Smith Chart. (6)
  - c. For a transmission line with  $Z_0 = 50\Omega$  and terminated by  $Z_L = 180 + j40\Omega$ , design a double stub matching network to match  $Z_L$  to  $Z_0$ . The 1<sup>st</sup> stub is located at the load, and the two stubs are separated by a distance of  $0.125\lambda$ . The length of each stub should be  $\leq 0.25\lambda$ . (10)
3.
  - a. Explain briefly what Signal Flow Diagrams analysis are used to represent, and what are the two basic components of any SFD. (4)

- b. Find the S parameters for the series and shunt loads shown in Figure 1. Show that  $S_{12}+S_{11}=1$  for the series case and  $S_{12}-S_{11}=1$  for the shunt case. Assume a characteristic impedance of  $Z_0$  in both cases

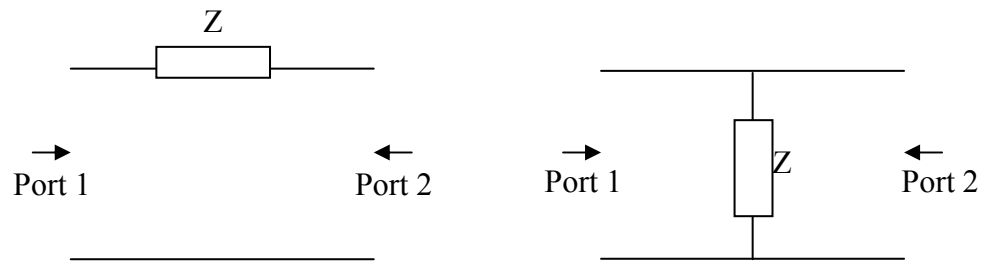


Figure 1

(8)

- c. Find the transmission, ABCD, parameters for the network shown in Figure 2

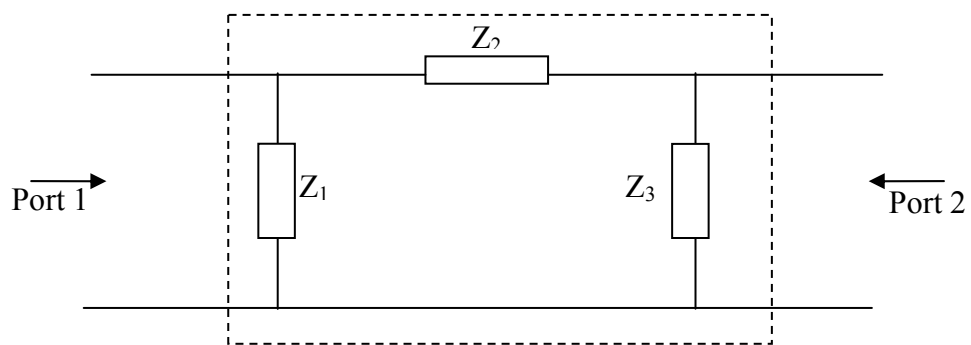


Figure 2

(8)

4. a. Explain why sometimes it is preferable to design an amplifier for less than the maximum obtainable gain? How this can be achieved?

(4)

- b. An amplifier is characterised by the following S-parameters:  $S_{11}=0.78\angle -65^\circ$ ,  $S_{21}=2.2\angle 78^\circ$ ,  $S_{12}=0.11\angle -21^\circ$ ,  $S_{22}=0.9\angle -29^\circ$ . The input side of the amplifier is connected to a source impedance of  $Z_s=80\Omega$ . The output side is connected to a load of  $Z_L=90\Omega$ . Assuming that the S parameters are measured with reference to a characteristic impedance of  $Z_0=50\Omega$ . Determine the stability and the power gains of this amplifier.

(8)

- c. An amplifier has the following scattering and noise parameters

F GHz	$S_{11}$	$S_{21}$	$S_{12}$	$S_{22}$
6.0	$0.6\angle -60^\circ$	$2.0\angle 81^\circ$	0	$0.7\angle -60^\circ$

$$Z_0=50\Omega \quad R_N=20\Omega \quad NF_{\min}=2\text{dB} \quad \Gamma_{\text{opt}} = 0.62\angle 100^\circ$$

Design an amplifier having a 2.5dB noise figure with the maximum gain that is compatible with this noise figure.

(8)

**You may find the following information useful:**

The constant gain and noise figure circles can be plotted using the following set of equations

$$C_s = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2}$$

$$r_s = \frac{\sqrt{1 - g_s} (1 - |S_{11}|^2)}{1 - (1 - g_s) |S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$

$$r_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$

$$C_{NF} = \frac{\Gamma_{opt}}{(N + 1)}$$

$$r_{NF} = \frac{\sqrt{N(N + 1 - |\Gamma_{opt}|^2)}}{(N + 1)}$$

**SKK / AT**