



The  
University  
Of  
Sheffield.

## DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Spring Semester 2015-16 (2.0 hours)

### EEE6208 Advanced Integrated Electronics

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

**You may require the following:**

*The Shichman-Hodges model:*

In the *triode* region:

$$I_D = K_n \frac{W}{L} \left( V_{OV} - \frac{V_{DS}}{2} \right) V_{DS}$$

In the *saturation* region:

$$I_{D0} = K_n \frac{W}{L} \frac{V_{OV}^2}{2}$$

In the *ohmic* region:

$$I_D \approx K V_{OV} V_{DS}$$

Regardless of the region:

$$I_S = I_D$$

$$I_G = 0$$

*Channel length modulation:*

$$I_D = I_{D0}(1 + \lambda V_{DS})$$

*The overdrive voltage:*

For an NMOS device:  $V_{GS} = V_{TO} + V_{OV}$

For a PMOS device:  $V_{GS} = -(|V_{TO}| + |V_{OV}|)$


*MOSFET output resistance:*

$$r_o = \frac{1}{\lambda I_{D0}}$$

*MOSFET transconductance:*

$$g_m = K_{n,p} \frac{W}{L} V_{OV}$$

1. a. An NMOS transistor has the following parameters:  $K_n=150\mu\text{A}/\text{V}^2$ ,  $\lambda=0.05\text{V}^{-1}$ ,  $W/L=10\mu\text{m}/0.5\mu\text{m}$ ,
- What drain current results when this transistor runs with an overdrive voltage of  $0.5\text{V}$  and a drain-source voltage,  $V_{DS}$ , of  $2\text{V}$ ? (2)
  - What is the transistor's drain-source resistance,  $r_o$ , under these conditions? (1)
  - If  $V_{DS}$  increases to  $2.5\text{V}$ , what is the corresponding change in drain current? (2)
- b. The transistor described in **part a** is to be used, together with a PMOS active load transistor (M2), in the common-source amplifier configuration shown in **Figure 1.1**. Transistor M2 has an output resistance,  $r_o=200\text{k}\Omega$ , transconductance parameter,  $K_p=200\mu\text{A}/\text{V}^2$ , turn-on voltage  $V_{TO}= -0.25\text{V}$  and channel aspect ratio  $W/L=20\mu\text{m}/2\mu\text{m}$ . The amplifier is to be operated with a bias current of  $150\mu\text{A}$ .

 

**Figure 1.1:** An actively-loaded common source amplifier.

- Calculate a suitable value for  $V_{bias}$  - the voltage at the gate of transistor M2. (3)
- Draw the small signal model of the circuit in **Figure 1.1** and calculate values of output resistance,  $r_o$ , and transconductance,  $g_m$ , to include in your diagram. (5)
- Calculate the gain of the amplifier from the small signal model. Show your working. (3)
- To realise the biasing of transistor M1, a current mirror or a resistor could be attached at the point labelled 'S(M1)' in **Figure 1.1**. Briefly describe the advantages of biasing at point S(M1) rather than using a potential divider at the gate of M1. Also briefly describe the advantages of using a current mirror rather than a resistor. (4)

2. a.

 


Figure 2.1: A basic current mirror

**Figure 2.1** shows a simple n-channel current mirror, implemented using two identical NMOS transistors, M1 and M2. Both transistors have transconductance parameter  $K_n = 200 \mu\text{A}/\text{V}^2$  and turn-on voltages of  $V_{TO} = 0.6\text{V}$ . They have channel dimensions  $W/L = 8\mu\text{m}/1\mu\text{m}$ .

- i) Ignoring channel length modulation effects, calculate the value of R required to set the drain current through M1 at  $100\mu\text{A}$ . (4)
- ii) What is the minimum value of the voltage across M2,  $V_{out}$ , in order that the mirror operates correctly? What region of operation will M2 fall into if  $V_{out}$  falls below this value? (2)
- iii) Given that the transistors have a channel length modulation parameter  $\lambda = 0.04\text{V}^{-1}$ , find the change in the current through M2 if  $V_{out}$  reduces by  $1\text{V}$ . (3)

b.

 


Figure 2.2: The output side of a source-degenerated current mirror.

**Figure 2.2** shows the output side of a source-degenerated current mirror, with source resistance  $R_1$ .


- i) Draw the small-signal model of this circuit. (3)
- ii) Use nodal analysis to show that the output resistance,  $R_{out}$ , of the current mirror in Figure 2 is given by:

$$R_{out} = \frac{1}{g_o} (1 + R_1(g_o + g_m)) \quad (6)$$

Where  $g_m$  is the transconductance of transistor M2,  $g_o=1/r_o$  is the drain-source conductance of transistor M2.

- iii) Give conditions under which  $R_{out}$  can be approximated by:  $R_{out} \approx g_m R_1 r_o$  (2)


3. a. i) Explain what is meant by *strained silicon* technology. How does this improve the performance of CMOS transistors? (4)
- ii) Describe what you understand by the term *FinFET*. What are the advantages of FinFET technology? (4)
- b. Consider the circuit shown in **Figure 3.1**. You may assume that the inverter switches at  $V_{DD}/2$ .

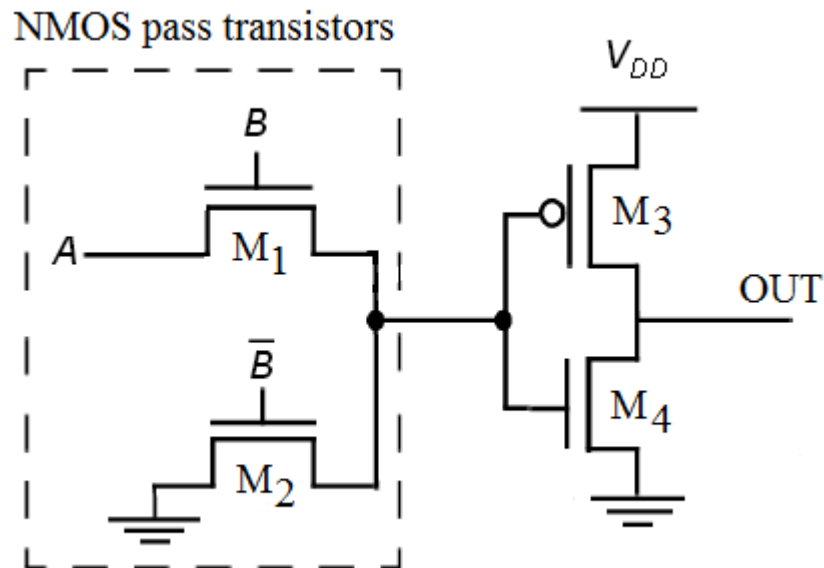

**Figure 3.1** Pass transistor circuit

- i) Determine the logic function performed by this circuit. (3)
- ii) Assuming that gate leakage can be ignored, explain why the circuit has non-zero static power dissipation. (4)
- iii) Using only one additional transistor, show how the circuit can be modified to reduce the static power dissipation. (2)
- iv) Explain how you would determine the size of the additional transistor. (3)

4. a. Two NMOS transistors are to be connected in series using a bulk CMOS process. Describe with the aid of a diagram what is meant by:
- i) Isolated contacted diffusion (2)
  - ii) Shared contacted diffusion (2)
  - iii) Merged diffusion (2)
- b. i) Describe the capacitances associated with a MOSFET device. (3)
- ii) The diagram in **Figure 4.1** shows a unit inverter driving a unit inverter load. Explain with the aid of a diagram why the equivalent RC load of the driving inverter has a resistance of  $R$  and a capacitance of  $6C$ . You may ignore interconnect capacitance. (4)

 

**Figure 4.1** Unit inverters

- c. i) Draw the circuit diagram for a static CMOS 2-input NOR gate. Determine the transistor widths required to achieve effective rise and fall resistances equivalent to that of a unit size inverter. (3)
- ii) The NOR gate is required to drive  $h$  identical NOR gates. Using the Elmore delay model, derive an expression for the RC propagation delay of the driving NOR gate for a rising transition on its output. Assume that isolated contacted diffusions are used for every source and drain. (4)

AM/NJP/IF