

## Wave reflection and voltage standing wave ratio (VSWR)

$$V = V(x, t)$$

$$= V_0^+ e^{j\omega t} e^{-j\tilde{k}x} + V_0^- e^{j\omega t} e^{j\tilde{k}x}$$

(forwards travelling)

(backwards travelling)

where

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{is voltage reflection coefficient}$$

$$\Rightarrow V = V_0^+ e^{j\omega t} (e^{-j\tilde{k}x} + \Gamma e^{+j\tilde{k}x}) \quad \text{and analogous for current}$$

→ need to distinguish several cases:

① line matched case:  $Z_L = Z_0$

$$\rightarrow \Gamma = 0$$

$$\rightarrow V(x, t) = V_0^+ e^{j\omega t} e^{-j\tilde{k}x} \quad (\text{no reflected wave})$$

Of both oscillations (time and space) we can only measure the real component. It is common to use as boundary conditions  $V(x=0, t=0) = 0$ , which reduces to the sine (imaginary) component; i.e.

$$\text{Im } V(x, t) = V_0^+ \sin(\omega t - \tilde{k}x)$$

describes a freely propagating wave.

② open circuit :  $Z_L = \infty$

$$\rightarrow \Gamma = +1$$

$$\begin{aligned} \rightarrow V(x, t) &= V_0^+ e^{j\omega t} \underbrace{(e^{-j\tilde{k}x} + e^{+j\tilde{k}x})}_{\cos \tilde{k}x - j \sin \tilde{k}x} \\ &= 2V_0^+ e^{j\omega t} \underbrace{\cos \tilde{k}x}_{\cos \tilde{k}x} \end{aligned}$$

$$\rightarrow \text{Im } V(x, t) = 2V_0^+ \sin \omega t \cos \tilde{k}x$$

describes a wave with zero amplitude at positions  $\tilde{k}x = \text{odd multiple of } \pi/2$

③ short-circuited transmission line:  $\bar{Z}_L = 0$

$$\Rightarrow \Gamma = -1$$

$$\Rightarrow V(x, t) = V_0^+ e^{j\omega t} \left( \underbrace{e^{-j\tilde{\ell}x}}_{\cos \tilde{\ell}x - j \sin \tilde{\ell}x} - \underbrace{e^{+j\tilde{\ell}x}}_{\cos \tilde{\ell}x + j \sin \tilde{\ell}x} \right)$$

$$= -2V_0^+ \underbrace{e^{j\omega t}}_{\cos \omega t + j \sin \omega t} j \sin \tilde{\ell}x$$

$$\Rightarrow \operatorname{Im} V(x, t) = -2V_0^+ \cos \omega t \sin \tilde{\ell}x$$

describes a wave with zero amplitude if  $\tilde{\ell}x = n \cdot \pi$

④ general case

set  $\Gamma = \gamma e^{j\varphi}$  as complex wave reflection coefficient with amplitude  $\gamma$  and phase angle  $\varphi$

$$\Rightarrow V(x, t) = V_0^+ e^{j\omega t} (e^{-j\tilde{\ell}x} + \gamma e^{j\varphi} e^{j\tilde{\ell}x})$$

$$= V_0^+ e^{j\omega t} e^{j\frac{\varphi}{2}} [e^{-j(\tilde{\ell}x + \frac{\varphi}{2})} + \gamma e^{j(\tilde{\ell}x + \frac{\varphi}{2})}]$$

define new angle by  $\Theta := \tilde{\ell}x + \frac{\varphi}{2}$

$$\Rightarrow V(x, t) = V_0^+ e^{j\omega t} e^{j\frac{\varphi}{2}} \underbrace{(e^{-j\Theta} + \gamma e^{+j\Theta})}_{\cos \Theta - j \sin \Theta + \gamma \cos \Theta + j \gamma \sin \Theta}$$

$$= (1 + \gamma) \cos \Theta - j (1 - \gamma) \sin \Theta$$

$$\Rightarrow |V(x, t)| = V_0^+ [(1 + \gamma)^2 \cos^2 \Theta + (1 - \gamma)^2 \sin^2 \Theta]^{1/2}$$

expand brackets and use  $\cos^2 \Theta + \sin^2 \Theta = 1$  and also  $\cos^2 \Theta - \sin^2 \Theta = \cos(2\Theta)$

$$\Rightarrow |V(x, t)| = V_0^+ [\cos^2 \Theta + 2\gamma \cos^2 \Theta + \gamma^2 \cos^2 \Theta + \sin^2 \Theta - 2\gamma \sin^2 \Theta + \gamma^2 \sin^2 \Theta]^{1/2}$$

$$= V_0^+ [1 + \gamma^2 + 2\gamma \underbrace{\cos(2\Theta)}_{= -1, \dots, +1}]^{1/2}$$

$|V(x)|$  is max., if  $\cos(2\theta) = 1$ .

Then:

$$|V(x)|^{\max} = V_0^+ \left( \underbrace{(1+\gamma^2 + 2\gamma)}_{(1+\gamma)^2} \right)^{1/2} = (1+\gamma) V_0^+$$

$|V(x)|$  is min., if  $\cos(2\theta) = -1$ .

Then:

$$|V(x)|_{\min} = V_0^+ \left( \underbrace{(1+\gamma^2 - 2\gamma)}_{(1-\gamma)^2} \right)^{1/2} = (1-\gamma) V_0^+$$

Define voltage standing wave ratio as

$$\boxed{VSRW = \frac{|V(x)|^{\max}}{|V(x)|_{\min}} = \frac{1+\gamma}{1-\gamma} = \frac{1+|\Gamma|}{1-|\Gamma|}}$$

→ again, distinguish special cases:

① line matched case:  $z_L = z_0$

$$\rightarrow \Gamma = 0 \rightarrow VSRW = 1, \text{ as } |V(x,t)| = V_0^+ = \text{const.}$$

② open circuit:  $z_L = \infty$

$$\rightarrow \Gamma = 1 \rightarrow VSRW = +\infty, \text{ as } |V(x,t)|_{\min} = 0$$

③ short-circuited case:  $z_L = 0$

$$\rightarrow \Gamma = -1 \rightarrow VSRW = +\infty \text{ as above for ②.}$$

Summary:

When transmission line and load are mismatched, part of the voltage (and current) waves are reflected so that

$$V(x,t) = V_0^+ e^{j\omega t} (e^{-j\tilde{k}x} + \Gamma e^{j\tilde{k}x})$$

with

$$\Gamma = \frac{z_L - z_0}{z_L + z_0} = \gamma e^{j\varphi}$$


This yields a standing wave as solution to the time-independent wave equation where the actual voltage (or current) varies sinusoidally within the

standing wave envelope

$$|V(x)| = V_0^+ [ \gamma^2 + 1 + 2\gamma \cos(2\tilde{k}x + \psi) ]^{1/2}$$

Note that the oscillation period is  $2\theta = 2\tilde{k}x + \psi$ , i.e. peaks are separated by  $\lambda/2$ .

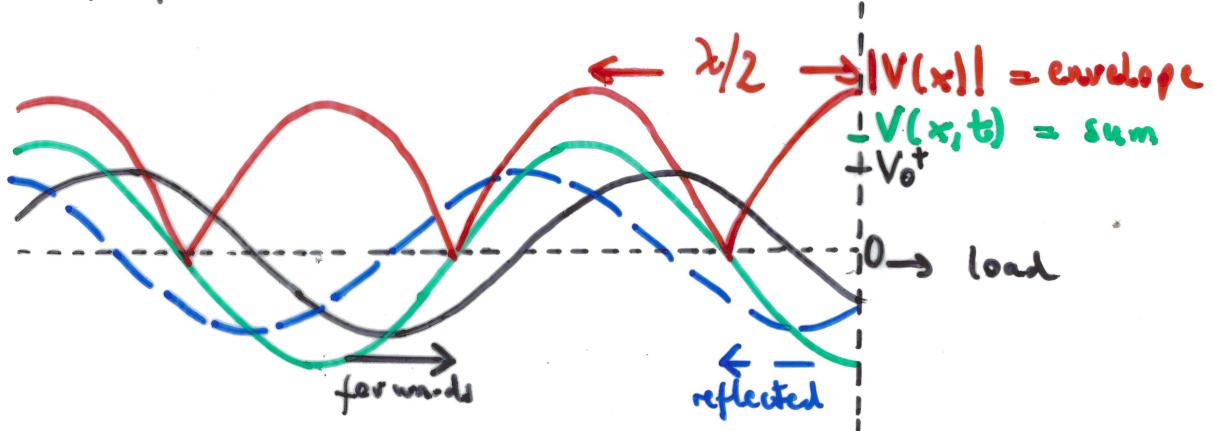example for open circuit ( $\Gamma = 1$ ):



example for short circuit ( $\Gamma = -1$ ):

