

# Sequential Logic Design


- System States
- State Diagrams & Transition Tables
- Sequential Circuit Analysis
- Sequential Circuit Design

# System States

The state diagram shows a traffic light sequence with four states.

The states are represented by circles and the transitions between the states by directed arrows.

 For a synchronous system, movement between states will happen when an active edge from a free running clock is applied.



# Sequential Circuit States

- At any point in time, a sequential circuit can be said to be in a certain **state**.
- The state is defined by the outputs of the flip-flops in the sequential circuit.
- In a synchronous sequential circuit, movement between states only occurs in response to a clock edge.
- A state diagram can be used to graphically show the progression from one state to the next.
- The state is represented by a circle and the transitions between states are represented by directed lines joining one state to the next.

# State Diagrams


The state of a single flip-flop is one of the two stable conditions that the output can take ( **0** or **1** ).

A state diagram can be used to graphically show the progression from one state to the next. The state is represented by a circle and the transitions between states are represented by directed lines joining one state to the next.


Consider the D-Type flip-flop:

D	$Q_{(next)}$
0	0
1	1

$$Q_{(next)} = D$$

 


# T-Type Flip-Flop

 


T	$Q_{(next)}$	
0	$Q$	← unchanged
1	$\overline{Q}$	← Toggle
 
$$Q_{(next)} = T \cdot \overline{Q} + \overline{T} \cdot Q$$




# JK Flip-Flop

 

J	K	$Q_{(next)}$	
0	0	Q	← unchanged
0	1	0	← reset
1	0	1	← set
1	1	$\bar{Q}$	← Toggle


$$Q_{(next)} = J\bar{Q} + \bar{K}Q$$

 
 
# Analysis of Clocked Sequential Circuits

The output of a clocked sequential circuit depends upon its inputs and the state of the flip-flops. Its behaviour can be described by a state equation (sometimes called transition equation). Consider the circuit below.

The next state of F, one clock edge later, is denoted by  $F(t + 1)$ .



$$F(t + 1) = F(t).X(t) + Y(t).\overline{X}(t)$$


The right hand side is the Boolean expression that will make the next state equal to '1'. It is usual to omit the designation (t) giving:

$$F(t + 1) = F.X + Y.\overline{X}$$
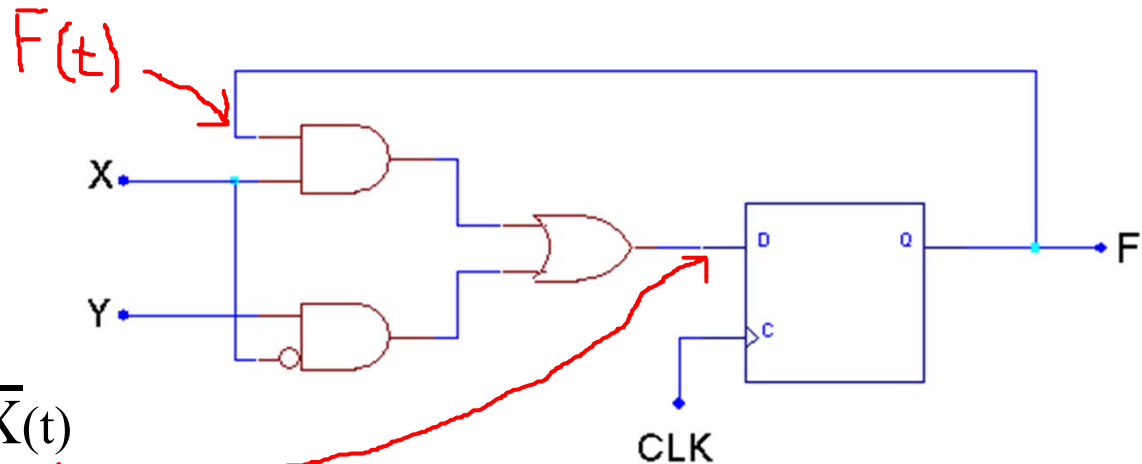
# Analysis of Clocked Sequential Circuits

The output of a clocked sequential circuit depends upon its inputs and the state of the flip-flops. Its behaviour can be described by a state equation (sometimes called transition equation). Consider the circuit below.

The next state of  $F$ , one clock edge later, is denoted by  $F(t + 1)$ .



$$F(t + 1) = F(t).X(t) + Y(t).\overline{X}(t)$$


The right hand side is the Boolean expression that will make the next state equal to '1'. It is usual to omit the designation (t) giving:

$$F(t + 1) = F.X + Y.\overline{X}$$



Write down state equations for A,B,C.

Remember  $Q_{(next)} = D$

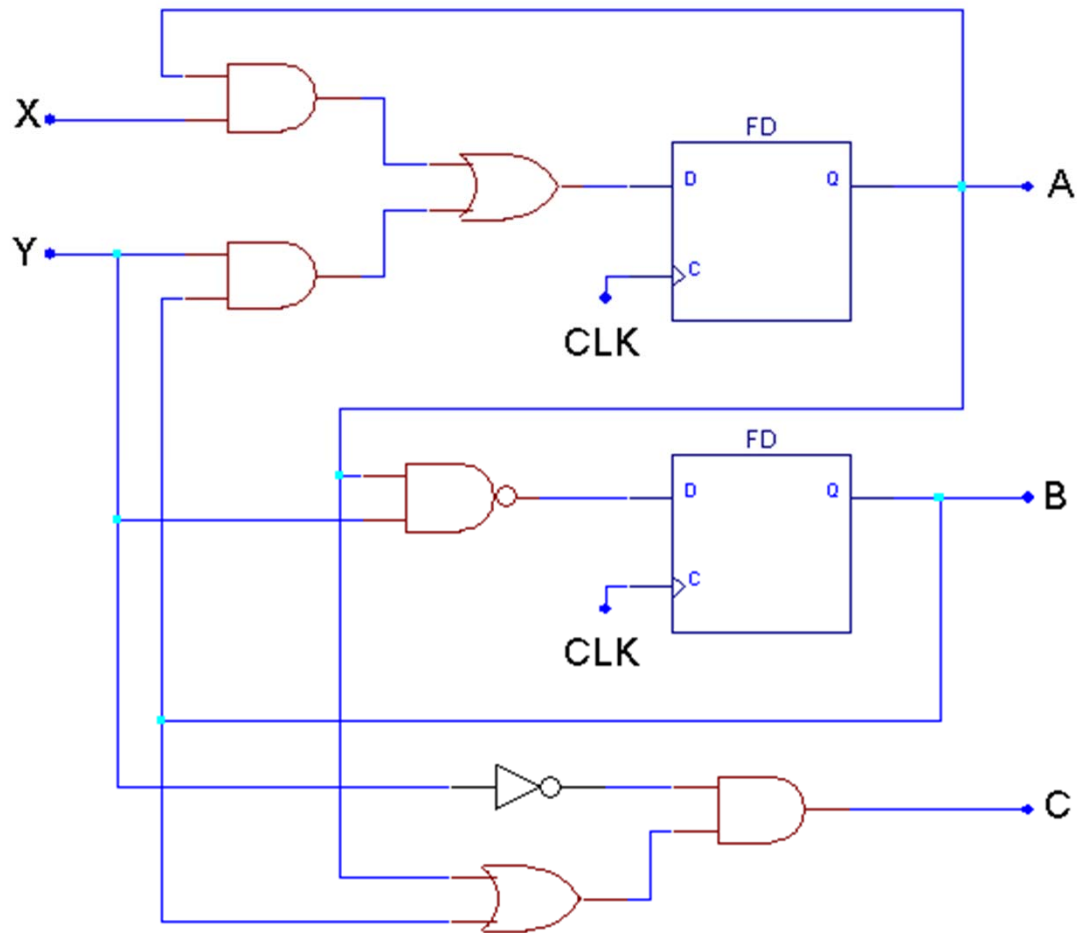


$$A_{(t+1)} =$$

$$B_{(t+1)} =$$

$$C =$$

Write down state equations for A,B,C.

Remember  $Q_{\text{(next)}} = D$

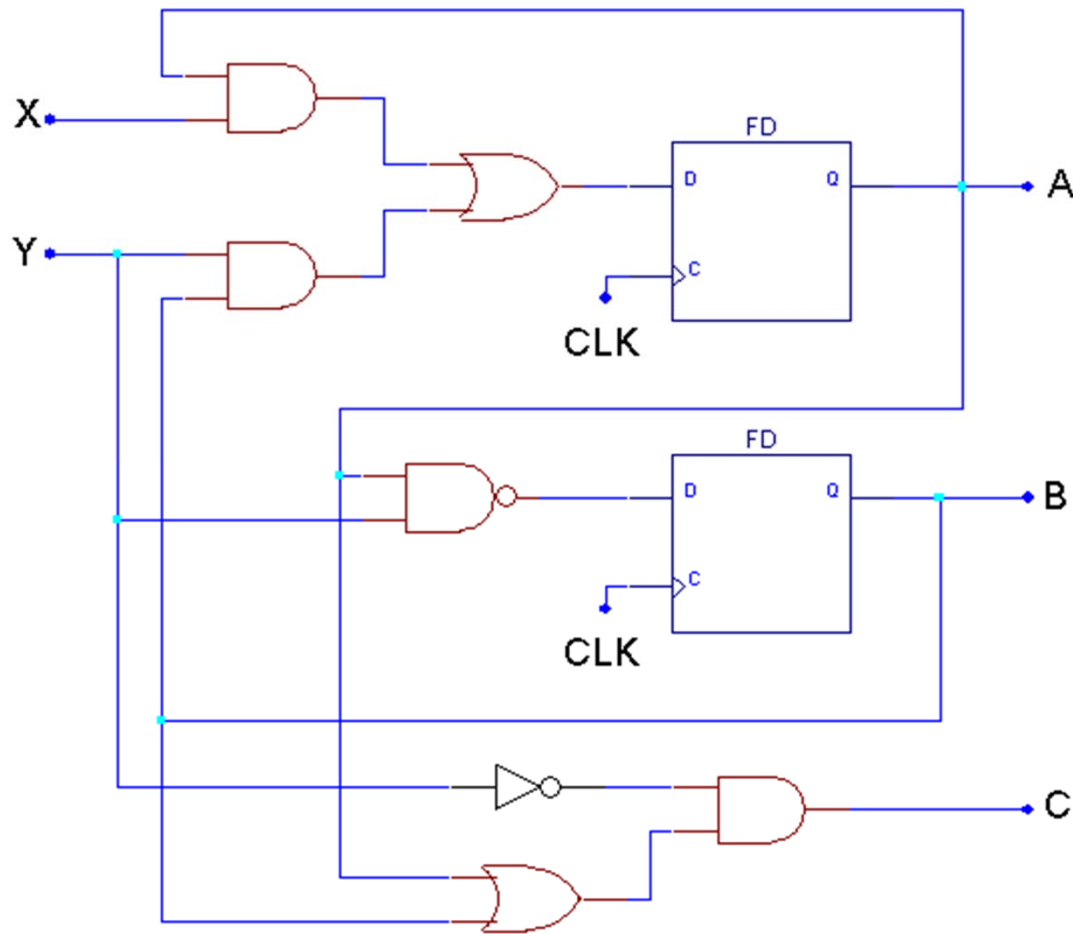

$$A_{(t+1)} = A.X + Y.B$$

$$B_{(t+1)} = \overline{A.Y}$$

$$C = \overline{Y}.(A + B)$$

# State Tables

The time sequence of inputs, outputs and flip-flop states can be represented by a state table (sometimes called state transition table).

$$F(t + 1) = FX + \overline{X}Y$$

A sequential circuit with  $m$  flip-flops and  $n$  inputs needs  $2^{m+n}$  rows in the state transition table.

A state table is a truth table that takes into account the time dependant nature of a synchronous sequential circuit.

Present State	Input		Next State
F	X	Y	$F_{(t+1)}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Sequential Circuit Design

A synchronous sequential circuit is required with two inputs **D**, **E** and one output **Q**. The output will be unchanged when the enable signal **E** is '0' and will take the value of the **D** input when **E** = '1'.

First, produce the state table:

present state Q	Inputs E D		next state $Q_{(t+1)}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

# Sequential Circuit Design

A synchronous sequential circuit is required with two inputs **D**, **E** and one output **Q**. The output will be unchanged when the enable signal **E** is '0' and will take the value of the **D** input when **E** = '1'.

First, produce the state table:

present state Q	Inputs E D		next state $Q_{(t+1)}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

# Sequential Circuit Design

A synchronous sequential circuit is required with two inputs **D**, **E** and one output **Q**. The output will be unchanged when the enable signal E is '0' and will take the value of the D input when E = '1'.

First, produce the state table:

present state Q	Inputs E D		next state $Q_{(t+1)}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

# Sequential Circuit Design

A synchronous sequential circuit is required with two inputs **D**, **E** and one output **Q**. The output will be unchanged when the enable signal E is '0' and will take the value of the D input when E = '1'.

First, produce the state table:

present state Q	Inputs E D		next state Q <sub>(t+1)</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Then solve for Q(t+1):


$$Q(t + 1) = \overline{Q}ED + Q\overline{E}\overline{D} + Q\overline{E}D + QED$$

$$Q(t + 1) = Q\overline{E}(\overline{D} + D) + ED(\overline{Q} + Q)$$

$$Q(t + 1) = Q\overline{E} + ED$$

State Equation:  $Q(t + 1) = Q\bar{E} + ED$

 The state equation gives the combinational logic that is required as the input to the D-type flip-flop. This will then give the required next state after the next active clock edge.



In this example, we have produced a D-type flip-flop with enable. The logic circuit is that for a 2-to-1 multiplexer. The enable line **E** selects between keeping the same state when **E** = 0 or clocking in a new value for **D** when **E** = 1.



# Summary

- Sequential circuit outputs depend upon current and previous inputs.
- Changes in synchronous sequential circuits happen on active clock edges.
- There are three types of flip-flop : D-type, T-type and JK
- D-Type flip flops are generally used for sequential design.