

Data Provided: None

EEE310



The University of Sheffield


DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Spring Semester 2002-2003 (2 hours)

Introduction to VLSI

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

 1. The pull-down network for a CMOS logic gate is:



- i) Draw the corresponding pull-up network. (4)
- ii) Determine the logical function of the logic gate. (4)
- iii) Size the transistors for a minimum-sized gate. (4)

The output of this gate must drive a load capacitance of 140fF. Show how this would be done to minimise the overall delay. (8)

($\mu_n = 0.08 \text{ m}^2/\text{Vs}$, $\mu_p = 0.04 \text{ m}^2/\text{Vs}$, $t_{OX} = 10 \text{ nm}$, $W_{min} = 1 \mu\text{m}$, $L_{min} = 0.25 \mu\text{m}$, $e = 3.45 \times 10^{-11} \text{ F/m}$, $V_{DD} = 3.3 \text{ V}$, $V_{TN} = -V_{TP} = 0.6 \text{ V}$)

2. You have to make a decision about how to implement a system with a digital part and an analogue part. Your market studies indicate that you might expect to sell 200,000 of these systems.

You have two options:

- a) separate digital and analogue ICs. You will need to design the digital part yourself but you find that there is a standard analogue part that will meet your specification at a cost of \$4 in large volume quantities.
- b) A mixed-signal ASIC containing an analogue sub-system.

Identify the arguments and issues that might affect the decision.

(8)

You estimate that the basic cost of each packaged digital part in option a), in the quantity that you require, will be \$3 and the overall yield will be 70%. You estimate that the basic cost of the mixed signal device in option b) will be \$5 but the overall yield will be 65%. The design of the digital part will consume about 6 person months and the mixed-signal device about 9 person months. On the basis of this limited information, which option would you choose. Give reasons to support your answer.

(12)

3. Derive expressions for the small-signal impedance of a (switched on) pass transistor for the cases where the input voltage equals 0V and V_{DD} .

(6)

What are the problems associated with using such a pass transistor as a switch and how they are overcome in a transmission gate.

(2)

Draw the transistor-level schematic of a multiplexer, based on transmission gates, to form a 4-input, 1-output multiplexer.

(4)


Using 2-input, 1-output multiplexers and inverters as basic building blocks, construct the following logic gates:

- i) A AND B
- ii) A XOR B
- iii) A OR B
- iv) NOT A (using only a multiplexer)

(8)

 4. Draw a circuit to generate two complementary clock signals that overlap in the high state but are never low at the same time. Show how this circuit can be made to drive a large capacitive load. (6)

With reference to the following master-slave flip flop



Show how this sort of circuit behaves as an edge-triggered flip-flop and why clocks that overlap in the low state might cause a problem. (6)

More generally, describe how the *synchronous design methodology* for designing digital circuits operates, the requirements that it places on the generation of clocks and the organisation of circuits (e.g. what is allowed and what is not allowed). (6)

What is the role of *design for testability* in this methodology. (2)