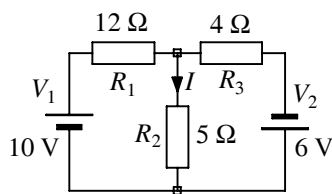


**The University of Sheffield**  
**Department of Electronic and Electrical Engineering**


**EEE117 Problem Sheet**

**dc Circuit Analysis**


- Q1** For the circuit of figure 1 find  $I$  using any method you like. What is the power dissipation in  $R_1$ ? [-0.25 A, 10.5 W]
- Q2** Using any method you like, find the values of  $I$  and  $V$  in figure 2. [-2.89 A, 16.89 V]
- Q3** In figure 3,  $I$  is initially 1 A. Use nodal analysis to find  $V_R$  and hence find  $I_S$ . What value of  $I$  is necessary to give  $V_R = -4$  V? [3.2 V, 0.6 A, -5 A]



**Figure 1**

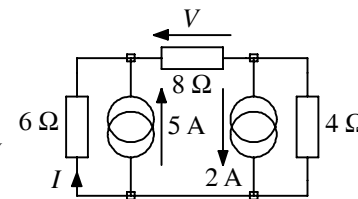


**Figure 2**

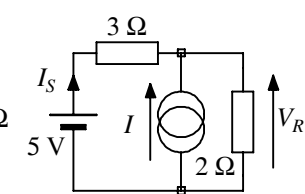


**Figure 3**


- Q4** For the circuit of figure 4, use nodal analysis and superposition to find  $I_1$  and the potential difference  $V_4 - V_3$ ,  $V_{4-3}$ . What is the power dissipation in  $R_4$ ? [-0.15 A, 15.38 V, 23.2 W]
- Q5** Use loop analysis and superposition to find  $I_2$  and  $I_4$  in the circuit of figure 5. State with brief reasoning which component could be replaced by a short circuit without affecting either of these currents. [2.93, -2.18, 12 Ω]
- Q6** Find  $V_2 - V_3$ ,  $V_{23}$ , in the circuit of figure 6 using any method you like. [1 V]

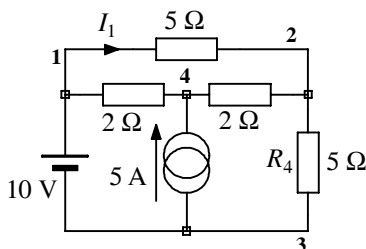

**Figure 4**

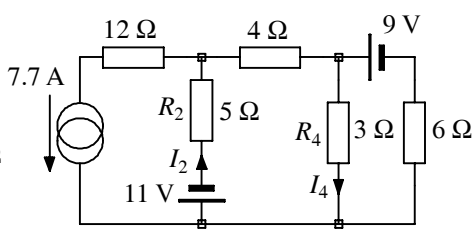

**Figure 5**

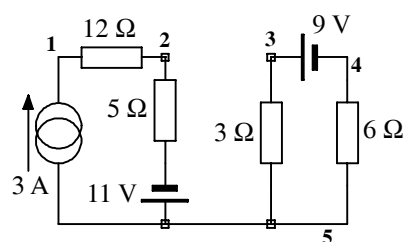

**Figure 6**

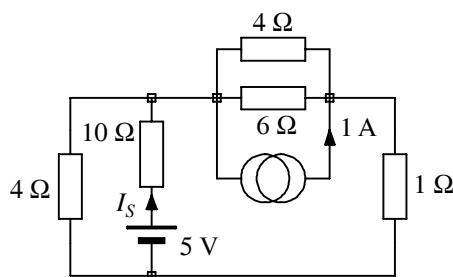


Figure 7

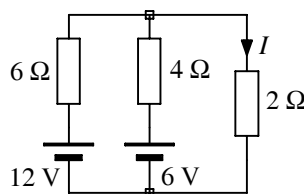


Figure 8

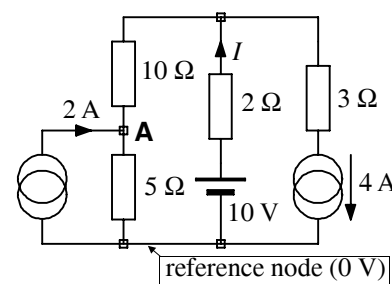


Figure 9

- Q7** Use the principle of superposition to work out  $I_s$  in figure 7.
- Q8** Use the principle of superposition to find  $I$  in figure 8.
- Q9** Use nodal analysis to find the voltage at node **A** with respect to the reference node in figure 9. Check your answer using the principle of superposition. Using your knowledge of  $V_A$ , or by other means, calculate the value of  $I$ .
- Q10**
- Use (i) nodal analysis and (ii) loop analysis to work out the value of current  $I$  in the circuit of figure 10.
  - Which of the five resistors dissipates the largest power?
  - Evaluate the power in part (b).

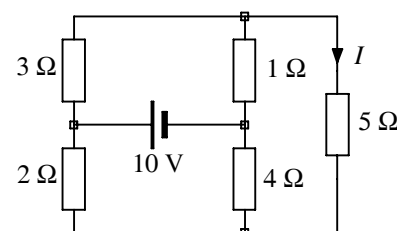


Figure 10

- Q11** This question is quite challenging - attempt it only if you have completed all the rest. Use the principle of superposition to find  $I_s$  and  $V_R$  in the circuit of figure 11. [1 A, 5 V].

(Hint: draw out the partial circuit for each source you consider and look for ways to simplify these circuits by combining resistors. You may have to use loop or nodal methods on the partial circuits. To help you check each of your superposition calculations, the voltage at nodes 2, 3, 4 and 5 for each source, with respect to node 0, is given. Node 1 is straightforward. It is easy to evaluate  $V_R$  and  $I_s$  for each source from these.

$V_1$ : 7.2222, 3.8889, 7.2222, 5.0000.  
 $V_2$ : 4.1667, -0.8333, -5.8333, -2.5000  
 $I_1$ : 1.1111, -5.5556, 1.1111, -10.0000)

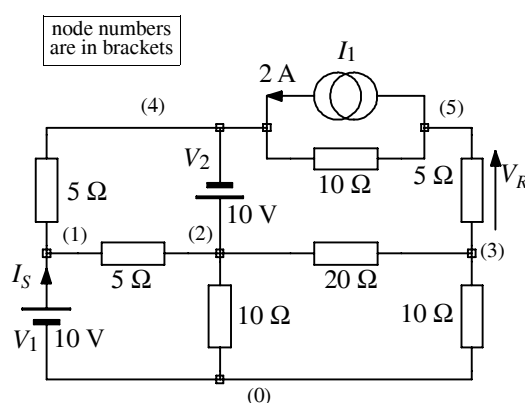


Figure 11