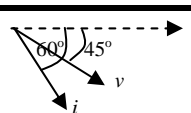
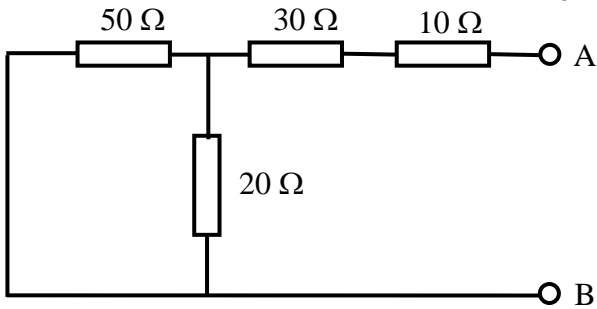
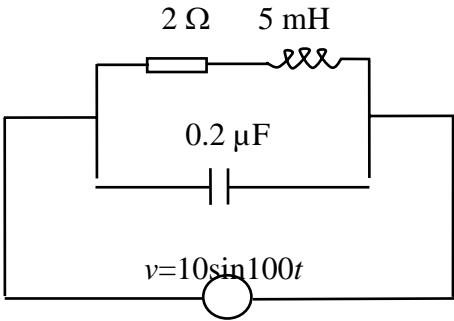


## EEE101 – Circuits and Signals - Interim Test 2008

**Answer All Questions by writing the answer clearly in the appropriate box provided – you do not need to show working on this sheet**

1	Which <b>one</b> of the following statements is correct? <b>A</b> – Energy is <b>dissipated</b> in an ideal inductor through the magnetic field <b>B</b> – Energy is <b>stored</b> in an ideal capacitor through the magnetic field <b>C</b> – Energy is <b>dissipated</b> in a resistor due to the current flow <b>D</b> – Energy is <b>stored</b> in a resistor due to the applied voltage	C
2	From the definition of voltage, what is the <b>energy gained</b> in Joules by 1 electron when moving between two points with a potential difference of 10 volts? (charge on an electron = $1.6 \times 10^{-19}$ C)	Energy gained = volt drop x charge = $10 \times 1.6 \times 10^{-19}$ = <b><math>1.6 \times 10^{-18}</math> J</b>
3	A 12 V source is applied to a $6 \Omega$ resistor. What is the <b>total charge</b> flow in a 0.5 second period?	$I = 12/6 = 2\text{A}$ , charge = $2 \times 0.5 =$ <b>1C</b>
4	The voltage across a capacitor is observed to increase linearly with time. Under these conditions, the charging current is: <b>A</b> – linearly increasing with time <b>B</b> – linearly decreasing with time <b>C</b> – constant with time <b>D</b> – zero Which <b>one</b> of these is correct?	C
5	Two capacitors of value $5 \mu\text{F}$ and $10 \mu\text{F}$ are connected in parallel to a DC supply. Which <b>one</b> of the following statements is correct? <b>A</b> – the charge on each capacitor is the same <b>B</b> – the $10 \mu\text{F}$ capacitor holds twice the charge of the $5 \mu\text{F}$ capacitor <b>C</b> – the voltage on the $10 \mu\text{F}$ capacitor is twice that on the $5 \mu\text{F}$ capacitor <b>D</b> – the voltage and charge are the same for each capacitor	B
6	Calculate the <b>induced voltage</b> across a 1 H inductor if the current passing through it is linearly reduced at a rate of 10 A in 1 ms.	$V = L di/dt = 1 \times (10/10^{-3})$ = <b><math>10^4</math> V</b>
7	A particular circuit draws a current of $i = 10 \sin(314t - 60^\circ)$ when driven by a voltage of $v = 50 \sin(314t - \pi/4)$ . What is the <b>phase angle</b> between the current and voltage?	 $\alpha = 60 - 45 =$ <b><math>15^\circ</math></b>
8	What is the <b>magnitude of the impedance</b> of the circuit of Q7?	$ Z  = V/I = 50/10 =$ <b><math>5 \Omega</math></b>
9	What is the <b>power dissipated</b> in the circuit of Q7?	$P = V_{rms} \times I_{rms} \cos \alpha$ $= [(50 \times 10)/2] \cos 15^\circ$ = <b>241 W</b>

<p>10 An AC voltage source is applied to <math>L</math>, <math>C</math>, and <math>R</math> components connected in series. The impedances at the source frequency are <math>12\ \Omega</math>, <math>10\ \Omega</math> and <math>5\ \Omega</math> respectively. Decide on which <u>one</u> of the following is a true statement (hint - use a phasor diagram):</p> <p><b>A</b> – The applied voltage leads the current  <b>B</b> – The applied voltage lags the current  <b>D</b> – The current and voltage are in phase</p>	<p><b>A</b></p>
<p>11 Find the <b>equivalent resistance</b> between A and B of the circuit given below.</p> 	$R_{AB} = 10 + 30 + (50 // 20)$ $= 40 + (20 \times 50) / (20 + 50)$ $= 40 + 14.3$ $= \mathbf{54.3\ \Omega}$
<p>12 Calculate the peak current flowing in the capacitor of the circuit illustrated below.</p> 	$X_C = 1 / \omega C$ $= 1 / (100 \times 0.2 \times 10^{-6})$ $= 5 \times 10^4\ \Omega$ $I = V / X_C$ $= 10 / 5 \times 10^4$ $= \mathbf{2 \times 10^{-4}\ A}$

Examiner Use Only:

**/12**