

Tutorial Sheet 6

1. A two-pole, star-connected, three phase induction motor exhibits no saliency and is connected to a 415V(rms line to line voltage) 50Hz three-phase mains supply. The total machine iron loss is 560W, which can reasonably be assumed not to vary significantly with speed or load. The motor has the following per-phase equivalent circuit parameters:

Stator resistance = 0.16Ω

Stator leakage reactance = 0.26Ω

Referred rotor leakage reactance = 0.24Ω

Magnetising reactance = 50Ω

- a) Calculate the motor input current when operating on no-load.
- b) When driving a load, the motor operates at a slip of 0.05 producing a torque of 100 Nm. The magnitude of the input current at this operating point is 45A. Calculate the following:
 - i) Referred rotor resistance
 - ii) The efficiency at this operating point
- c) The load is reduced such that the motor speeds up to 2920 rpm. Using the per phase equivalent circuit for the induction motor, calculate the following:
 - i) Phase current drawn
 - ii) Power factor of the motor at this operating condition
 - iii) The torque produced by the motor at this operating point
 - iv) The efficiency at this operating point