

EEE331 Analogue Electronics

10th lecture:

- Active analogue filters
 - passive *LC* filters: only inductors & capacitors: difficult at low *f*
 - active *RC* filters: *R*, *C* & op-amps: thick or hybrid thin-film technol.
 - switched capacitor filters: fully IC-compliant

EEE331 Analogue Electronics

2nd order filters: review of the standard form

All 2nd order filters are biquadratic transfer functions of the standard form

$$T(s) = \text{numerator} / (1 + s\tau/q + s^2\tau^2)$$

where the **numerator** decides what type of filter we have:

1	= low pass
$s\tau$	= band pass
$s^2\tau^2$	= high pass
$1 + s^2\tau^2$	= band stop or notch

and the **denominator** decides the

time constant: $\tau = (LC)^{1/2}$,

pole frequency: $\omega_0 = 1/\tau = (LC)^{-1/2}$ and

quality factor: $q = 1/(\omega_0 RC) = \tau/(RC)$

EEE331 Analogue Electronics

Insufficiencies of passive LC-filters: geometric problems due to L

Consider capacitor:

impedance: $X_C = 1/(sC)$, where $s = j\omega$

current: $I = dQ/dt = d(CV)/dt = C dV/dt$ is linear to C times rate of voltage change

capacitance: $C = \epsilon_0 \epsilon_r A/d$, scales linearly with area A and inversely with thickness d , hence is well-behaved and can be easily implemented in CMOS technology

Consider inductor:

impedance: $X_L = sL$

voltage: $V_{ind} = -L dI/dt$ is linear to L times the rate of current change


inductance: $L = \mu_0 \mu_r N^2 A/l$ scales quadratic with number of windings N , linearly with area A in cross-section and inversely with length l

1. problem: **geometry needs to be implemented in 3D, which is a problem for CMOS and indeed any planar thin film layout**
2. problem: **at low frequencies L must be huge for reasonable X_L**

EEE331 Analogue Electronics

Insufficiencies of passive RC-filters: problems due to limited q

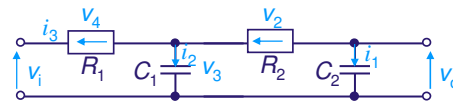Consider combination of pure RC-filters, e.g. 2nd order low pass obtained by putting two 1st order low pass filters in series ('synthesis by factors')



apply leap-frog ladder step-by-step (always easiest to work out from end!):

$$v_o = i_1 / (sC_2)$$

$$v_2 = i_1 R_2 = v_o s C_2 R_2$$

$$v_3 = v_o + v_2 = v_o (1 + s C_2 R_2)$$

$$i_2 = v_3 s C_1 = v_o s C_1 (1 + s C_2 R_2)$$

$$i_3 = i_1 + i_2 = v_o [s C_2 + s C_1 (1 + s C_2 R_2)]$$

$$v_4 = i_3 R_1 = v_o R_1 [s C_2 + s C_1 (1 + s C_2 R_2)]$$

$$v_1 = v_3 + v_4 = v_o \{ (1 + s C_2 R_2) + R_1 [s C_2 + s C_1 (1 + s C_2 R_2)] \}$$


$$= v_o [1 + s(R_2 C_2 + R_1 C_2 + R_1 C_1) + s^2 (R_1 R_2 C_1 C_2)]$$

$$T(s) = v_o / v_i = 1 / \{ 1 + s[(R_1 + R_2)C_2 + R_1 C_1] + s^2 (R_1 R_2 C_1 C_2) \}$$

EEE331 Analogue Electronics

Insufficiencies of passive RC-filters: problems due to limited q

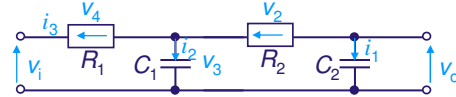Consider combination of pure RC-filters, e.g. 2nd order low pass obtained by putting two 1st order low pass filters in series ('synthesis by factors')



Now consider $R_1 + R_2 = R$ where $R_1 = (1-b)R$, $R_2 = bR$ with some constant $0 \leq b \leq 1$:

$$T(s) = 1 / \{1 + s[RC_2 + (1-b)RC_1] + s^2[b(1-b)RC_1RC_2]\}$$

$$\equiv 1 / \{1 + s(\tau_2 + \tau_1/b) + s^2 \tau_1 \tau_2\}$$

with $\tau_1 = RC_1 b(1-b)$, $\tau_2 = RC_2$ and $\tau = (\tau_1 \tau_2)^{1/2}$

Then this is of the standard form for $\omega_0 = 1/\tau = (\tau_1 \tau_2)^{-1/2}$ and

$$q = (\tau_1 \tau_2)^{1/2} / (\tau_1/b + \tau_2) = [C_1 C_2 (1-b)]^{1/2} / [C_1 (1-b) + C_2]$$

Dividing both numerator and denominator of q by τ_2 and setting $x = \tau_1/\tau_2$

we obtain $q = \sqrt{x} / (x/b + 1)$. Differentiating yields:


$$dq/dx = [(x/b+1)/(2\sqrt{x}) - \sqrt{x}/b] / [x/b+1]^2 = [(x/b+1) - 2x/b] / [2\sqrt{x}(x/b+1)]^2 = 0 \text{ if } x=b.$$

As $d^2q/dx^2 < 0$ for $x=b$, this is a maximum, i.e.: $q \leq q^{\max} = 1/2\sqrt{b} \leq 1/2$ is very small.

EEE331 Analogue Electronics

Improving pure RC-filters: incorporating amplification+feedback

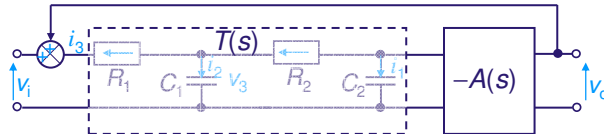Most filters will demand $q \gg 1$ in at least some frequency bands. In order to enhance q , a system is needed where energy is transferred from one part with a certain time constant to another, e.g. by using **negative feedback**:



output voltage: $v_o = (v_i + v_o) T(s) [-A(s)]$

$$v_o [1 + T(s)A(s)] = -v_i T(s)A(s)$$

$$v_o/v_i = -T(s)A(s) / [1 + T(s)A(s)] = -A(s) / [A(s) + 1/T(s)]$$

putting in the relationship $T(s) = 1 / \{1 + s(\tau_2 + \tau_1/b) + s^2 \tau_1 \tau_2\}$ then yields

$$v_o/v_i = -A / [1 + A] \times 1 / [1 + s(\tau_2 + \tau_1/b) / (A+1) + s^2 \tau_1 \tau_2 / (A+1)],$$

i.e. both ω_0 and q have been multiplied by a common factor of $[A(s)+1]^{1/2}$:

$$\omega_0' = \omega_0 [A(s)+1]^{1/2}, \quad q' = q [A(s)+1]^{1/2}. \text{ Differentiation and re-writing yields the } A(s)$$

dependence as $\Delta \omega_0' / \omega_0' = \Delta q' / q' = \Delta A / [2(A+1)]$, which tells us how sensitive the new centre frequency and the quality factor are to changes in the gain.

EEE331 Analogue Electronics

two different possible technological solutions:

always:

- eliminate L
- adjust q by feedback

then:

1. - adjust/increase gain by restoring some of the energy dissipated by R by
 - a) adding an op-amp to obtain an **active RC-filter** or
 - b) using transistors with voltage controlled output currents as trans-conductance amplifiers (g_m **C-filters**)

or

2. replace R by two MOSFET switches and one C in a so-called **switched capacitor filter** (SCF, fully CMOS compliant)

EEE331 Analogue Electronics

Active filters: Sallen-Key filters with single amp.+ passive RC circuit

use again leap-frog ladder, starting at output:

$$v_1 = v_o / A$$

$$i_1 = v_1 s C_1 = v_o s C_1 / A$$

$$v_2 = i_1 [Rb + 1/(sC_1)] = v_o s C_1 / A [Rb + 1/(sC_1)]$$

And summing currents at v_2 node:

$$v_o s C_1 / A = (v_1 - v_2) / [R(1-b)] + (v_o - v_2) s C_2$$

Inserting the above expression for v_2 yields:

$$T(s) = v_o / v_i = A / \{1 + s[\tau_1 + (1-A)\tau_2/b] + s^2 \tau_1 \tau_2\}$$

with time constants $\tau_1 = C_1 R$, $\tau_2 = C_2 Rb(1-b)$


This is again a 2nd order filter of general form

$1/[1 + s\tau_1 + s^2 \tau_1 \tau_2]$ with


$$\tau = (\tau_1 \tau_2)^{1/2}$$

and now
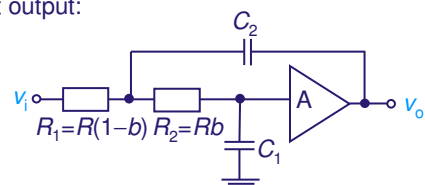
$$1/q = [\tau_1 + (1-A)\tau_2/b] (\tau_1 \tau_2)^{-1/2} = (\tau_1/\tau_2)^{1/2} + (1-A)/b (\tau_2/\tau_1)^{1/2}$$



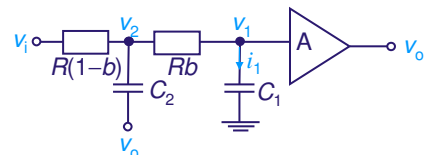equiv. circuit for negligibly small output resistance of amp. A



EEE331 Analogue Electronics

Active filters: Sallen-Key filters with single amp.+ passive RC circuit

$$1/q = [\tau_1 + (1-A)\tau_2/b](\tau_1\tau_2)^{-1/2} \\ = (\tau_1/\tau_2)^{1/2} + (1-A)/b (\tau_2/\tau_1)^{1/2}$$

Note for $A=1$:

$$q = (\tau_2/\tau_1)^{1/2} = (C_2(1-b)b/C_1)^{1/2}$$

Note for $A=1$, $b=0.5$, $C_1=C_2$ (symmetry):


$q_{\max} = 1/2$ as before for the buffered RC-filter

Note that changing C_2/C_1 ratio changes q without affecting τ , provided the product $C_1C_2 = \text{const.}$

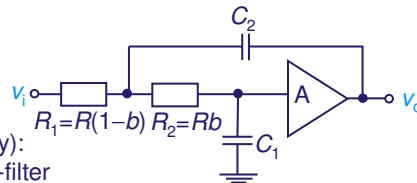Example: $A=1$, $b=0.5$, $C_2=10C_1$:

$$q = \sqrt{2.5} \approx 1.58 \text{ is modest}$$

q can become quite large if A and b are modified accordingly ($1/q \rightarrow 0$), but then it depends sensitively on gain A !




EEE331 Analogue Electronics

Switched capacitor filters (SCF): principle

aim: get close tolerance high resistance on an IC without use of R .

principle: use MOSFETs as switches plus capacitance

Consider the following network:

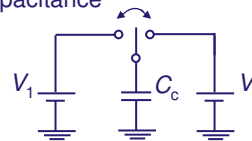

switch to the left: $Q_c = C_c V_1$

switch to the right: $Q_c = C_c V_2$

Hence, charge $\Delta Q_c = C_c(V_1 - V_2)$ must flow from V_1 to V_2 , and when the switch returns to left, ΔQ_c must be replaced. Now assume the switch is moved back and forth (one cycle) f_s times per sec.

Then the current is: $i = \Delta Q_c / \Delta t = f_s C_c (V_1 - V_2)$

Thus the effective resistance is: $R_c = (V_1 - V_2) / i = 1 / (f_s C_c)$, i.e. the combination of switch and capacitor behaves like a resistance, with $1/f_s = R_c C_c$, as long as the bandwidth is limited to $< 1/2 f_s$.

example: $C = 1 \text{ pF}$, $f_s = 1 \text{ MHz} \rightarrow R_c = 1 / (10^{-12} \text{ F} \times 10^6 \text{ 1/s}) = 10^6 \Omega = 1 \text{ M}\Omega$

This is larger than what would be possible using discrete resistors. For a typical thermal gate oxide: $d = 100 \text{ nm}$, $\epsilon_r \approx 4$. 1 pF then requires an area of $\sim 3 \times 10^{-9} \text{ m}^2$ $\approx 50 \mu\text{m} \times 50 \mu\text{m}$. This can be controlled to within $\sim 1\%$ and R_c only depends on f_s .

EEE331 Analogue Electronics

Switched capacitor filters (SCF): applications

switched capacitor (inverting) integrator:

charge entering C_i per cycle: $\Delta Q_c = C_c(v_i - v_x)$
 charge entering C_i per sec.: $\Delta Q_c f_s = C_c f_s (v_i - v_x)$
 charge entering C_i in time δt : $\delta Q = \Delta Q_c f_s \delta t$
 current: $i = dQ/dt = C_c f_s (v_i - v_x)$
 where $v_x = 0$ is a virtual earth

Hence, the output voltage is


$$v_o = -1/C_i \int \delta Q / \delta t dt = -1/C_i \int C_c f_s v_i dt = -f_s C_c / C_i \int v_i dt,$$

advantage:

The integrator gain is controlled by f_s and the ratio of MOS capacitors C_c/C_i . The latter is given by their areal ratios, which can be controlled highly accurately by the lithography.

disadvantages:

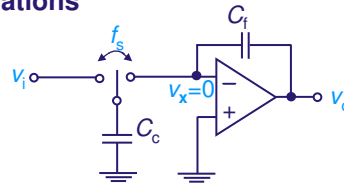- MOS capacitors are leaky due to thermal electron-hole recombination at Si/SiO₂ interface and in the bulk (and some diffusion of minority carriers to the surface). This limits max. storage time for charge to the 1-2ms range.
- Input node must be low-pass filtered to prevent unwanted down-conversion (aliasing).



EEE331 Analogue Electronics



Switched capacitor filters (SCF): applications

switched capacitor (inverting) integrator:

general treatment of transfer function:

$$T(s) = v_o/v_i = -Z_2/Z_1 = -1/(sC_i R_c) = -1/(j\omega R_c C_i)$$

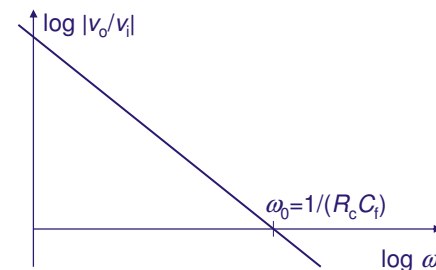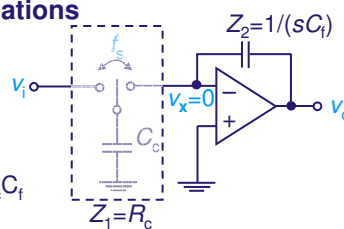is a **low pass filter** with time constant $1/\omega_0 = R_c C_i$



EEE331 Analogue Electronics

Switched capacitor filters (SCF): applications

summing and subtracting integrator:

switches to the left: $Q_c = C_c(v_1 - v_2)$
 switches to the right: $Q_c = C_c(v_x - v_3)$
 charge flow: $\Delta Q_c = C_c(v_1 - v_2 + v_3)$
 charge entering C_f in time δt :

$$\delta Q = \Delta Q_c f_s \delta t$$

$$= C_c f_s (v_1 - v_2 + v_3) \delta t$$


Hence, the output voltage is

$$v_o = -1/C_f \int \delta Q / \delta t dt = -f_s C_c / C_f \int (v_1 - v_2 + v_3) dt$$

NB 1: Input to v_2 with $v_3=0$ yields an inverting subtracting integrator.

NB 2: Input to v_3 with $v_2=0$ yields an inverting summing integrator.

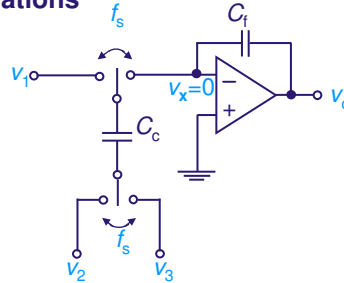NB 3: Input to v_2 with $v_1+v_3=0$ would yield a non-inverting integrator.



EEE331 Analogue Electronics



Switched capacitor filters (SCF): applications

switched capacitor (inverting) differentiator:

general treatment of transfer function:

$$T(s) = v_o/v_i = -Z_2/Z_1 = -R_c/[1/(sC_i)] = -j\omega R_c C_i$$

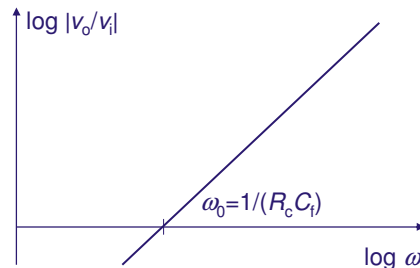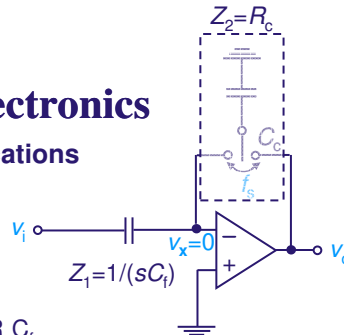is a **high pass filter** with time constant $1/\omega_0 = R_c C_i$



Note:

current through C_i : $i = dQ/dt = C_i dv_i/dt$
 This directly flows through the feedback resistor R_c to the output:

$$v_o(t) = -R_c C_i dv_i/dt$$

is a **differential signal**, i.e.

it suppresses slowly varying signals but amplifies high- f details.

Can also get **band pass filter** using switched capacitors $C_c \parallel C_f$ at both input & output!

EEE331 Analogue Electronics

Questionnaire on lecture series

Please tick all appropriate boxes and return anonymously after the last lecture. Thank you!

- | | |
|----------------------------|--|
| The lecture content was | <input type="checkbox"/> demanding but manageable
<input type="checkbox"/> far too difficult
<input type="checkbox"/> mostly easy
<input type="checkbox"/> all familiar |
| The presentations were | <input type="checkbox"/> of high standard, combining computer presentations and illustrations on the white board in about the right amount
<input type="checkbox"/> entertaining and/or interesting
<input type="checkbox"/> way too fast
<input type="checkbox"/> too general without enough practical examples
<input type="checkbox"/> too abstract and/or too mathematical |
| The lecture scripts were | <input type="checkbox"/> very good and understandable
<input type="checkbox"/> of acceptable standard
<input type="checkbox"/> too poor in quality for revision |
| The general atmosphere was | <input type="checkbox"/> relaxed; lecturer answered questions appropriately
<input type="checkbox"/> sometimes a bit tense; lecturer was not always well prepared
<input type="checkbox"/> rather stiff; lecturer did not interact enough with the students |

Any other comment you may want to make: