



The
University
Of
Sheffield.

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Autumn Semester 2008-2009 (2 hours)

High Speed Circuit Design 6

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1.
 - a. Explain briefly what is meant by a conjugate impedance matching. (3)
 - b. A lossless transmission line with an electrical length of 0.15λ and a real characteristic impedance of 50Ω is terminated with complex load impedance of $70-j30\Omega$. Find the reflection coefficient at the load, the VSWR on the line and the input impedance. (4)
 - c. Consider a lossless transmission line which has a characteristic impedance of Z_0 and terminated by a load impedance of Z_L . Show that the voltage reflection coefficient at the load is given by $\Gamma = (Z_L - Z_0) / (Z_L + Z_0)$. (7)
 - d. A lossless quarter wavelength transformer with $Z_0 = 100\Omega$ is terminated by a load impedance of $Z_L = 210\Omega$. Calculate the impedance and voltage at the sending end when the voltage at the receiving end is 80V. (6)

2.
 - a. Explain briefly how the Smith chart can be used to solve transmission line problems. (4)
 - b. A lossy line with attenuation of 15 dB/m at 300 MHz, is terminated by a load with a normalized impedance of $z = 2.5 + j0$. Use the Smith chart to find the VSWR at a distance of 20cm from the load. (6)
 - c. For a transmission line with $Z_0 = 50\Omega$ and terminated by $Z_L = 110 + j50\Omega$, design a double stub matching network to match Z_L to Z_0 . The 1st stub is located at the load, and the two stubs are separated by a distance of 0.125λ . The length of each stub should be $\leq 0.25\lambda$. (10)

Note: Find one possible solution for each design.

3. a. List and explain briefly the decomposition rules of a signal flow diagram (SFD). (4)
- b. Find the transmission, ABCD, parameters of the transmission line shown in Figure 1

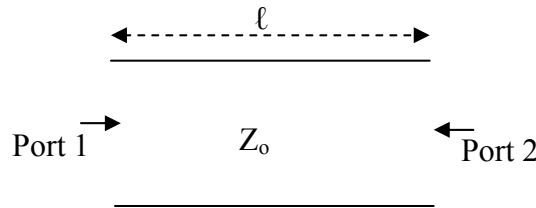


Figure 1

(8)

- c. Calculate the scattering parameters of the two-port network shown in Figure 2. Assume the characteristic impedances for the input and output ports are equal ($Z_{o1}=Z_{o2}$).

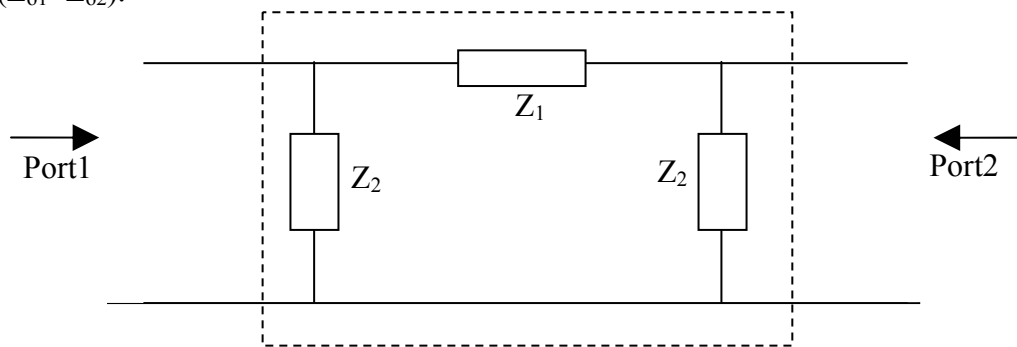


Figure 2

(8)

4. a. Explain with the aid of diagrams what is meant by the unconditional stability of an amplifier. (4)
- b. An amplifier has the following S-parameters: $S_{11} = 0.7\angle -70^\circ$, $S_{21} = 5.5\angle 85^\circ$, $S_{12} = 0.2\angle -10^\circ$, $S_{22} = 0.7\angle -45^\circ$. Determine the stability of this transistor and plot the corresponding stability circles. (8)
- c. Design an amplifier for maximum gain at 4.0 GHz. Use a GaAs FET with the following parameters ($Z_0=50\Omega$): $S_{11} = 0.72\angle -116^\circ$, $S_{21} = 2.6\angle 76^\circ$, $S_{12} = 0.03\angle 57^\circ$, $S_{22} = 0.73\angle -54^\circ$. (8)

You may find the following information useful:

The equations of input and output stability circles are

$$r_{\text{in}} = \left| \frac{S_{12}S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

$$C_{\text{in}} = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2}$$

$$r_{\text{out}} = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$$C_{\text{out}} = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2}$$

SKK/AT