



The  
University  
Of  
Sheffield.

## DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Autumn Semester 2009-2010 (2 hours)

### High Speed Electronic Circuit Design 6

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1.
  - a. Prove that the characteristic impedance of a lossless  $0.25\lambda$  transmission line is given by  $Z_o = \sqrt{Z_{in} Z_L}$ . (4)
  - b. Calculate the inductance per unit length and the phase velocity for a lossless transmission line with a characteristic impedance of  $50\Omega$  and a capacitance of  $67 \text{ pF/m}$ . (5)
  - c. A lossless transmission line with an electrical length of  $0.1\lambda$  and a real characteristic impedance of  $75\Omega$  is terminated with complex load impedance of  $50+j20\Omega$ . Find the input impedance, the reflection coefficient at a distance of  $0.05\lambda$  from the load and the VSWR on the line. (5)
  - d. Using the appropriate transmission lines equations, show how the input impedance of a lossless transmission line can be made equivalent to a lumped capacitor or inductor when the line is terminated by a short or an open circuit load. (6)
  
2.
  - a. Explain how the Smith chart can be used in the analyses of lossy transmission lines. (4)
  - b. A coaxial cable of a characteristic impedance  $Z_o=50\Omega$  and a  $5 \text{ cm}$  length is terminated by a load impedance of  $Z_L=40+j35\Omega$ . Find the input impedance of the line at a frequency of  $1\text{GHz}$  assuming the guided wavelength is  $77\%$  of the free space wavelength. (6)
  - c. For a transmission line with  $Z_o=50\Omega$  and terminated by  $Z_L=150-j50\Omega$ , design a double stub matching network to match  $Z_L$  to  $Z_o$ . The 1<sup>st</sup> stub is located at the load, and the two stubs are separated by a distance of  $0.125\lambda$ . The length of each stub should be  $\leq 0.25\lambda$ . (10)

Note: Find one possible solution for each design.

3. a. Describe briefly what is meant by the transducer and the available power gains of a two port network. (4)
- b. Explain with the aid of diagrams what is meant by the transmission matrix representation, ABCD, and why it is useful when analysing the cascade of two networks. (4)
- c. A two port network is driven at both ports using  $V_1 = 10\angle 0^\circ$ ,  $I_1 = 0.1\angle 30^\circ$ ,  $V_2 = 12\angle 90^\circ$ ,  $I_2 = 0.15\angle 120^\circ$ . Determine the incident and reflected voltages at both ports assuming a characteristic impedance of  $50\Omega$  for each port. (4)
- d. Find the scattering parameters of the two ports network shown in Figure 1. The characteristic impedance of each port is  $50\Omega$ . (4)

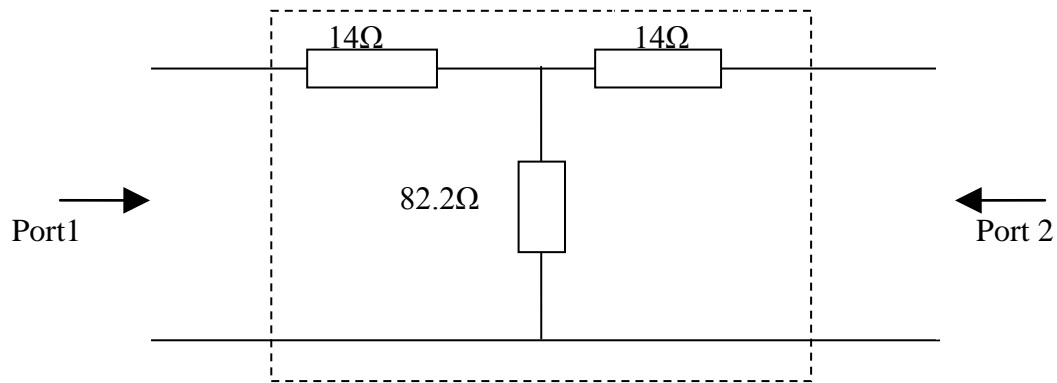


Figure 1

- e. What value of gain/attenuation is provided from the above network? (3)
4. a. Explain briefly the required conditions to achieve an unconditionally stable amplifier operation. (3)
- b. Explain why sometimes it is preferable to design an amplifier for less than the maximum obtainable gain? How this can be achieved? (4)
- c. An amplifier has the following S parameters at 500 MHz;  $S_{11} = 0.655\angle -57^\circ$ ,  $S_{21} = 10.5\angle 136^\circ$ ,  $S_{12} = 0.04\angle 47^\circ$ ,  $S_{22} = 0.79\angle -33^\circ$ . Determine whether the amplifier is unconditionally or conditionally stable. (3)
- d. An amplifier has the following S-parameters that are measured at 6GHz with respect to a  $50\Omega$  reference characteristics impedance:  $S_{11} = 0.655\angle -140^\circ$ ,  $S_{21} = 2.4\angle 50^\circ$ ,  $S_{12} = 0.0$ ,  $S_{22} = 0.707\angle -83^\circ$ . Design the input and output matching networks of the amplifier so that an overall gain of 10dB is achieved. Plot and use constant gain circles for  $G_L = 2\text{dB}$  and  $3\text{dB}$ , and  $G_s = 1\text{dB}$  and  $0\text{dB}$ . (10)

**You may find the following information useful:**

The constant gain circles can be plotted using the following set of equations

$$C_S = \frac{g_S S_{11}^*}{1 - (1 - g_S) |S_{11}|^2}$$

$$r_S = \frac{\sqrt{1 - g_S} (1 - |S_{11}|^2)}{1 - (1 - g_S) |S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$

$$r_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$

**SKK**