

EEE 103 → EEE students
 EEE 121 → Aerospace students
 EEE 141 → Physics / Comp Sci
 EEE 151 → ACSE students.

About EEE103/121/141/151

- about application of active (non-linear) devices → the things that make electronics useful!
- diodes → only allow current to flow in one direction used in a wide variety of applications.
- transistors → basis of amplifying devices and of switches.
- transistors as switches
- transistors as amplifiers
- operational amplifiers — someone has done all the hard design work and produced a near perfect amplifier.

Horowitz & Hill The Art of Electronics

Cambridge

Smith R.T. Circuits Devices +
Systems

Sedra & Smith "Microelectronic
Circuits" Oxford.

ACSE prob class PC-09

Course Material

- these are on the eee teaching resources web page

<http://hercules.shef.ac.uk/eee/teach/resources/>

nr index.html

P 1.

Weeks

Robert Spence Introductory Circuits
Wiley. 2008.

① open browser from within the
UoS network

② find [see home page](http://shef.ac.uk/see)

shef.ac.uk/see


- ③ select "Information for Staff/Student"
- ④ select "EEE Teaching Resources"
- ⑤ select modules of interest.

Setting up a VPN connection

described on

www.shef.ac.uk/cics/remote.
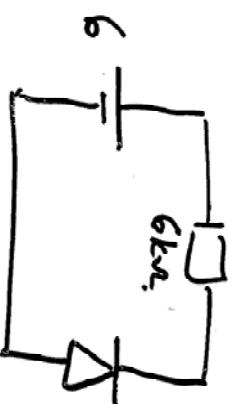
$$I = I_0 \left(\exp\left(\frac{eV}{kT}\right) - 1 \right)$$



$$\frac{6}{I} + \frac{V_A - V_C}{6k\Omega} = 0 \quad \text{or} \quad 6 = -6(V_A - V_C)$$


Using "reference node" V_A

using the "conduction for $V \geq 0.7$ " model.

if $V_A - V_C > 0.7$ diode conducts
if $V_A - V_C < 0.7$ diode doesn't conduct — ie blocks.

Assume diode is conducting
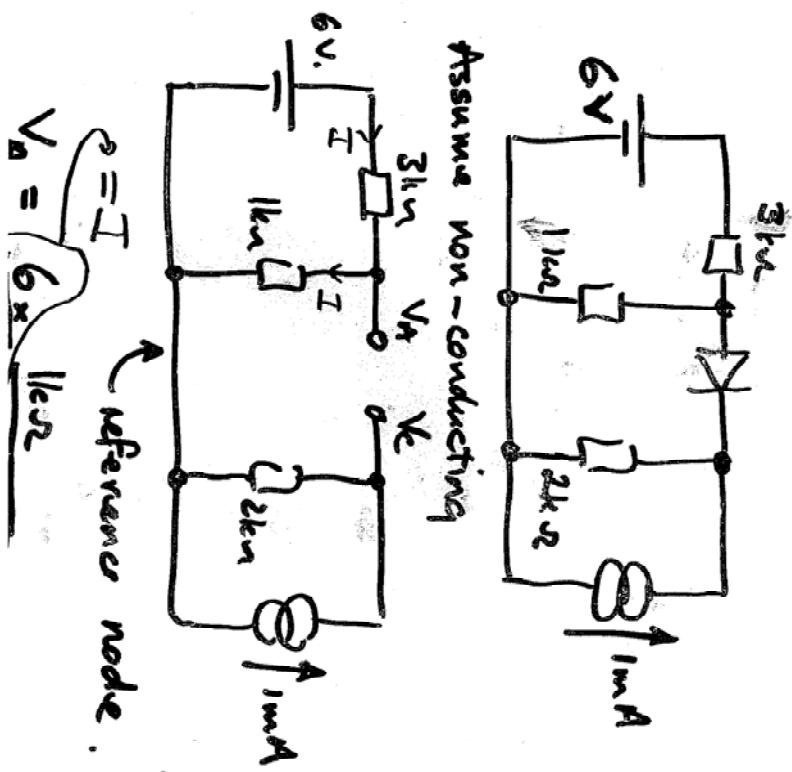
$$T = T_0 / \left(\exp\left(\frac{eV}{kT}\right) - 1 \right)$$



$$I = -\frac{6 \cdot 7}{6k\Omega}$$


$$\frac{6}{1k\Omega + 3k\Omega} = 6 \times \frac{1}{4} = \frac{3}{2} = 1.5 \text{ V.}$$

I must be
in this
direction if
assumption
is correct.

$$\begin{aligned} V_A - V_C &= 1.5V - 2V \\ &= -0.5V. \end{aligned}$$

Try the same circuit with
 $1k\Omega + 3k\Omega$ interchanged.

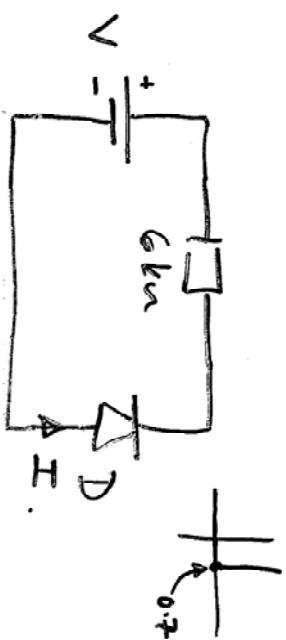
The other question that it is useful to know is "what is the boundary between conducting & non-conducting states"?



What value of V will put it on the point of conduction?

Diode is on the point of conduction when $V_A - V_C = 0.7$ (assuming 0.7V model) AND $I = 0$

i.e

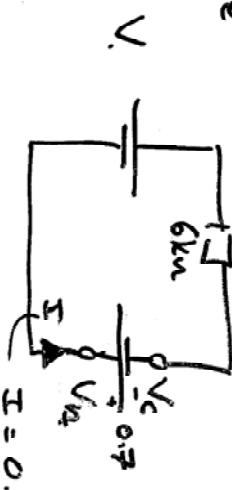


\checkmark must be $-0.7V$ to get the

diode terminal voltage, $V_A - V_C$ to 0.7 with OA flowing through it.

if $V > -0.7$ diode will be non conducting
 $V < -0.7$ diode will be conducting.

Example of application of diodes

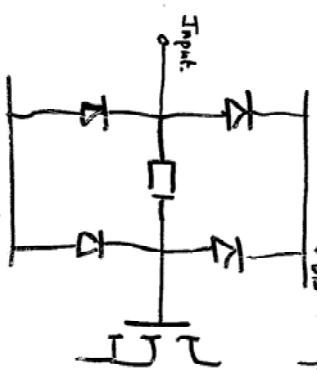



$V_S \leftarrow$ negative supply

If input voltage $> V_{DD} + 0.7$, diodes with cathodes connected to V_{DD} will conduct & limit input voltage.

If input voltage $< V_{SS} - 0.7$, similar behaviour occurs.

Challenge was

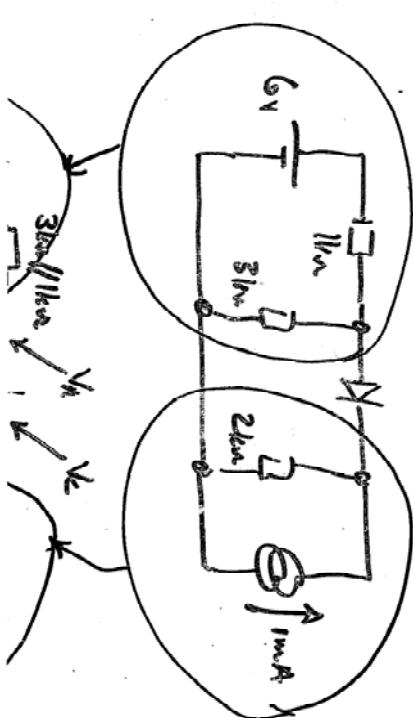

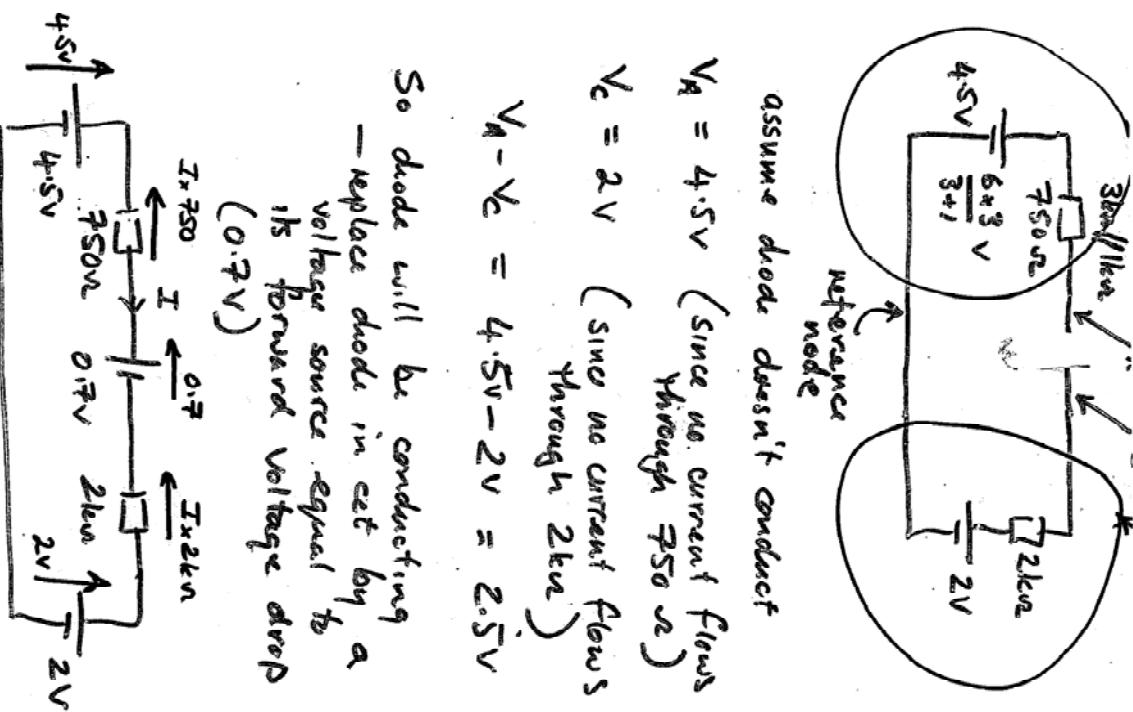

assume diode doesn't conduct


$$V_A = 4.5V \quad (\text{since no current flows through } 2k\Omega \text{ }\Omega)$$

$$V_C = 2V \quad (\text{since no current flows through } 2k\Omega \text{ }\Omega)$$

$$V_A - V_C = 4.5V - 2V = 2.5V$$

So diode will be conducting

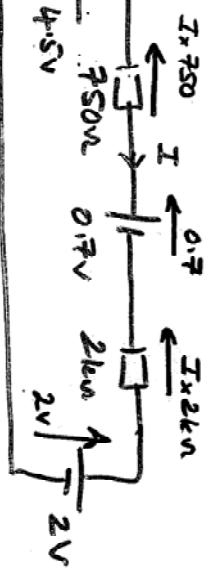- replace diode in cat by a voltage source equal to its forward voltage drop (0.7V)



$$4.5 = I \cdot 2750 + 0.7 + I \cdot 2k\Omega + 2$$

$$1.8 = I \cdot 2750$$



$$\text{or } I = \frac{1.8}{2750} \text{ A}$$

$$\text{or } = \frac{1.8}{2.75} \text{ mA}$$


Back to diodes as limiters ...

Diodes as waveform shapers ...

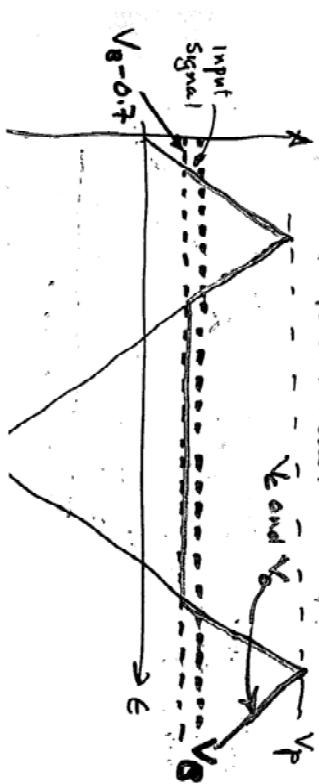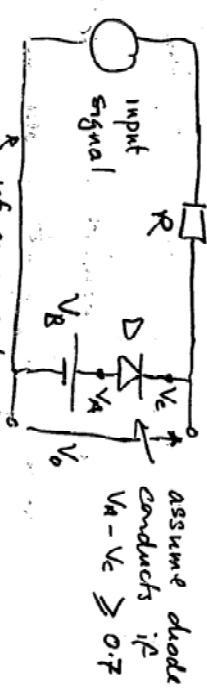Limiting is the same as "clipping" - a form of waveform shaping.




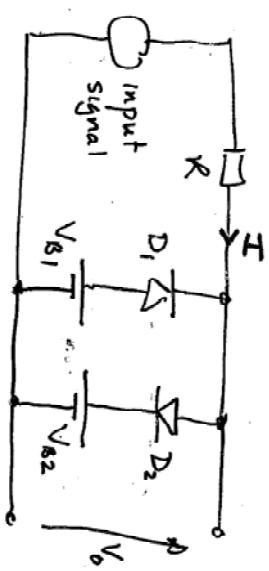Can clip positive & negative extremes
simultaneously



try sketching V_o for triangular
input with $V_{B1} < V_{B2}$



what might go wrong if $V_{B1} > V_{B2}$

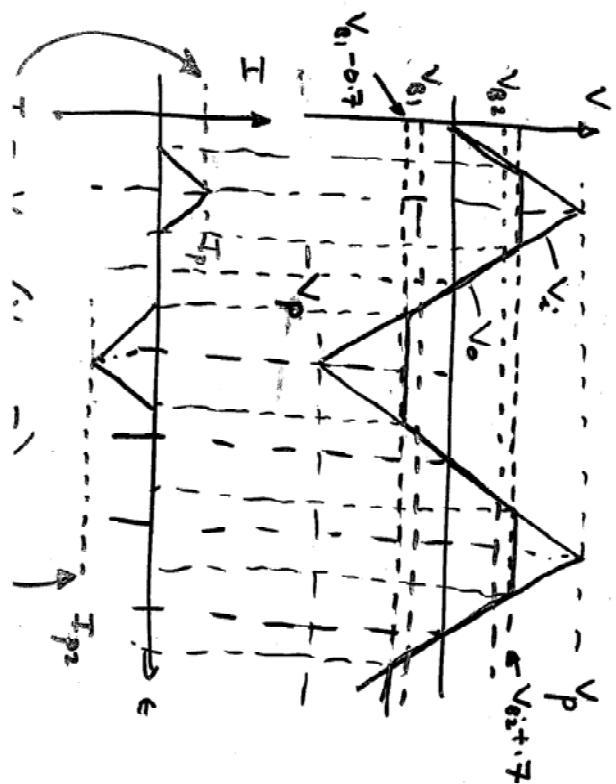

$$I_{P1} = \frac{V_p - (V_{B2} + 0.7)}{R}$$

$$-\frac{V_p - (V_{B1} - 0.7)}{R} = I_{P2}$$

Soft limiting.

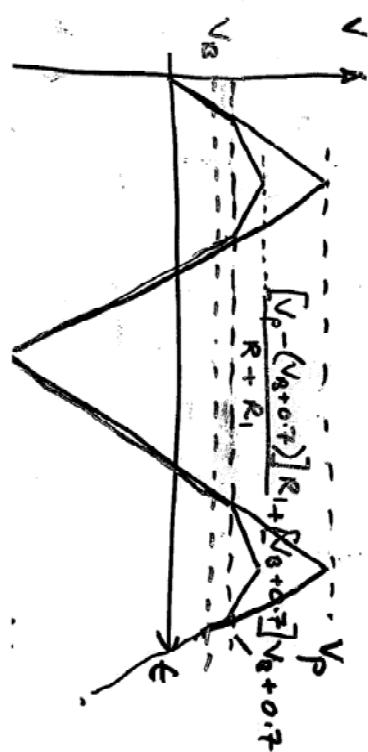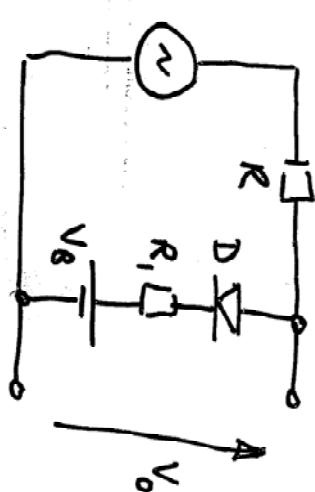

Changes of V_i are operated on by a potential divider behaviour


$$\Delta V_o = \Delta V_i \times \frac{R_2}{R_1 + R_2}$$

where ΔV = change of voltage.


- cct can be extended to include many diodes + many resistors giving many changes of gain over input signal range.

- Used to convert triangular waves into sine waves in cheap function generator applications.

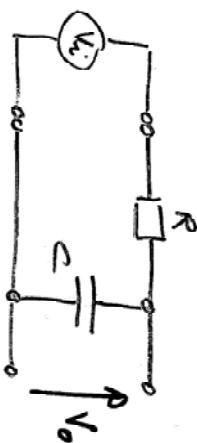Review of R-C ccts. from a transient point of view.



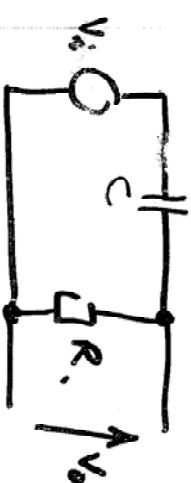Sometimes the cct might be a bit more complicated ...




V_o

initially V_o follows V_i because there can be no change of charge in C .

$$t=0, \tau = RC$$

$$V(t) = V_i e^{-t/\tau}$$


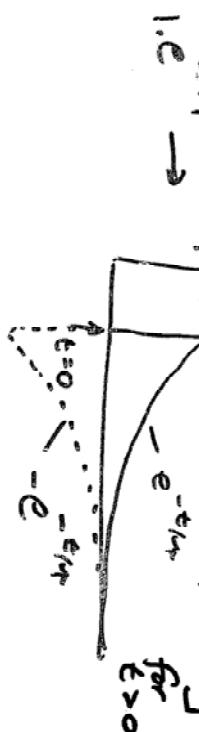


$$t=0, \tau = RC$$

$$V(t) = V_i e^{-t/\tau}$$



$$= V_i (1 - e^{-t/\tau})$$

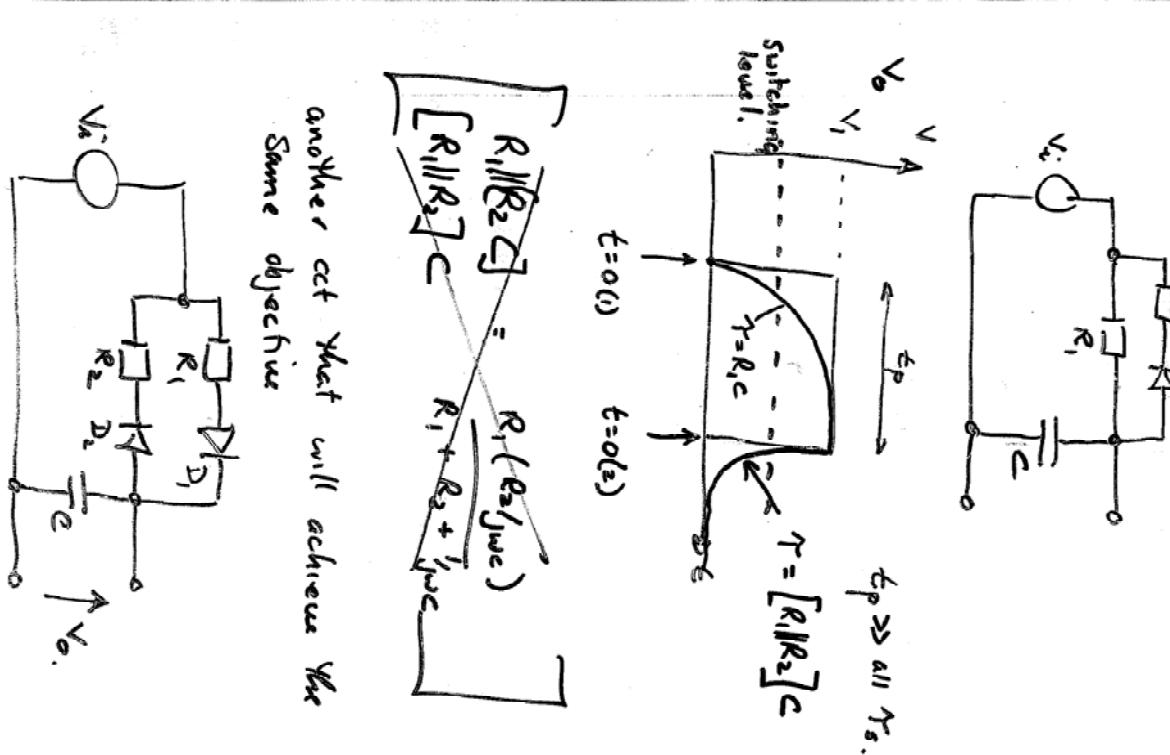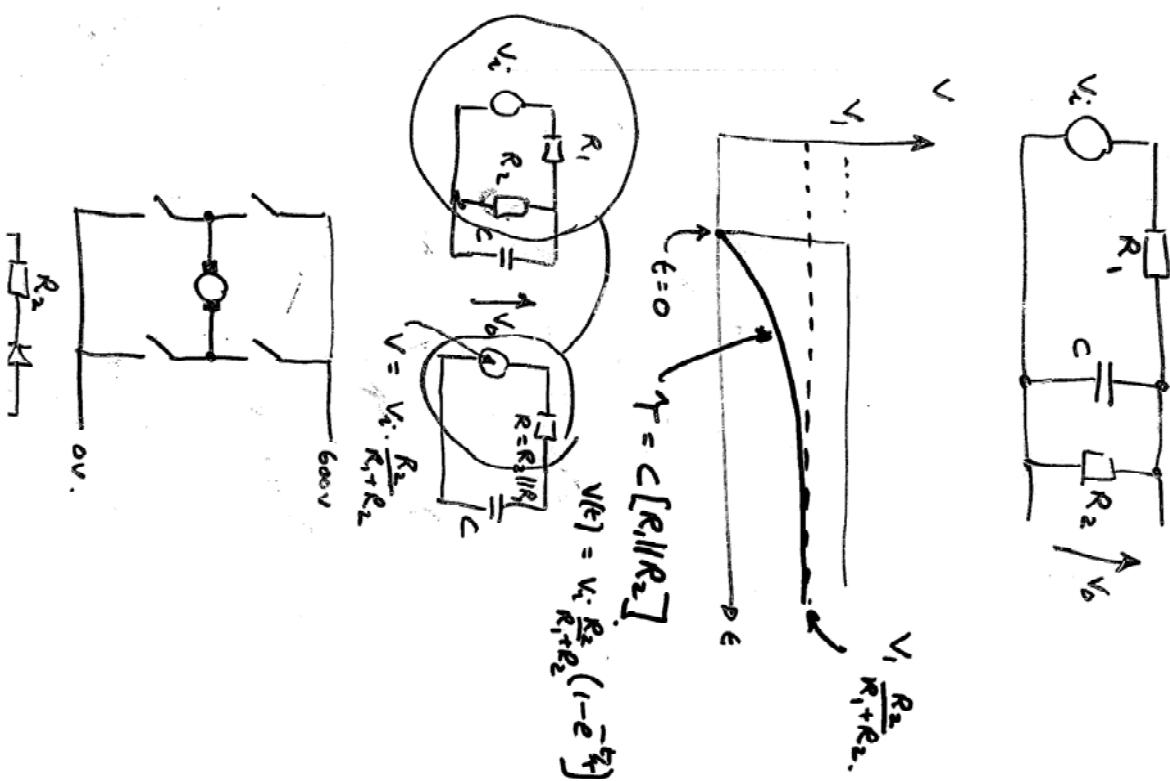How would V_o change if $C + R$ were interchanged?



" V_1 would conduct on rising pulse edges; $R_2 D_2$ would conduct on falling pulse edges



Can hence time constant control on

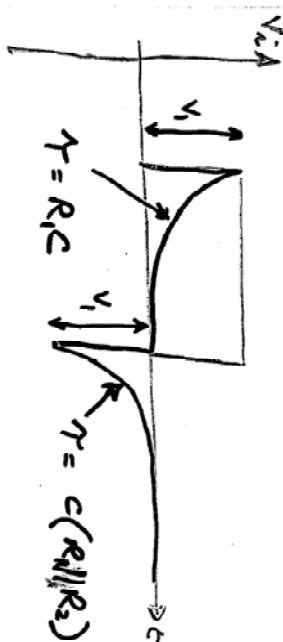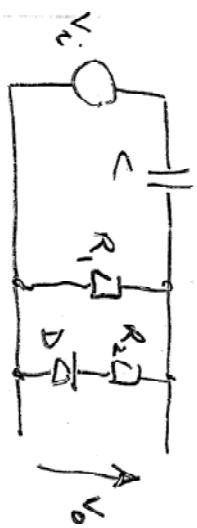

$$\tau = R_1 C$$


$$\tau = C(R_1 \parallel R_2)$$

What happens if $t_p \approx \tau$

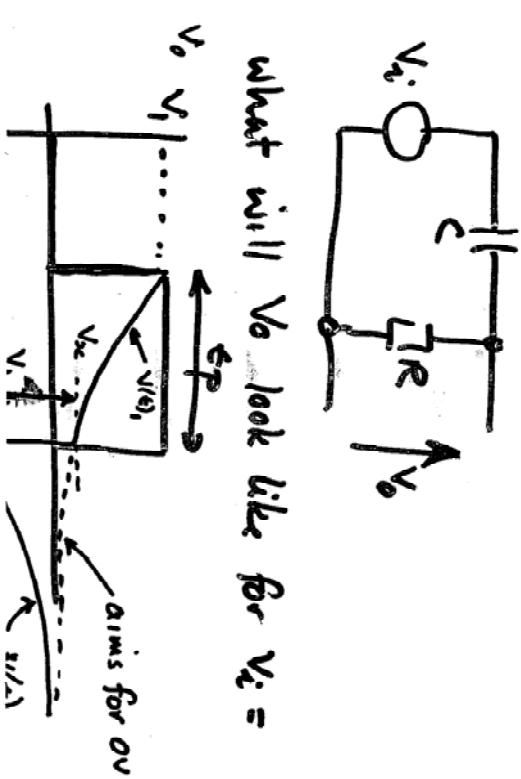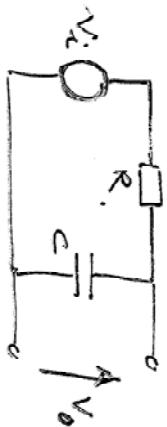


What will V_0 look like for $V_1 =$

Think about ...

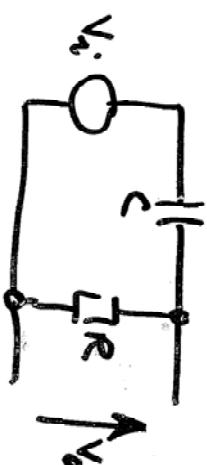

$$V_{2c} = \text{value of } V(t) \text{ at } t = t_p.$$
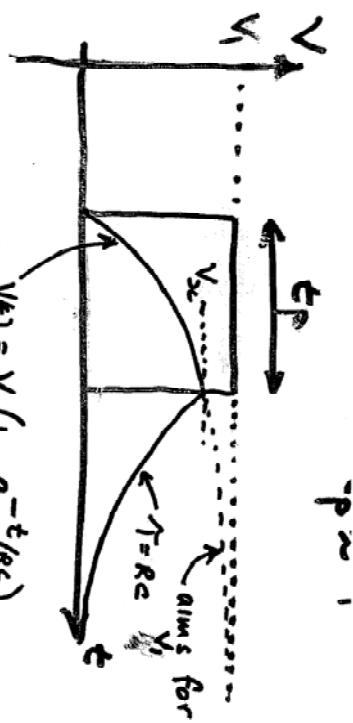
$$\text{falling } V(t) \text{ is } V(t) = V_{2c} e^{-t/R_C}$$



$$V_1 \downarrow V_{(t)_2} = (V_x - V_1)$$

where $t_p \approx \tau$.

$$V(t)_1 = V_1 e^{-t/\tau} \quad (\tau = RC)$$


$$\text{so } V_x = V_1 e^{-t_p/\tau}$$

$$V(t)_2 = (V_x - V_1) e^{-t/\tau}$$


Basic clamp circuit

Detectors and Clamps.

Peak detector

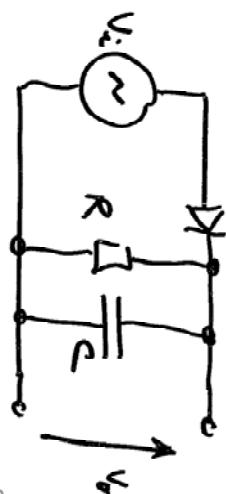


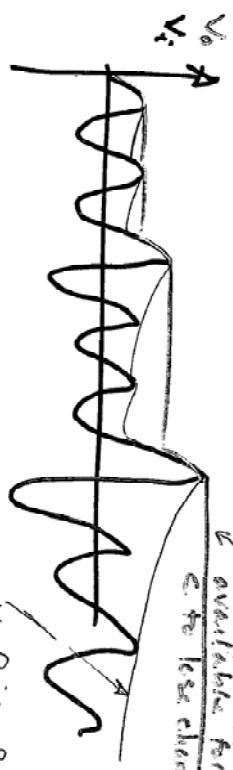Output with
no R - we
need some
overhead for
C to lose charge



with finite R.

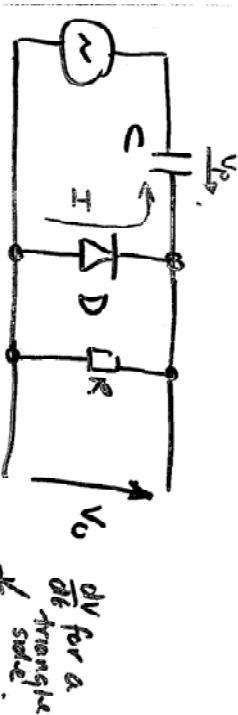Purpose of a clamp is to anchor, or clamp some part of a waveform — either positive peak or negative peak — to a defined potential — often to zero.




$$I = C \frac{dV}{dt} = C \frac{V_p - V_o}{R}$$




$\frac{dV}{dt}$ for a triangle side.

replaces charge lost through R.

Signal starts here.

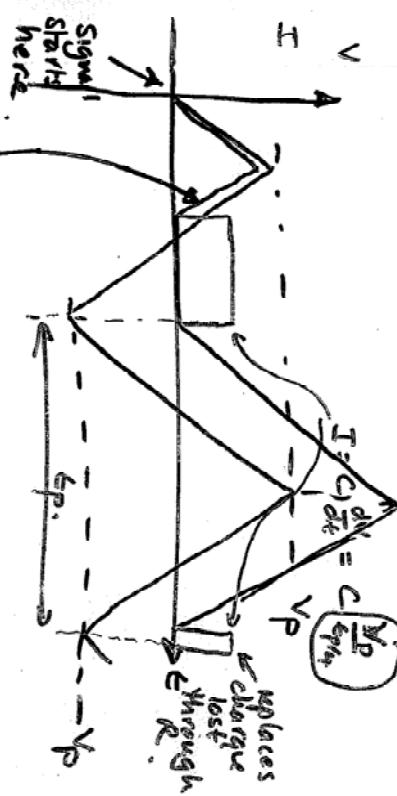

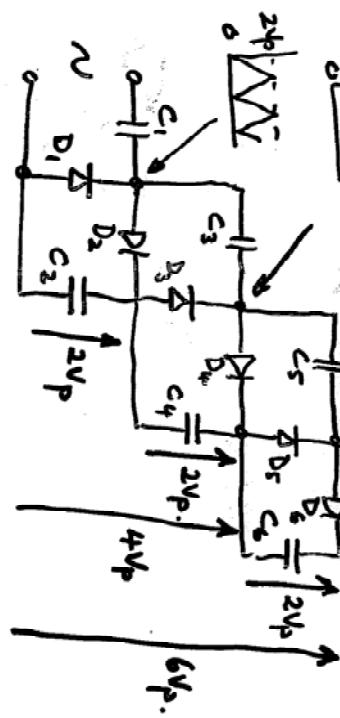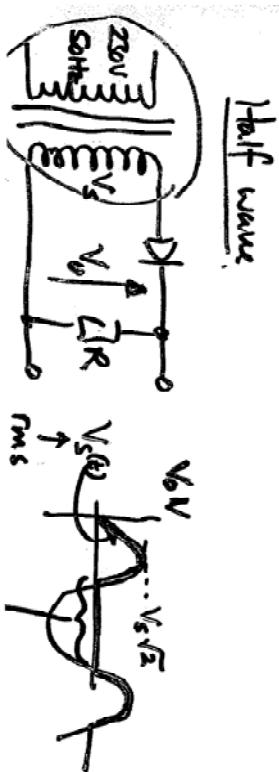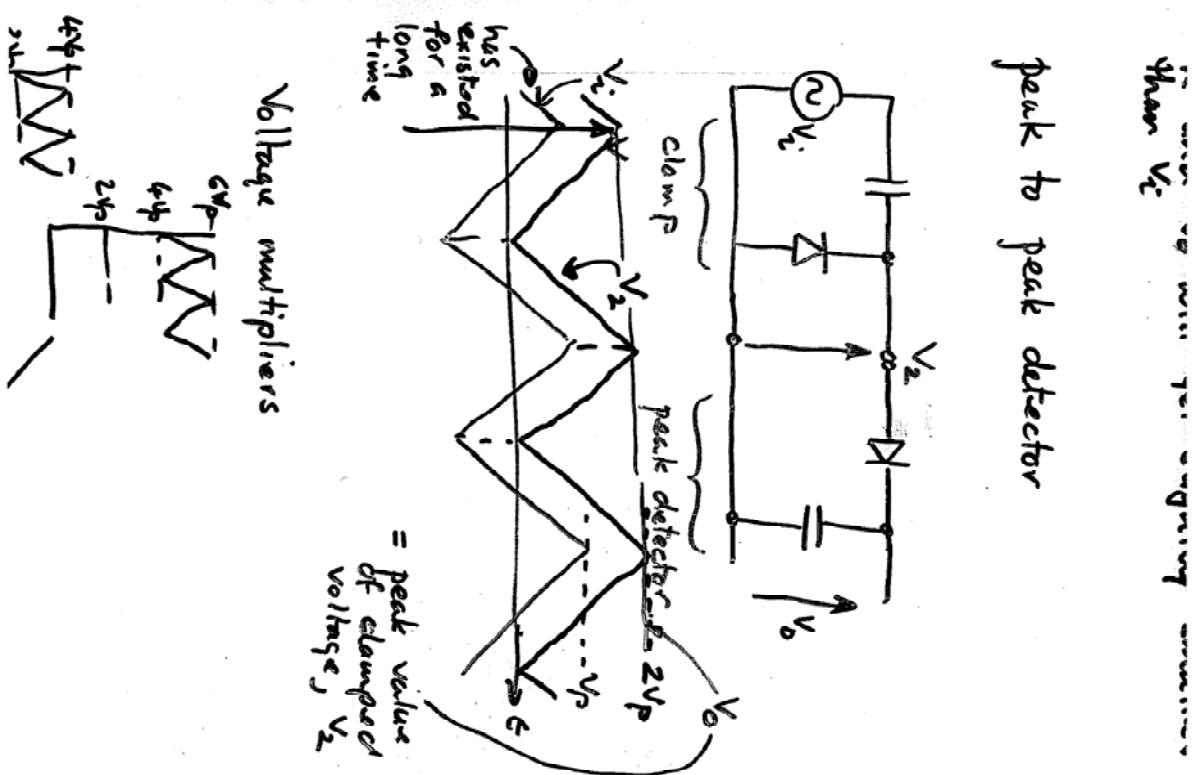V_o will follow V_i because D will not conduct ... but over the half cycle, some charge will leak through




- two types of rectifier
 - full wave \rightarrow makes use of whole input cycle
 - half wave \rightarrow makes use of the half cycle or - in half cycle only.

This is perfect
for this
module.


need an
energy store
What can be
changed when
diode conducts
and supply the
load with energy
when diode doesn't
conduct.

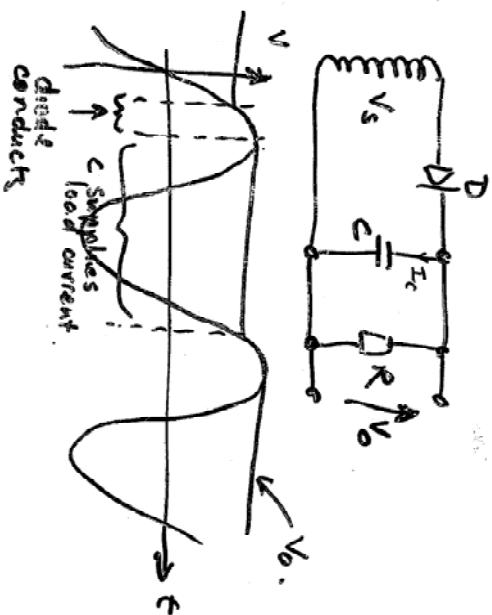For low voltage + static, C is usually
used ...



designing a circuit like this makes
extensive use of approximations.

MUST WRITE DOWN APPROXIMATIONS USED.

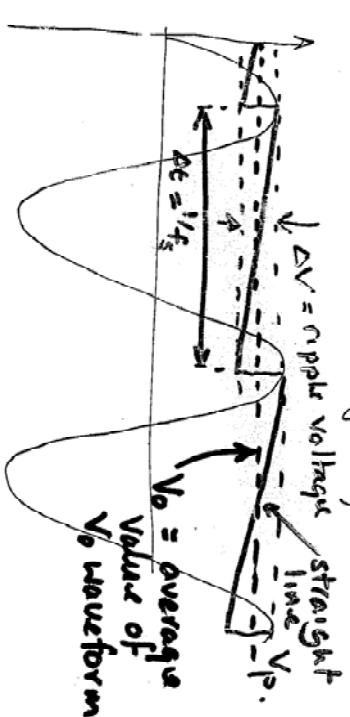

$$f_s = \text{supply frequency}.$$

$$\text{Since } I_c = C \frac{dV_o}{dt}$$

It's easy to make an equation
linking ΔV , Δt , I_c + C

$$I_c = C \frac{\Delta V}{\Delta t}$$


assume this is constant at
its peak value which is
 $\frac{V_p}{R_f}$

putting this all together

- Assume capacitor discharges linearly
 - implies that $I_c = \text{constant}$.
- Assume that discharge occurs for whole interval between half cycle peaks


$$\frac{V_p}{R_L} = C \frac{V_k}{f_s} = C f_s V_R$$

Full wave rectifier cct.

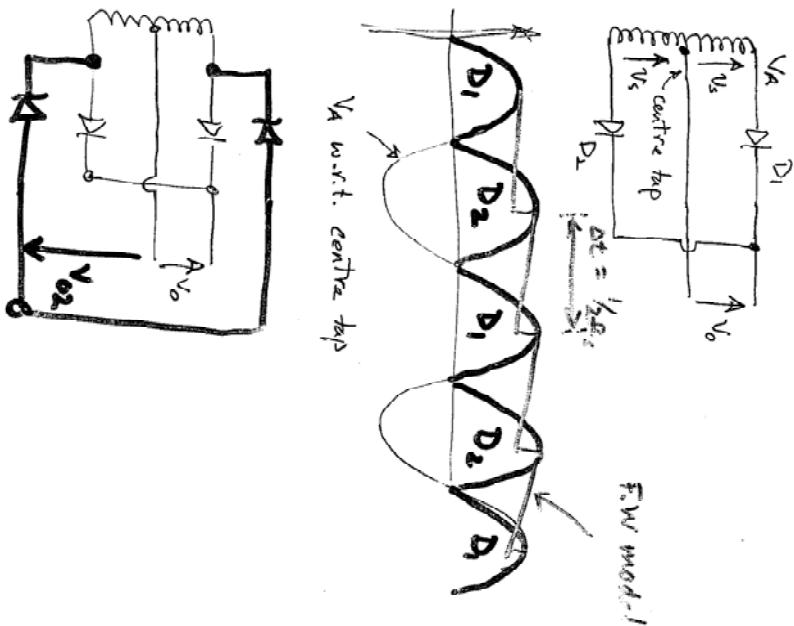

F.W mod.-I.

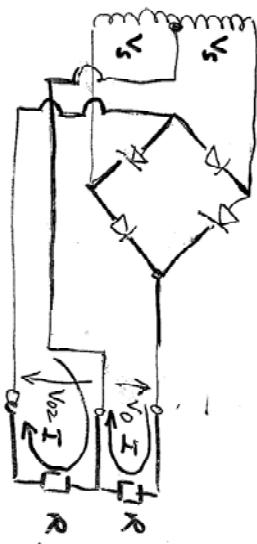Since $V_{o2} = -V_o$, and same R is on both outputs — current I will flow as shown. Total ~~out~~ current in centre tap arm of V_{o2} cct = 0
Sum of two I_s , identical but opposite in direction



Output from a capacitor (or inductor) smoothed rectifier cct is not good enough for most modern equipment — good quality dc needs a regulator to be used

regulators regulate the flow of current in order to maintain a constant potential at a node in a circuit.


two types → series regulator
shunt regulator.

series



controlled node.


Shunt.

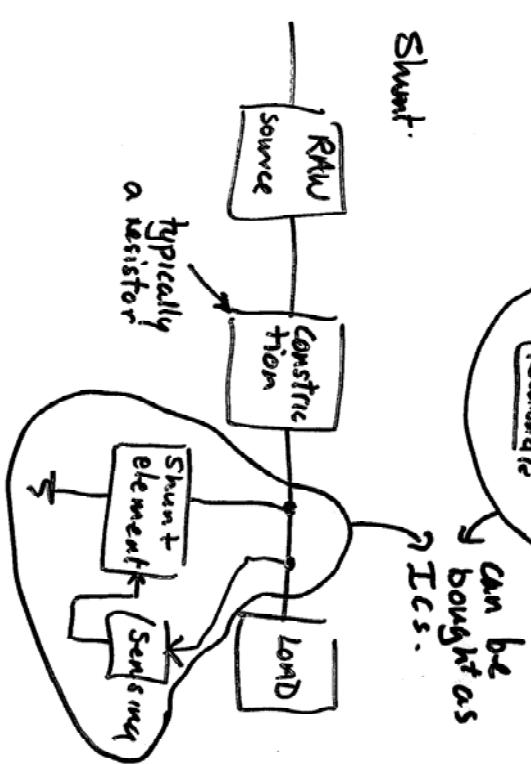

can be bought as
ICs.


Zener Diode
P-n junction designed to breakdown in a reverse direction at a well defined voltage.

characteristic

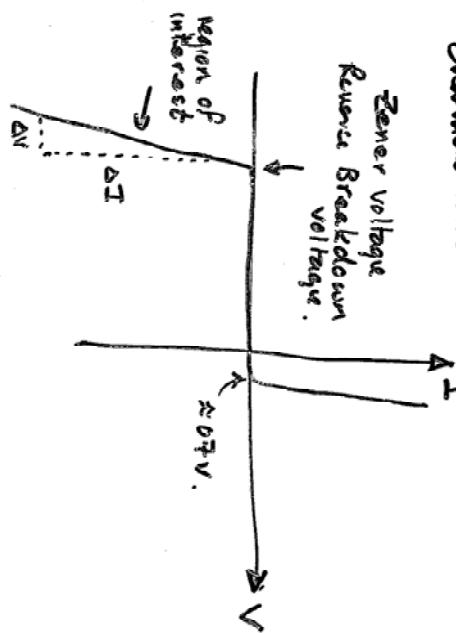

$$\frac{\Delta V}{\Delta I} = r_z = \text{Zener slope resistance}$$

Typical Zener diode regulator circuit

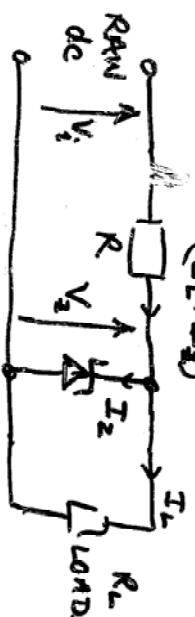

For proper operation

$$I_2 > I_{2\min} \text{ at all times}$$

— In some cases $I_{2\min}$ can be taken as zero

$$(I_L + I_2) = I_L + I_2$$

— conditions that threaten $I_2 > I_{2\min}$

are as V_i gets smaller

and as I_L gets bigger

\rightarrow minimum V_i and maximum I_L must be known design inputs.


Need to find maximum value of R that can be used for a particular set of circumstances.

$$\text{ie } \frac{V_{min}}{R} = I_{2\min} + I_{Lmax}$$

$\rightarrow V_{imin}, I_{2\min}, I_{Lmax} \rightarrow$ specified


What happens to the ripple ??

— described by a small signal model.

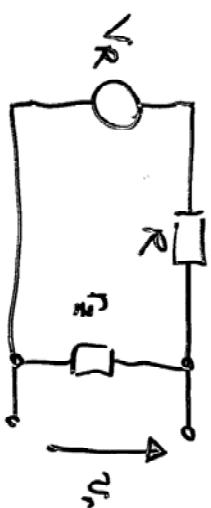

$$V_r = \text{output ripple} = \frac{V_R}{R + r_2} \cdot \frac{r_2}{R + r_2}$$

Can extend zener regulators

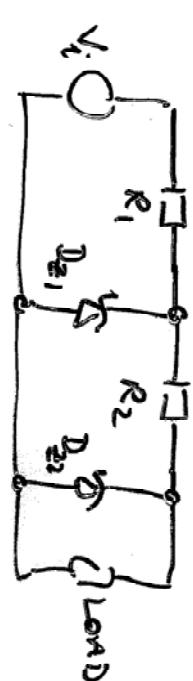


$I_{2\min} + I_{Lmax}$ must be current that flows through R at minimum V_i

$V_i - V_o = \dots$



Other small signal diode application....

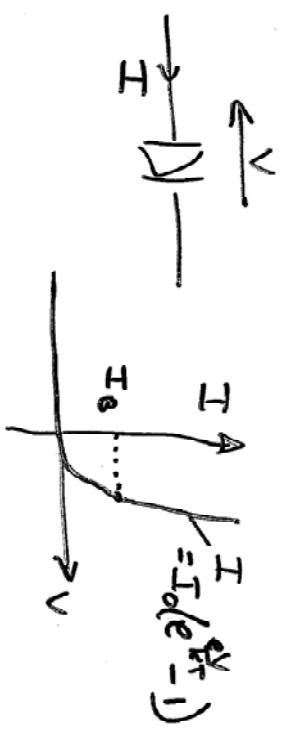

slope at I_0

$$\text{slope at } I_0 \text{ is } \frac{dI}{dV} = I_0 e^{\frac{qV}{kT}} \cdot \frac{e}{kT}$$


$$= \frac{eI_0}{kT} \cdot e^{\frac{qV}{kT}}$$

$$I = I_0 \left(e^{\frac{qV}{kT}} - 1 \right) \approx I_0 e^{\frac{qV}{kT}} \text{ for small } V.$$

$$\therefore \frac{dI}{dV} \approx \frac{e}{kT} \cdot I$$


$$\frac{dI}{dV} = \frac{1}{R_a}$$

Suppose Σ have a cut

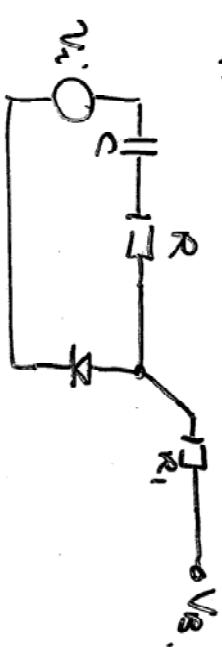


Let $R_1 \gg R$

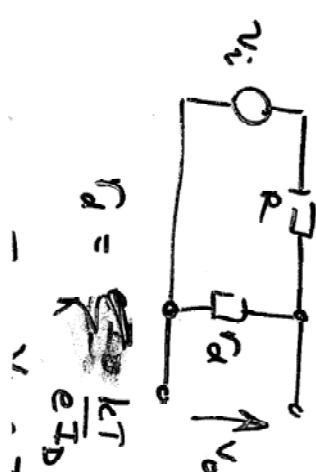Let X_C be $\ll R$ at all frequencies of interest.



$$\Delta v = \frac{v_o - v_i}{R_1}$$


Bipolar Transistor

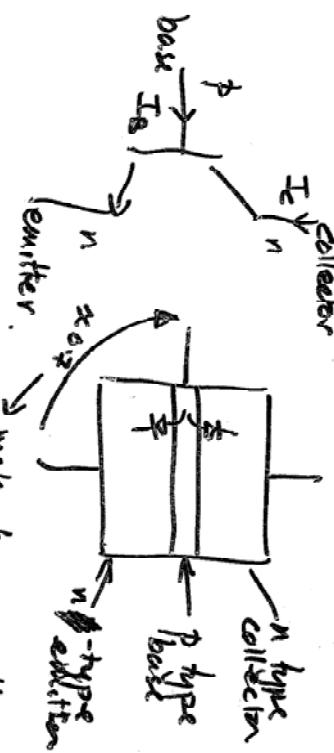

h_{FE} = forward current transfer ratio.

- d.e. ratio.

JFET

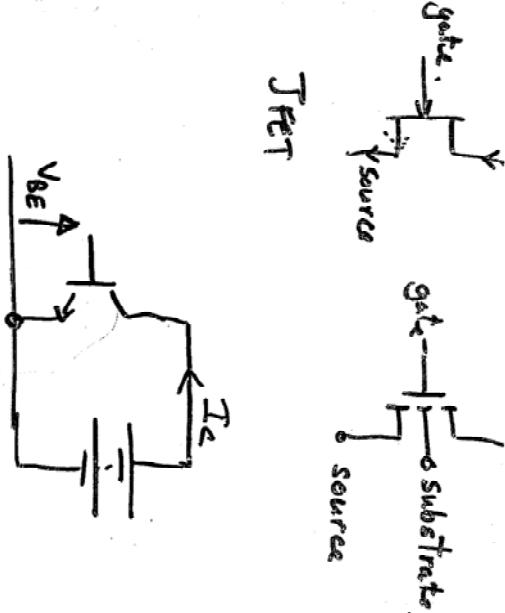

I_d is controlled by V_{GS}

Transistors as switches

- A bit about switches

Switch open, ideally $I \approx 0$

$V_{supply} = V_s$

$$I = \frac{V_s}{R_{load}}$$

FET
— both work by constricting channels.

i_{drain} i_{drain}


$$[V_{switch} = 0]$$

$$\frac{V_{switch}}{I} = 0.$$

Electronic switches

- Off state $I \approx 0 \rightarrow$ no healthy theme is a leakage current.
- but can usually be ignored.
- On state $V_{switch} \rightarrow$ small.

tends to be constant in BJTs but increases with on-state current in FETs.

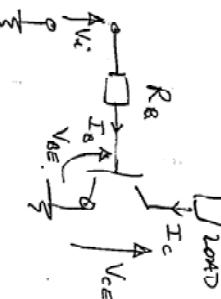BJT switches

May or may not be calculated using $V_{BE(on)}$

(sometimes called $V_{CE(on)}$)

$$\text{If } I_{CON} = \frac{V_s}{R_{LOAD}} \quad I_B \text{ must be at least } \frac{I_{CON}}{h_{FE}} = \frac{V_s}{h_{FE} R_{LOAD}}$$

$$\text{and } I_B = \frac{V_{BE(on)} - V_{CE(on)}}{R_B}$$

To work out power loss in "on" state

$$\text{power loss} = I_{CON} \times V_{CE(on)}$$

need to supply a big enough I_B to ensure that on-state I_C can be supported.

— relationship between I_C + I_B is given by manufacturer as $h_{FE} = \frac{I_C}{I_B}$

$$\text{If } I_{CON} = \frac{V_s}{R_{LOAD}} \quad I_B \text{ must be at}$$