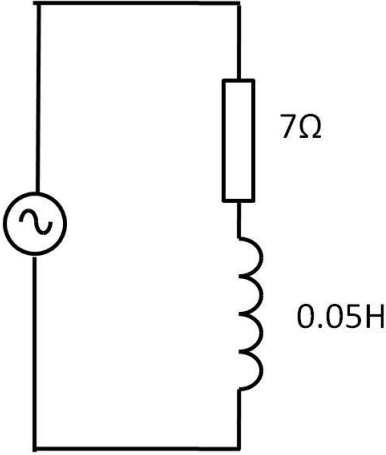
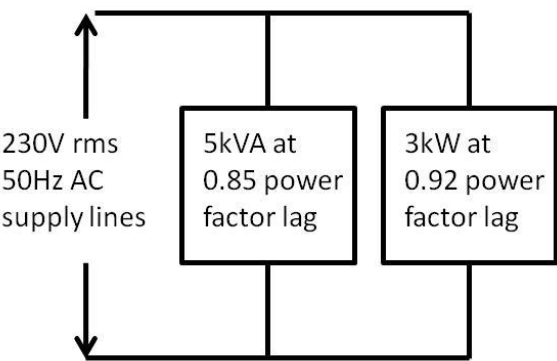


Constants required: $\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$

1

3	<p>Calculate the impedance of the circuit below; the magnitude and phase of the current drawn from the supply; the VA, VAR, and the real power supplied to the load; and finally the peak energy stored in the inductor</p> <div style="display: flex; align-items: center; justify-content: center;"> <div style="text-align: right; padding-right: 10px;"> 230V rms 50Hz AC sinusoidal supply </div>  </div>	Impedance:	[1]
		Current:	[1]
		VA:	[1]
		VAR:	[1]
		Real power:	[1]
		Peak energy stored in the inductor:	[1]

4	<p>Calculate the total Watts, VA and VAr drawn by the combination of loads shown below and hence calculate the current drawn from the supply</p>	<p>Show all your intermediate calculations in the box and state the final answers at the bottom of the box</p>	
	 <p>230V rms 50Hz AC supply lines</p> <p>5kVA at 0.85 power factor lag</p> <p>3kW at 0.92 power factor lag</p>	<p>Watts:</p> <p>VA:</p> <p>VAr:</p> <p>Current drawn from supply:</p>	<p>[5]</p>

END OF QUESTION PAPER