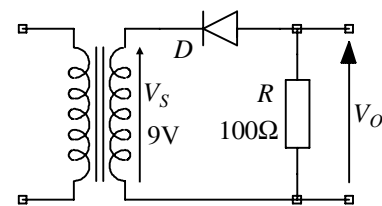


## EEE103/EEE121/EEE141 Problem Sheet

# Rectifiers and Smoothing

*Note: All a.c. voltages are r.m.s. quantities unless otherwise stated and unspecified frequencies are 50Hz.*

**Q1** In the half wave rectifier circuit of figure 1 both the diode and the transformer are ideal (ie,  $D$  conducts with zero voltage drop for forward bias and is an infinite resistance for reverse bias and the transformer has zero series resistance).



**Figure 1**

- (i) Sketch the shape of the voltage  $V_O$  as a function of time for at least one period of  $V_S$ .
- (ii) What is the peak value of  $V_O$ ? (-12.73V)
- (iii) What is the average value of  $V_O$ ? (-4.05V)
- (iv) What is the r.m.s. value of  $V_O$ ? (6.36V)
- (v) What is the power dissipated in  $R$ ? (405mW)

If the transformer has a total effective resistance of  $10\Omega$  in series with its secondary winding.


- (vi) What is the new peak value of  $V_O$ ? (-11.57V)
- (vii) What is the new power dissipated in  $R$ ? (335mW)

**Q2** What value of smoothing capacitor is required across the  $100\Omega$  load of figure 1 in order to achieve a ripple voltage of 0.3V peak to peak? What assumptions have been made in order to arrive at an answer? Estimate the power dissipated in the  $100\Omega$  load with this value of  $C$  connected. Assume that transformer and diode are ideal. (8500mF, 1.58W)

**Q3** For the circuit of figure 3 what are the peak values of the voltage differences:

- (a)  $V_B - V_A$  ? (25.5V)
- (b)  $V_A - V_C$  ? (25.5V)
- (c)  $V_C - V_B$  ? (-51V)

Is the rectifier a full wave or a half wave type? *Note: The answers given ignore the diode forward voltage drop.*

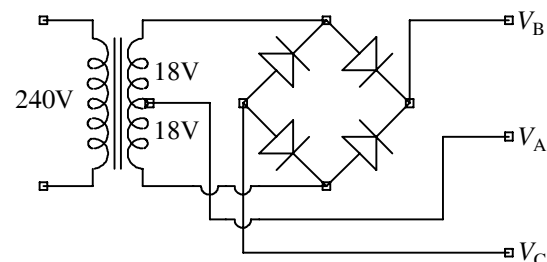

**Figure 3**

**Q4** The circuit of figure 3 is to be used to supply an amplifier which requires nominally balanced positive and negative power supplies with respect to zero. The amplifier demands a current of 2A and at this current the ripple voltage must be less than 1V pk to pk on each supply rail.

- (i) Redraw the circuit to include the capacitors necessary for capacitor input filtering of the rectifier output.
- (ii) Estimate a suitable value for each capacitor. (20mF)
- (iii) What d.c. component of output voltage will the smoothed supply provide? (24.3V)
- (iv) What peak reverse voltage (PIV) must the diodes be capable of handling if reverse breakdown is to be avoided? (51V)

*The answer to part (iii) will be very dependent on the assumptions and approximations made. Assume here that all components used are ideal.*


**Q5** The preamplifier section (tone controls etc) of the amplifier of question 4 requires a +10V supply at a current that may vary between 20mA and 50mA. This supply is to be derived from the main supply worked out in question 4 using a resistor and a zener diode.

- (i) What zener breakdown voltage is required? (10V)
- (ii) What value of series resistance is required if the current through the zener diode must be a minimum of 10mA? (230Ω)
- (iii) What power rating must the zener diode have if a worst case condition is the disconnection of the preamplifier from its supply? (600mW)
- (iv) What power rating must the resistor have if a worst case condition is the short circuiting of the preamplifier supply? (2.72W)
- (v) What are the normal operating power dissipations in the resistor and zener diode? (980mW and 400mW respectively - when  $I_L$  can vary, worst case normal operating dissipations must be used)
- (vi) What is the maximum zener diode slope resistance,  $r_z$ , that can be tolerated if the pk to pk ripple voltage on the preamplifier supply must be  $\leq 10\text{mV}$ ? (2.3Ω)

### AND FOR EXPERTS

**Q6** The circuit of figure 6 is sometimes called a full wave voltage doubler. (*The diode clamp - peak detector combination is sometimes called a half wave voltage doubler*)

- (i) Sketch the shape of  $V_O$  that you would expect to observe, taking special care with the ripple.
- (ii) If  $V_S = 20\text{V}$ ,  $I_L = 100\text{mA}$  and the components are ideal, what value of  $C_1$  and  $C_2$  is necessary if the peak to peak ripple must be 5V or less? (400μF)
- (iii) What is the average  $V_O$  under the conditions of part (ii)? (51.6V)
- (iv) What PIV must  $D_1$  be able to withstand? (54.1V)

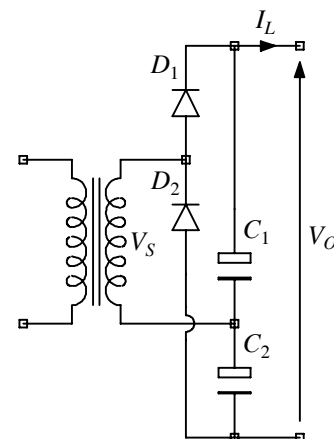

**Figure 6**