



The
University
Of
Sheffield.

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Spring Semester 2015-16 (2.0 hours)

EEE119 Digital System Engineering

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1. a. i) Find the decimal equivalent of the largest binary number that can be made with 7 bits. (2)
- ii) Find the binary equivalent of the Binary Coded Decimal **0011 0010**. (2)
- iii) What decimal number is represented by the 2s complement binary number **1101**? (2)
- iv) How many bits of memory are available from the hexadecimal addresses **CE6** to **FD2** inclusive, if each location is 4 bits wide? (3)
- b. Draw the truth table for a three input Exclusive OR function. Show how this could be implemented using only a 3-to-8 line decoder with active low outputs, plus one other logic gate. (6)
- c. A synchronous sequential circuit is required that checks for even parity on an incoming serial data sequence. The circuit input *I*, presents a new data bit on each rising clock edge. The output *Z* must be high whenever the parity of the sequence received up to that point is even. *Z* must be a function of the present state only.
Define the required states and hence draw a state diagram for this circuit.
(a state transition table, state equations and a circuit diagram are not required) (5)

2. a. i) Explain the terms 'setup time' and 'hold time' for a flip-flop. (2)
- ii) Explain the term 'critical path' when applied to a sequential logic circuit. (2)
- iii) Explain what you understand by the term 'metastability' when applied to sequential logic circuits. (3)
- b. A shift register is constructed with four flip-flops, and the output from the last flip-flop is inverted and then fed to the input of the first flip-flop. The initial state of the register is set to 0110.
- i) Draw a circuit diagram for this configuration and describe, using a table of sequential values, what happens when a series of clock pulses is applied to the register. (5)
- ii) Does the register ever return to its original state? If not, why not? If it does, how many clock pulses are needed? (2)
- iii) How are your results changed if the initial state is set to 1111 instead? (2)
- iv) What will happen if any other initial state is chosen? (1)
- v) What is the maximum theoretical frequency of operation of this shift register if the propagation delay of the inverter is 2ns, the propagation delay of a flip-flop is 5ns and the setup time of a flip-flop is 3ns. Assume that the hold time is negligible. (3)
3. a. The Consensus theorem in Boolean Algebra is given by:
- $$X.Y + X'.Z + Y.Z = X.Y + X'.Z \quad (\text{where } X' \text{ represents NOT } X)$$
- i) Write down the dual of this expression. (2)
- ii) Prove the Consensus theorem by truth table or otherwise. (4)
- b. Draw a truth table for the Boolean function **F**, described by the maxterm list $F(A,B,C) = \Pi (0,2,3,7)$ (2)
- Show how this could be implemented using:
- i) 8-to-1 multiplexer (2)
- ii) 4-to-1 multiplexer and a logic inverter (4)
- c. Show how you could construct a 2K byte wide Read Only Memory (ROM) using two 1K byte wide ROM chips. Clearly show any required control lines and describe how your addressing scheme works. (6)

4. a. Explain, with the aid of a truth table, the function of:
- i) 2-to-1 logic multiplexer. (4)
 - ii) 2-to-4 line decoder with active high outputs (4)
- b. Draw the truth table for a two input XNOR gate. Show, using Boolean Algebra and a circuit diagram, how this XNOR gate could be implemented using only AND gates and inverters. (4)
- c. A Moore type state machine is required that can detect a sequence of three consecutive 1's on its serial input line. It has a single bit output Z and a single bit input I which receives the serial input sequence. When a sequence has been detected, the output Z should be set high. The machine should then reset and look for a new sequence, with the next input I .
- Draw a state diagram for this system and a state transition table, clearly labelling the states. A circuit implementation is not required. (8)

NJP/MPF/PIR