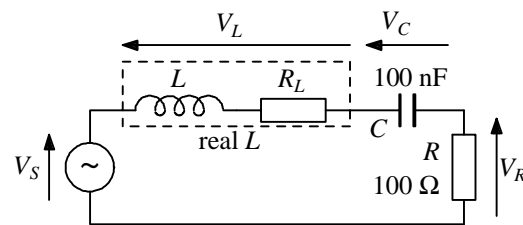


## EEE101 Problem Sheet

# Resonance and Transients

- 1** Measurements on the circuit of figure 1 revealed a resonant frequency of 1.59 kHz and a 3 dB bandwidth,  $\Delta f$  of 199 Hz.

- (i) What is the circuit  $q$  factor? [8]
- (ii) Find the value of  $L$ . [100 mH]
- (iii) What is the value of  $R_L$ . [25  $\Omega$ ]
- (iv) What voltages would be measured at  $V_R$  and  $V_C$  at resonance? [ $0.8V_S$ ,  $8V_S$ ]
- (v) What is the amplitude and phase of  $V_L$  with respect to  $V_R$ ? (a positive value of phase is a phase lead) [ $8V_S$ ,  $+88.6^\circ$ ]




**Figure 1**

- 2** Show that the impedance of the circuit of figure 2 is

$$Z = \frac{j\omega L (1 + j\omega CR)}{1 - \omega^2 LC + j\omega CR}$$

and that its resonant frequency is

$$f = \frac{1}{2\pi\sqrt{LC - C^2 R^2}}.$$

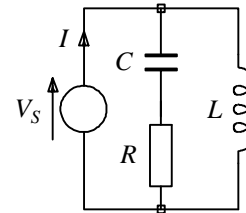


**Figure 2**

- 3** Assume initially that in the circuit of figure 3  $R_C = R_L = R$ . In terms of  $L$  and  $C$ , find the value for  $R$  that will make the circuit resonant at all frequencies. (This one is for experts)

Show that  $R_C = R_L$  is necessary for the "resonant at all frequencies" property to be achieved. (This one is for **real** experts)

**Hint:** For both parts, get the impedance in a form of a ratio of two complex numbers of the form  $(a + jb)/(c + jd)$ . Then try to find a constant,  $k$ , such that  $k(a + jb) = (c + jd)$ . The complex numbers will then cancel out leaving you with impedance =  $k$ .

The combination  $L$  and  $R_L$  can be used to model a wide range of electromagnetic energy converters. One example is a loudspeaker;  $R_L$  is the voice coil resistance and  $L$  is the voice coil inductance. At high audio frequencies, the impedance of the loudspeaker is primarily inductive and this can cause problems for some amplifiers.  $R_C$  and  $C$  form what is called a "Zobel" network (after its inventor) that compensates for the loudspeaker reactance and presents the power amplifier with a resistive load.

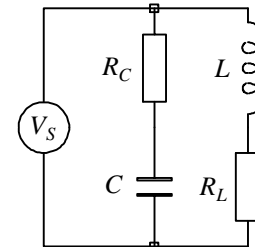

**Figure 3**

- 4 In figure 4,  $V_S$  is a step waveform changing from 0 V to 10 V at time  $t = 0$ . Write down

- (i)  $I$  at  $t = 0^-$ ,  $t = 0^+$  and  $t \Rightarrow \infty$ , [0, 5 mA, 0]  
(ii)  $V_C$  at  $t = 0^-$ ,  $t = 0^+$  and  $t \Rightarrow \infty$ . [0, 0, 10 V]

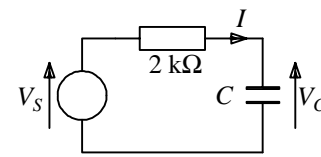


Figure 4

- 5 In the circuit of figure 5,  $V_S$  is a step waveform that is 3 V for all  $t < 0$  and  $-6$  V for all  $t > 0$ . Write down

- (i)  $I_L$  at  $t = 0^-$ ,  $t = 0^+$  and  $t \Rightarrow \infty$ , [1.5 mA, 1.5 mA,  $-3$  mA]  
(ii)  $I$  at  $t = 0^-$ ,  $t = 0^+$  and  $t \Rightarrow \infty$ , [1.5 mA,  $-7.5$  mA,  $-3$  mA]  
(iii)  $V_L$  at  $t = 0^-$ ,  $t = 0^+$  and  $t \Rightarrow \infty$ . [0,  $-9$  V, 0]

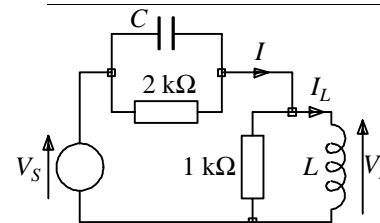


Figure 5

- 6 In the circuit of figure 6,  $V_S$  is a step waveform that is  $-6$  V for all  $t < 0$  and 12 V for all  $t > 0$ . Write down

- (i)  $I$  at  $t = 0^-$ ,  $t = 0^+$  and  $t \Rightarrow \infty$ , [ $-1$  mA,  $-1$  mA, 2 mA]  
(ii)  $V_R$  at  $t = 0^-$ ,  $t = 0^+$  and  $t \Rightarrow \infty$ . [ $-2$  V, 7 V, 4 V]

Note: You may need to do some working out for part (ii).

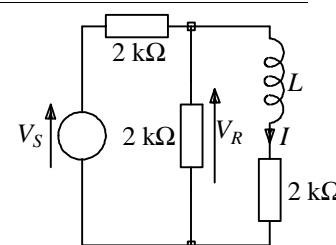


Figure 6

- 7 The switch in figure 7 has been in position **B** for a long time. At  $t = 0$  the switch is switched to position **A**. Find  $I$ , and hence  $V_L$ , as functions of time.

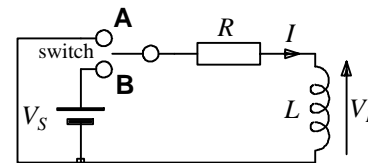


Figure 7

- 8 The circuit of figure 5 is fed by the step waveform shown. Derive a differential equation relating  $V_C$  to  $t$  and solve it to find  $V_C$  as a function of time.

From your expression for  $V_C(t)$ , derive an expression describing  $I_C(t)$ .

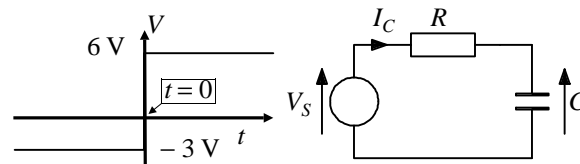


Figure 8

- 9 In figure 9, the switch has been in position **B** for a long time and is suddenly switched to position **A**. Find an expression that gives  $I_L$  as a function of time following the switch from **B** to **A**. Use your result to calculate the voltage across  $R_1$  as a function of time. If  $R_1 = 5$  kΩ and  $R_2 = 1$  kΩ what is the peak voltage across  $R_1$ ? [50 V]

After spending a long time at position **A** the switch is returned to position **B**. Find an expression that describes  $I_L$  as a function of time following the switch from **A** to **B**.

Treat each transient (**B** to **A** and then **A** to **B**) as occurring at  $t = 0$ , that is, be prepared to move your time origin to the point of interest.

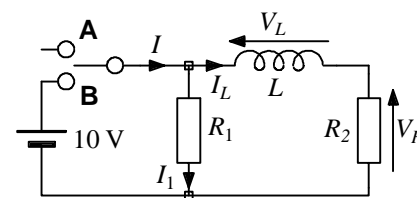


Figure 9