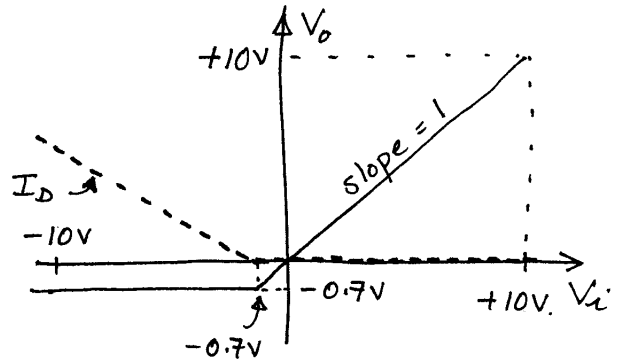


## EEE123 Problem Sheet Solutions


### Diode, Resistor and Capacitor Circuits

- Q1 The diode is on the point of conduction when  $V_o = -0.7V$ . For  $V_i < -0.7V$ , the diode conducts and  $V_o = -0.7V$ . For  $V_i > -0.7V$  the diode does not conduct, no current flows through  $R$  so  $V_o = V_i$ .



$$I_D = \frac{-0.7V - V_i}{R} \text{ for } V_i < -0.7V.$$

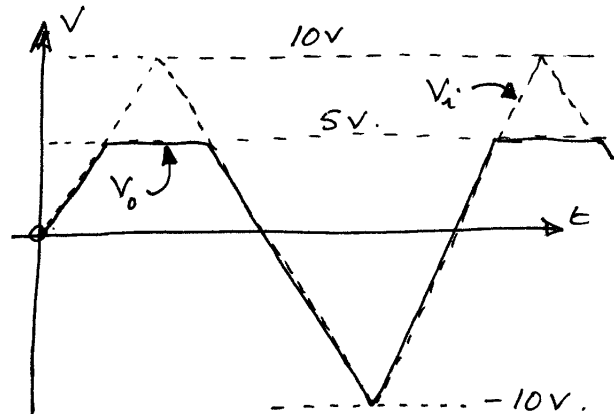- Q2 The diode will be on the point of conduction when  $V_o = 4.3V + 0.7V = 5V$ . For  $V_i > 5V$ ,  $D$  will conduct and  $V_o$  will be held (by  $D$ ) at  $5V$ . For  $V_i < 5V$ , no current flows through  $R$  and so  $V_o = V_i$ .



$I_{f \max}$  occurs when the biggest  $V$  exists across  $R$  — ie, at the positive peak of  $V_i$ .  $I_{f \max} = \frac{10V - 5V}{R} = \underline{\underline{5mA}}$ .


- Q3 It will be  $D_1$  that clips voltages that are too high and  $D_2$  that clips voltages that are too low.

For  $D_1$  to clip  $V_i$  at  $3.3V$ ,  $V_1 = 3.3V - 0.7V = \underline{\underline{2.6V}}$ .

For  $D_2$  to clip  $V_i$  at  $0V$ ,  $V_2 = 0 + 0.7V = \underline{\underline{0.7V}}$ .

(2)

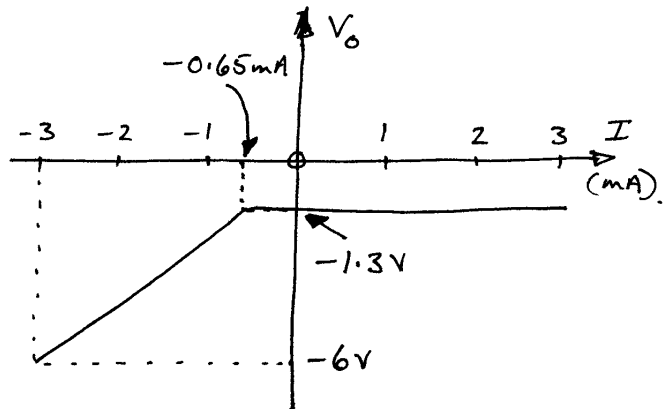Q4 The diode will be on the point of conduction if  $V_o = -2V + 0.7V = -1.3V$ . The value of  $I_i$  that will give a  $V_o$  of  $-1.3V$  with a diode current of zero is  $I_i = \frac{-1.3V}{2k\Omega} = -0.65mA$ .




For  $I_i < -0.65mA$ , there is no conduction through the diode so all  $I_i$  goes through  $R$  and  $V_o = I_i R$ . For  $I_i > -0.65mA$ , the diode conducts and  $V_o$  is held at  $-1.3V$ .

(3)

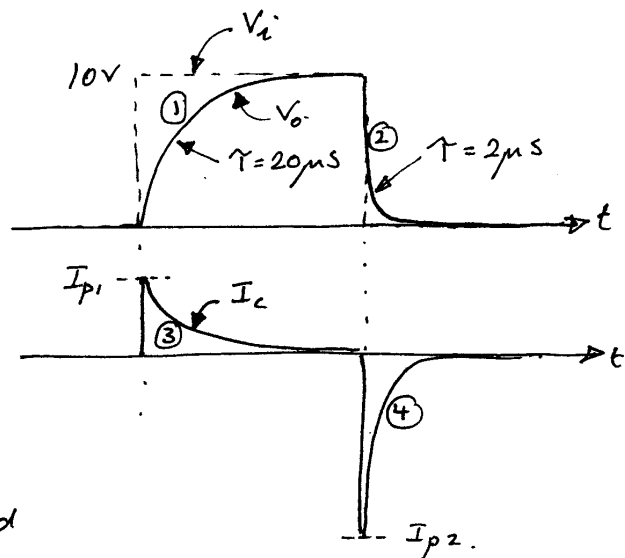Q5 (a)  $\tau$  is much shorter than the pulse width so  $V_o$  has reached  $V_i$  by the end of the pulse.

On rising edge, D is reverse biased so current flows through  $R_2$  to charge C.

On falling edge, D is forward biased so C discharges through  $R_1$  and  $R_2$  in parallel.



$I_{p1}$  occurs on leading edge transient....

$$I_{p1} = \frac{V_i}{R_2} = \frac{10V}{2k\Omega} = \underline{\underline{5mA}}$$

$I_{p2}$  occurs on trailing edge transient....

$$I_{p2} = -\frac{V_i}{R_1 \parallel R_2} = -\frac{10V}{200\Omega} = \underline{\underline{-50mA}}$$

The four exponential relationships are.

$$\textcircled{1} V(t) = 10(1 - e^{-t/20\mu s})$$

$$\textcircled{2} V(t) = 10e^{-t/2\mu s}$$

$$\textcircled{3} I(t) = 5mA e^{-t/20\mu s}$$

$$\textcircled{4} I(t) = -50mA e^{-t/2\mu s}$$

Output pulse width at half height....

→ time for ① to reach half height is given by

$$5 = 10(1 - e^{-t_1/20\mu s})$$

which leads to  $t_1 = 13.86\mu s$ .

→ time for ② to fall to half height is given by

$$5 = 10e^{-t_2/2\mu s}$$


which leads to  $t_2 = 1.37\mu s$ .

$$\begin{aligned} \therefore \text{output pulse width} &= 100\mu s - t_1 + t_2 \\ &= (100 - 13.86 + 1.37)\mu s \\ &= \underline{\underline{87.53\mu s}} \end{aligned}$$

(4)

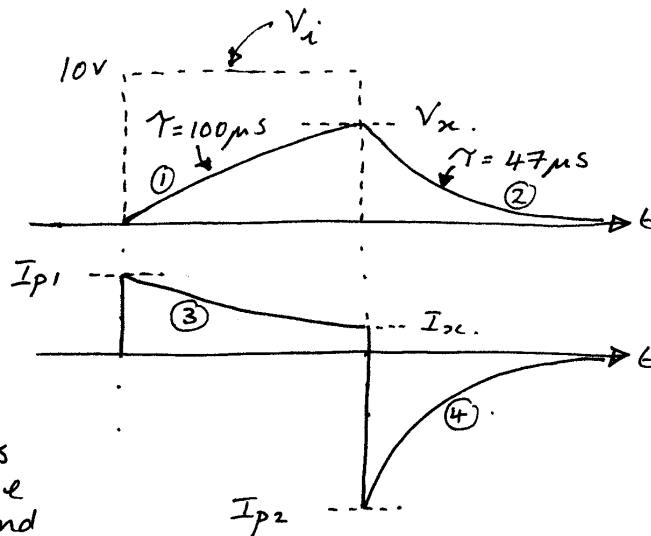Q5 (b) In this circuit  $D_2$  is forward biased by the leading edge and  $D_1$  by the trailing edge. In

other words, C charges via  $R_2$  and discharges via  $R_1$ . The charging time constant,  $CR_2$  is of the same order as the pulse width so the value of  $V_o$  at the end of the pulse,  $V_x$ , will have to be calculated.



The four exponentials are ....

$$\textcircled{1} \quad V(t) = 10(1 - e^{-t/100\mu s})$$

$$\textcircled{2} \quad V(t) = V_x e^{-t/47\mu s}$$

$$\textcircled{3} \quad I(t) = I_{p1} e^{-t/100\mu s}$$

$$\textcircled{4} \quad I(t) = I_{p2} e^{-t/47\mu s}$$

We need  $V_x$  in order to find  $I_{p1}$  and  $I_{p2}$ , so using  $\textcircled{1}$   $V_x = 10(1 - e^{-100\mu s/100\mu s}) = 6.32V$

$$I_{p1} = \frac{V_i}{R_2} = \frac{10V}{10k\Omega} = 1mA$$

$$I_{xc} = \frac{V_i - V_x}{R_2} = \frac{10 - 6.32}{R_2} = 0.368mA$$

$$I_{p2} = -\frac{V_x}{R_1} = -\frac{6.32}{4.7k\Omega} = -1.34mA$$


time for  $\textcircled{1}$  to reach 5V given by  
 $5 = 10(1 - e^{-t_1/100\mu s})$  or  $t_1 = 69.3\mu s$

time for  $\textcircled{2}$  to fall to 5V given by  
 $5 = 6.32 e^{-t_2/47\mu s}$  or  $t_2 = 11\mu s$

$$\begin{aligned} \text{output pulse width} &= 100\mu s - 69.3\mu s + 11\mu s \\ &= \underline{41.7\mu s} \end{aligned}$$

(5)

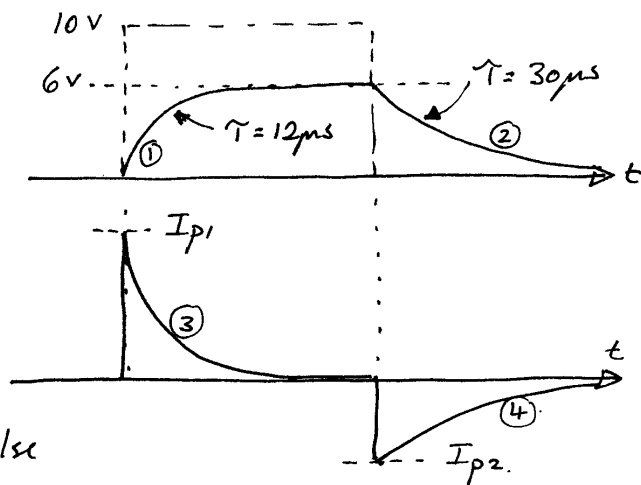Q5 (c) In this circuit the diode conducts when  $V_i = 10\text{V}$  but does not conduct for  $V_i = 0\text{V}$ . During the pulse,  $C$  charges via  $R_1$  but  $R_1$  also supplies current through  $R_2$  leading to an aiming voltage that is a potentially divided version of the input pulse amplitude.



The four exponentials are

①  $V(t) = 6(1 - e^{-t/\tau_1})$  where  $\tau_1 = CR_1 || R_2 = 12\mu\text{s}$ .

②  $V(t) = 6e^{-t/\tau_2}$  where  $\tau_2 = CR_2 = 30\mu\text{s}$ .

③  $I(t) = I_{p1} e^{-t/\tau_1}$

④  $I(t) = I_{p2} e^{-t/\tau_2}$

$I_{p1} = \frac{V_i}{R_1} = 5\text{mA}$ . [On the leading edge,  $V_o$  is initially zero so all  $V_i$  appears across  $R_1$ .]

$I_{p2} = -\frac{6\text{V}}{R_2} = -2\text{mA}$ . [On the trailing edge,  $D$  is reverse biased so  $C$  discharges through  $R_2$ ]

Half height of  $V_o$  is  $3\text{V}$ . The time it takes ① to reach  $3\text{V}$  is given by

$$3 = 6(1 - e^{-t_1/12\mu\text{s}}) \quad \text{or} \quad t_1 = 8.3\mu\text{s}.$$

Time taken for  $V_o$  to fall to  $3\text{V}$  after trailing edge is given by

$$3 = 6e^{-t_2/30\mu\text{s}} \quad \text{or} \quad t_2 = 20.8\mu\text{s}.$$

$$\begin{aligned} \text{pulse width} &= 100\mu\text{s} - 8.3\mu\text{s} + 20.8\mu\text{s} \\ &= \underline{\underline{112.5\mu\text{s}}}. \end{aligned}$$