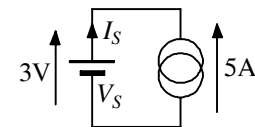


## EEE101 Problem Sheet

# Sources, Resistors and Circuits


**Q1** The circuit of figure 1 shows a 5A current source connected to a 3V voltage source.

- (i) What is the value of  $I_S$ ? [-5A]
- (ii) One source is acting as an energy source and the other as an energy sink; which one is acting as an energy source? [5A]
- (iii) How much power is the driving source delivering? [15W]



**Figure 1**

**Q2** For the circuit diagrams of figure 2, identify the the circuits by which the source can drive current from its positive end, around a circuit to its negative end. Define the circuits by writing down the current path in terms of node numbers and components (eg: 7,  $R_4$ , 3,  $R_6$ , 1,  $R_2$ , 5). [1,  $R_1$ , 2; 1,  $R_1$ , 2,  $R_2$ , 4; 1,  $R_1$ , 2,  $R_3$ , 4,  $R_2$ , 3; 1,  $R_1$ , 3,  $R_2$ , 2 and 1,  $R_1$ , 3,  $R_3$ , 2; 1,  $R_1$ , 2 and 1,  $R_2$ , 3,  $R_4$ , 2 and 1,  $R_3$ , 3,  $R_4$ , 2; 1,  $R_1$ , 2 and 1,  $R_3$ , 4,  $R_5$ , 2]

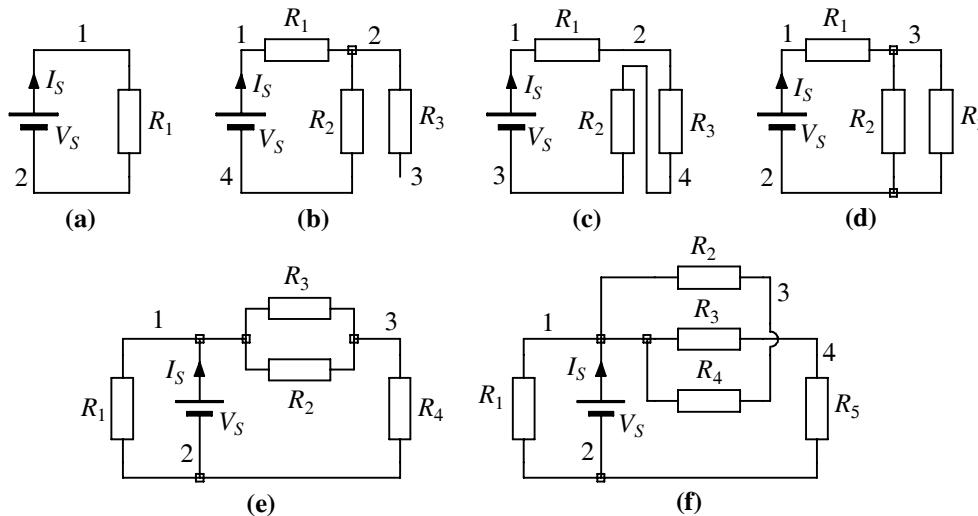


**Figure 2**

**Q3** In the circuits of figure 2,  $R_1=1\Omega$ ,  $R_2=2\Omega$ ,  $R_3=3\Omega$ ,  $R_4=4\Omega$ ,  $R_5=5\Omega$  and  $V_S=10V$ .


- (i) Find  $I_S$  for each circuit. [10.00A, 3.33A, 1.67A, 4.55A, 11.92A, 11.25A]
- (ii) Find the voltage across  $R_3$  for each of circuits (b) to (e) giving the node number at the positive end of that voltage difference in each case. [0V; 5V,2; 5.45V,3; 2.31V,1; 3.75V,1]
- (iii) For each circuit, find the power delivered by the source and the power dissipated in  $R_2$  (where  $R_2$  exists). [100,-; 33.3,22.2; 16.7,5.6; 45.5,14.9; 119.2,2.7; 112.5,0; units all W]

**Q4** The resistors in this question all have a resistance of  $1\text{ k}\Omega$  unless indicated otherwise. For parts (4.1) to (4.9) of this question evaluate

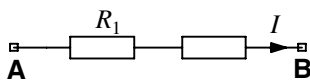
- (i) the resistance between terminals **A** and **B**
- (ii) the current,  $I$ , assuming that the network is driven by a  $10\text{ V}$  source with its positive end at **A**
- (iii) the voltage across  $R_1$  in each circuit.
- (iv) the value of  $I$  if the  $10\text{ V}$  voltage source was changed into a  $10\text{ mA}$  current source driving a positive current into node **A**




4.1

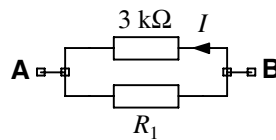


4.2

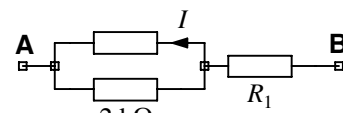


4.3

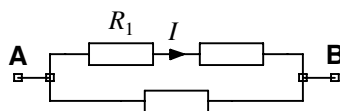


4.4

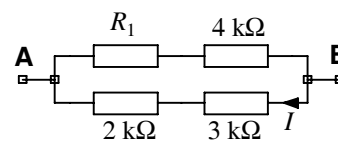


4.5

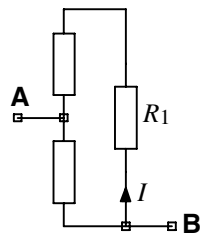


4.6

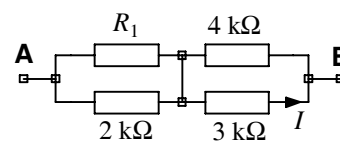

4.7

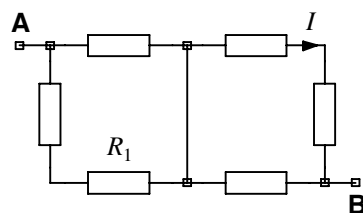

4.8

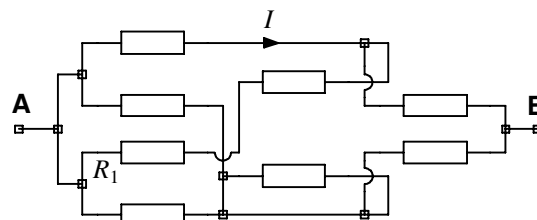

4.9