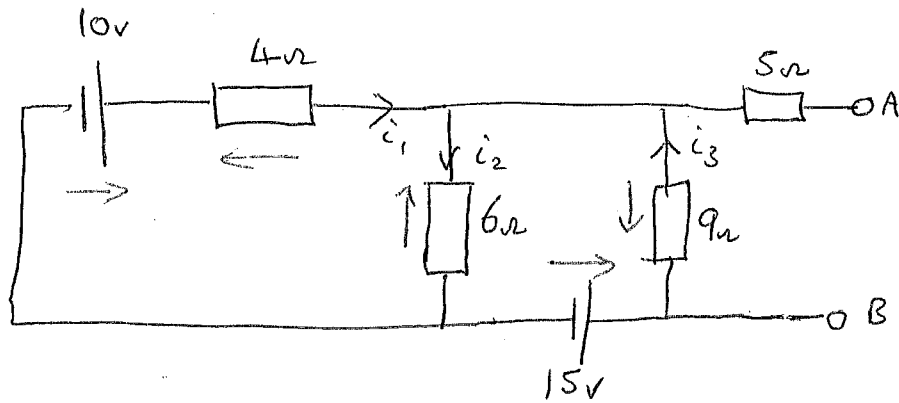


# QUESTION 1

1

(a) (i)



Clearly current through  $5\Omega = 0A$ .

Using Kirchhoff's laws:

$$10 - 4i_1 - 6i_2 = 0 \quad (1)$$

$$15 - 9i_3 - 6i_2 = 0 \quad (2)$$

$$i_1 + i_3 = i_2 \quad (3)$$

Substituting (3) into (1) and (2) gives

$$10 - 4i_1 - 6i_1 - 6i_3 = 0 \Rightarrow 10 - 10i_1 - 6i_3 = 0 \quad (4)$$

$$15 - 9i_3 - 6i_1 - 6i_3 = 0 \Rightarrow 15 - 15i_3 - 6i_1 = 0 \quad (5)$$

Multiply (4) by 5 and (5) by 2 gives

$$50 - 50i_1 - 30i_3 = 0$$

$$30 - 12i_1 - 30i_3 = 0$$

Subtracting:  $20 - 38i_1 = 0 \Rightarrow i_1 = \frac{20}{38} = \underline{\underline{0.526A}} \rightarrow$

Back substituting into (4):

$$10 - 5.26 = 6i_3 \Rightarrow i_3 = \underline{\underline{0.79A}} \uparrow$$

and into (3):

$$i_2 = 0.526 + 0.79 = \underline{\underline{1.316A}} \downarrow$$

(5)


QUESTION 1 (CONTINUED)

2

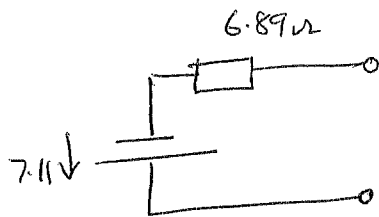- (ii) For Thevenin we require the open circuit voltage between A & B, which is equal to the voltage across the  $9\Omega$  resistor:

$$V_{TH} = i_3 \times 9 = 0.79 \times 9 = \underline{\underline{7.11\text{ V}}} \downarrow$$

$$R_{TH} = 5 + \frac{1}{\frac{1}{4} + \frac{1}{6} + \frac{1}{9}} = \underline{\underline{6.89\Omega}}$$



(3)

(b) (i)

$$\text{Since } P = VA \cos \phi \Rightarrow VA = \frac{P}{\cos \phi} = \frac{400}{0.8} = \underline{\underline{500\text{ KVA}}}$$

$$\text{and the current is } I = \frac{VA}{V} = \frac{500000}{6600} = \underline{\underline{75.8\text{ A}_{rms}}}$$

(1)

- (ii) The reactive power is:

$$Q = 500 \sin(\cos^{-1} 0.8) = \underline{\underline{300\text{ KVAR}}}$$

(1)

- (c) (i) For the motor load,  $360\text{ KVA}$  at  $0.7$  lagging:

$$P = 360 \times 0.7 = 252\text{ kW}$$

$$Q = 360 \times \sin(\cos^{-1} 0.7) = 257\text{ KVAR}$$

For the heaters:

$$P = 100\text{ kW} \quad Q = 0\text{ KVAR}$$

Hence the total real and reactive power is:

$$P_T = 400 + 100 + 252 = 752\text{ kW}$$

$$Q_T = 300 + 0 + 257 = 557\text{ KVAR}$$

$$\therefore \text{KVA} = \sqrt{752^2 + 557^2} = \underline{\underline{935.8\text{ KVA}}}$$

(5)

# QUESTION 1 (CONTINUED)

3

(ii) Power factor =  $\cos \phi$

$$= \frac{P}{S} = \frac{752}{935.8} = \underline{\underline{0.803 \text{ lagging}}} \quad (1)$$

(iii) To correct the power factor to unity the capacitor must supply 557 KVAR.

$$\text{Since } \frac{V^2}{X_c} = Q \Rightarrow X_c = \frac{V^2}{Q} = \frac{6600^2}{557000} = 78.2 \Omega$$

$$\text{Since } X_c = \frac{1}{2\pi f C} \Rightarrow C = \frac{1}{2\pi f X_c} = \frac{1}{2\pi \cdot 50 \cdot 78.2} = \underline{\underline{40 \mu F}} \quad (3)$$

(iv) The peak voltage seen by the capacitor is:


$$V_{c \text{ peak}} = 6600 \times \sqrt{2} = \underline{\underline{9334 V}} \quad (1)$$

and  $I_{c \text{ peak}} = \frac{9334}{78.2} = \underline{\underline{119.4 A}}$

## QUESTION 2

4

(a) (i)

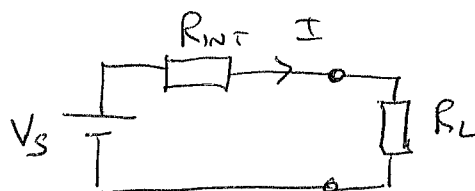

The current flowing in the load is given by:

$$I = \frac{V_s}{(R_{INT} + R_L)}$$

Therefore the power dissipated in the load is

$$P_L = I^2 R_L = \frac{V_s^2 \cdot R_L}{(R_{INT} + R_L)^2}$$

①

(ii) For maximum power in the load, rearrange above expression:

$$P_L = \frac{V_s^2 R_L}{(R_{INT} + R_L)^2} = \frac{V_s^2}{\frac{R_{INT}^2}{R_L} + \frac{2R_{INT} \cdot R_L}{R_L} + \frac{R_L^2}{R_L}}$$

$P_L$  is maximum when the denominator is minimum:

$$\text{i.e. } \frac{d}{dR_L} \left( \frac{R_{INT}^2}{R_L} + 2R_{INT} + R_L \right) = 0$$

$$\therefore -\frac{R_{INT}^2}{R_L^2} + 1 = 0 \Rightarrow R_L^2 = R_{INT}^2$$

or  $R_L = R_{INT}$

③

(iii)

$$\text{Efficiency} = \frac{I^2 R_L}{I^2 (R_{INT} + R_L)} \times 100 = \frac{R_L}{R_{INT} + R_L} \times 100\%$$

$$\text{When } R_{INT} = R_L \text{ efficiency} = \frac{R_L}{2R_L} \times 100 = \underline{\underline{50\%}}$$

①

## QUESTION 2 (CONTINUED)

5

(b) (i) The resistance of the network is:

$$R_T = \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}} = \frac{1}{\frac{1}{45} + \frac{1}{90}} = \underline{\underline{30\Omega}} \quad (1)$$

(ii) The current flowing through  $R_3 + R_4$ :

$$I_{34} = \frac{V}{R_3 + R_4} = \frac{60}{90} = \underline{\underline{0.667A}} \quad (1)$$


(iii) The power dissipated in  $R_3 = I_{34}^2 \cdot R_3 = 0.667^2 \cdot 50 = \underline{\underline{22.24W}}$

The total power dissipated in the network is:

$$P_T = \frac{V^2}{R_T} = \frac{60^2}{30} = \underline{\underline{120W}} \quad (2)$$

(iv) The voltage across  $R_2$  is  $\frac{30}{45} \times 60 = \underline{\underline{40V}} \quad (1)$

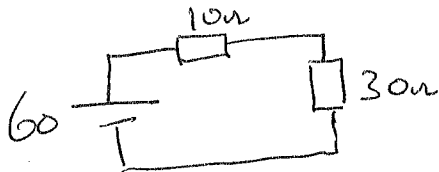(c) The internal resistance is now  $10\Omega$ :



Therefore the total current flowing reduces to  $\frac{60}{40} = 1.5A$

and hence the voltage across each branch of the load will be

$$30 \times 1.5 = 45V$$

$$(\text{or alternatively } 60 - 10 \times 1.5 = 45V)$$

The voltage across  $R_1$  is:

$$V_{R1} = \frac{15}{45} \times 45 = \underline{\underline{15V}} \quad (3)$$

## QUESTION 2 (CONTINUED)

6

(ii) The current through  $R_3$  is:

$$I_{34} = \frac{45}{90} = 0.5 \text{ A}$$

Hence power dissipated in  $R_3$

$$P_{R3} = I_{34}^2 \cdot R_3 = 0.5^2 \cdot 50 = \underline{\underline{12.5 \text{ W}}}$$

Power dissipated in the internal resistance is:

$$P_{INT} = 1.5^2 \times 10 = \underline{\underline{22.5 \text{ W}}}$$

3


(iii) The total power drawn from the source is

$$P_T = V \cdot I = 60 \times 1.5 = 90 \text{ W}$$

$$\therefore \text{Efficiency} = \frac{90 - 22.5}{90} \times 100 = \underline{\underline{75\%}}$$

1

(iv) The circuit now becomes:

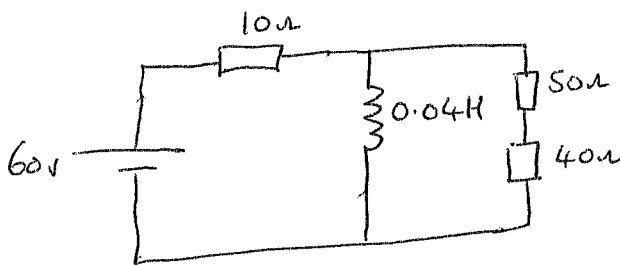

On DC the inductor appears as a short circuit since

$$\frac{dI}{dt} = 0 \text{ and hence } V_L = L \frac{dI}{dt} = 0 \text{ so there can be}$$

no current flowing down the branch containing  $R_3$  and  $R_4$   
and hence the power dissipated in  $R_3$  is zero

3

$$\text{The current is then } I = \frac{60}{10} = 6 \text{ A}$$

$$\text{Hence the energy stored in the inductor} = \frac{1}{2} L I^2 = \frac{1}{2} \cdot 0.04 \cdot 6^2 = \underline{\underline{0.72 \text{ J}}}$$

### QUESTION 3

7

(a) Since the secondary impedance  $Z_2 = \frac{V_2}{I_2}$  and given that  $\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$


$$\text{then } Z_2 = \frac{V_2}{I_2} = \frac{V_1 N_2}{N_1} \times \frac{N_2}{N_1 I_1} = \left( \frac{N_2}{N_1} \right)^2 \cdot \frac{V_1}{I_1}$$

Therefore the reflected impedance at the primary side

$$Z_1 = \frac{V_1}{I_1} = \left( \frac{N_1}{N_2} \right)^2 \cdot Z_2$$

2

(b)

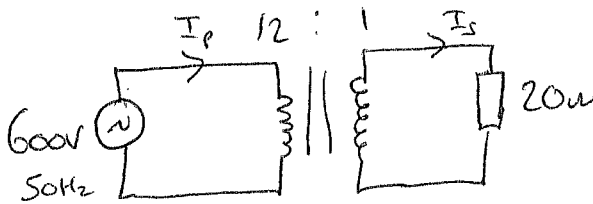

$$\text{Since } \frac{V_p}{V_s} = \frac{N_p}{N_s} \Rightarrow V_s = \frac{V_p \cdot N_s}{N_p} = \frac{600 \cdot 1}{12} = \underline{\underline{50V}}$$

$$\text{Now } I_s = \frac{V_s}{R_s} = \frac{50}{20} = \underline{\underline{2.5 \text{ Arms}}}$$

$$\text{and since } \frac{I_p}{I_s} = \frac{N_s}{N_p} \Rightarrow I_p = \frac{I_s \cdot N_s}{N_p} = \frac{2.5 \times 1}{12} = \underline{\underline{0.208 \text{ Arms}}}$$


$$\text{The power dissipated in the load} = I_s^2 R_s = 2.5^2 \times 20 = \underline{\underline{125W}}$$

3

# QUESTION 3 (CONTINUED)

8

(ii) The load now comprises:

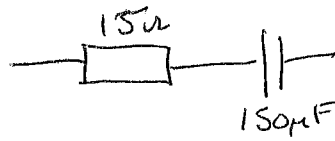

$$\therefore Z = 15 - \frac{j}{2\pi \times 50 \times 150 \times 10^{-6}} = 15 - j21.22 = 25.98 \angle -54.7^\circ$$

The secondary voltage remains unchanged at 50Vrms

$$I_s = \frac{50 \angle 0^\circ}{25.98 \angle -54.7^\circ} = \underline{\underline{1.925 \angle 54.7^\circ \text{ Arms}}}$$

$$I_p = \frac{1.925 \angle 54.7^\circ}{12} = \underline{\underline{0.16 \angle 54.7^\circ \text{ Arms}}}$$

④

Power dissipated in the load is,  $P = I_s^2 R_L = 1.925^2 \times 15 = \underline{\underline{55.6 \text{ W}}}$

(iii) The input power factor is  $\cos 54.7^\circ = \underline{\underline{0.58 \text{ leading}}}$

The VA rating is  $600 \times 0.16 = \underline{\underline{96 \text{ VA}}}$   
(or  $50 \times 1.925 = 96 \text{ VA}$ )

②


(iv) Since  $V_p = 4.44 f N \phi_{\text{MAX}}$

$$600 = 4.44 \times 50 \times N_p \times 5 \times 10^{-3} \Rightarrow N_p = \underline{\underline{541 \text{ TURNS}}}$$

and  $50 = 4.44 \times 50 \times N_s \times 5 \times 10^{-3} \Rightarrow N_s = \underline{\underline{45 \text{ TURNS}}}$

①

c.

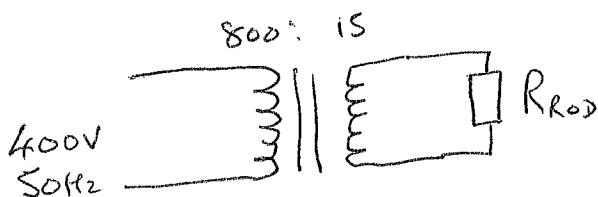

$$(v) V = 4.44 \times 60 \times 541 \times 5 \times 10^{-3} = \underline{\underline{720.6 \text{ V}}}$$

①

First calculate the resistance of the rod at both temperatures:

$$R_o = \frac{\rho L}{A} = \frac{8.33 \times 10^{-8} \times 0.6 \times 4}{\pi \times 0.008^2} = 9.94 \times 10^{-4} \Omega$$



### QUESTION 3 (CONTINUED)

9

Now at  $40^{\circ}\text{C}$

$$R_{40} = R_0(1 + \alpha_0 T) = 9.94 \times 10^{-4} (1 + 6 \times 10^{-3} \times 40) \\ = 1.23 \times 10^{-3} \Omega$$

$$R_{650} = R_0(1 + \alpha_0 T) = 9.94 \times 10^{-4} (1 + 6 \times 10^{-3} \times 650) \\ = 4.87 \times 10^{-3} \Omega$$

The secondary voltage of the transformer is:

$$V_s = \frac{400}{800} \times 15 = 7.5 \text{ V}_{\text{rms}}$$

At  $40^{\circ}\text{C}$  the power dissipated is:

$$P_{40} = \frac{V^2}{R_{40}} = \frac{7.5^2}{1.23 \times 10^{-3}} = \underline{\underline{45.7 \text{ kW}}}$$

At  $650^{\circ}\text{C}$  the power dissipated is:

$$P_{650} = \frac{7.5^2}{4.87 \times 10^{-3}} = \underline{\underline{11.5 \text{ kW}}}$$

5

(ii) Since the load is purely resistive the power factor is unity

$$P_{40} = V_p \cdot I_{P40} \Rightarrow I_{P40} = \frac{45700}{400} = \underline{\underline{114.25 \text{ Arms}}}$$

1

$$P_{650} = V_p I_{P650} \Rightarrow I_{P650} = \frac{11500}{400} = \underline{\underline{28.75 \text{ Arms}}}$$



(iii) If the transformer has an efficiency of 96% then if the output is 45.7 kW the input power is:

$$P_{\text{IN}} = \frac{45.7}{0.96} = \underline{\underline{47.6 \text{ kW}}}$$

1

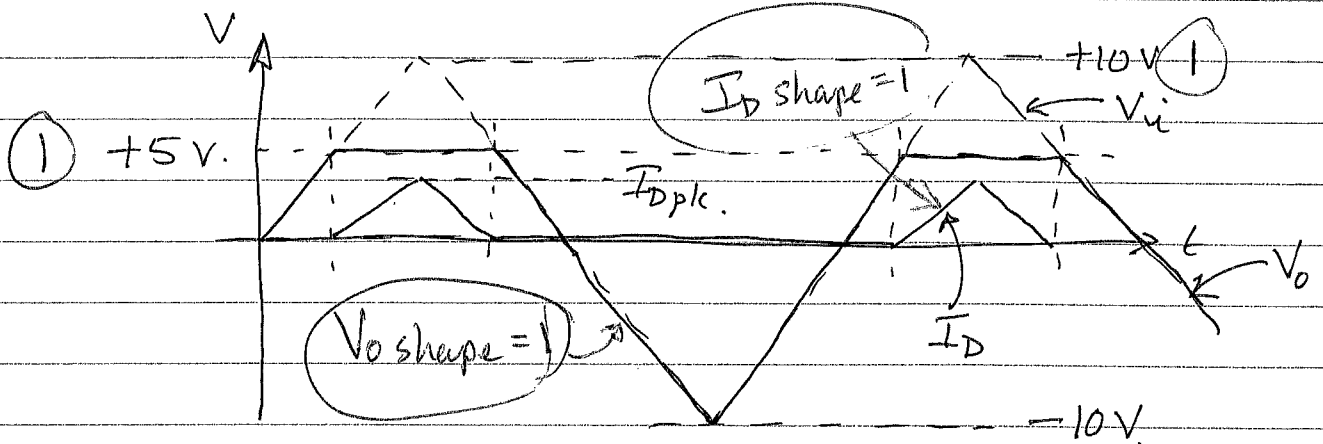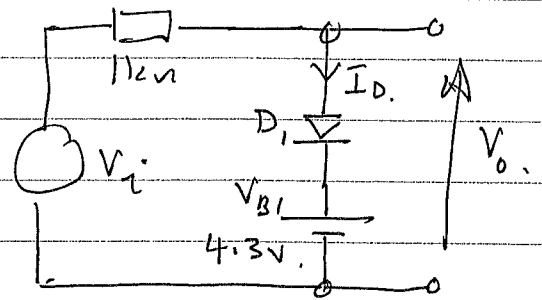Q4 a

$D_1$  will be on the point of conduction when  $V_i = 5V (= 4.3 + 0.7)$ .  $D_1$  will conduct for  $V_i > 5V$ .




$$I_{DPK} = \frac{10V - 5V}{1k\Omega} = \underline{5mA} \quad (1)$$

If  $D_2$  &  $V_{B2}$  are now added,  $D_2$  will be on point of conduction when  $V_i = V_{B2} - 0.7$  and will conduct for  $V_i < V_{B2} - 0.7$ . If the point of conduction of  $D_2$  is required to be  $-1V$

$$-1 = V_{B2} - 0.7 \quad \text{or} \quad \underline{V_{B2} = -0.3V} \quad (1)$$


b (i) The ckt is a half-wave rectifier. (1)

(ii)

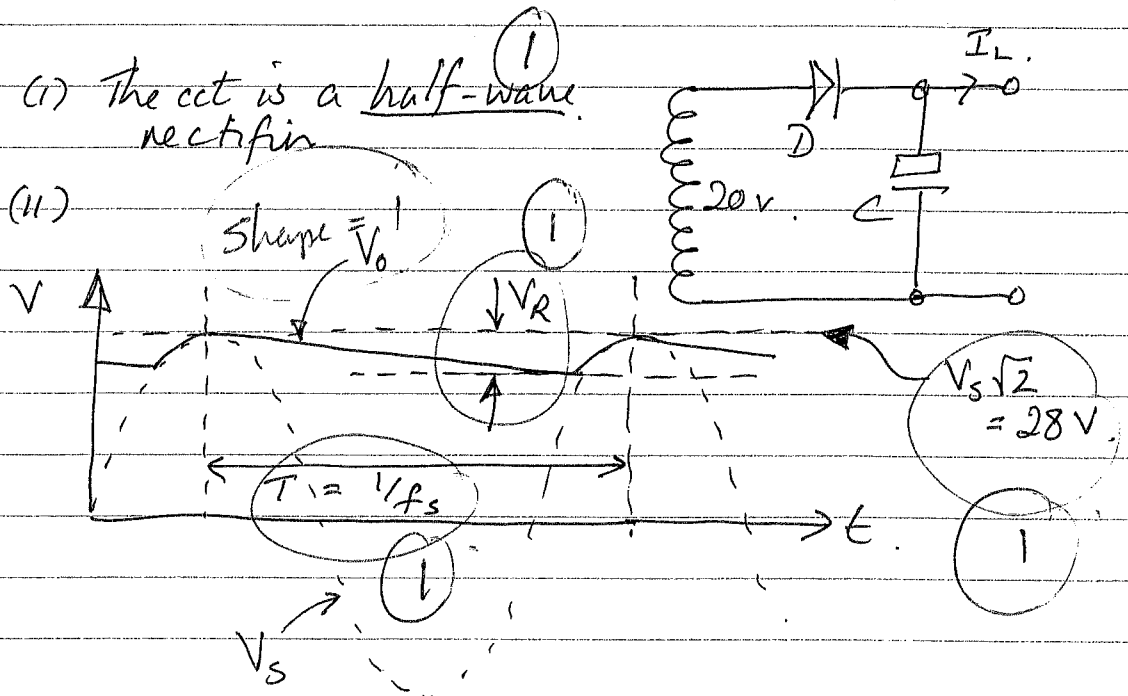

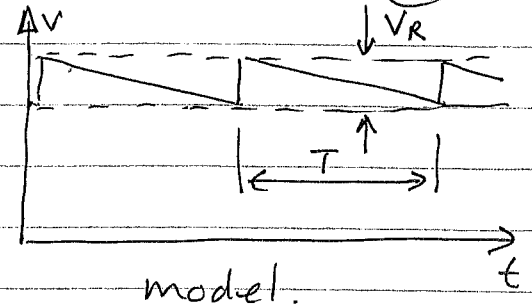- (iii) assume that  $C$  charges instantaneously (1)  
 assume that  $I_L$  remains constant... (1)

$$I_L = C \frac{dV}{dt} = C \frac{V_R}{T} \quad (1)$$



The longer  $T$  is, the bigger will be  $V_R$  for a given  $C$  so we must choose the lowest possible input frequency as the basis for  $T$ . (1)


$$\therefore I_L = 0.15 = C \frac{2}{1/380} \quad (1)$$

$$\text{or } C = \frac{0.15}{2 \times 380} = \underline{\underline{197 \mu F}} \quad (1)$$

- (iv) The energy supplied to the load during the discharge period is replaced over a short interval near the peaks of the charging half cycles (true half cycles in this case). (1)

This kind of very peaky current demand creates a significantly higher loss in the generation and distribution system than a sinusoidal current demand with equivalent load power. (1)

Q5 (a)

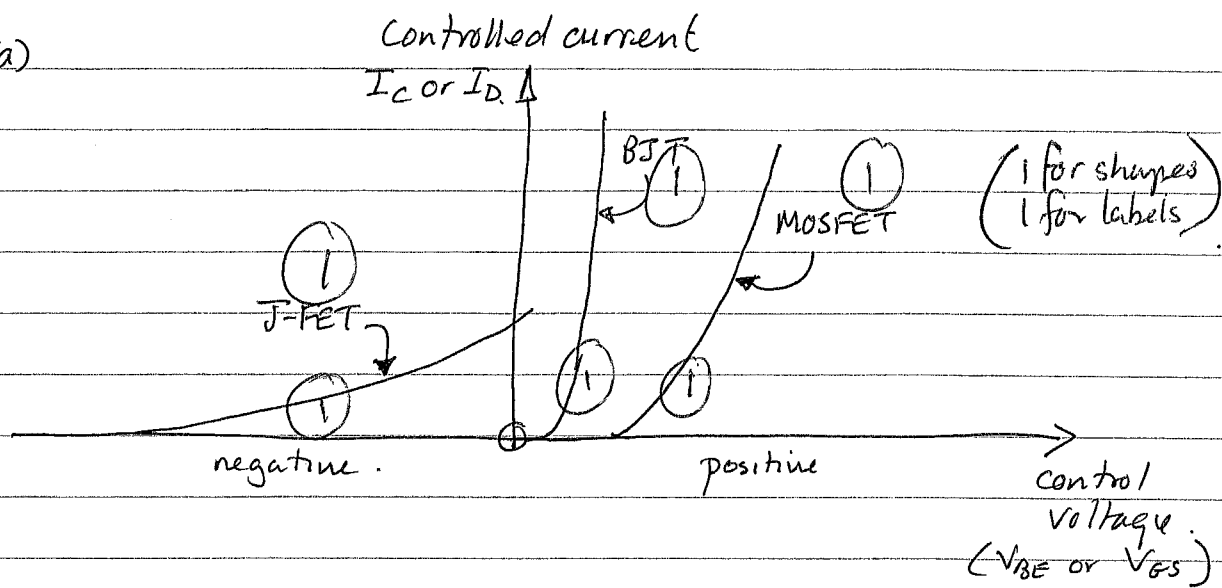

(b)(i) cold lamp resistance =  $0.6 \Omega$

$\therefore$  Initial current

$$= \frac{12}{0.6} = 20A$$

(2)

(ii) under normal running conditions the lamp dissipates 50W with a 12V supply. (1)

$$\therefore 50 = \frac{12^2}{R_{\text{lamp (hot)}}$$

$$R_{\text{lamp (hot)}} = 2.88 \Omega$$


$$\text{normal running current} = \frac{50W}{12V} = 4.17A$$

(iii) worst case  $I_B$  required =  $\frac{\text{worst case } I_C}{h_{FE}}$  (1)

$$= \frac{20A}{h_{FE}} = 0.2A$$


$$\text{Voltage across } R_B = 5 - 0.7$$
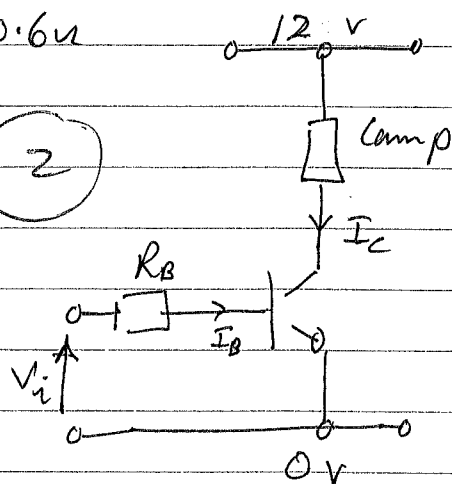
$$\therefore R_B = \frac{5 - 0.7}{I_{B \max}} = \frac{5 - 0.7}{0.2A} = 21.5 \Omega$$



c The problem with inductive loads is that they store energy. (1)

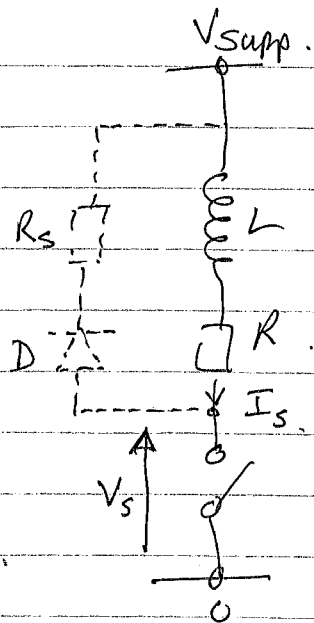When the switch switches off the inductive stored energy tries to keep the current flowing so  $V_s$  rapidly rises and, if not controlled, will rise to levels that will cause damage. (1)



One way of limiting the rise of  $V_s$  is to provide a path for the inductive current —  $D$  +  $R_s$  will provide such a path in the circuit above.  $R_s$  is not essential but  $D$  is... when  $V_s$  rises to  $V_{supp} + 0.7$   $D$  conducts and provides a path for the inductor current. The inductive stored energy is then dissipated in  $R$  and  $D$  (and  $R_s$  if it is present). (1)

Q6 a

analogue

low output resistance

high voltage gain

high input impedance

differential input

(1)  
(1)  
(1)  
(1)  
(1)


b

(i) inverting

(1)

(ii) The op-amp's inverting input is the virtual earth node.

(1)

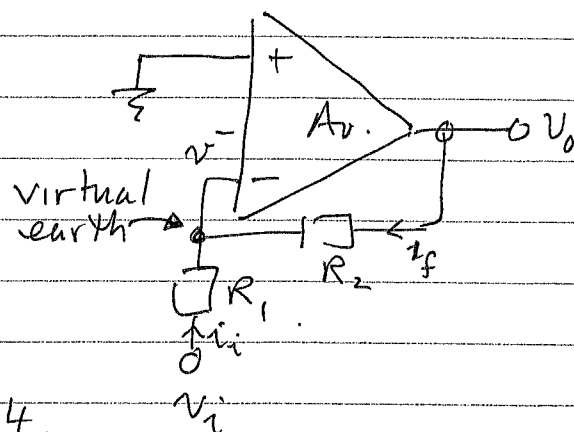

to get a gain of 24,

$$R_2/R_1 = 24$$

(1)

$v_o$  is  $\pm 180^\circ$  w.r.t.  $v_i$

(1)

(iii) If  $A_v$  is finite ... sum currents at  $v^-$  node

$$i_i + i_f = 0$$

(1)

$$\frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} = 0$$

$$\text{or } v^- = \frac{v_i R_2}{R_1 + R_2} + \frac{v_o R_1}{R_1 + R_2}$$

(1)

using the op-amp equation ...

$$v_o = A_v (v^+ - v^-) = -A_v v^- \quad (\text{since } v^+ = 0)$$


(1)

$$\text{or } \frac{v_o}{A_v} = v^- = -\frac{v_i R_2}{R_1 + R_2} - \frac{v_o R_1}{R_1 + R_2}$$

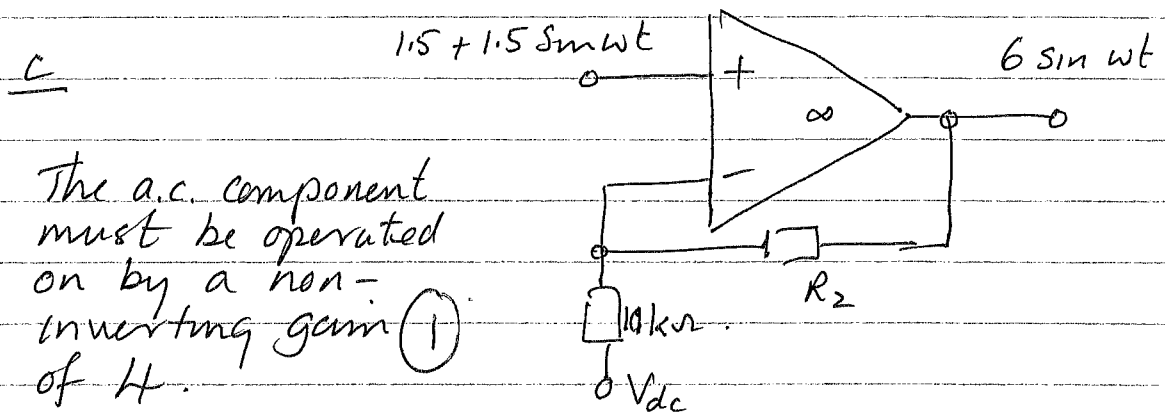(1)

$$\text{or } v_o \left[ \frac{1}{A_v} + \frac{R_1}{R_1 + R_2} \right] = -\frac{v_i R_2}{R_1 + R_2}$$

or 
$$\frac{V_o}{V_i} = - \frac{R_2 / (R_1 + R_2)}{\frac{1}{A_v} + R_1 / (R_1 + R_2)} \quad (1)$$



$$4 = \frac{10k\Omega + R_2}{10k\Omega}$$

$$\therefore \underline{R_2 = 30k\Omega} \quad (1)$$

The total dc component at the output must be zero ....

$$V_o / \text{due to } 1.5V \text{ on } v^+ = 4 \times 1.5 = 6V \quad (1)$$

$$V_o / \text{due to } V_{dc} = - \frac{R_2}{10k\Omega} \times V_{dc} = -3V_{dc} \quad (1)$$

$$\text{Total must} = 0$$

$$\text{so } 6V + (-3V_{dc}) = 0 \quad (1)$$

$$\text{or } \underline{V_{dc} = 2V} \quad (1)$$