

① VSI

SPWM

linear op. mode

$R_L \quad R = 1 \Omega \quad L = 3 \text{ mH}$

$\hat{V}_{oN} = 250 \text{ V}$

$V_d = 600 \text{ V}$

$f_o = 50 \text{ Hz}; \omega_o = 2\pi f_o = 314 \frac{\text{rad}}{\text{s}}$


$\hat{I}_{pN} = 10 \text{ A}$

$\cos \theta = 0.7 \Rightarrow \theta = 45.6^\circ$


1 a) 4

$f_{sw} = 50 \cdot 200 \text{ Hz} = 10000 \text{ Hz}; T_{sw} = \frac{1}{f_{sw}} = 100 \mu\text{s}$

carrier sig. \Rightarrow


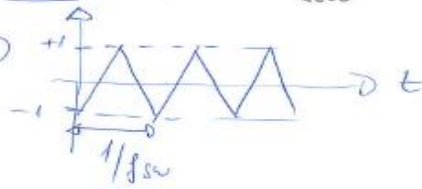


mod. sig. \Rightarrow

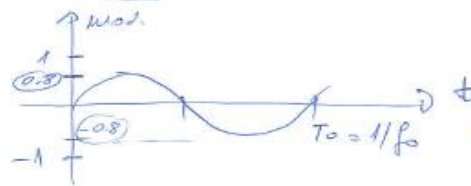

$$M_a = \frac{\hat{V}_{pN}}{\frac{V_{dc}}{2}} = \frac{250}{\frac{600}{2}} = 0.8$$

ph A

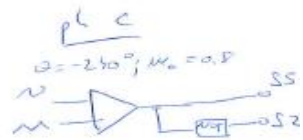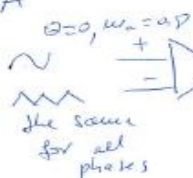

no deadtime considered

1 b) nonideal switches

$t_{on} = 0.3 \mu\text{s}$


2

$t_{off} = 0.65 \mu\text{s}$

In order to avoid shoot-through of the DC-link, a delay should be inserted in the turn-on time of PWM pulses.

This delay is usually called: deadtime.

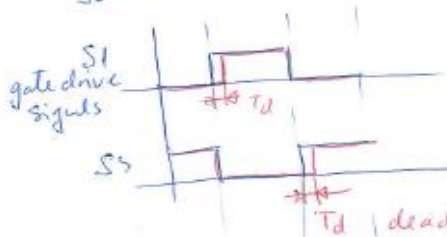Ideal PWM for S1 & S4 (two complementary)







$\rightarrow T_d$ should be long enough to make sure S4 is off before S1 starts turning on.

T_d deadtime (only at turn on)

$T_d > T_{off}$
 $\rightarrow T_d$ should be long enough to make sure S1 is completely off before S4 starts turning on

$T_d \sim 1 \mu\text{s}$

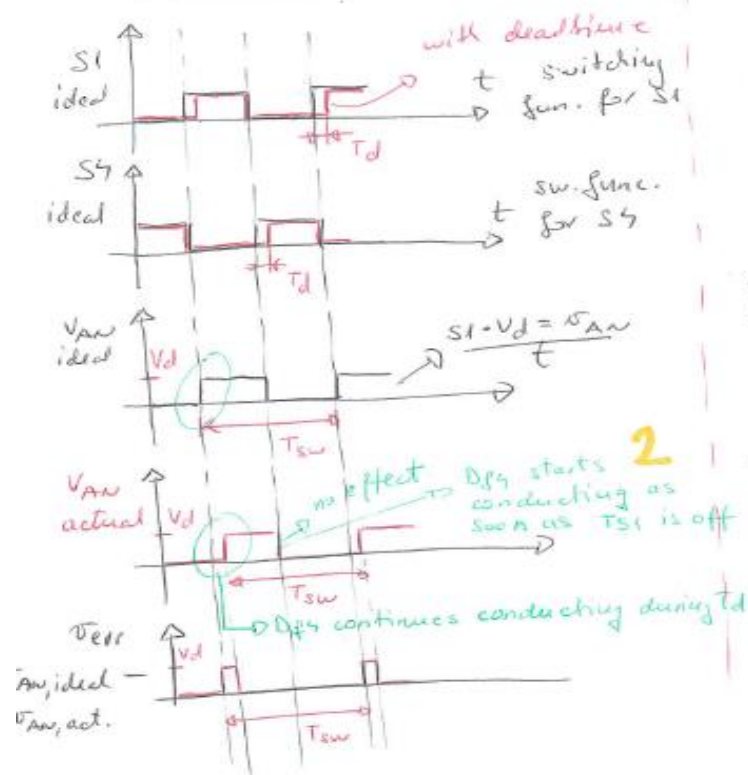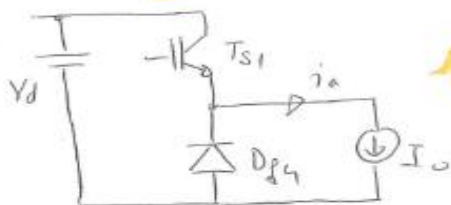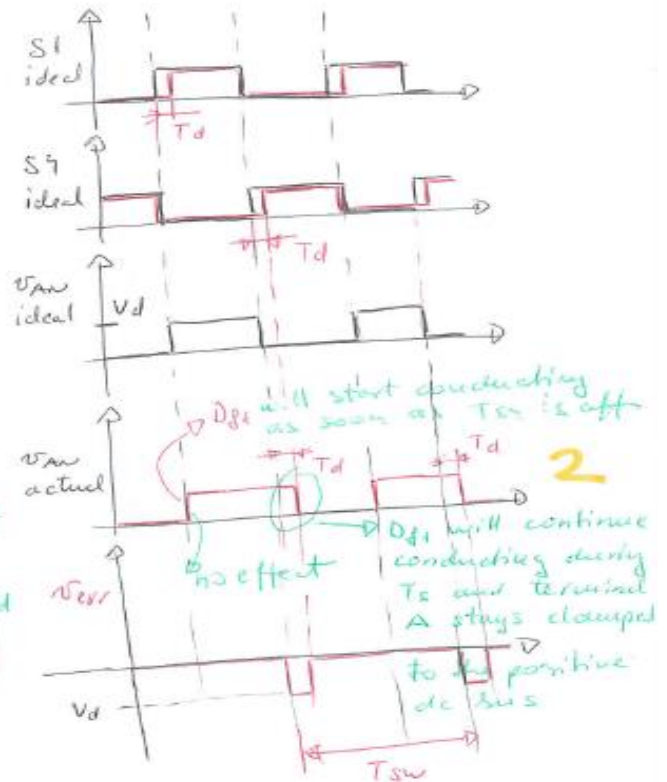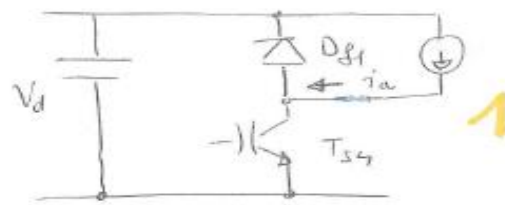c) $i_a > 0$ [6] $i_a < 0$ 

d) [4]

$$v_{A2, \text{fund.}}(t) = m_a \cdot \frac{V_d}{2} \cdot \sin(\omega_0 t) - \frac{4}{\pi} \cdot V_d \cdot \frac{T_d}{T_s} \cdot \sin(\omega_0 t - \theta)$$

$$= 0.8 \cdot \frac{600}{2} \cdot \sin(315t) - \frac{4}{\pi} \cdot 600 \cdot \frac{1 \mu s}{100 \mu s} \cdot \sin(315t - 45.6 \cdot \frac{\pi}{180})$$

$$= 240 \cdot \sin(315t) - 7.64 \cdot \sin(315t - 0.79587)$$

$$= 240 \cdot \sin(315t) - 7.64 \left\{ \sin(315t) \cdot \cos(0.79587) - \cos(315t) \cdot \sin(0.79587) \right\}$$

$$= 240 \cdot \sin(315t) - 5.348 \cdot \sin(315t) + 5.4588 \cdot \cos(315t)$$

$$= 234.6520 \cdot \sin(315t) + 5.4588 \cdot \cos(315t)$$

$$a \cos x + b \sin x = R \cos(x - \alpha)$$

$$R = \sqrt{a^2 + b^2} \quad ; \quad \alpha = \arctan\left(\frac{b}{a}\right)$$

$$= R \cos(315t - \alpha)$$

$$R = \sqrt{5.4588^2 + 234.6520^2} = 234.72V$$



$$\alpha = \arctan\left(\frac{234.6520}{5.4588}\right) = 1.5475$$

(2)



a)

S_{1i}	S_{2i}	\bar{S}_{2i}	\bar{S}_{1i}	v_{in}
1	1	0	0	V_{DC}
0	0	1	1	0
1	0	1	0	$V_{DC} - v_{C2i}$
0	1	0	1	v_{C2i}

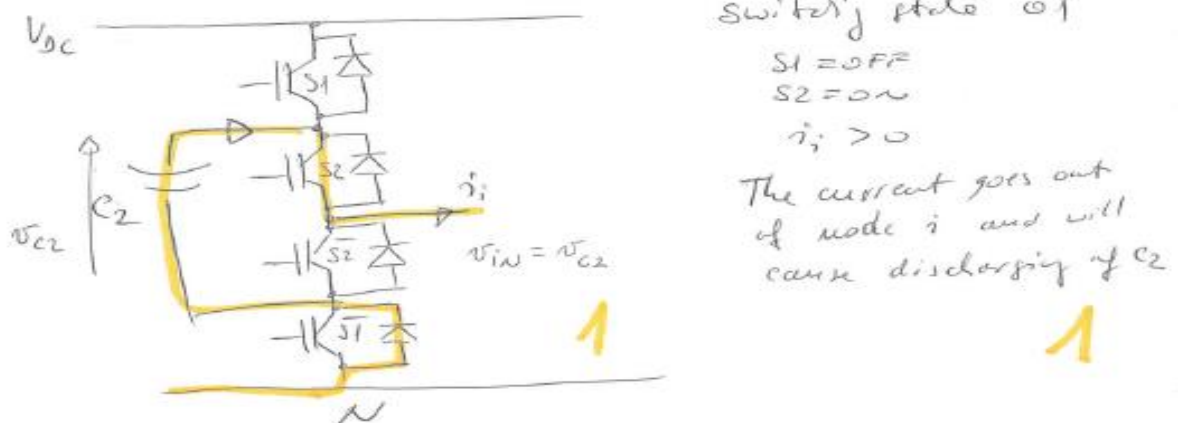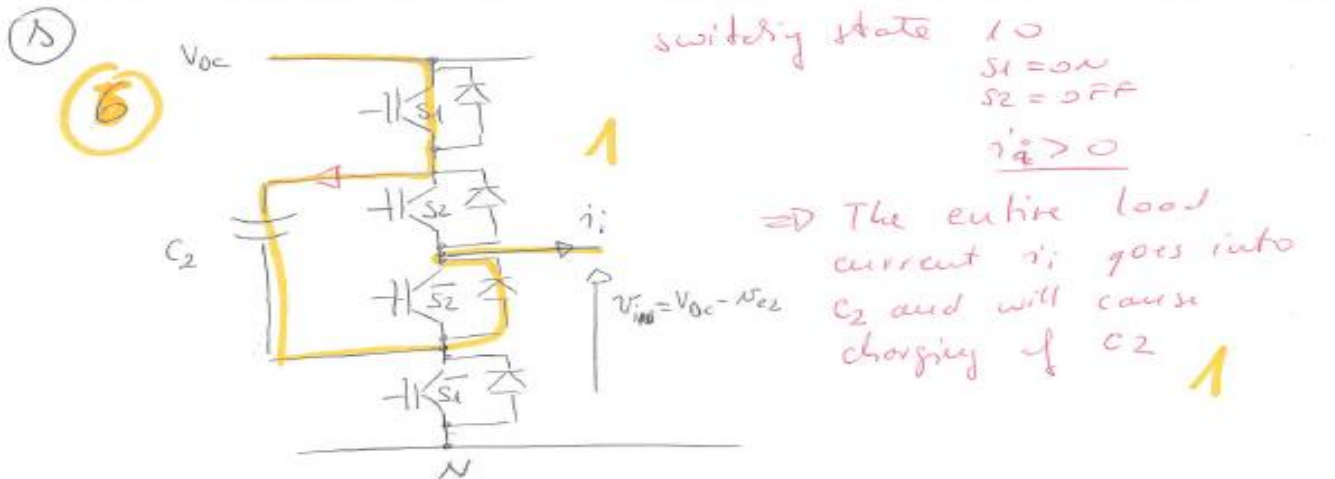if $v_{C2i} = \frac{V_{DC}}{2}$ then these are redundant states



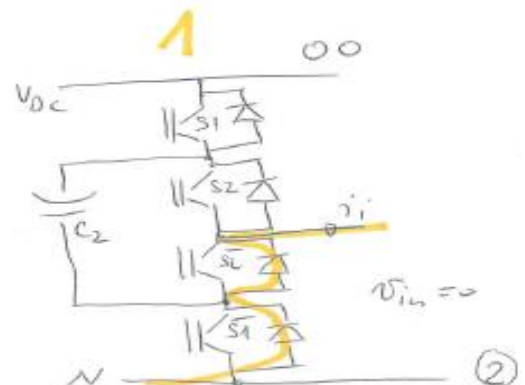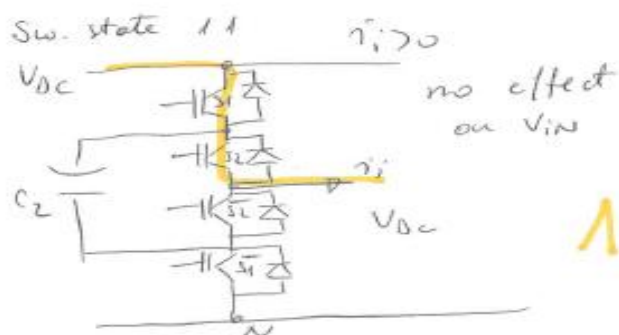
For $i_i < 0$ the effect is opposite.
 Therefore if v_{C2} is not balanced v_{in} during sw states 10 & 01 are a function of load current.



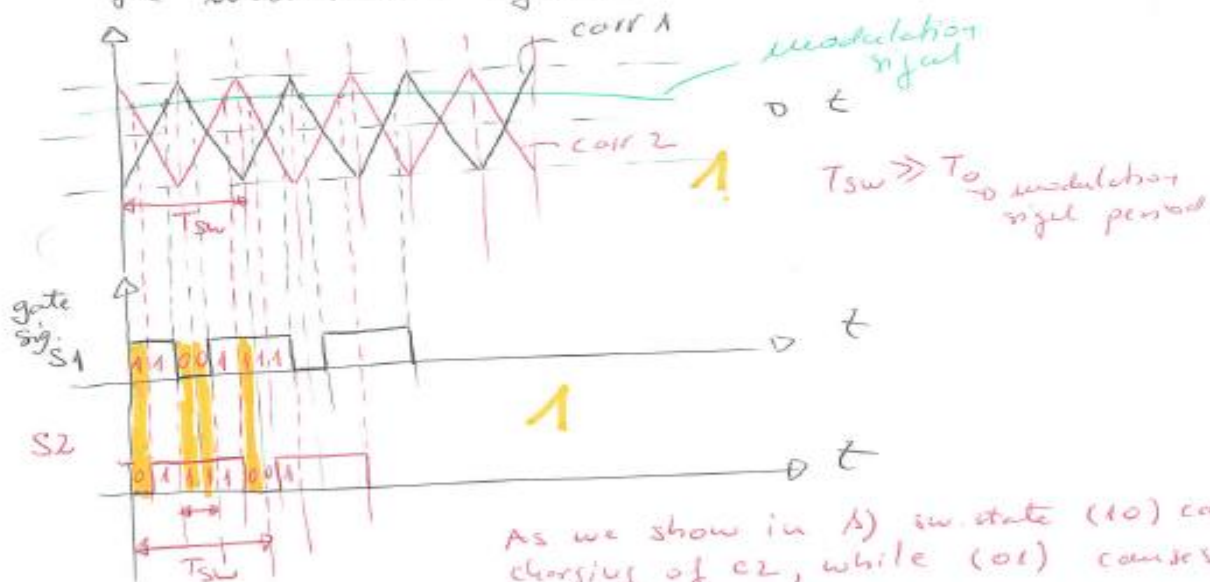c) Phase-shifted carrier PWM

For 3-level Flying capacitor multilevel converter we have common modulation signal for all switches in one leg and two carrier signals (one for modulation of S_1 & \bar{S}_1 and the another for modulation of S_2 & \bar{S}_2) which are phase-shifted by $\delta = \frac{2\pi}{n-1}$ ($n=3$) = 180°

The carrier freq. is much higher than the freq. of the modulation signal.



As we show in A) sw. state (10) causes charging of C_2 , while (01) causes discharging of C_2 .


The inherent characteristic of PSC PWM is that maintaining ^{almost} ^{time} equal intervals of states (10) & (01) during one sw. period and on this way keeps the voltage across C_2 constant.

d) PSC PWM

$$\Delta v_{C2i} = ?$$

$$C_{2i} = 1200 \mu F ; V_{dc} = 1 kV ;$$

charge in
charge on $C_{2i} = \Delta Q$

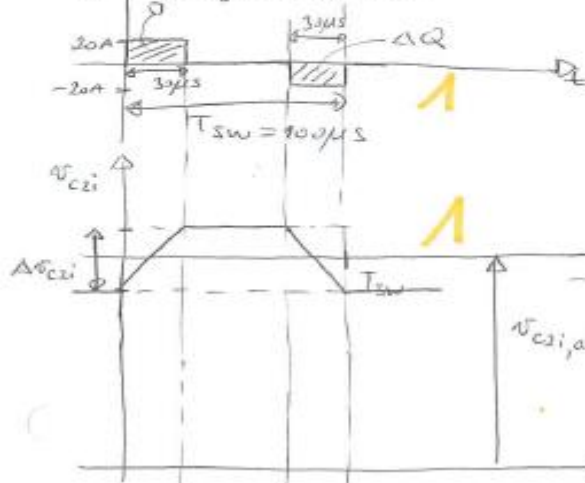

$$i_i = I_o = 20 A$$

$t_{r_{C2i}} = 30 \mu s = t_{f_{C2i}}$ in one $T_{sw} = \frac{1}{10 kHz} = 10 \mu s$
inherent to PSC PWM is at $v_{C2i} \approx 0$ in each switching period



• The change in charge on C_{2i} , will cause the change in the voltage across it:

$$\Delta v_{C2i} = \frac{\Delta Q}{C_{2i}} = \frac{20 A \cdot 30 \mu s}{1200 \mu F}$$

$$v_{C2i,av} = \frac{V_{dc}}{2} = \frac{1000}{2} = 500 V$$

$$= 0.5 V$$

a) 4

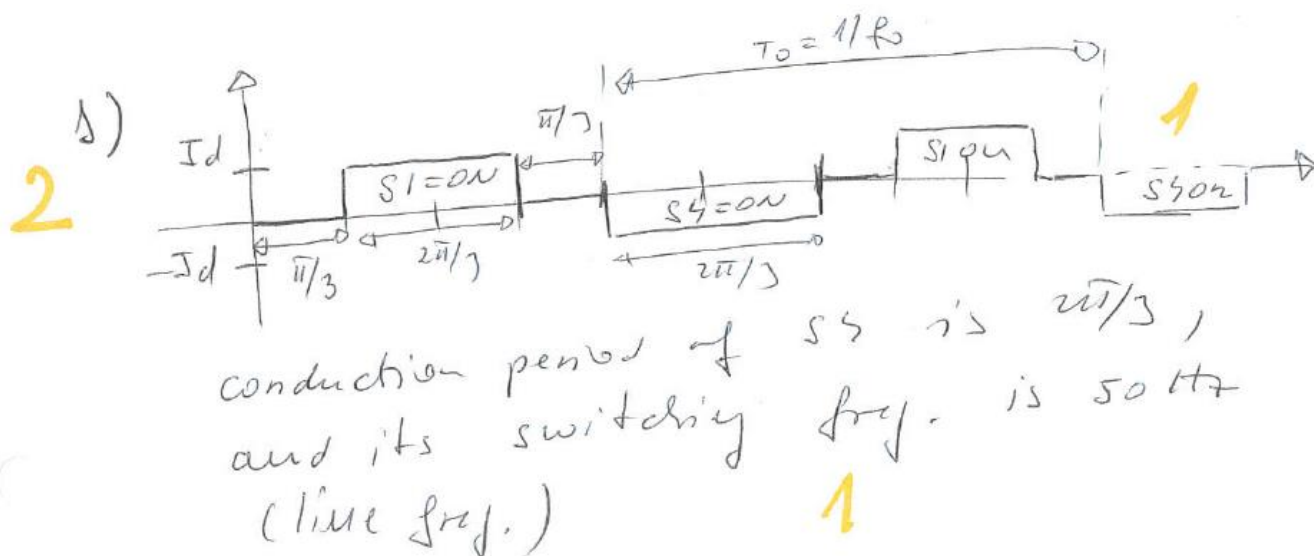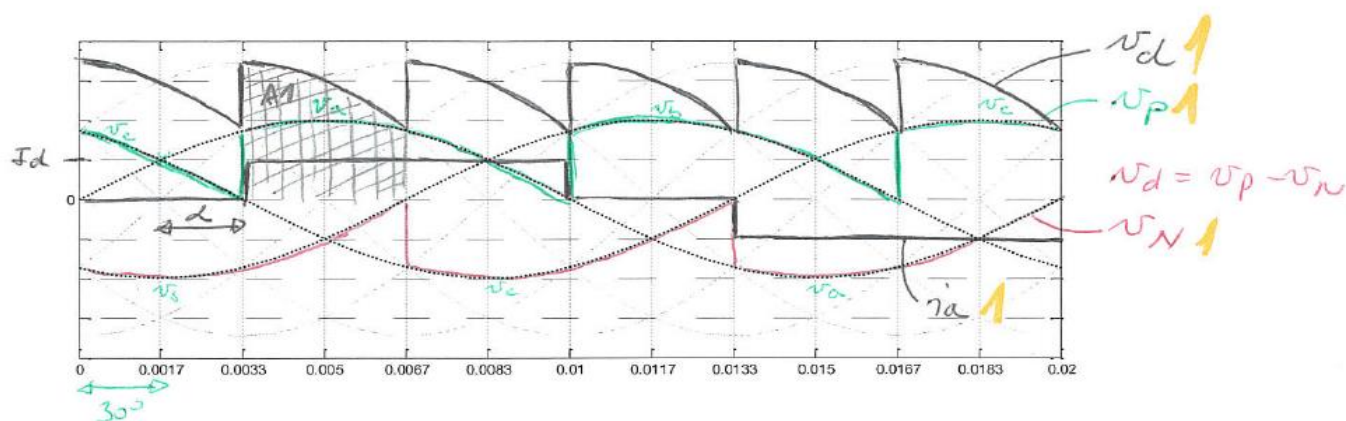

c) $V_d = \frac{\text{area } A1}{\pi/3} = \frac{1}{\pi/3} \int_{\pi/6+\alpha}^{\pi/6+\alpha+\pi/3} v_{as} \cdot d(\omega t) = \int_{\pi/6+\alpha}^{\frac{\pi}{2}+\alpha} \sqrt{2} \cdot V_{ll,rms} \sin(\omega t + \frac{\pi}{6}) \cdot d(\omega t) =$

4


$$= \frac{3}{\pi} \sqrt{2} \cdot V_{ll,rms} \left\{ \cos\left(\frac{\pi}{6} + \alpha + \frac{\pi}{6}\right) - \cos\left(\frac{\pi}{6} + \alpha + \frac{\pi}{6}\right) \right\} =$$

$$= \frac{3}{\pi} \cdot \sqrt{2} \cdot V_{ll,rms} \left\{ \cos\left(\alpha + \frac{\pi}{3}\right) - \cos\left(\alpha + \frac{2\pi}{3}\right) \right\} =$$


$$= \frac{3}{\pi} \cdot \sqrt{2} \cdot V_{ll,rms} \left\{ \cos \alpha \cdot \cos \frac{\pi}{3} - \sin \alpha \cdot \sin \frac{\pi}{3} - \left(\cos \frac{2\pi}{3} \cdot \cos \alpha - \sin \frac{2\pi}{3} \cdot \sin \alpha \right) \right\}$$

$$= \frac{3}{\pi} \cdot \sqrt{2} \cdot V_{ll,rms} \cdot 2 \cdot \frac{1}{2} \cdot \cos \alpha = \frac{3}{\pi} \cdot \sqrt{2} \cdot V_{ll,rms} \cdot \cos \alpha$$

$$\begin{aligned}
 d_i) \quad \hat{I}_{a1} &= \frac{1}{\pi} \int_{\pi/6}^{\pi/6 + \frac{2\pi}{3}} I_d \cdot \sin(\omega t) d\omega t + \frac{1}{\pi} \int_{\frac{7\pi}{6}}^{\frac{7\pi}{6} + \frac{2\pi}{3}} (-I_d) \cdot \sin(\omega t) d\omega t = 1 \\
 &= \frac{1}{\pi} \cdot I_d (-\cos \omega t) \Big|_{\pi/6}^{5\pi/6} + \frac{1}{\pi} \int_{\frac{7\pi}{6}}^{\frac{11\pi}{6}} (-I_d) \cdot \sin(\omega t) d(\omega t) = \\
 &= \frac{1}{\pi} \cdot I_d \cdot (\cos \frac{\pi}{6} - \cos \frac{5\pi}{6}) + \frac{1}{\pi} I_d \cdot (\cos(\frac{11\pi}{6}) - \cos(\frac{7\pi}{6})) \\
 &= \frac{1}{\pi} \cdot I_d \cdot (\frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2}) + \frac{1}{\pi} \cdot I_d \cdot (\frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2}) = \frac{2}{\pi} \cdot I_d \cdot \sqrt{3} = 1.1 I_d
 \end{aligned}$$

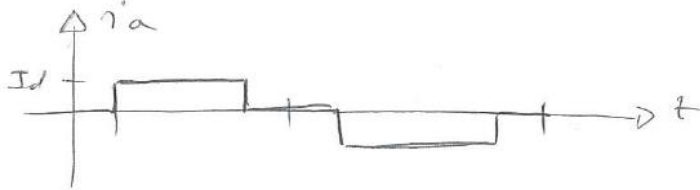

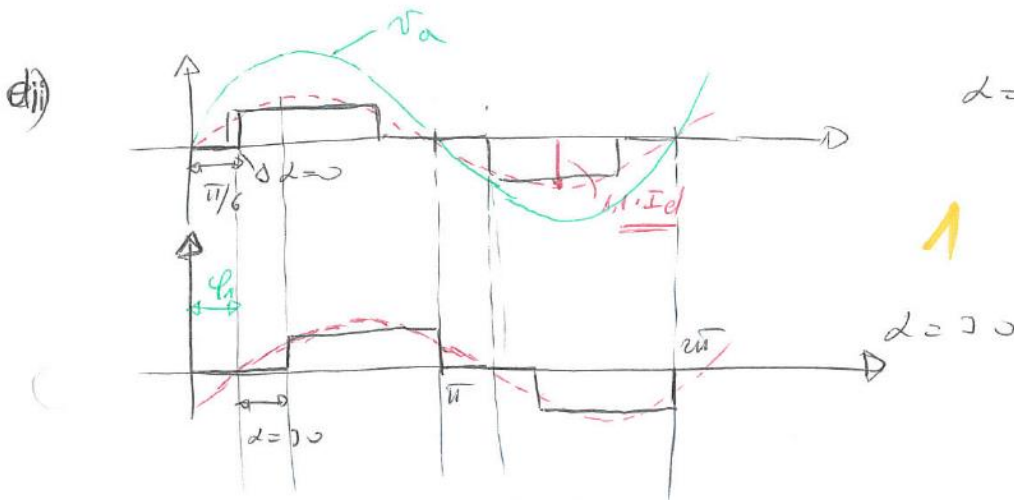for $\alpha = 0$
the amplitude is
the same
only the component
is shifted by α



ϕ_1 - phase shift between v_a & i_{a1}

$$= \frac{\pi}{6}$$

Reactive power

$$\begin{aligned}
 Q &= 3 \cdot V_{p, rms} \cdot I_{p, rms} \cdot \sin(\phi_1) \\
 &= 3 \cdot \frac{V_{l, rms}}{\sqrt{3}} \cdot I_{p, rms} \cdot \sin(\phi_1) \\
 &= \sqrt{3} \cdot 2300 \cdot 1.1 \cdot I_d \cdot \sin(\frac{\pi}{6}) \\
 &= 325.8 \text{ kVA}
 \end{aligned}$$

$$I_d = \frac{P}{U_{d, av}} = \frac{400 \text{ kW}}{\frac{3}{\pi} \cdot \sqrt{2} \cdot 2300 \cdot \cos(\frac{\pi}{6})} = 148.7 \text{ V}$$

$\cdot \frac{1}{\sqrt{2}}$

(6) a) **14**

$$\Delta\theta = 73.6^\circ - 70^\circ = \underline{3.6^\circ} = 2\pi f_0 T_s \cdot \frac{180}{\pi}$$

$$T_s = \frac{1}{f_{sw}} = \frac{1}{10\text{kHz}} = 100\mu\text{s}$$

$$f_0 = \frac{\Delta\theta}{2\pi T_s} = \frac{3.6 \cdot \frac{\pi}{180}}{2\pi \cdot 100\mu\text{s}}$$


$$f_0 = 100\text{kHz} \quad \mathbf{2}$$

The rotation freq. of the ref. vector corresponds to the fundamental freq. of the inverter. The ref. vec. is synthesised a finite, discrete number of times (N) during one rotation period which corresponds to the fund. period of the output voltage. N in our case is $N = \frac{T_0}{T_s} = \frac{10\text{ms}}{100\mu\text{s}} = \underline{100\text{ times}}$

1) **4**


The zero & large vectors do not affect the neutral point Z , as no current flows through the neutral point.

for example: zero vector [PPF]

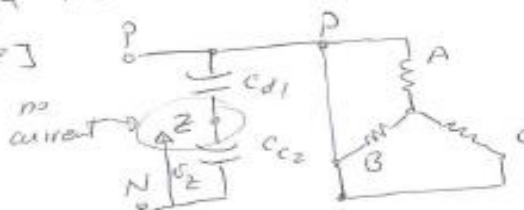


95
 v_z not affected

large vector [PNN]

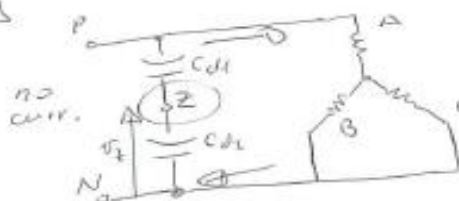

95


For medium vector it is not defined:

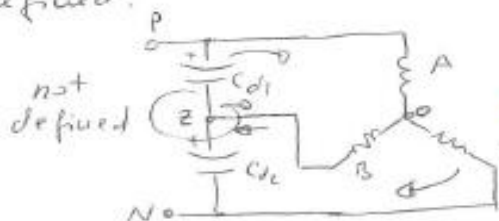

1

Small vectors have dominant influence on v_z .

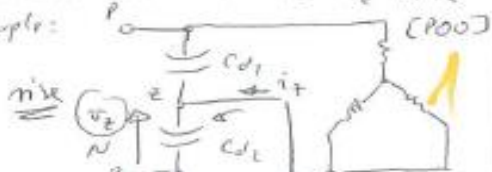P-type small vector makes v_z rise
for example: [P00]




N-type small vector makes v_z decline
[0NN]



1

c) [P0N]

4

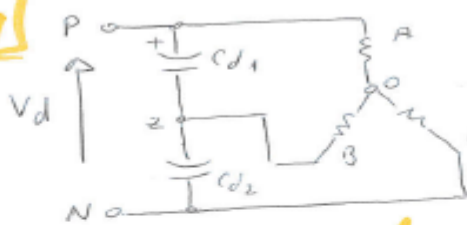


$$\begin{aligned} V_{PN} &= V_d \\ V_{AO} &= V_d/2 \\ V_{CO} &= -V_d/2 \\ V_{CO} &= 0 \end{aligned}$$

$$\begin{aligned} \vec{V}(t) &= \frac{2}{3} [v_{Ao}(t) \cdot e^{j0} + v_{Bo}(t) \cdot e^{j\pi/3} + v_{Co}(t) \cdot e^{j2\pi/3}] \\ &= \frac{2}{3} \left[\frac{V_d}{2} e^{j\phi} - \phi \cdot e^{j2\pi/3} - \frac{V_d}{2} e^{j\pi/3} \right] \\ &= \frac{2}{3} \left[\frac{V_d}{2} - \frac{V_d}{2} \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2} \right) \right] \\ &= \frac{2}{3} \left[\frac{V_d}{2} + \frac{V_d}{4} + j\frac{V_d}{4} \cdot \sqrt{3} \right] \\ &= \frac{2}{3} \left[\frac{3V_d}{4} + j\frac{V_d}{4} \cdot \sqrt{3} \right] = \\ &= \frac{2}{3} \cdot \frac{\sqrt{3}}{2} \left[\frac{\sqrt{3}V_d}{2} + j\frac{V_d}{2} \right] \\ &= \frac{V_d \cdot \sqrt{3}}{3} \cdot e^{j\pi/6} \end{aligned}$$

d) 5


	S1	S2	S3	S4	VAN	
I	0	1	1	0	Vd/2	$i_A > 0$ & $i_A < 0$
II	1	0	0	1	0	$i_A > 0$
III	1	0	0	1	Vd	$i_A < 0$

for hidden state

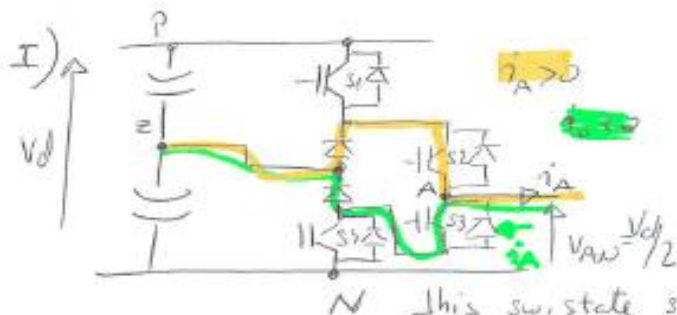

This sw. state synthesizes the voltage $V_d/2$ independent of the sign of curr. in A
 \Rightarrow VALID STATE

II)

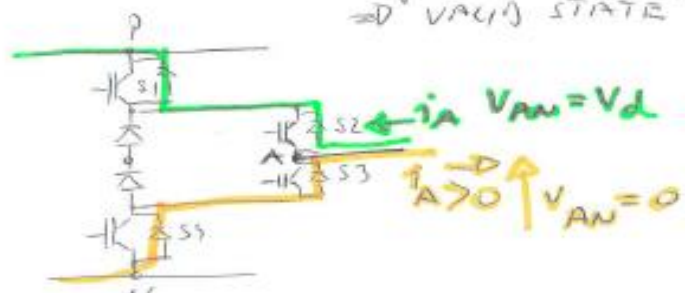

$V_{AN} = f(\text{sign of load current})$
 \Rightarrow for hidden state


③ a) In the res. dc-link voltage inverter, input voltage remains zero during a finite period of time when the inverter switches can change their states at zero voltage.



The operat. cycle can be divided in 3 parts:

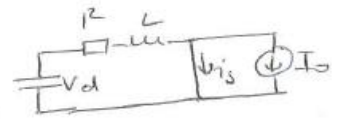
1) $S=on$ - charging of L

Assumption: capacitor C is discharged in the preceding resonance cycle so S is turned on at ZERO voltage. \Rightarrow



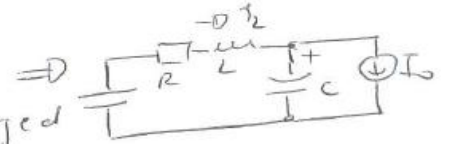
2) $S=off$; diode D is off \Rightarrow resonance

S opens & energy stored in L is discharged through the capacitor C .



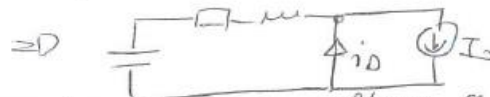
3) Diode D is on

At the instant when voltage V_c drops to zero, the freewheeling diode D becomes forward biased & it shorts the output of the circuit.




The output remains at zero voltage as long as the diode is conducting. Therefore, switch S has to be turned on before the diode current reaches zero so that the switch is turned on at zero voltage.

⑥

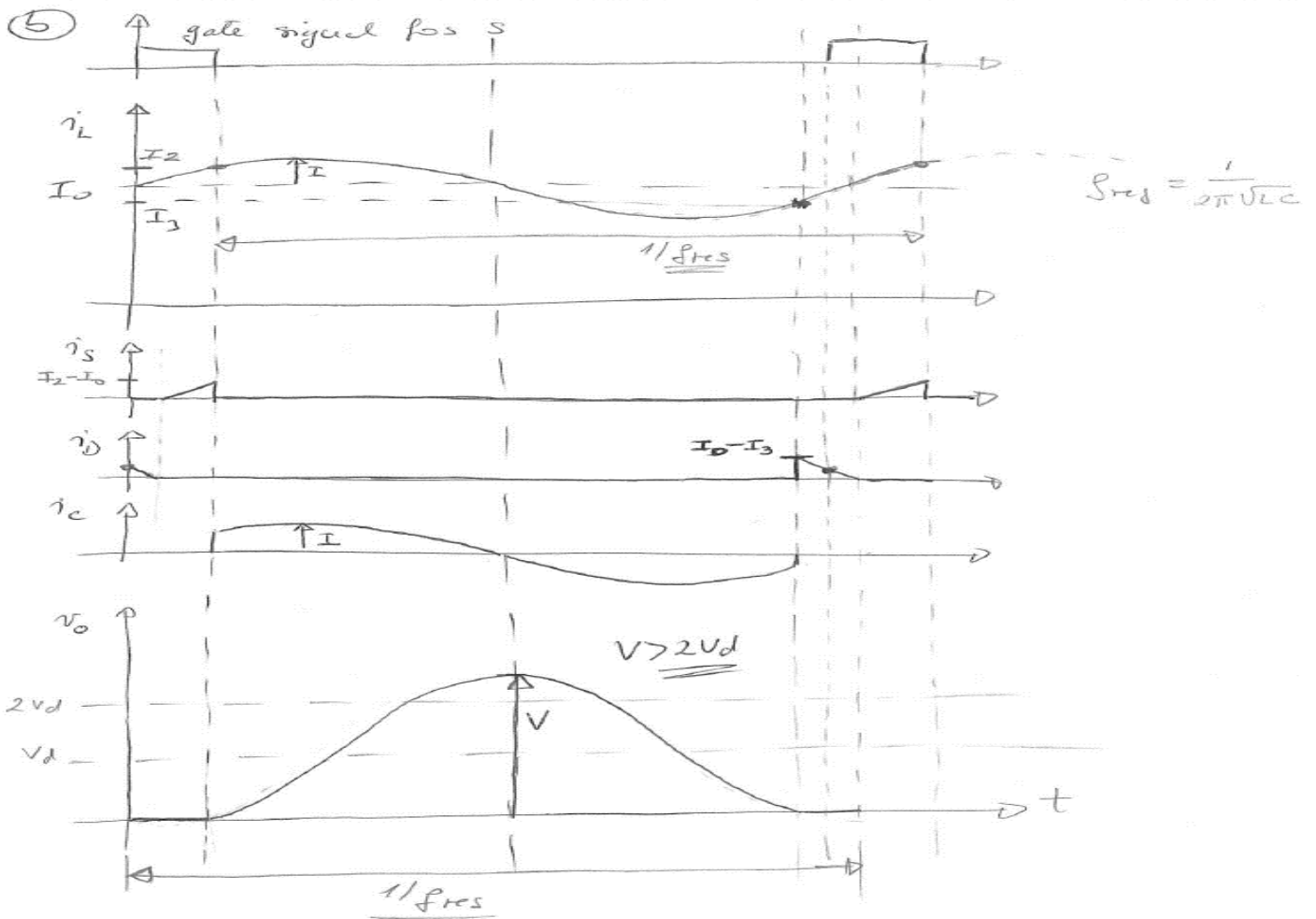

c) 4

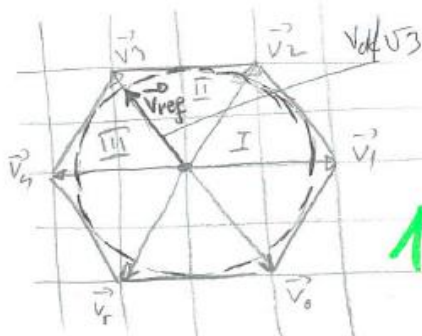

$$|\vec{V}_{ref}| = \frac{V_{dc}}{\sqrt{3}} \quad (\text{max achievable})$$

$$m_a = \frac{|\vec{V}_{ref}|}{\frac{V_{dc}}{\sqrt{3}}} = 1$$

$\theta = 120^\circ \Rightarrow$ Sector II; \vec{V}_{ref} can be synthesised by \vec{V}_2, \vec{V}_3 and \vec{V}_0 .

Eg. (3.1) & (3.2) are valid for Sector I
For Sector II we have:

$$T_{V_2} = \sqrt{3} \cdot \frac{V_{ref}}{V_{dc}} \cdot T_s \cdot \sin\left(\frac{\pi}{3} - \theta'\right)$$

$$T_{V_3} = \sqrt{3} \cdot \frac{V_{ref}}{V_{dc}} \cdot T_s \cdot \sin(\theta')$$

$$0 < \theta' < \frac{\pi}{3}$$

$$\theta' = 120^\circ - \frac{\pi}{3} = \frac{\pi}{3}$$

$$T_a = T_{V_2} = m_{a,max} \cdot T_s \cdot \sin\left(\frac{\pi}{3} - \frac{\pi}{3}\right) = 0$$

$$T_b = T_{V_3} = m_{a,max} \cdot T_s \cdot \sin\left(\frac{\pi}{3}\right) = 1 \cdot 200\mu s \cdot \frac{\sqrt{3}}{2} = 173\mu s$$

$$T_0 = T_s - T_{V_2} - T_{V_3} = 200\mu s - 173\mu s = 27\mu s$$

d) Sector S

7-segment S
sw. sequence S

V_0	V_3	V_2	V_0	V_3	V_2	V_3
0	0	1	1	1	1	0
0	1	1	1	1	1	0
0	0	1	1	0	0	0

$$T_{sw} = T_s$$

$$T_{sw} = T_s$$

$$T_{sw} = T_s$$

V_0	V_2	V_3	V_0	V_3	V_2	V_0
0	1	0	1	0	1	0
0	1	1	1	1	1	0
0	0	0	1	0	0	0

more than one sw. per T_s

one sw. per T_s

one switch chg per T_s

4


1

✓
Better option to minimise switching and losses


1

1

1

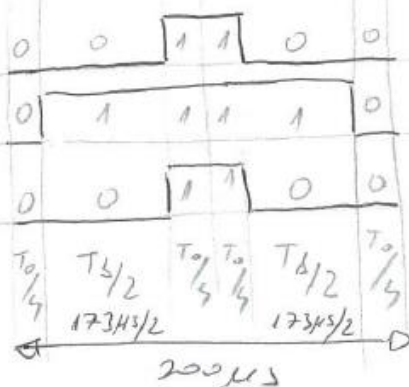



Question 4

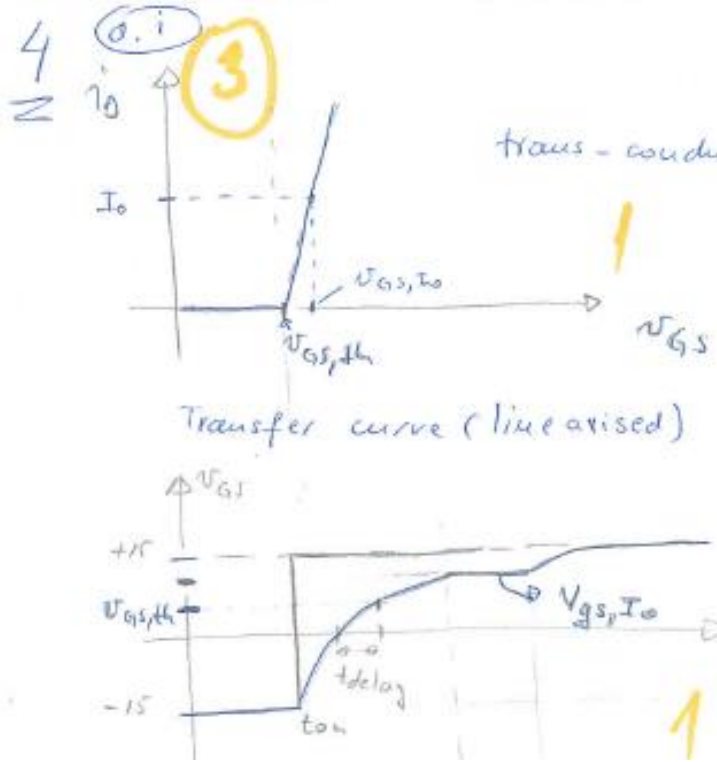

$$I_0 = g_{fs} (v_{GS,I_0} - v_{GS,th})$$


$$\frac{I_0}{g_{fs}} + v_{GS,th} = v_{GS,I_0}$$

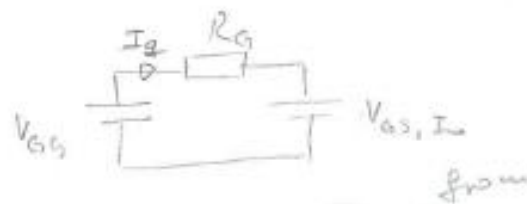
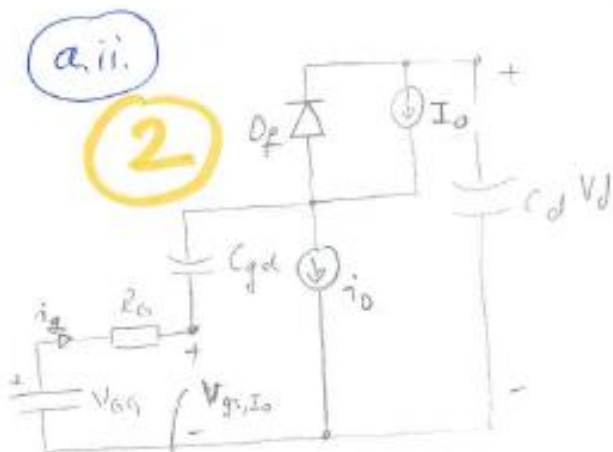
$$\frac{300}{60} + 6 = \underline{\underline{11V}}$$



$$I_g = \frac{V_{GG} - v_{GS,I_0}}{R_G} = \frac{15 - 11}{2} = \underline{\underline{2A}}$$

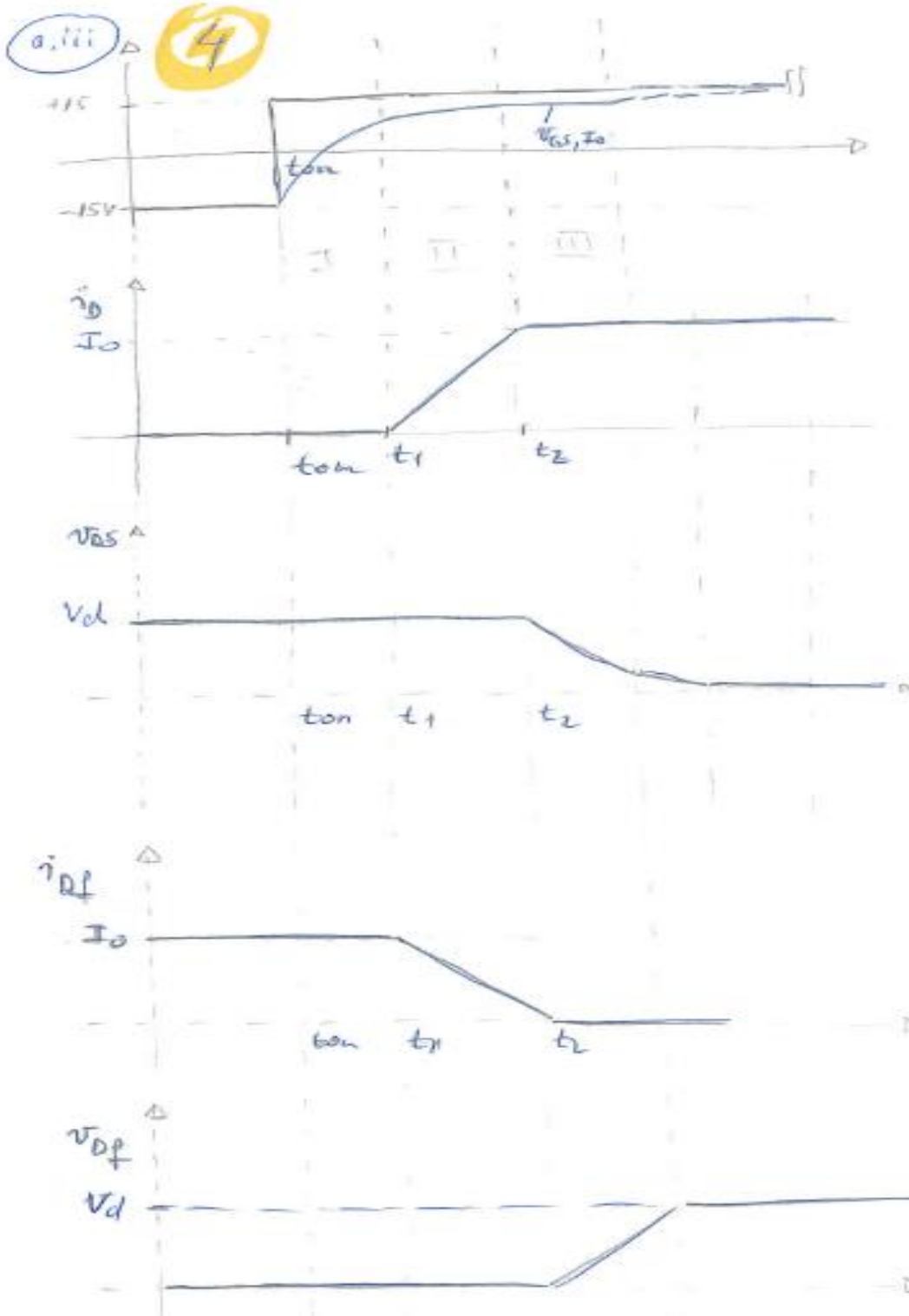$C_{gs} \rightarrow$ fully charged and no current flows through C_{gs} (voltage across $C_{gs} = \text{const.} = v_{GS,I_0}$)



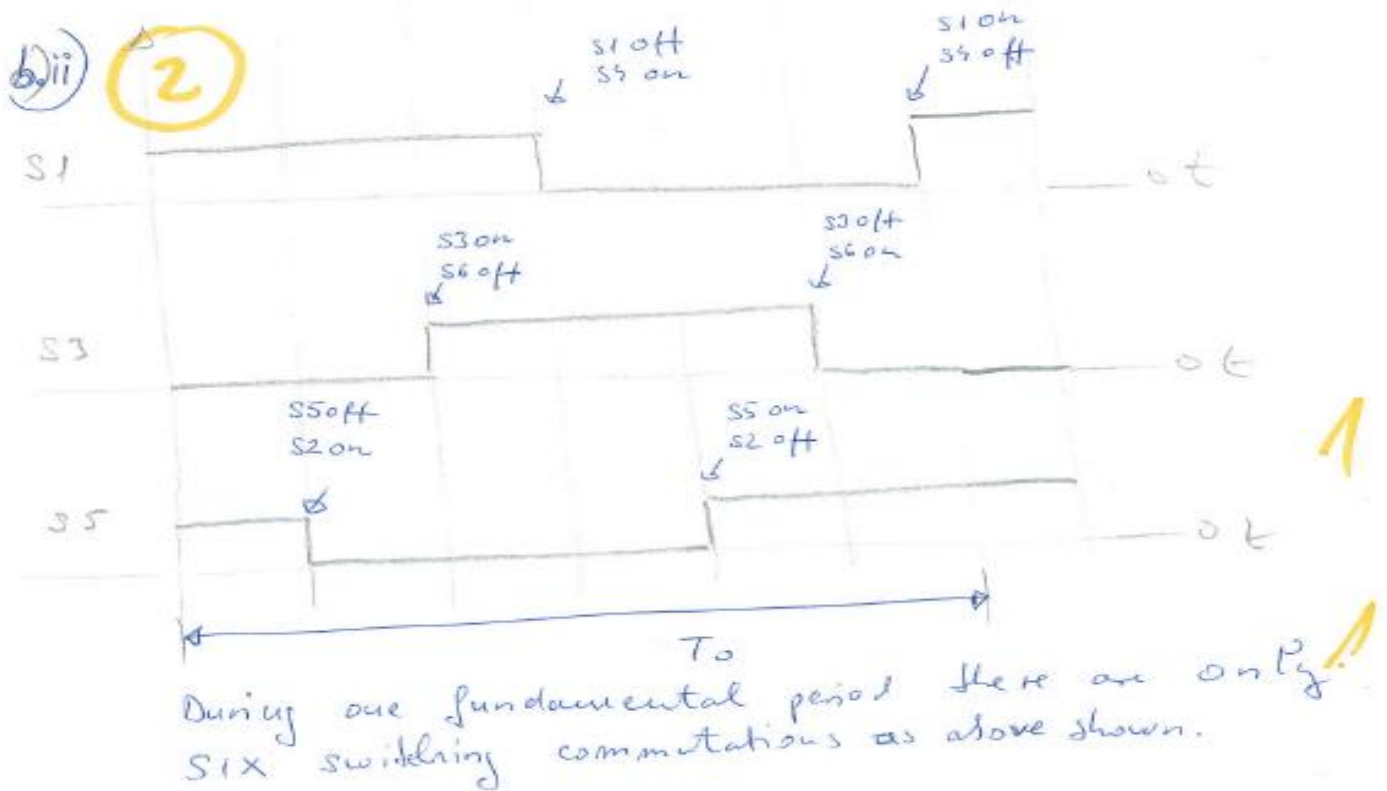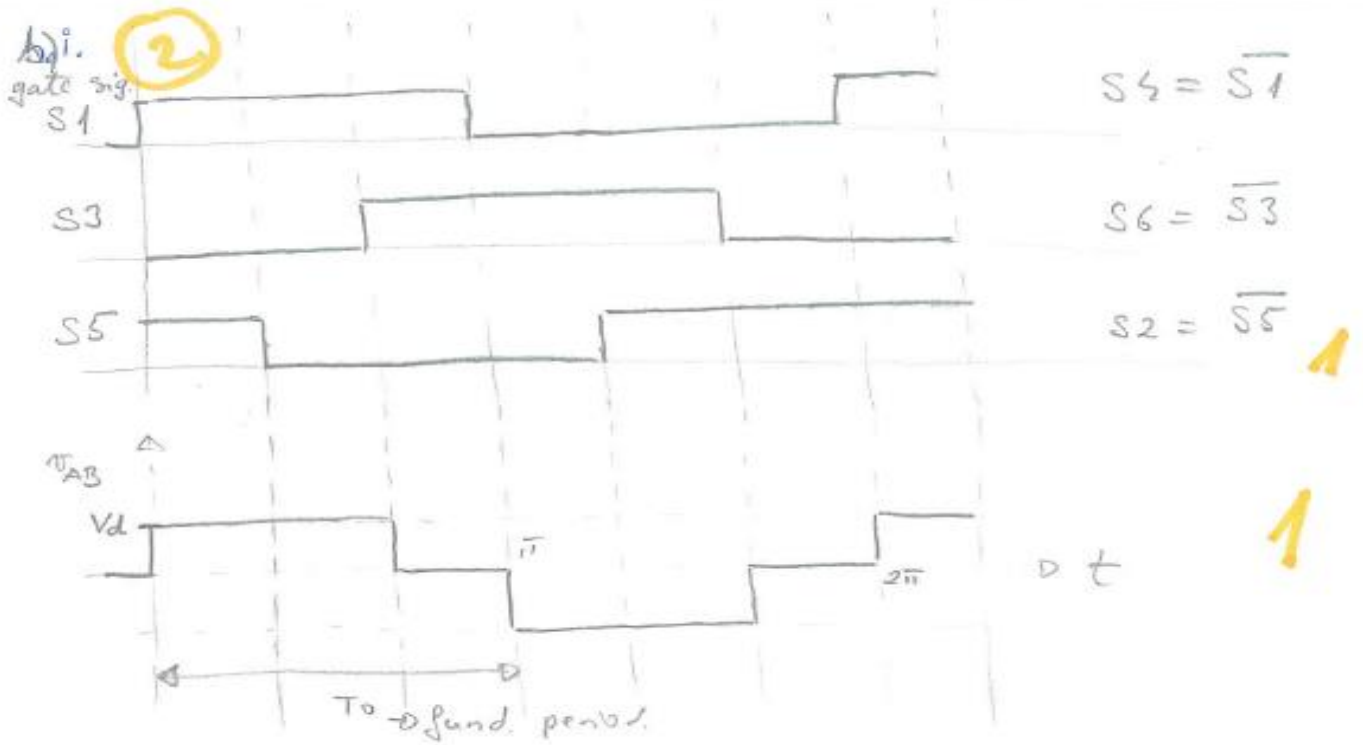



$$A_1 = \frac{1}{\pi} \int_0^{2\pi} u(\omega t) \cdot \sin(\omega t) \cdot d\omega t = \frac{1}{\pi} \int_0^{\pi} V_d \cdot \sin(\omega t) \cdot d\omega t =$$

$$= \frac{V_d}{\pi} (-\cos \omega t) \Big|_0^{\pi} = \frac{V_d}{\pi} (\cos 0 - \cos \pi) = \frac{2V_d}{\pi}$$

rms line-to-line voltage:

$$V_{AB, \text{rms}} = \sqrt{3} \cdot \frac{2V_d}{\pi} \cdot \frac{1}{\sqrt{2}}$$

$$460 = \frac{\sqrt{3} \cdot 2 \cdot V_d}{\sqrt{2} \cdot \pi}$$

$$V_d \approx 589,97V$$

$$V_d \approx 600V$$