
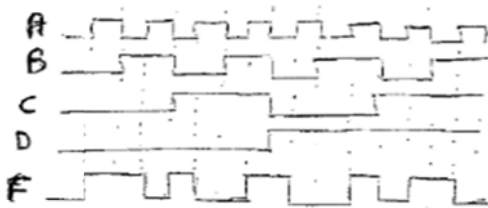


1.

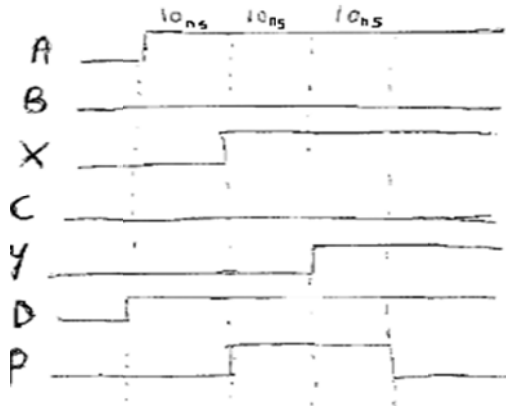

XOR gates give 'odd' function.
Output is '1' when there is an odd number of '1's on ABCD.
∴ the output will indicate odd parity. Maximum delay =
 $10 + 10 + 10 = 30\text{ ns}$ $f_{\text{max}} = \frac{1}{30\text{ ns}} = 33.3\text{ MHz}$



P should remain at '0' as '0000' and '1001' are both even parity. It is seen that there is a static '0' hazard on the output. It can be eliminated as shown.



Delays are now equal.

2.

- (a) See lecture notes } bookwork
(b) see lecture notes }

$$(c) S_0 = (A \oplus B) \oplus C_i$$

$$C_0 = AB + C_i(A+B)$$

when $B = \phi$, $S_0 = A \oplus C_i$


$$C_0 = C_i A$$

$$(d) B=1, C_i=0$$

$$S_0 = \bar{A}, C_0 = A$$

$$(A \oplus 0 = A, A \oplus 1 = \bar{A})$$

(e) invert all bits and add 1

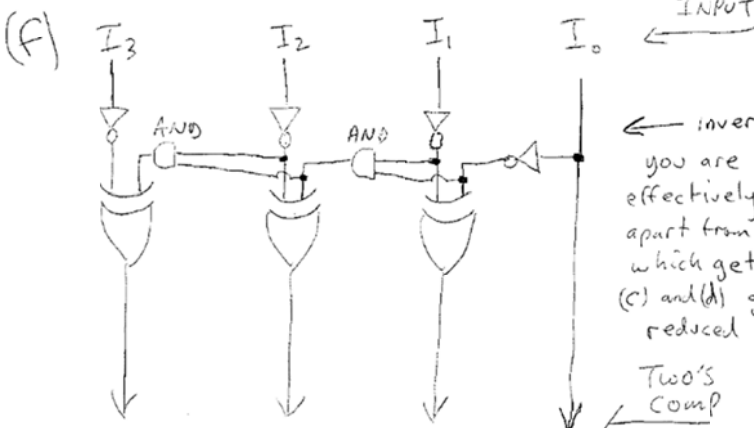

← invert all bits.
you are then effectively adding 0 apart from the LSB which gets '1'. Par (c) and (d) give the reduced adder circuit.

Two's Comp

3. In a Moore type machine, the outputs depend on only the present state. They may be the state itself or decoded from the state. In a Mealy type machine, the outputs are a function of the state and current inputs.
4. In binary encoding, n bits can be used to represent 2^n states. In one-hot encoding, one bit is required for each state. When in a certain state, one bit is active or *hot*. This could be the output of a flip-flop where n flip-flops would be required to represent n states.
- 5.

