



The
University
Of
Sheffield.

**Data Provided: Smith Chart (4 copies),
Useful equations are given at the end
of the paper**

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Autumn Semester 2011-2012 (2 hours)

High Speed Electronic Circuit Design

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1.
 - a. Explain briefly what is meant by a conjugate impedance matching. (3)
 - b. A lossless transmission line with a length of 5 cm and a characteristic impedance of 50Ω is terminated with a complex load impedance of $(60-j20)\Omega$ at a frequency of 1GHz. Use the required transmission line equations to calculate the reflection coefficient at the load, the input impedance, voltage standing wave ratio, and the input reflection coefficient. (5)
 - c. A load impedance of $Z_L=50-j10\Omega$ is to be matched to a 75Ω source using a lossless transmission line of characteristic impedance Z_o and length ℓ . Find the required Z_o (real) and ℓ . (6)
 - d. Consider a lossless transmission line that is terminated by a load impedance of Z_L . Show that the reflection coefficient at a distance d from the load can be expressed as $\Gamma_{(d)} = \Gamma e^{-j2\beta d}$, where Γ is the reflection coefficient at the load, and β is the phase constant. (6)
2.
 - a. Explain briefly how the Smith chart can be used for admittance transformation. (4)
 - b. A lossy line with attenuation of 15 dB/m at 300 MHz, is terminated by a load with a normalized impedance of $z=4+j0$. Use the Smith chart to find the voltage standing wave ratio, VSWR, at a distance of 10cm from the load. (6)
 - c. For a transmission line with a characteristic impedance of $Z_o=50\Omega$ and terminated by a load impedance $Z_L=(140-j110)\Omega$, design a double stub matching network to match Z_L to Z_o . The 1st stub is located at the load, and the two stubs are separated by a distance of 0.125λ . The length of each stub should be $\leq 0.25\lambda$. (10)

Note: Find one possible solution for each design.

3. a. Explain the limitations of basic circuit theory in the design of high frequency electronic circuits. (4)
- b. Explain the difference between the input reflection coefficient and the S_{11} scattering parameter in a two ports network. (4)
- c. Find the transmission parameters for the network shown in Figure 1

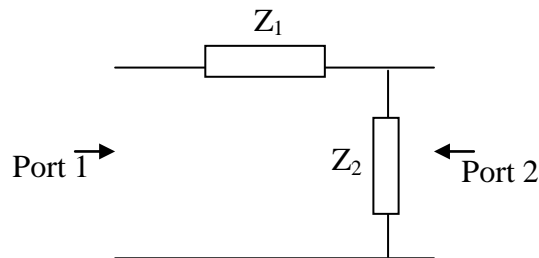


Figure 1

- d. Determine the scattering parameters of the two-port network shown in Figure 2. Assume the characteristic impedances for the input and output ports are equal ($Z_{o1}=Z_{o2}$).

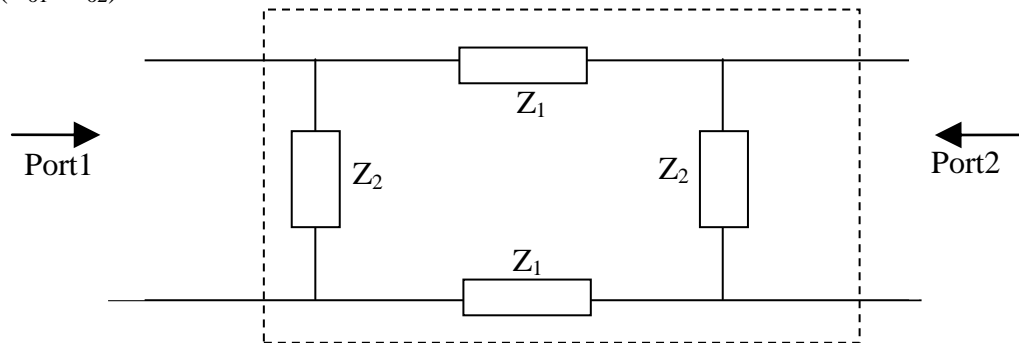


Figure 2

4. a. Explain the difference between conditional and unconditional stability. (2)
- b. Explain briefly what is meant by constant gain circles. (2)
- c. Consider a BJT with the following parameters: $S_{11} = 0.3\angle 30^\circ$, $S_{21} = 2.5\angle -80^\circ$, $S_{12} = 0.2\angle -60^\circ$, $S_{22} = 0.2\angle -15^\circ$. Determine whether the transistor is unconditionally stable, and design an amplifier with a power gain of 8 dB. In addition ensure that $\Gamma_{in} = \Gamma_s^*$, where Γ_{in} and Γ_s^* have their usual meaning. (6)
- d. Design an amplifier to have a gain of 10dB at 6GHz using a transistor with the following S parameters ($Z_o=50\Omega$): $S_{11} = 0.61\angle -70^\circ$, $S_{21} = 2.24\angle 32^\circ$, $S_{12} = 0$, $S_{22} = 0.72\angle -83^\circ$. Plot, and use, constant gain circles for $G_s=0.5\text{dB}$, $G_s=1.5\text{dB}$, $G_L=1.5\text{dB}$, and $G_L=2.5\text{dB}$, where G_s and G_L have their usual meaning. (10)

You may find the following information useful:

The gain circles can be plotted using the following set of equations

$$C_s = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2}$$

$$r_s = \frac{\sqrt{1 - g_s} (1 - |S_{11}|^2)}{1 - (1 - g_s) |S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$

$$r_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$

$$C_{g_o} = \frac{g_o (S_{22} - \Delta S_{11}^*)^*}{1 + g_o (|S_{22}|^2 - |\Delta|^2)}$$

$$r_{g_o} = \frac{\sqrt{1 - 2Kg_o |S_{12}S_{21}| + g_o^2 |S_{12}S_{21}|^2}}{|1 + g_o (|S_{22}|^2 - |\Delta|^2)|}$$

SKK