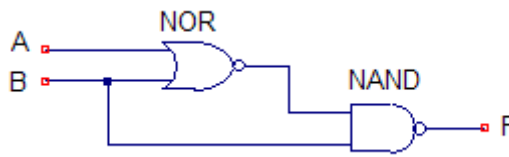
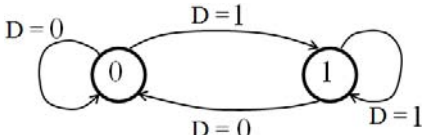
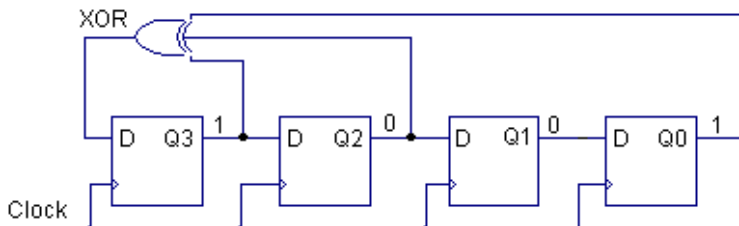


EEE104 – Digital Systems - Interim Test 2009

Answer All questions by writing the answer in the appropriate box provided

1	Write down the value for A B C D that will satisfy the Boolean expression below. $\overline{A.B.C.D} = 0$	<table><tr><th>A</th><th>B</th><th>C</th><th>D</th></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr></table>	A	B	C	D	1	1	0	0																
A	B	C	D																							
1	1	0	0																							
2	Complete the following Boolean expressions: (where A' represents NOT A)	i. $A + 1 = 1$ ii. $A + A' = 1$ iii. $A + A = A$ iv. $A + 0 = A$																								
3	Express the decimal number -39 as an eight bit binary 2's complement number.	11011001																								
4	Complete the truth table for the circuit below. 	<table><tr><th>A B</th><th>F</th></tr><tr><td>0 0</td><td>1</td></tr><tr><td>0 1</td><td>1</td></tr><tr><td>1 0</td><td>1</td></tr><tr><td>1 1</td><td>1</td></tr></table>	A B	F	0 0	1	0 1	1	1 0	1	1 1	1														
A B	F																									
0 0	1																									
0 1	1																									
1 0	1																									
1 1	1																									
5	Write down the dual of the expression $X.0 = 0$ (duality principle)	$X + 1 = 1$																								
6	Complete the truth table for the 2-to-1 multiplexer given by: <table><tr><th>S</th><th>Y</th></tr><tr><td>0</td><td>A</td></tr><tr><td>1</td><td>B</td></tr></table> where S is the select line, A,B are the data inputs Y is the output	S	Y	0	A	1	B	<table><tr><th>S A B</th><th>Y</th></tr><tr><td>0 0 0</td><td>0</td></tr><tr><td>0 0 1</td><td>0</td></tr><tr><td>0 1 0</td><td>1</td></tr><tr><td>0 1 1</td><td>1</td></tr><tr><td>1 0 0</td><td>0</td></tr><tr><td>1 0 1</td><td>1</td></tr><tr><td>1 1 0</td><td>0</td></tr><tr><td>1 1 1</td><td>1</td></tr></table>	S A B	Y	0 0 0	0	0 0 1	0	0 1 0	1	0 1 1	1	1 0 0	0	1 0 1	1	1 1 0	0	1 1 1	1
S	Y																									
0	A																									
1	B																									
S A B	Y																									
0 0 0	0																									
0 0 1	0																									
0 1 0	1																									
0 1 1	1																									
1 0 0	0																									
1 0 1	1																									
1 1 0	0																									
1 1 1	1																									

Please Turn Over

7	What binary number is represented by the hexadecimal number DA	11011010															
8	Express the function $F(A,B) = A \text{ XNOR } B$ as a fundamental product of sums.	$(A + \overline{B})(\overline{A} + B)$															
9	Complete the truth table for a half adder with inputs A and B	<table><tr><th>A B</th><th>SUM</th><th>CARRY</th></tr><tr><td>0 0</td><td>0</td><td>0</td></tr><tr><td>0 1</td><td>1</td><td>0</td></tr><tr><td>1 0</td><td>1</td><td>0</td></tr><tr><td>1 1</td><td>0</td><td>1</td></tr></table>	A B	SUM	CARRY	0 0	0	0	0 1	1	0	1 0	1	0	1 1	0	1
A B	SUM	CARRY															
0 0	0	0															
0 1	1	0															
1 0	1	0															
1 1	0	1															
10	Complete the state diagram for a D-Type flip-flop, by filling in the D input values on the directed lines.																
11	What is the frequency in MHz of a clock waveform that has a pulse width of 10ns and a duty cycle of 20%	20 MHz															
12	<p>The linear feedback shift register shown below is in the state 1001. What will the new stable state be after the next two clock pulses have been applied?</p> 	<p>Q3 = 1</p> <p>Q2 = 0</p> <p>Q1 = 1</p> <p>Q0 = 0</p>															

Examiner Use Only: