

USEFUL EQUATIONS – EEE123

Electric Circuits

Resistance (R) – units Ohms (Ω)

Resistors in series

$$R_{TOT} = R_1 + R_2 + R_3 + \cdots R_n$$

Resistors in parallel

$$\frac{1}{R_{TOT}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \cdots \frac{1}{R_n}$$

Resistance (Ohms law)

$$R = \frac{V}{I}$$

Resistance

$$R = \frac{\rho l}{A} = \frac{l}{\sigma A}$$

(l =length, m; A = cross-sectional area, m^2 ; ρ = resistivity, Ωm ; σ = conductivity, S/m)

Temperature dependence of resistors

$$R_{T_1} = R_0(1 + \alpha_0 T_1)$$

α_0 = temperature coefficient of resistance

R_0 = Resistance (Ω) at 0 °C

R_{T_1} = Resistance (Ω) at T_1 °C

T_1 = Temperature in °C

For temperatures T_1 and T_2 use ratio

$$\frac{R_{T_1}}{R_{T_2}} = \frac{(1 + \alpha_0 T_1)}{(1 + \alpha_0 T_2)}$$

Voltage across a resistor

$$V_R = IR$$

Power dissipated in a resistor

$$P = I^2 R = \frac{V^2}{R} = V \cdot I$$

Energy dissipated in a resistor

$$E = I^2 R t = \frac{V^2 t}{R} = V \cdot I \cdot t$$

Capacitance (C) – units Farads (F)

Charge (Q)

$$Q = I \cdot t \quad (\text{Constant current , } I)$$

$$Q = \int_0^t i(t) dt \quad (\text{Time varying current, } i(t))$$

$$Q = CV \quad (\text{Capacitance} \times \text{Voltage})$$

Capacitors in series

$$\frac{1}{C_{TOT}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \cdots \frac{1}{C_n}$$

Capacitors in parallel

$$C_{TOT} = C_1 + C_2 + C_3 + \cdots C_n$$

Voltage across a capacitor

$$V_c = \frac{Q}{C}$$

Energy stored in a capacitor

$$E = \frac{1}{2} CV^2$$

Inductance (L) – units Henrys (H)

Inductors in series

$$L_{TOT} = L_1 + L_2 + L_3 + \cdots L_n$$

Inductors in parallel

$$\frac{1}{L_{TOT}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots \frac{1}{L_n}$$

Voltage across an inductor

$$V_L = L \frac{dI}{dt}$$

Energy stored in an inductor

$$E = \frac{1}{2} LI^2$$

A.C. Circuits

Power dissipated in a resistance

$$P = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

For other circuits having capacitance and/or inductance, there is a phase shift, ϕ , between the current and voltage waveforms.

Real Power (P) (*Watts*)

$$P = V_{rms} I_{rms} \times \cos \phi$$

Reactive Power (Q) (*VARs*)

$$Q = V_{rms} I_{rms} \times \sin \phi$$

Power factor (p.f. or $\cos \phi$)

$$0 < \cos \phi < 1$$

Power = Energy s^{-1}

$$\text{Watts}(W) = Js^{-1}$$

Capacitive reactance

$$X_c = \frac{1}{j\omega C} = \frac{1}{j2\pi f C} = \frac{-j}{\omega C} = \frac{-j}{2\pi f C}$$


(ω = electrical frequency in rad/s (= $2\pi f$); f is the electrical frequency in Hz)

Inductive reactance

$$X_L = j\omega L = 2\pi f L$$

(ω = electrical frequency in rad/s (= $2\pi f$); f is the electrical frequency in Hz)

Series Resonant Circuit

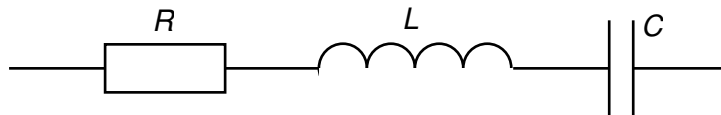

At resonance

$$X_c = X_L \quad \text{and} \quad Z = R$$


Frequency for resonance

$$\omega_r = \frac{1}{\sqrt{LC}} \quad \text{or} \quad f_r = \frac{1}{2\pi\sqrt{LC}}$$

Q factor

$$Q = \frac{\omega_r L}{R} = \frac{1}{\omega_r C R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Parallel Resonant Circuit

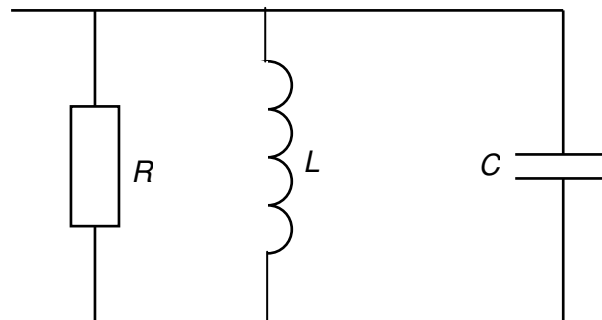

At resonance

$$X_c = X_L \quad \text{and} \quad Z = R$$

Frequency for resonance

$$\omega_r = \frac{1}{\sqrt{LC}} \quad \text{or} \quad f_r = \frac{1}{2\pi\sqrt{LC}}$$

Q factor

$$Q = \frac{R}{\omega_r L} = \omega_r C R = R \sqrt{\frac{C}{L}}$$

Transient Circuits

Current growth in an inductive circuit containing inductance and resistance:

Instantaneous current $i = I_0(1 - e^{-t/\tau})$ where $\tau = L/R$

Current decay in an inductive circuit containing inductance and resistance:

Instantaneous current $i = I_0 e^{-t/\tau}$ where $\tau = L/R$

Charging a capacitor through a resistor:

Instantaneous voltage $v = V_0(1 - e^{-t/\tau})$ where $\tau = RC$

Instantaneous current $i = I_0 e^{-t/\tau}$ where $\tau = RC$

Discharging a capacitor through a resistor:

Instantaneous voltage $v = V_0 e^{-t/\tau}$ where $\tau = RC$

Instantaneous current $i = -I_0 e^{-t/\tau}$ where $\tau = RC$

Magnetic Circuits

Reluctance (S) – units H^{-1}

$$S = \frac{l}{\mu_0 \mu_r A}$$

(l =length, m; A = cross-sectional area, m^2 ; μ_0 = permeability of free space (Hm^{-1}); μ_r = relative permeability)

Inductance (L)

$$L = \frac{N^2}{S}$$

(N = number of turns on the coil)

Flux density (B) – units Tesla (T)

$$B = \mu_0 \mu_r H = \frac{\phi}{A}$$

(H = magnetic field strength(A/m); ϕ = flux (Wb))

MagnetoMotive Force – MMF

$$F = H \cdot l = N \cdot I = \phi S$$

Induced EMF (E) – units Volts (V)

$$E = N \frac{d\phi}{dt}$$

Transformers (ideal)

Voltage ratio

$$\frac{V_{in}}{V_{out}} = \frac{N_1}{N_2} = \text{turns ratio}$$

Current ratio

$$\frac{I_{in}}{I_{out}} = \frac{N_2}{N_1} = \frac{1}{\text{turns ratio}}$$

Impedance ratio

$$\frac{Z_{in}}{Z_{out}} = \left(\frac{N_1}{N_2} \right)^2 = (\text{turns ratio})^2$$

V_{in} = voltage across primary winding;

I_{in} = current through primary winding;

V_{out} = voltage across secondary winding;

I_{out} = current through secondary winding;

Induced voltage

$$V_{rms} = 4.44f \cdot N \cdot \phi_{max}$$

(ϕ_{MAX} = maximum flux in the transformer core (Wb); f = frequency (Hz))

Mechanics

Mechanical Power (W) $P_{mech} = \omega_{mech} \cdot T$

(T = torque (Nm); ω_{mech} = rotational speed (rad/s))

Rotational speed (rad/s) $\omega_{mech} = \frac{2\pi}{60} \cdot n$

(n = speed in revs per minute)

Torque $T = F \cdot r$

(F = force(Nm); r = radius (m))

Gearbox (no losses) $\omega_{in} T_{in} = \omega_{out} T_{out}$

DC motors

Force on a current carrying conductor $F = B \cdot I \cdot l$

(B = flux density (T); I = current (A); l = length (m))

DC motor armature voltage $V_A = E_A + I_A R_A$

(E_A = induced emf (V); I_A = armature current (A); R_A = armature resistance (Ω))

Induced voltage, E_A is proportional to the speed of rotation, ω (rad/s), and the flux, ϕ (Wb).
Torque, T is proportional to the armature current, I (A) and the flux, ϕ (Wb).

For a wound field machine:

Induced emf (V) $E_A = K I_F \omega$

Torque (Nm) $T = K I_F I_A$

(I_F = field current (A); K = constant)

For a permanent magnet machine:

Induced emf (V) $E_A = K_E \cdot \omega$

Torque (Nm) $T = K_T \cdot I_A$

(K_E (V/rad/s) and K_T (Nm/A) are constants with the same numerical values)

Electronic Circuits

$$g_m = \frac{e I_C}{kT} \quad r_{be} = \frac{\beta}{g_m} \quad h_{FE} = \frac{I_C}{I_B} \quad \beta = \frac{\Delta I_C}{\Delta I_B} = \frac{i_c}{i_b} \quad \tau = RC$$

$$I = C \frac{dV}{dt} \quad \omega = 2\pi f \quad V(t) = (V_{START} - V_{FINISH}) \exp\left(\frac{-t}{\tau}\right) + V_{FINISH}$$

$$V_{AVE} = \frac{V_P}{\pi} \text{ for a half-wave rectified sinusoid} \quad V_{rms} = \frac{V_P}{\sqrt{2}} \text{ for a sinusoid}$$

$$v_0 = A_v (v^+ - v^-) \quad \frac{kT}{e} = 0.026 \text{ V}$$

All the symbols have their usual meanings

Standard Unit Multipliers

$$p = \times 10^{-12}, \quad n = \times 10^{-9}, \quad \mu = \times 10^{-6}, \quad m = \times 10^{-3}, \quad k = \times 10^3, \quad M = \times 10^6, \quad G = \times 10^9$$