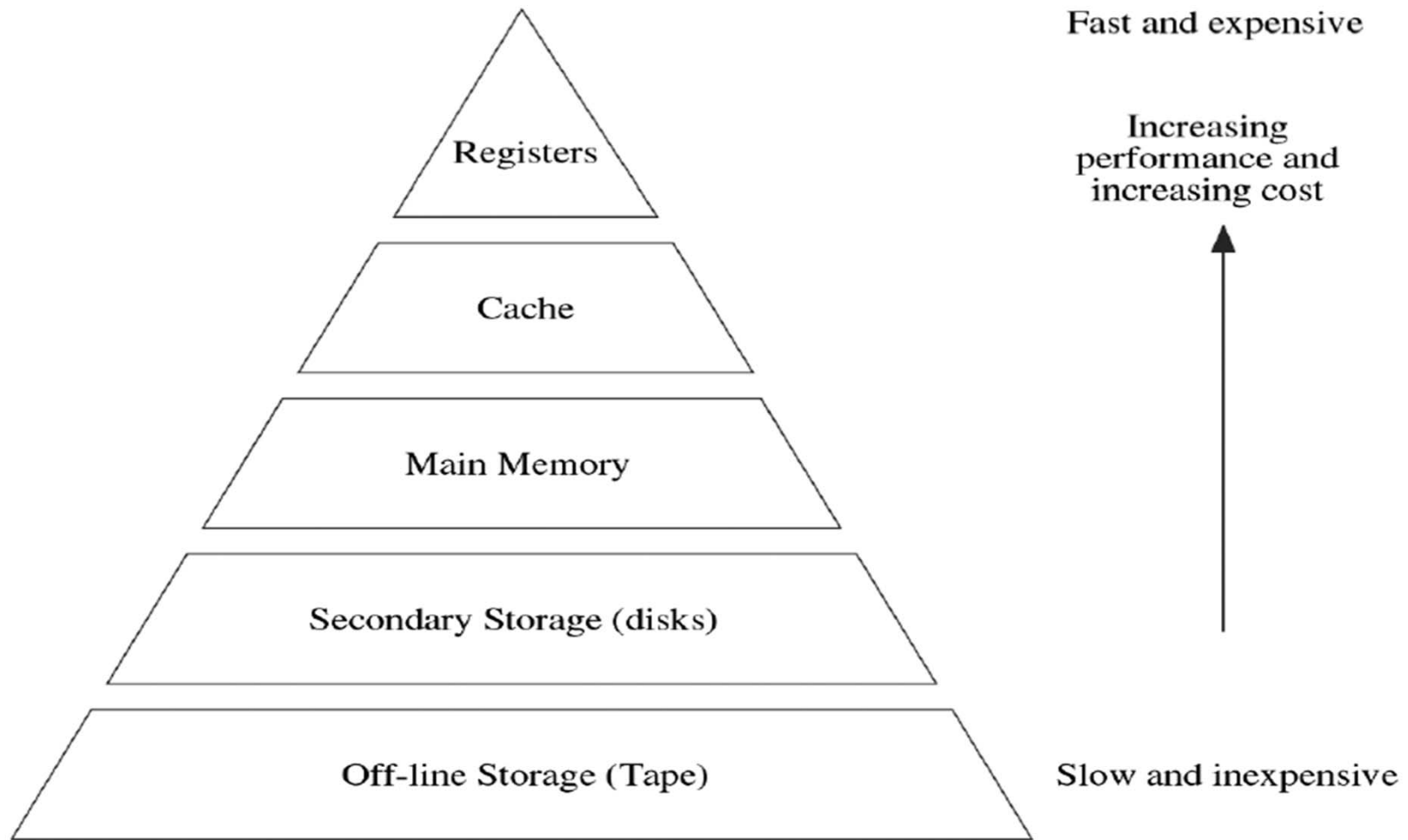


# Memory Sub-Systems

- Memory Hierarchy
- Principle of Locality
- Access Times
- Memory Map




# Principle of Locality

- ❑ This is really an observation, not a principle.
- ❑ Temporal Locality.
  - If a memory location has been accessed, it will *tend* to be accessed again soon
- ❑ Spatial Locality.
  - If a given memory location has been accessed, the next location to be accessed will *tend* to be nearby


Memory cache schemes aim to exploit both temporal and spatial locality.

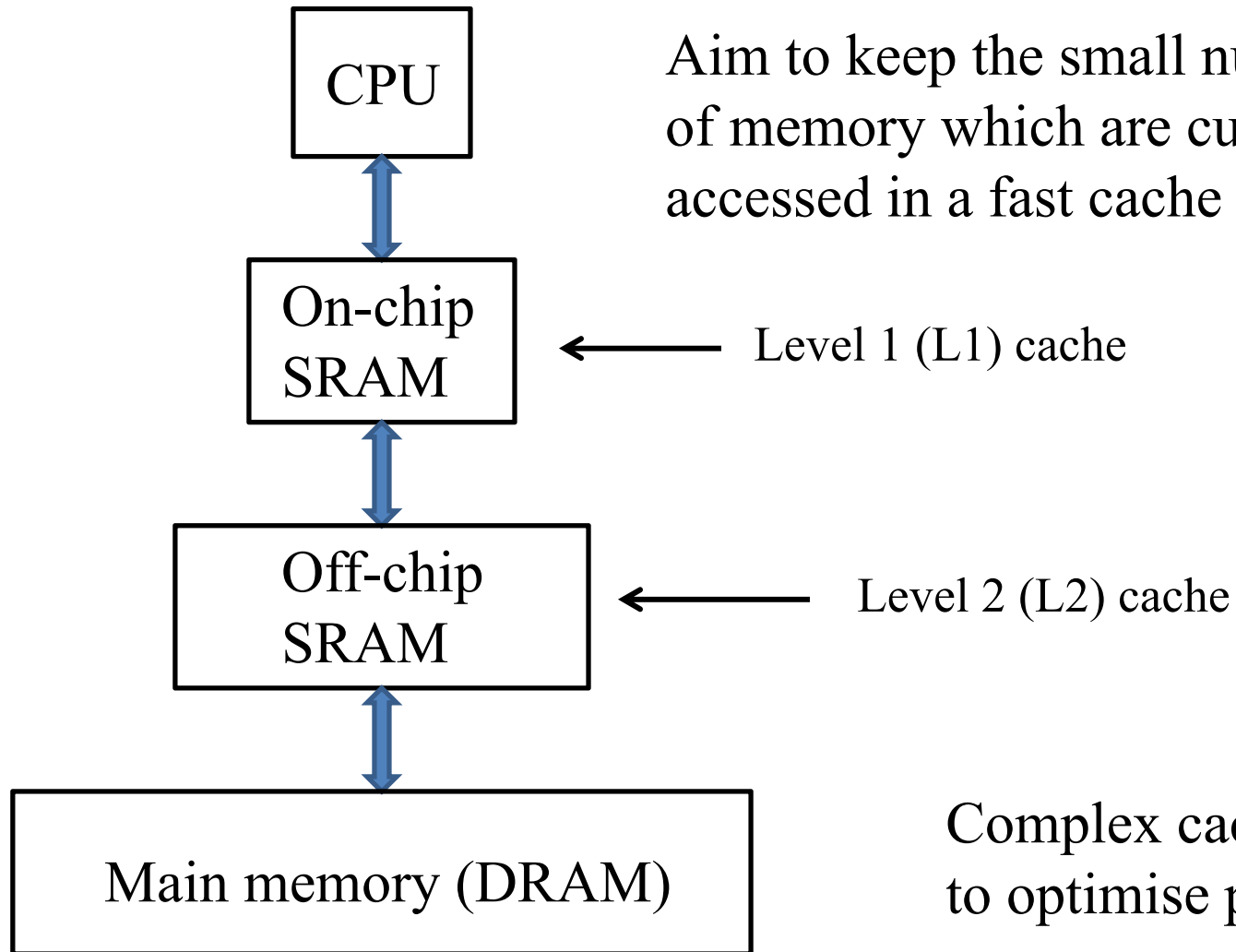Aim to keep the small number of blocks of memory which are currently being accessed in a fast cache memory



Complex cache schemes exist to optimise performance.

# CPU-Memory Interfacing

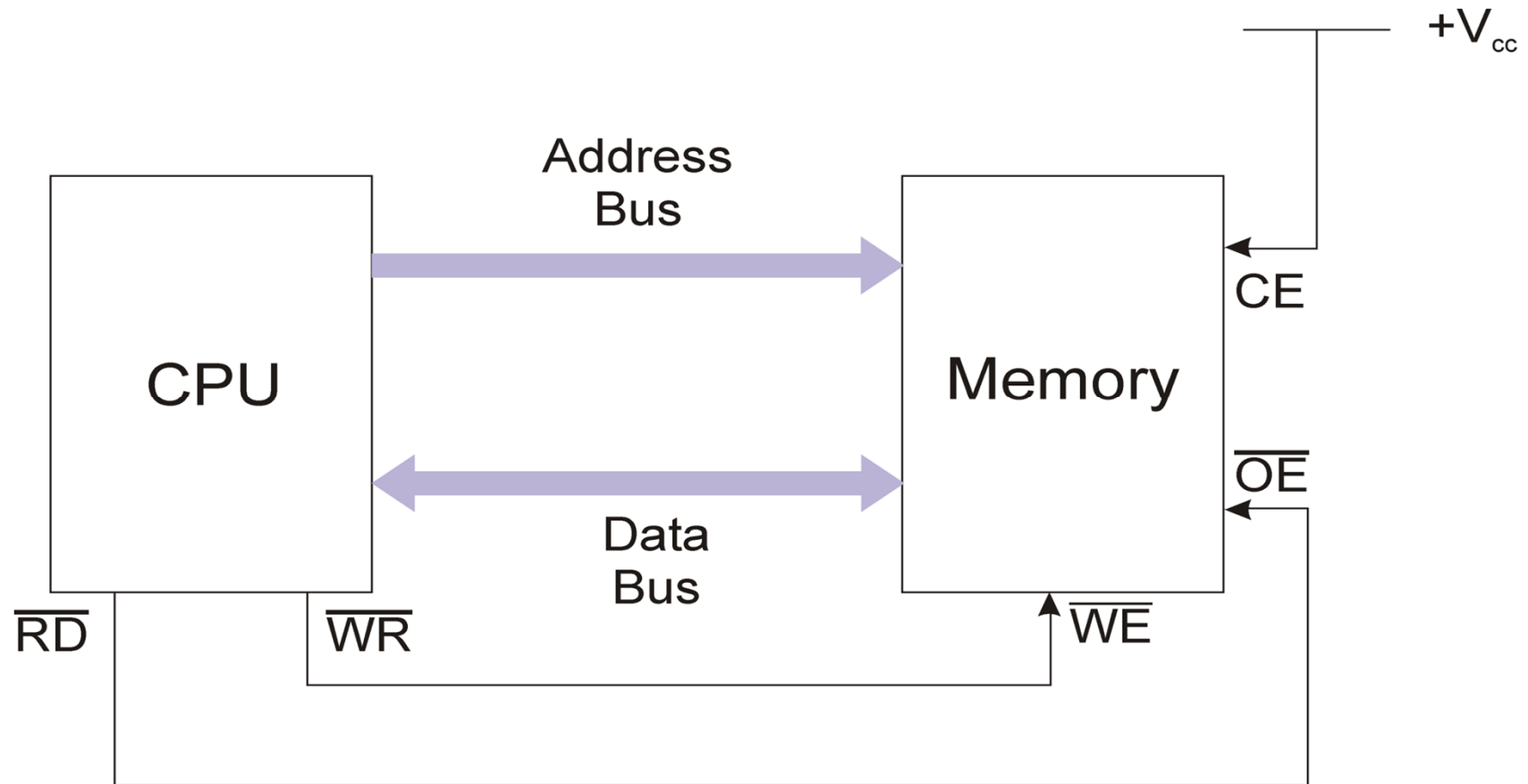


# Memory Cycles

The timing behaviour of a memory cycle is normally presented in a timing diagram where timings of signals are related back to the clock.

- For outputs: the timings are a guarantee of what the  $\mu\text{P}$  will do.
- For inputs: the timings are a specification to which the external system MUST adhere.
- All timing-relationships are relevant and during a design, the  $\mu\text{P}$  timing information must be related to timing information for devices to which it will be connected.

# Typical Memory Read

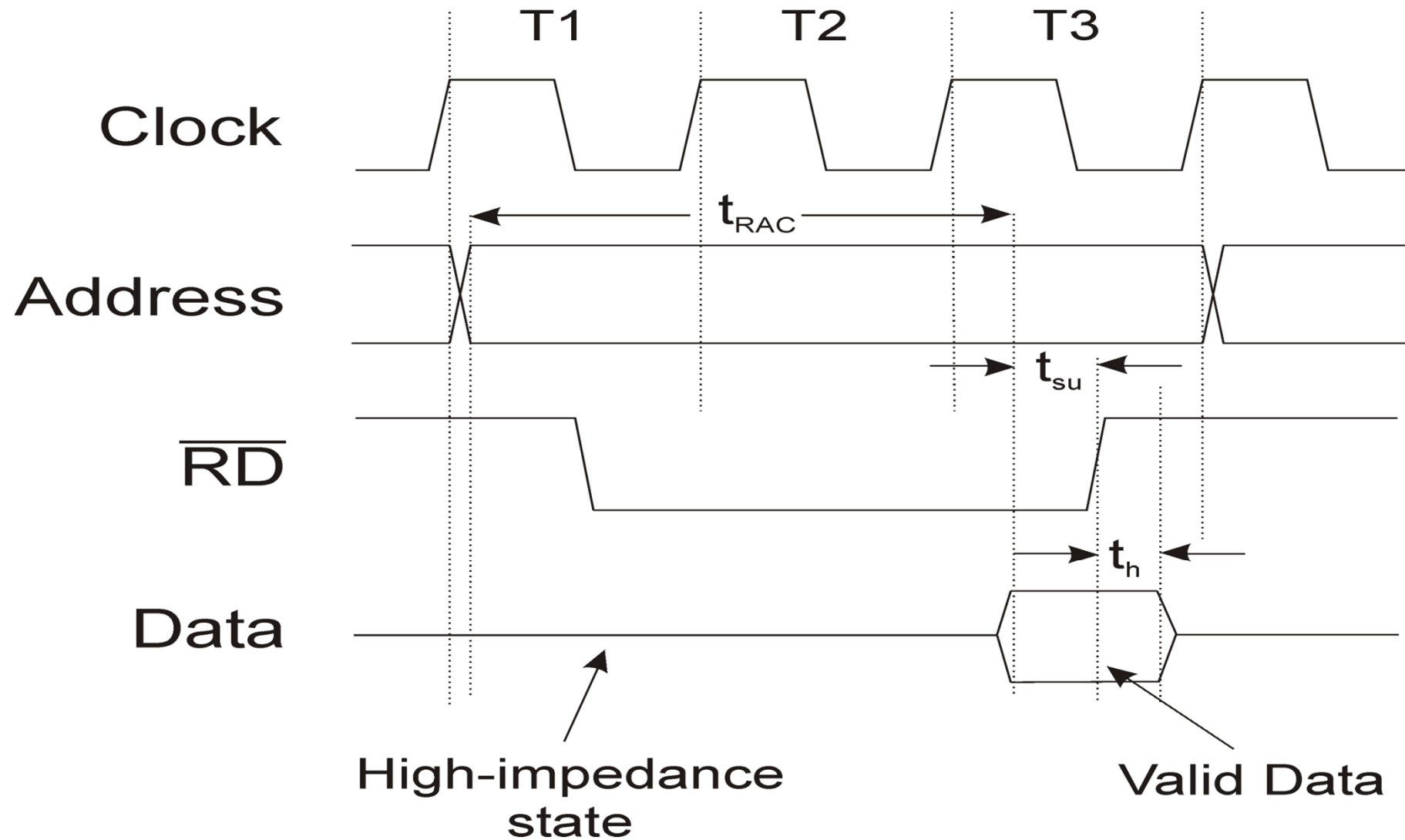


*if read*

- 1 Set up the address of the location to be accessed and enable the memory,
- 2 Wait,
- 3 Set up a signal indicating that data is to be retrieved ( $\overline{\mathbf{RD}}$ ),
- 4 Wait for the data to be retrieved from the memory and placed on the data bus inputs,
- 5 Sample the data on the data bus inputs,
- 6 Disable the memory.



# Typical Memory Write

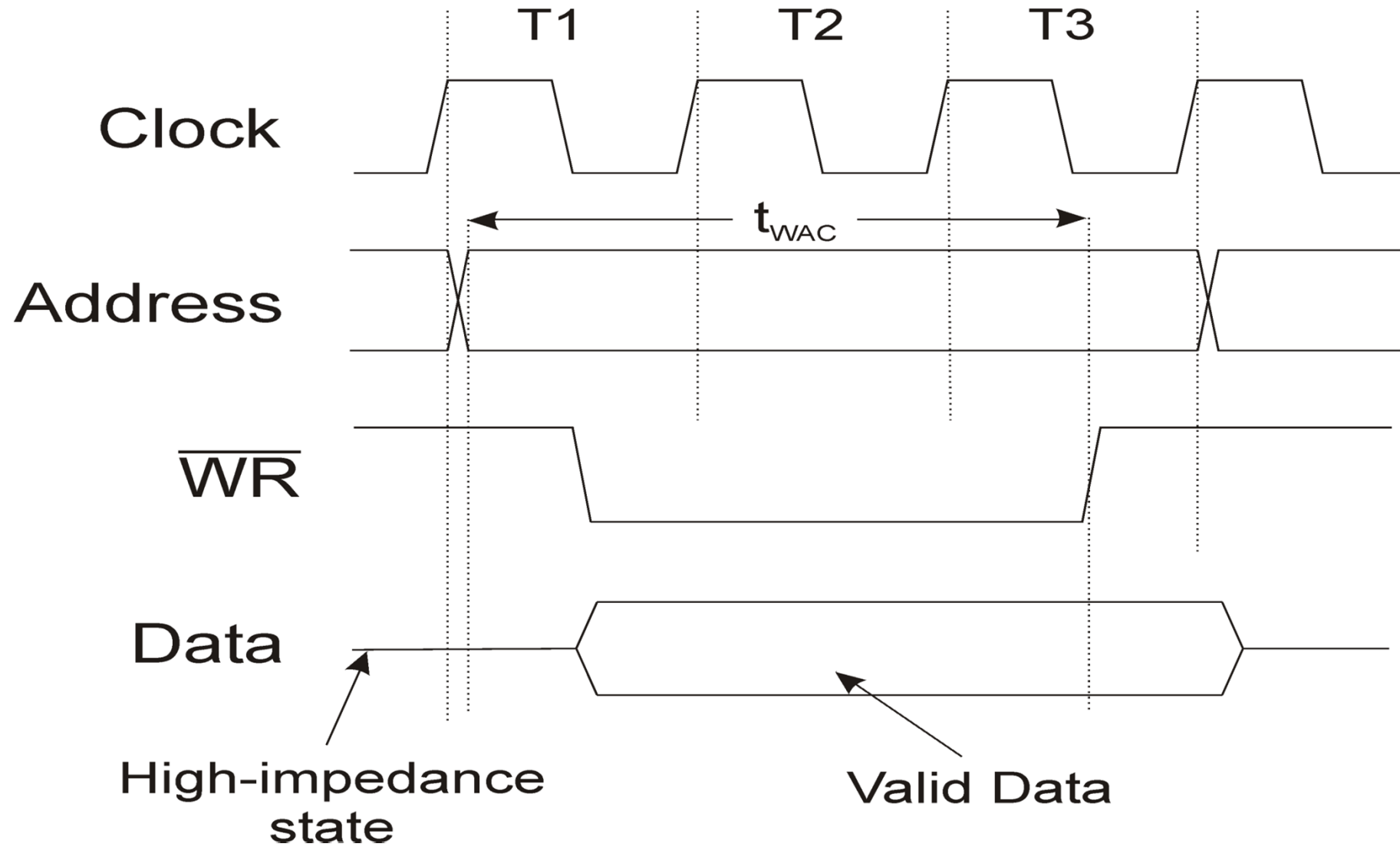


## *if write*


- 1 Set up the address of the location to be accessed and enable the memory,
- 2 Wait,
- 3 Set up a signal indicating that data is to be stored ( $\overline{WR}$ ),
- 4 Place the data to be written on the data bus outputs (which must be connected to the memory data inputs,
- 5 Wait for the memory device to store (or prepare to store) the data,
- 6 Signal the end of the write and disable the memory.
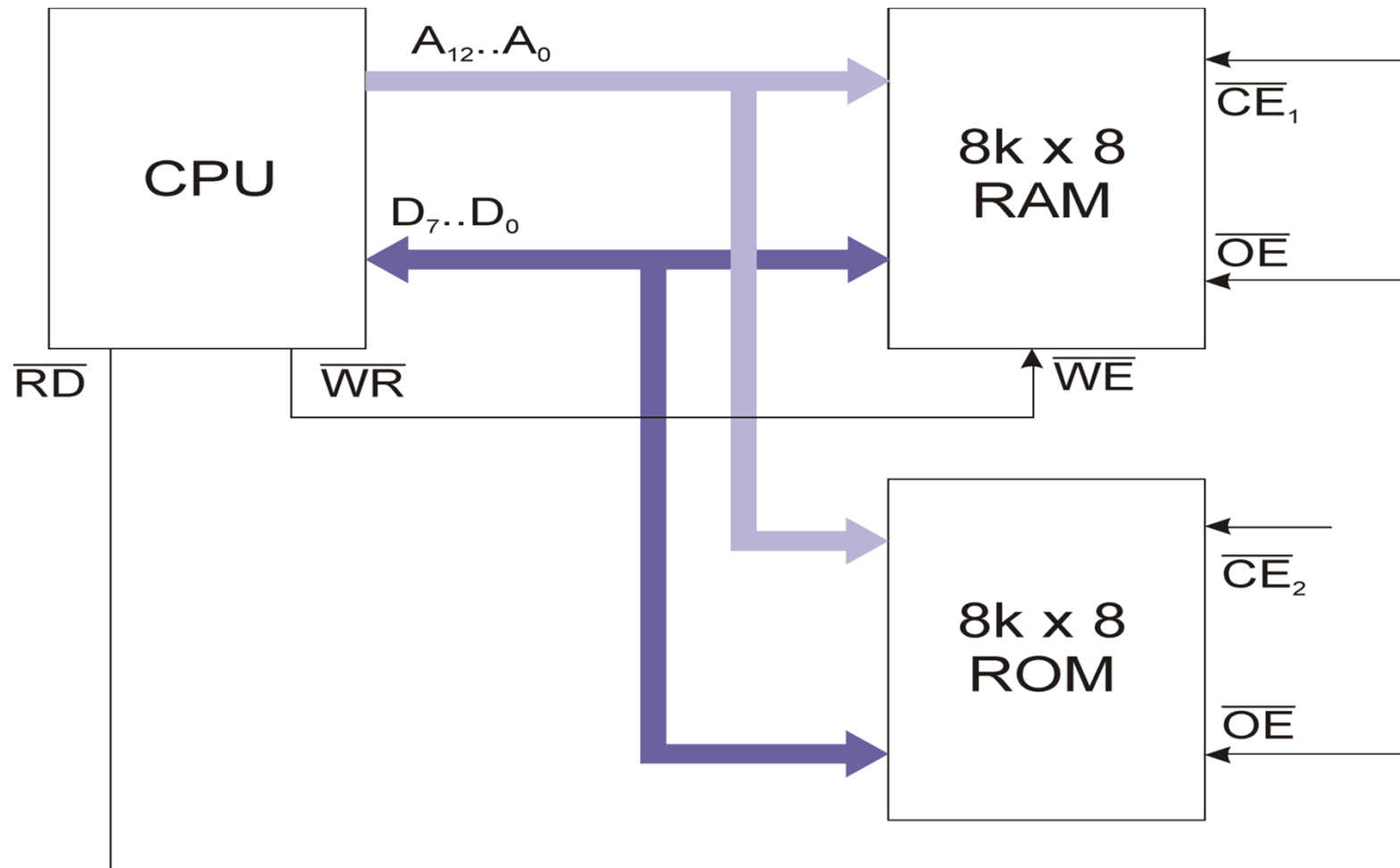
# Memory interfacing to two memory chips

CPU has 8 bit data bus  
and 16 bit address bus.




# Memory map

 

# Memory interfacing to two memory chips


## Example 2:

 


4 address bits gives 16  
addressable locations

8 bit data bus can write  
a byte of data to the  
memory

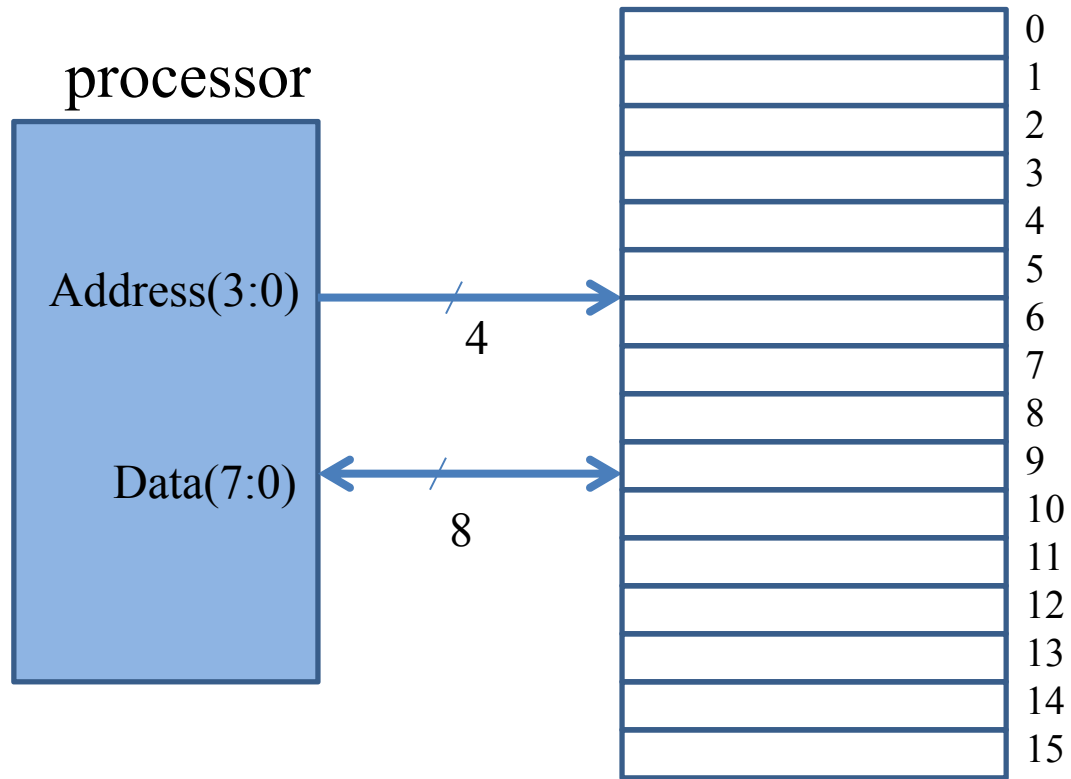
single memory with 16 addressable locations



 the single 16 row memory could be replaced by  
two 8 row memory chips




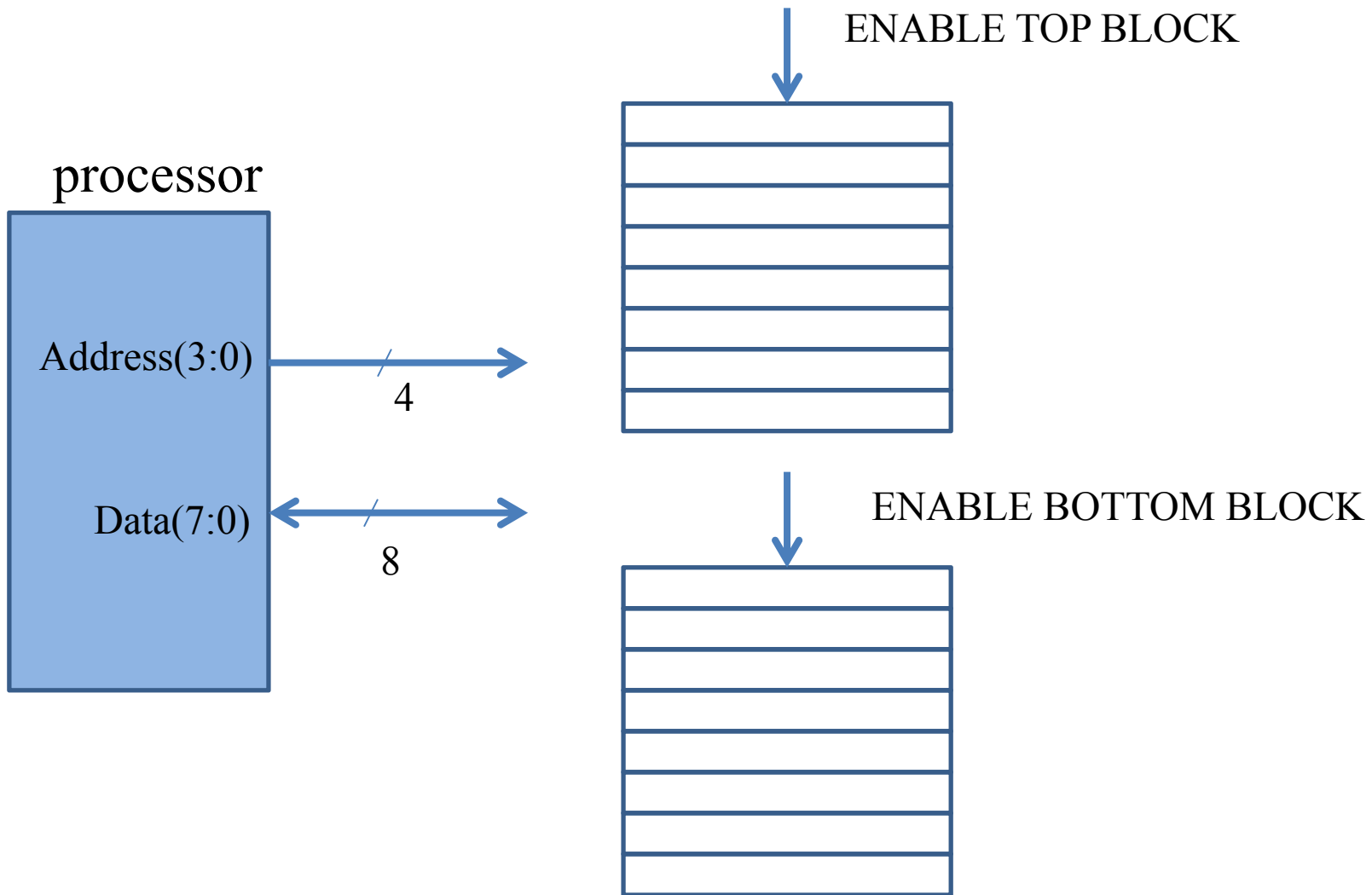note how the msb  
changes in the  
count sequence







Use A(3) to select

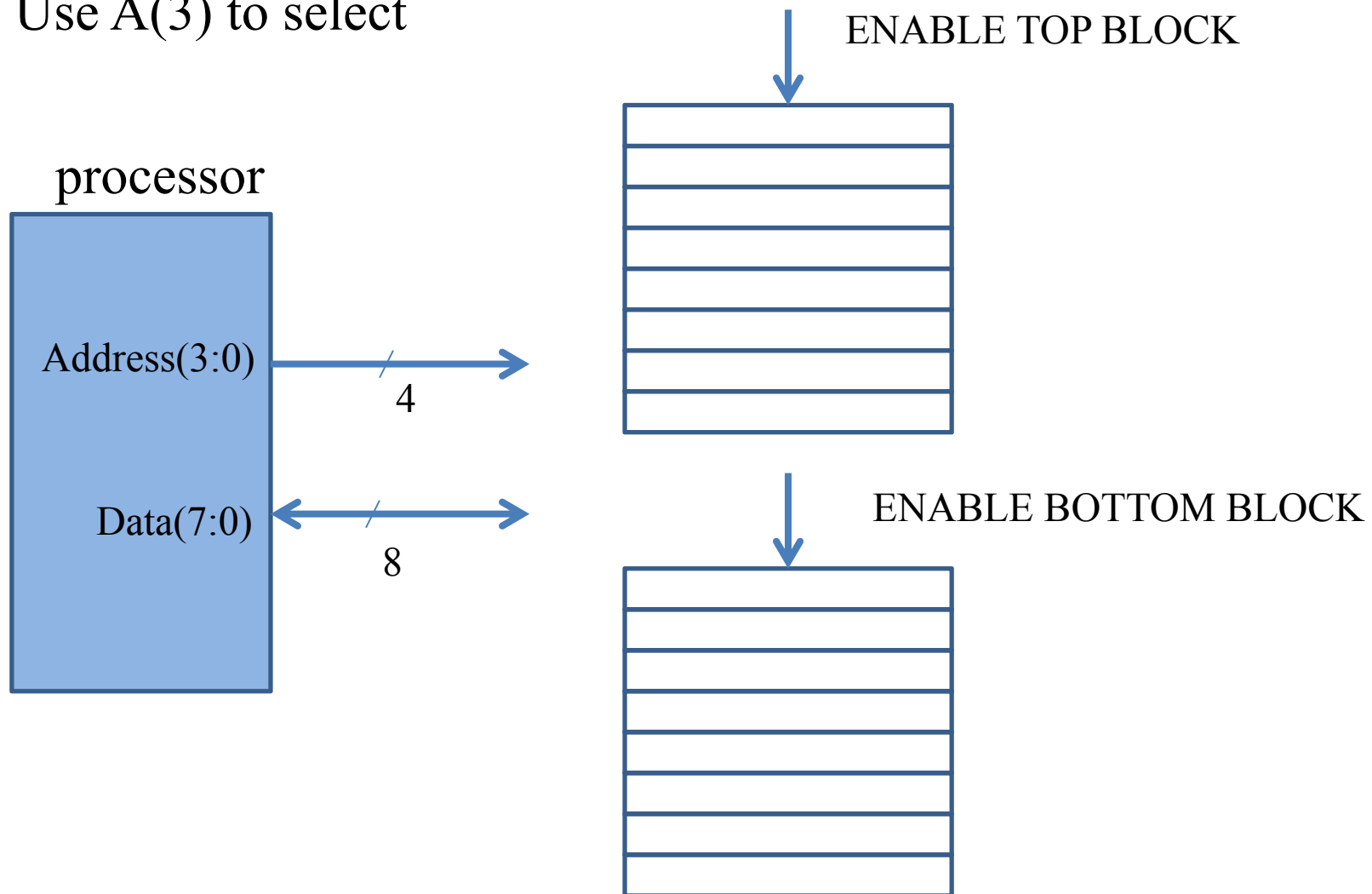

Use A(3) to select

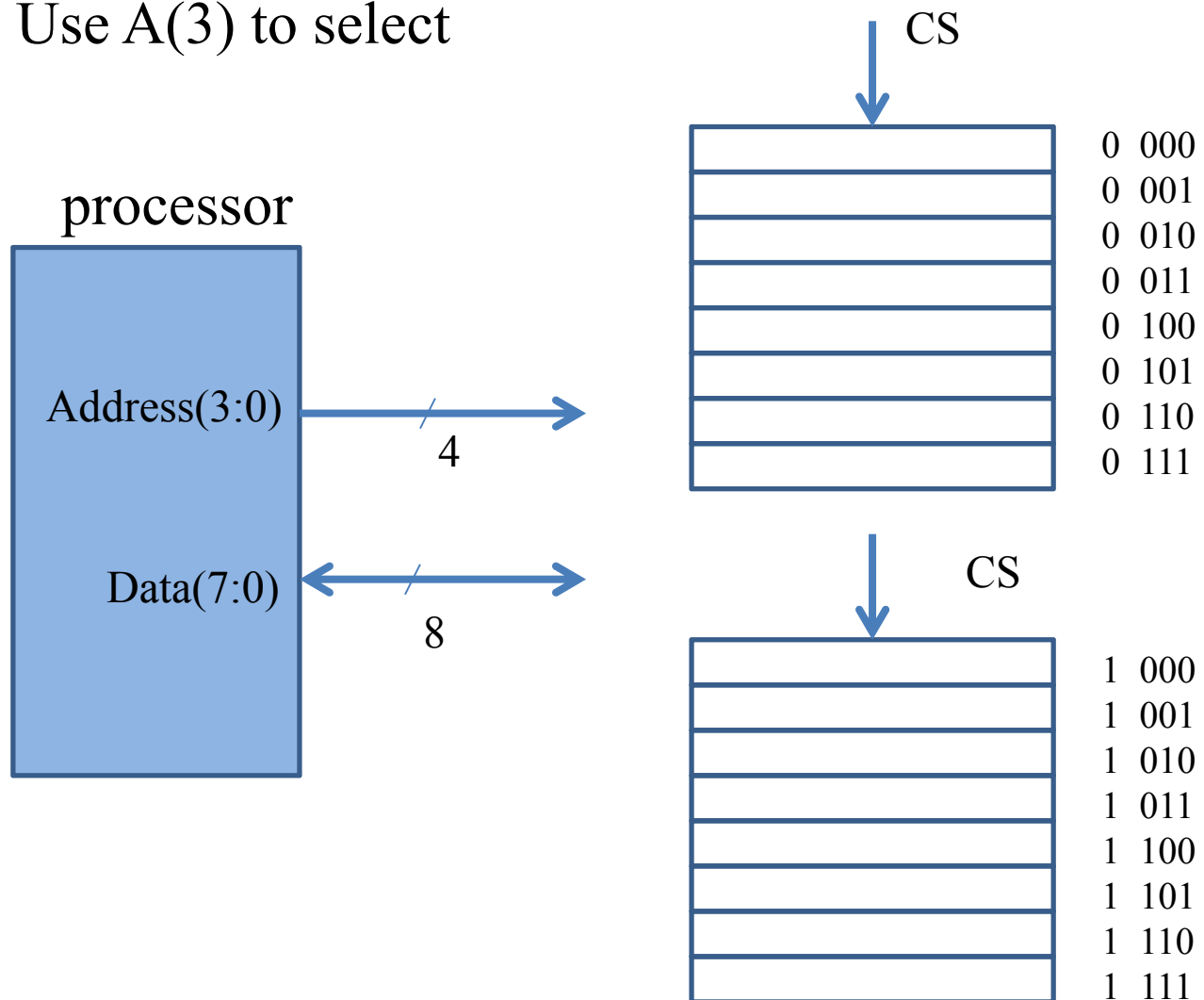


Use A(3) to select

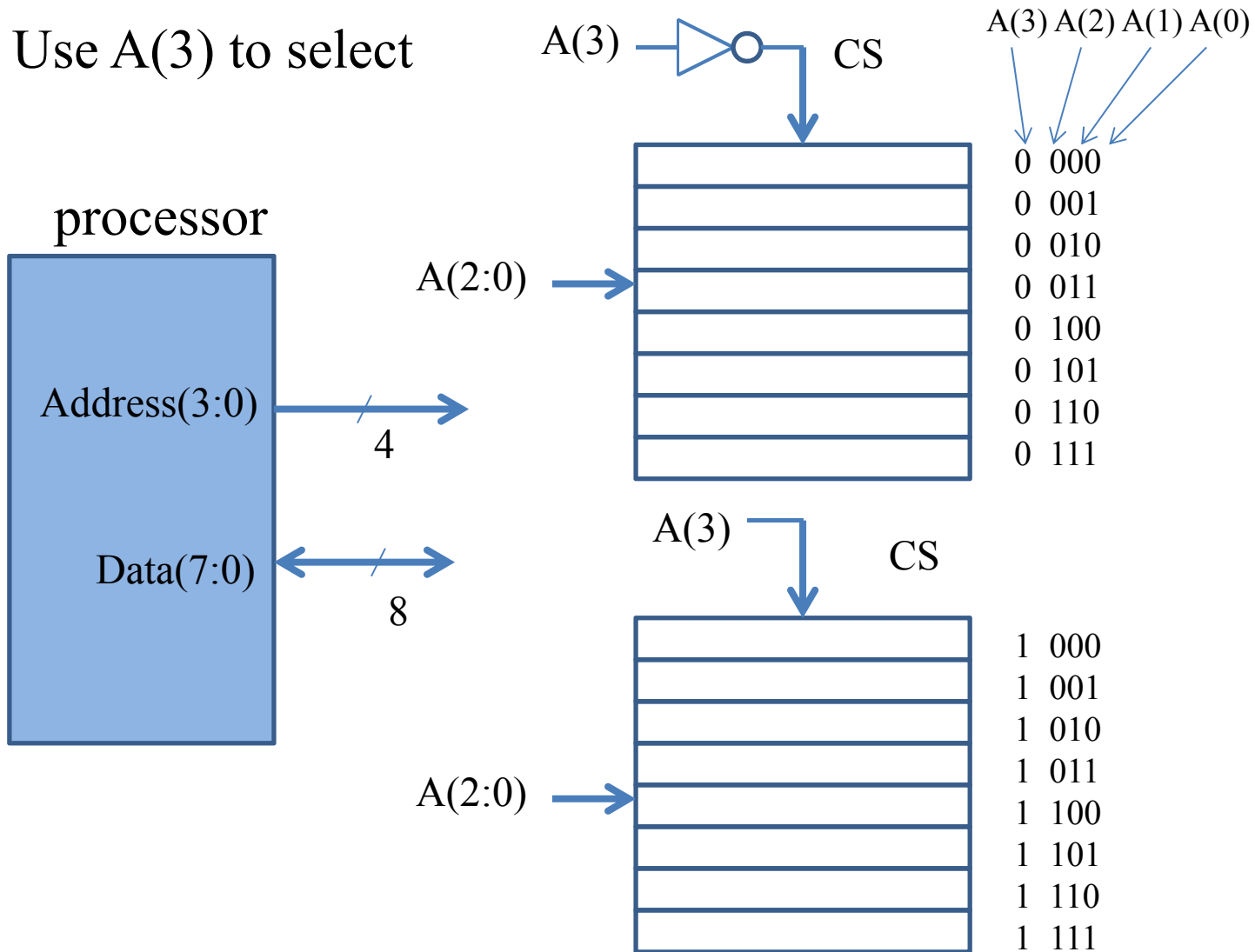

However, the device is unlikely to occupy the whole address space. How is the device placed into the address map?


- The least significant address bits are routed to the address inputs, the most significant are routed to an 'address decoder' which generates the CS input.
- If CS is inactive the device ignores all their inputs and keeps its outputs inactive.
- 'Decoding' the address corresponds to driving CS active only when a certain pattern of bits appears on the decoded address bits.

# Decoders

 

An  $n$ -input decoder has  $2^n$  output lines.

 - In this case,  $A(7:0)$  are inputs to the device (256 internal locations).  $A(15:8)$  are decoded, say at  $83_H$ , by the decoding logic.
- The device will be activated at any address beginning  $83_H$ . This is the range  $8300_H$  to  $83FF_H$ .



- Devices usually occupy address ranges which are a power of 2, and are based at addresses which are a multiple of this power of 2. This simplifies the address decoding circuitry.
- Furthermore, sometimes all of the address bits are not decoded. This simplifies decoding even more but causes the block of memory to be 'mirrored', i.e. to appear at other addresses in the memory map.
- So, if only A15..12 were decoded at  $8_H$ , the device would appear between  $8000_H$  to  $80FF_H$ ,  $8100_H$  to  $81FF_H$  ..  $8F00_H$  to  $8FFF_H$ .
- Different devices can occupy different ranges of addresses. The only constraint is that *no two address ranges should overlap*.

# Endian-ness

Considering storing the data  $0A1B2C3D_H$  in a byte wide memory. There are two possibilities.

