

**The University of Sheffield**  
**Department of Electronic and Electrical Engineering**

**EEE101 Problem Sheet Solutions**

## dc Circuit Analysis

**Q1** For the circuit of figure 1 find  $I$  using any method you like.  
 What is the power dissipation in  $R_1$ ?

(i) Nodal analysis . . .

Choose node **B** as 0 V reference point and sum currents at node **A** . . .

$$I_3 = I_1 + I \quad \text{or} \quad \frac{-V_2 - V_A}{R_3} = \frac{V_A - V_1}{R_1} + \frac{V_A}{R_2}$$

$$\text{or} \quad -\frac{V_2}{R_3} + \frac{V_1}{R_1} = V_A \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]. \quad \text{Using } V_1 = 10 \text{ V and } V_2 = 6 \text{ V gives } V_A = -\frac{5}{4} \text{ V}$$

$$\text{Thus } I = \frac{V_A}{R_2} = -0.25 \text{ A and } P_{R1} = \frac{V_{R1}^2}{R_1} = \frac{(V_1 - V_A)^2}{R_1} = 10.5 \text{ W.}$$

(ii) Loop analysis . . .

Choose two loops - say  $V_1, R_1, R_2$  and  $R_2, R_3, V_2$  and call the circulating currents  $I_{L1}$  and  $I_{L2}$  respectively. Let  $I_{L1}$  circulate in a clockwise direction and  $I_{L2}$  in an anticlockwise one (you could choose different directions) . . .

$$\text{loop 1; } 10 = I_{L1}R_1 + (I_{L1} + I_{L2})R_2 \quad \text{or} \quad 10 = (R_1 + R_2)I_{L1} + R_2I_{L2} \quad \text{or} \quad 10 = 17I_{L1} + 5I_{L2}$$

$$\text{loop 2; } 6 + I_{L2}R_3 + (I_{L2} + I_{L1})R_2 = 0 \quad \text{or} \quad 6 + I_{L2}(R_3 + R_2) + I_{L1}R_2 = 0 \quad \text{or} \quad -6 = 5I_{L1} + 9I_{L2}$$

$$\text{Solve these two equations to get } I_{L1} = \frac{15}{16} \text{ A and } I_{L2} = -\frac{19}{16} \text{ A. } I \text{ is then given by } I = I_{L1} + I_{L2}.$$

(iii) Superposition . . .

Easiest approach is to find the voltage across  $R_2$  due to the sources  $V_1$  and  $V_2$  and then calculate  $I$

$$V_{R2} \text{ due to } 10\text{V is } V_{R2} = 10 \frac{R_2 // R_3}{R_1 + R_2 // R_3} = 10 \frac{20/9}{12 + 20/9} = \frac{200}{128} = \frac{25}{16} \text{ V}$$

$$V_{R2} \text{ due to } -6\text{V is } V_{R2} = -6 \frac{R_1 // R_2}{R_3 + R_1 // R_2} = -6 \frac{60/17}{4 + 60/17} = -\frac{360}{128} = -\frac{45}{16} \text{ V}$$

$$\text{Thus } V_{R2TOT} = \frac{25}{16} - \frac{45}{16} = -\frac{20}{16} = -1.25 \text{ V which gives the same } I \text{ as the other two methods.}$$


**Q2** Using any method you like, find the values of  $I$  and  $V$  in figure 2.

It is easiest here to sum voltages around the outer loop to find  $I$  . . .


$$6I + 8(I + 5) + 4(I + 5 - 2) = 0 \quad \text{or} \quad 18I + 52 = 0$$

$$\text{Thus } I = -2.89 \text{ A and } V = 8(-2.89 + 5) = 16.89 \text{ V}$$

It would also be easy to use Norton to Thevenin transformations on the  $6 \Omega$  and  $5 \text{ A}$  and the  $4 \Omega$  and  $2 \text{ A}$  combinations to find  $V$ .  $V$  will give the current through the  $8 \Omega$  so  $I$  can easily be found.

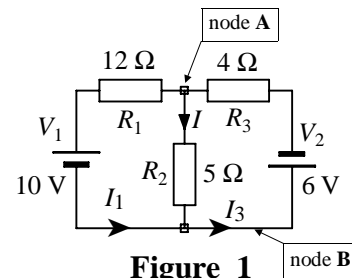

**Figure 1**

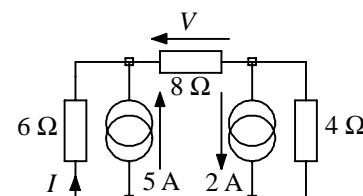

**Figure 2**

**Q3** In figure 3,  $I$  is initially 1 A. Use nodal analysis to find  $I_S$  and  $V_R$ . What value of  $I$  is necessary to give  $V_R = -4$  V?


Use node **B** as the reference potential. Sum currents at node **A** . . .

$$I_S + I = I_R \quad \text{or} \quad \frac{5 - V_A}{3} + 1 = \frac{V_A}{2} \quad \text{or} \quad V_A (= V_R) = 3.2 \text{ V.}$$

Thus  $I_R = V_R/2 = 1.6$  A and since  $I_S + I = I_R$ ,  $I_S = 0.6$  A

The current required to give  $V_R = -4$  V is easy to work out because that condition means that all node voltages are known so currents can be easily worked out . . .

$$I_S + I = I_R \quad \text{or} \quad \frac{5 - (-4)}{3} + I = \frac{(-4)}{2} \quad \text{or} \quad I = -5 \text{ A}$$

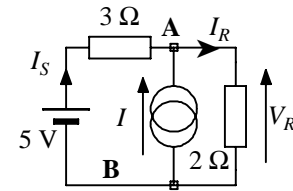

**Figure 3**

**Q4** For the circuit of figure 4, use nodal analysis and superposition to find  $I_1$  and the potential difference  $V_4 - V_3$ ,  $V_{4-3}$ . What is the power dissipation in  $R_4$ ?

(i) Nodal analysis

Take node **3** as the 0 V reference. The node voltages  $V_2$  and  $V_4$  are unknowns. Summing currents . . .

$$\text{at node 2; } I_1 + I_3 = I_4 \quad \text{or} \quad \frac{10 - V_2}{5} + \frac{V_4 - V_2}{2} = \frac{V_2}{5} \quad \text{or} \quad 20 = 9V_2 - 5V_4$$

$$\text{at node 4; } I_2 + 5 = I_3 \quad \text{or} \quad \frac{10 - V_4}{2} + 5 = \frac{V_4 - V_2}{2} \quad \text{or} \quad 20 = -V_2 + 2V_4$$

solving these equations yields  $V_4 = 200/13 = 15.39$  V and  $V_2 = 140/13 = 10.77$  V.

$$P_{R4} = \frac{V_2^2}{R_4} = \frac{10.77^2}{5} = 23.2 \text{ W}$$

$$I_1 = \frac{10 - \frac{140}{13}}{5} = -\frac{2}{13} = -0.15 \text{ A}$$

(ii) Superposition

$V_4$  due to 10V (replace 5 A source with an open circuit) . . .

Current from 10V source,  $I_S = \frac{10}{5/(2+2) + 5} = \frac{90}{65} = \frac{18}{13}$  A. So  $V_{R4} = \frac{18}{13} \times 5 = \frac{90}{13}$  V. The voltage at node **4** is 10 V minus the voltage across the left hand  $2\Omega$  resistor. The difference between 10 V and  $V_{R4}$  is shared equally

$$\text{between the two } 2\Omega \text{ resistors so } V_{4(10V)} = 10 - \frac{10 - \frac{90}{13}}{2} = \frac{110}{13} \text{ V.}$$

$V_4$  due to 5A (replace 10V with a short circuit) . . .


The current source sees a parallel combination of the left hand  $2\Omega$  and right hand  $2\Omega$  in series with the two  $5\Omega$  resistors in parallel. Thus  $V_{4(5A)} = 5 \times 2/(2+5/5) = 5 \times \frac{2 \times 4.5}{2+4.5} = 5 \times \frac{9}{6.5} = \frac{90}{13}$  V.

$$V_{4TOT} = 110/13 + 90/13 = 200/13 = 15.39 \text{ V}$$

$I_1$  due to 10 V is that portion of the total  $I_S$  that flows through the  $5\Omega$  arm of the parallel combination of the two  $2\Omega$  resistors and the top  $5\Omega$  resistor

$$I_{1(10V)} = \frac{18}{13} \times \frac{4}{9} = \frac{8}{13} \text{ A.}$$

$I_1$  due to the 5A source is the current flowing through one of the two parallel  $5\Omega$  resistors. This will be half the

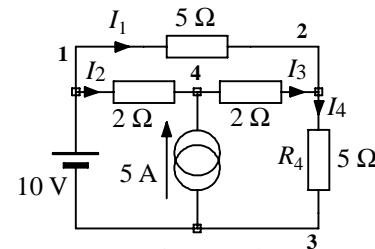


**Figure 4**

current that flows down the arm containing the  $5\ \Omega$  resistors and will be negative. Using current splitting,

$$I_{1(5A)} = -5 \times \frac{2}{6.5} \times \frac{1}{2} = -\frac{10}{13}\text{ A}.$$

Thus  $I_{1TOT} = 8/13 - 10/13 = -2/13 = -0.15\text{ A}$

**Q5** Use loop analysis and superposition to find  $I_2$  and  $I_4$  in the circuit of figure 5a. State with brief reasoning which component could be replaced by a short circuit without affecting either of these currents.

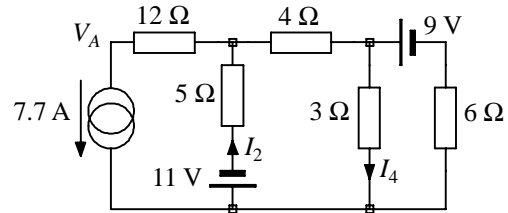

**Figure 5a**

(i) loop analysis

Choose three current loops. The choice here is three counter-clockwise loops;  $I_A$  through  $7.7\text{ A}$ ,  $11\text{ V}$ ,  $5\ \Omega$  and  $12\ \Omega$ ;  $I_B$  through  $3\ \Omega$ ,  $4\ \Omega$ ,  $5\ \Omega$  and  $11\text{ V}$ ;  $I_C$  through  $3\ \Omega$ ,  $6\ \Omega$  and  $9\text{ V}$ . Many other choices are possible. The thing to remember here is that the objective of the loop method is to leave you with the minimum number of unknowns necessary to solve the circuit. In loop A it is clear that  $I_A = 7.7\text{ A}$  so there is no need to investigate loop A further. (But if you did investigate further, you would need to define a voltage drop  $V_A$  across the current source in order to complete the sum of voltage drops around loop A.)

For loop B;  $11 = 3(I_B - I_C) + 4I_B + 5(I_B - I_A) = 12I_B - 3I_C - 5 \times 7.7$  or  $49.5 = 12I_B - 3I_C$

For loop C;  $9 = 3(I_C - I_B) + 6I_C = 9I_C - 3I_B$

There are many approaches that can be used to solve this pair of equations. Here we shall multiply the loop C equation by 4 and add it to the loop B equation to eliminate  $I_B$  . . .

$$49.5 + 36 = 0 + (36 - 3)I_C \text{ or } 85.5 = 33I_C \text{ or } I_C = 85.5/33 = 2.591\text{ A}$$

Substituting in the loop C equation,  $3 = 3I_C - I_B = \frac{85.5}{11} - I_B$  and so  $I_B = 52.5/11 = 4.773\text{ A}$

Then  $I_2 = I_A - I_B = 7.7 - 4.773 = 2.93\text{ A}$  and  $I_4 = I_C - I_B = 28.5/11 - 52.5/11 = -24/11 = -2.18\text{ A}$

(ii) superposition

The important issue here is to make sure the partial circuit is interpreted correctly in each case.

(a)  $I_2$  and  $I_4$  due to the  $7.7\text{ A}$  source - replace  $11\text{ V}$  and  $9\text{ V}$  with short circuits as shown in figure 5b . . .

The partial circuit consists of two parallel paths, one of  $5\ \Omega$  through which  $I_2$  flows and one through the series parallel combination of  $(6\ \Omega // 3\ \Omega)$  in series with  $4\ \Omega$ , which join forces at the top of  $5\ \Omega$  to return the  $7.7\text{ A}$  through the  $12\ \Omega$  to the source.

The combined resistance of  $(6\ \Omega // 3\ \Omega)$  in series with  $4\ \Omega$  is  $6\ \Omega$  so  $I_2$  is that fraction of  $7.7\text{ A}$  that takes the  $5\ \Omega$  route, ie


$$I_{2(7.7A)} = 7.7 \times \frac{6}{11} = 4.2\text{ A}$$

$I_4$  is the division of  $(7.7 - I_2)$  between  $3\ \Omega$  and  $6\ \Omega$ , ie


$$I_{4(7.7A)} = -(7.7 - 4.2) \times \frac{6}{9}\text{ A} = -\frac{7}{3}\text{ A}. \text{ Note the "-" sign.}$$

(b)  $I_2$  and  $I_4$  due to the  $11\text{ V}$  source - replace  $7.7\text{ A}$  with an open circuit and  $9\text{ V}$  with a short circuit as shown in figure 5c . . .

The  $11\text{ V}$  source sees  $9\ \Omega$  ( $5\ \Omega + 4\ \Omega$ ) in series with the parallel combination  $3\ \Omega // 6\ \Omega$  ( $= 2\ \Omega$ ). Thus

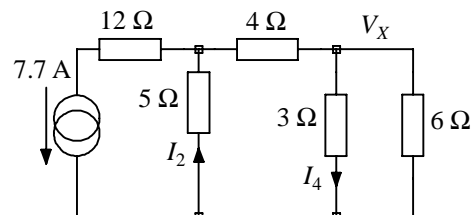

**Figure 5b**

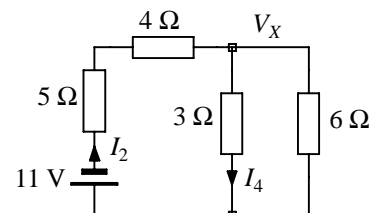

**Figure 5c**

$I_{2(11V)} = -\frac{11\text{ V}}{11\ \Omega} = -1\text{ A}$  and  $I_4$  is that part of  $I_2$  that flows through the  $3\ \Omega$  resistor, ie,

$$I_{4(11V)} = I_{2(11V)} \frac{6}{3+6} = -\frac{2}{3}\text{ A}$$


(c)  $I_2$  and  $I_4$  due to the  $9\text{ V}$  source - replace  $7.7\text{ A}$  with an open circuit and  $11\text{ V}$  with a short circuit as shown in figure 5d . . .

Here the  $9\text{ V}$  source sees  $(4 + 5)/3\ \Omega$  in series with  $6\ \Omega$ , a total of  $33/4\ \Omega$ . Thus the total current driven by the  $9\text{ V}$  source is  $9/(33/4) = 36/33 = 12/11\text{ A}$ . This current divides down the two parallel arms to give  $I_2$  and  $I_4$ ,

$$I_{2(9V)} = -\frac{12}{11} \times \frac{3}{3+9}\text{ A} = -\frac{3}{11}\text{ A} \text{ and } I_{4(9V)} = \frac{12}{11} \times \frac{9}{12}\text{ A} = \frac{9}{11}\text{ A}$$

Thus  $I_2 = I_{2(7.7A)} + I_{2(11V)} + I_{2(9V)} = (4.2 - 1 - 3/11)\text{ A} = \mathbf{2.93\text{ A}}$   
and

$$I_4 = I_{4(7.7A)} + I_{4(11V)} + I_{4(9V)} = (-7/3 - 2/3 + 9/11)\text{ A} = \mathbf{-2.18\text{ A}}$$

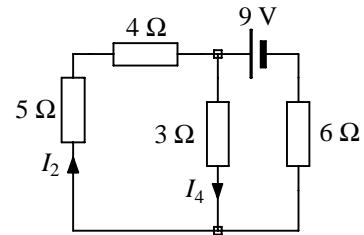

**Figure 5d**

**Q6** Find  $V_2 - V_3$ ,  $V_{2-3}$ , in the circuit of figure 6 using any method you like.

The key to solving this problem is the recognition that although node **5** is common to the left hand loop and the right hand loop, it is the **only** connection between those loops. Thus,  $I_2$  must equal zero.

Since node **5** is the only common node it makes sense to use it as the reference potential and to evaluate  $V_2$  and  $V_3$  with respect to node **5**.

**Left hand loop . . .**

The  $3\text{ A}$  source drives current around the loop and in doing so creates a voltage drop of  $15\text{ V}$  across the  $5\ \Omega$  resistor with its positive end at node **3**.


$$(V_2 - V_5) = (V_2 - V_6) + (V_6 - V_5) = 15 - 11 = 4\text{ V}$$

**Right hand loop . . .**

In the right hand loop,  $I_3 = 9\text{ V} / (3\ \Omega + 6\ \Omega) = 1\text{ A}$ . The voltage at node **3** with respect to node **5** is the voltage developed across the  $3\ \Omega$  resistor by  $I_3$ , i.e.,  $3\text{ V}$ . So

$$(V_3 - V_5) = 3\text{ V}$$

So  $(V_2 - V_3) = (V_2 - V_5) - (V_3 - V_5) = 4 - 3 = \mathbf{1\text{ V}}$

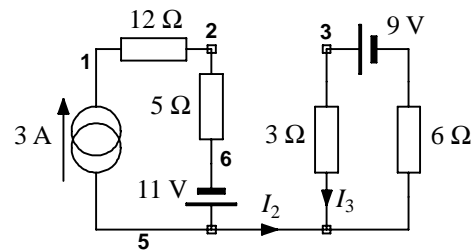

**Figure 6**