 
 


1. Design a switched-capacitor integrator (assuming CMOS VLSI) to implement the active RC integrator of Fig. 1a. Assume that the switching clock is equal to frequency of 512 KHz (50% duty cycle). You should assume that the operational amplifiers are not limited by bandwidth or slew rate. R is $1.5\text{ M}\Omega$ and C is 5 pF .



2. Describe the behaviour of a switched capacitor integrator in Fig. 1b with an equivalent active RC circuit. Assume that the switching clock is equal to frequency of 512 KHz (50% duty cycle). You should assume that the operational amplifiers are not limited by bandwidth or slew rate. C_s is 0.5 pF and C is 5 pF .



3. Describe the signal flow graph for the leap-frog implementation of LC ladder prototype filter in Fig. 2. (Use R , $C1$, $L2$, $C3$, $L4$, $C5$ as the value of each component)

