



The
University
Of
Sheffield.

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Spring Semester 2010-2011 (2 hours)

EEE6036 VLSI Design 6

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1. a. Show that the small-signal, on-state resistance of an n -type pass transistor as shown in **Figure 1(a)** is $r = \frac{1}{\beta_N \cdot (V_{DS} - V_T)}$ when $V_G = V_D$

 


Figure 1(a): n -type Pass Transistor

(4)

- b. Three n -type pass transistors are cascaded in series as shown in **Figure 1(b)**.

 


Figure 1(b): Cascaded n -type Pass Transistors

What will the approximate voltages at points X, Y, and Z be for the voltage conditions shown. State any assumptions that you make.

(4)

- c. State whether each transistor in **Figure 1(b)** would be in the ohmic or saturated region if a current were to flow. (4)
- d. In **Figure 1(b)**, the *substrate* connection is shown connected to the transistor's *source* connection. If this circuit were part of a digital MOS IC where would you normally expect the *substrate* to be connected for transistors such as these and why would this be the case? (4)
- e. Show how two transmission gates and two inverters can be combined together to create an XOR gate. (4)

2. A logic circuit is shown in **Figure 2**.

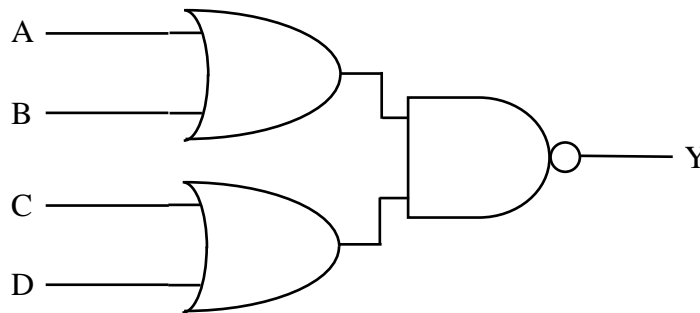


Figure 2: Logic Circuit

- a. Convert the logic circuit into a standard-CMOS transistor-level circuit. (8)
- b. Size the transistors (as a multiple of a minimum-sized n -type FET) for a minimum sized logic circuit, stating any assumptions that you make. (6)
- c. Estimate the capacitance associated with each of the inputs and wires within the circuit (you can neglect the interconnect capacitance), given that the gate capacitance of a minimum-sized n -type FET is 0.7fF. (4)
- d. Rather than implementing the circuit in **Figure 2** as a single, combined CMOS circuit, you decide to implement it as a combination of two separate CMOS OR gates and a CMOS NAND gate. How much less efficient will it be than the single CMOS circuit in terms of numbers of transistors used? (2)

3. a. i) What is *fault-coverage* when applied to testing? (3)
- ii) Why is *fault-coverage* so important in ensuring that systems manufactured using ICs can be sold? (1)
- iii) Show the effect of *fault coverage* using an IC yield of 0.7, with a *fault-coverage* of 98%.
 You should assume that the ICs are tested, then 20 ICs are assembled into a system where the manufacturing yield on the system assembly is 99.5% and, again, the *fault-coverage* on testing the systems is, again, 98%. (4)
- iv) How do IC designers achieve a high value of *fault-coverage*? (2)
- v) What sort of things tends to limit *fault-coverage*? (2)
- b. A section of combinatorial logic (between flip-flops) is shown in **Figure 3**.

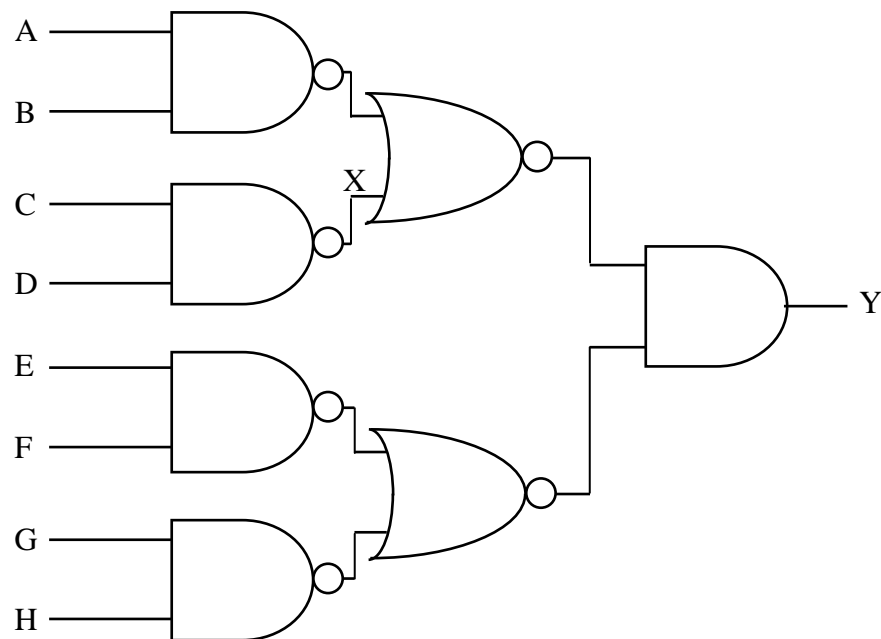


Figure 3: Combinatorial Logic to be Tested

- i) If this logic were to be tested exhaustively then how many individual tests would be required? (2)
- ii) Using a stuck-at fault-modelling approach, how many individual tests would be required? (2)
- iii) In fault-modelling what is the difference between sensitisation and propagation? (2)
- iv) Identify the input conditions that would be required to test node X for both stuck at 1 and stuck at 0. (2)

4. a. i) Describe the *Synchronous Design Methodology* and explain why it results in reliable designs. (4)
- ii) How does synchronous design relate to a *Register Transfer Level* description of circuits? (2)
- b. i) Languages used for hardware design, like VHDL, allow you to specify a delay between an input (on the RHS) in a logical expression changing state and the corresponding output (LHS) changing state. Why is this meaningless in logic synthesis? (3)
- ii) When functionally simulating logic designs, where the delay between inputs to and outputs from logical expressions is not specified, how would the simulator ensure that causality is obeyed? (3)
- iii) In this regard, what might happen if a simulator were to encounter the following statement (written in VHDL):
`a <= not a;` (2)
- iv) What is the difference between functional simulation and timing simulation? (2)
- v) Timing simulation can often be avoided by using static timing analysis. What is static timing analysis and why is it used? (4)

NLS