



The
University
Of
Sheffield.

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Spring Semester 2014-15 (2.0 hours)

EEE307 Power Electronics

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1. a. Explain the operation of an over-voltage snubber network applied to a BJT switching device and why it may be needed. Your answer should include a circuit diagram with voltage and current waveforms. (8)
- b. A 40kHz square wave voltage is applied across a load by a switching circuit with stray inductance of $6\mu\text{H}$. The supply voltage for the switching circuit is 350V and the load current is a constant 2A. Calculate suitable component values for the resistor and capacitor in an over-voltage snubber network if the maximum voltage seen by the switch is to remain below 400V. (6)
- c. Explain the problems which may be encountered when paralleling BJT switching devices directly, and outline a possible solution for reliable parallel operation of the BJT switching devices. (6)

2. a. The state-space equations for the inductor current and capacitor voltage, averaged over the duty cycle, for a Buck converter are below:

$$\dot{i}_L = \frac{dv_i}{L} - \frac{Ri_L}{L} + \frac{CR\dot{v}_o}{L} \quad \dot{v}_o = \frac{i_L}{C} - \frac{v_o}{CR}$$

where \dot{i}_L and \dot{v}_o denote the derivatives with respect to time

Prove the following small signal Audio Susceptibility transfer function for the converter is:

$$\frac{v_o}{v_i} = \frac{d}{LC \left(s^2 + \frac{s}{CR} + \frac{1}{LC} \right)} \quad (12)$$

- b. Calculate the values of capacitor and inductor required for use in a Buck converter that generates a regulated 24V dc output from a 36 to 48V input. The circuit is to supply an output current ranging from a minimum of 0.5A to a maximum of 6A. The output voltage ripple for the converter should be less than 1%. Ignore switch and diode voltage drops, and assume the converter is to operate at a frequency of 20kHz.

(4)

- c. With the aid of a circuit diagram, describe how an ideal Forward converter may be derived from a Buck converter (You may neglect the requirement for volt-second balance).

(4)

3. a. Derive an expression for the switching loss within a semiconductor switching device operating at a frequency 'f' with an inductive load. (8)
- b. Four MOSFET switching devices with parallel Schottky diodes are used in a H-bridge inverter configuration (as shown below in figure 1) to provide a near-constant 5A DC in the load. The inverter is to operate at 40kHz and the devices have the parameters given below:

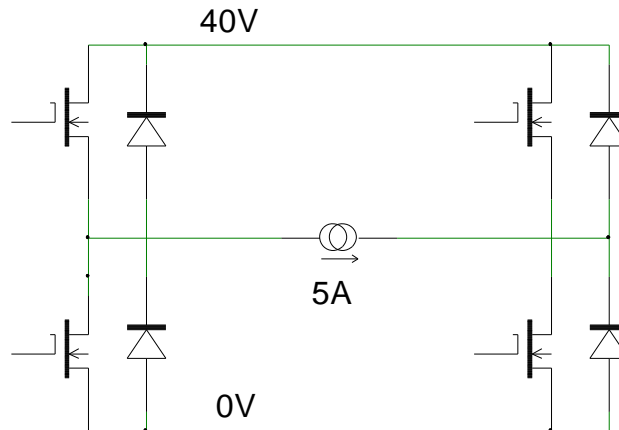


Figure 1. H-bridge inverter

Given that the duty cycle of the top-left switch is 33%, infer the duty cycles of the other devices and calculate the power dissipated in a common heatsink onto which all 8 devices are mounted. Also give a required thermal resistance for the heatsink if the devices are to be kept below 40°C in an environment where the ambient temperature is 18°C.

MOSFETS

$R_{ds(on)}$	=	0.5Ω
V_{max}	=	60V
I_{max}	=	10A
t_{on}	=	200ns
t_{off}	=	300ns

Diodes

V_{fwd}	=	0.5V
I_{max}	=	10A
V_{max}	=	50V

- c. Given that the circuit above was to operate at 100Hz, would Thyristors be a suitable choice in this circuit configuration? Justify your answer. (4)

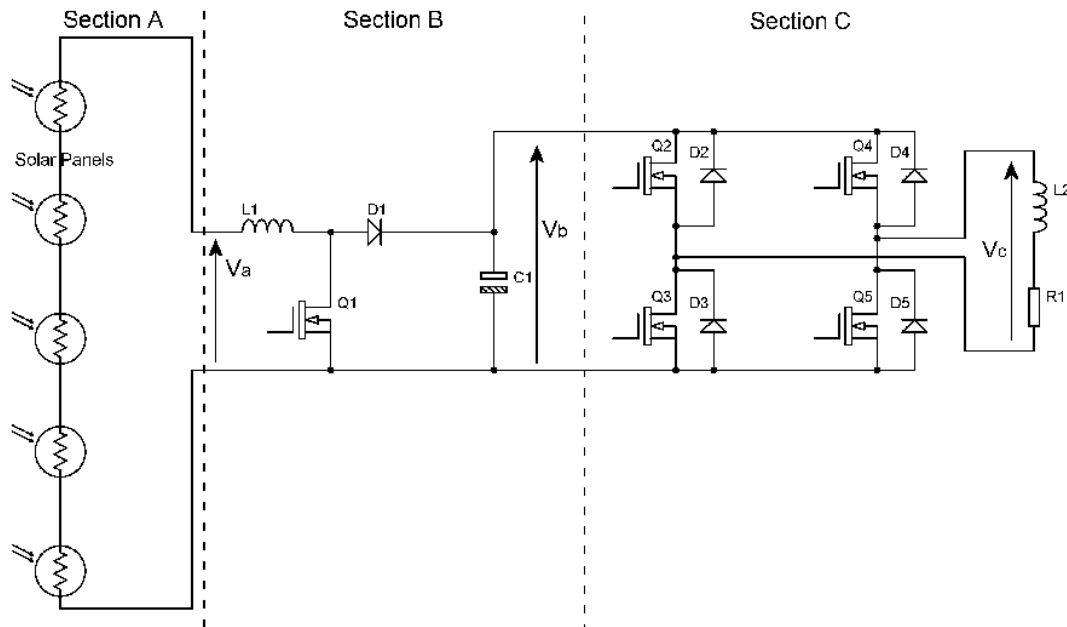


Figure 2 – Standalone solar power supply.

4. a. The circuit diagram of a standalone solar power supply shown in Figure 2 is divided into 3 sections, A, B & C by the vertical dotted lines. With the aid of circuit diagrams, voltage waveforms and current waveforms, derive the transfer function V_b/V_a for the DC-DC converter in section B. (8)
- b. If the total voltage output, V_a , of the solar panels in section A of Figure 2 varies between 120V and 300V, and the voltage output, V_b , of section B needs to be 400V and supply between 0.1A and 7A, find the values of the inductor and capacitor in the converter (L_1 and C_1), and suggest ratings for the switch and diode in the converter (Q_1 and D_1). Assume the converter operates at 100kHz and the output voltage of section B should have less than a 2% ripple. (8)
- c. Highlight and explain the key features of components D_1 and C_1 in the converter circuit. (4)

CG/SM