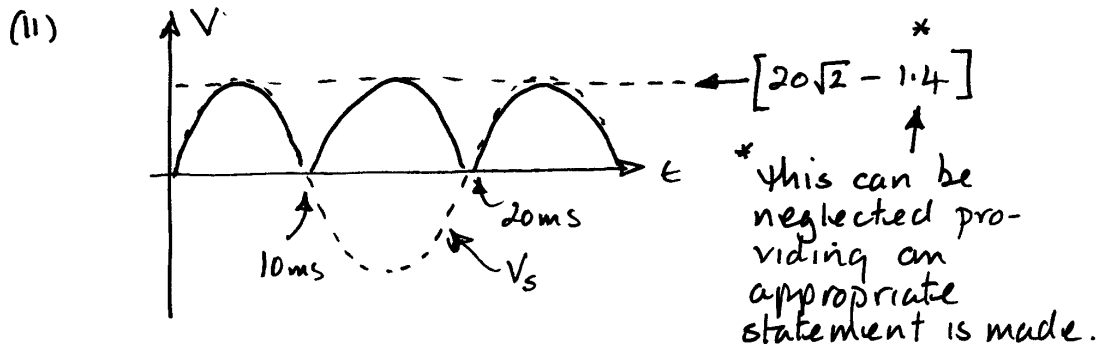


Q1 (i) B, F, E, A.



(iii) Average of half wave rectified sinusoid
 $= V_P / \pi$ (given in "useful information")


$$\begin{aligned} \therefore \text{Average of F.W.} &= 2 \frac{V_P}{\pi} \\ &\approx 2 \frac{(20\sqrt{2} - 1.4)^*}{\pi} \\ &= \underline{17.1 \text{ V.}} \end{aligned}$$

(iv) $I_{\max} = \frac{V_P - 1.4^*}{R}$


assume C discharges at I_{\max} for full 10ms

$$I_{\max} = C \frac{\Delta V}{\Delta t} = C \frac{V_R}{10\text{ms}}$$
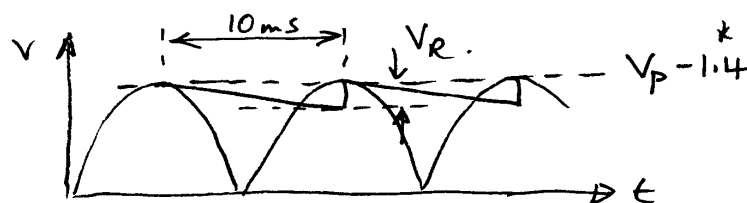
$$\begin{aligned} \therefore C &= \frac{I_{\max} \times 10\text{ms}}{V_R} = \frac{(V_P - 1.4)^* \times 10\text{ms}}{R V_R} \\ &= \underline{\underline{6.7 \times 10^{-3} \text{ F.}}} \end{aligned}$$



(v)

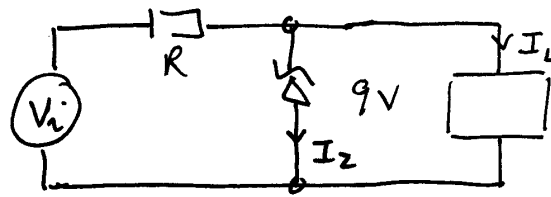

$$I_{Lmin} = 5mA$$

$$I_{Lmax} = 10mA$$

$$I_{Zmin} = 2mA.$$

$$V_{i max} - V_{i min} = 2V.$$


$$V_{i min} = 20\sqrt{2} - 1.4 - 2 = 24.9V.$$

$$R_{max} = \frac{V_{i min} - 9V}{I_{Lmax} + I_{Zmin}} = \frac{24.9 - 9}{10mA + 2mA}.$$

$$= \underline{\underline{1.3k\Omega}}.$$

(1.14k Ω if the 1.4V diode drop is neglected.)

(vi) ripple equivalent circuit ...

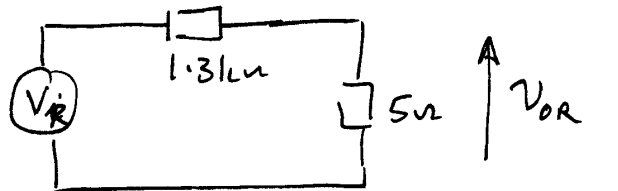


$$V_{OR} = V_R \cdot \frac{5\Omega}{5 + 1.3k\Omega} = 2 \times \frac{5}{1305}$$

$$= \underline{\underline{7.6mV \text{ pk-pk}}}$$

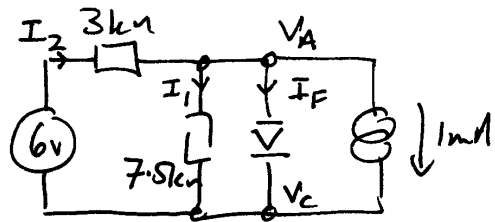Q2(a)(i) Try a test

Assume diode not conducting
..... diode is open ckt



by superposition, V_A w.r.t. V_C is

$$\begin{aligned} V_A - V_C &= 6 \times \frac{7.5}{3 + 7.5} - 1 \text{mA} \times \frac{3 \text{k}\Omega \times 7.5 \text{k}\Omega}{3 \text{k}\Omega + 7.5 \text{k}\Omega} \\ &= 6 \times \frac{7.5}{10.5} - \frac{22.5}{10.5} \\ &= \frac{45 - 22.5}{10.5} = \frac{22.5}{10.5} = 2.14 \text{V} \end{aligned}$$

so guess is wrong, diode conducts.

replace diode with $V_A - V_C = 0.7 \text{V}$ and work out I_F ...

$$I_2 = \frac{6 - 0.7}{3 \text{k}\Omega} = \frac{5.3}{3 \text{k}\Omega} = 1.77 \text{mA}$$


$$I_1 = 0.7 / 7.5 \text{k}\Omega = 0.093 \text{mA}$$

sum currents at V_A node



$$I_2 = I_1 + I_F + 1 \text{mA}$$

$$\therefore I_F = 1.77 - 0.093 - 1 = \underline{\underline{677 \mu\text{A}}}$$

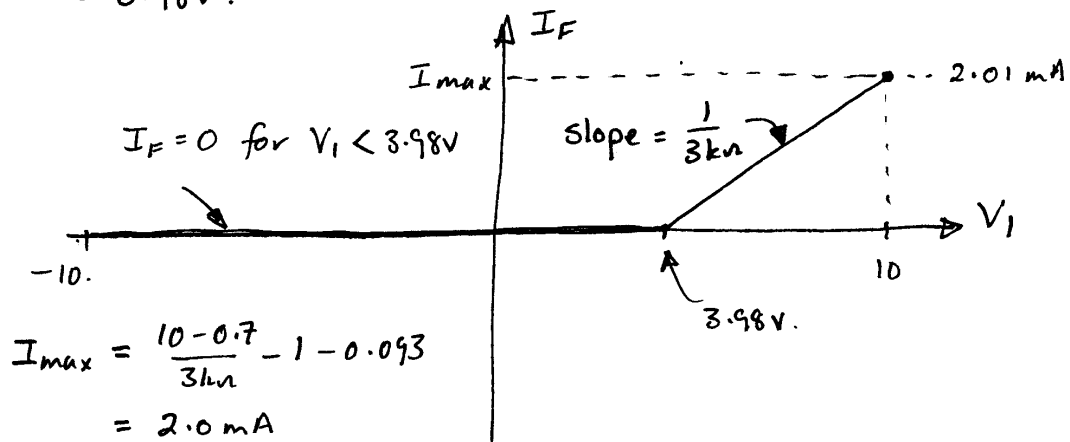(ii) diode on point of changing state when $I_F = 0$
and $V_A - V_C = 0.7$ ie when $I_2 = 1.093 \text{mA}$
ie when $V_{3 \text{k}\Omega} = 3 \times 1.093 = 3.28 \text{V} \therefore V_1 = 3.28 + 0.7$
 $= 3.98 \text{V}$.





Q2 b (i)

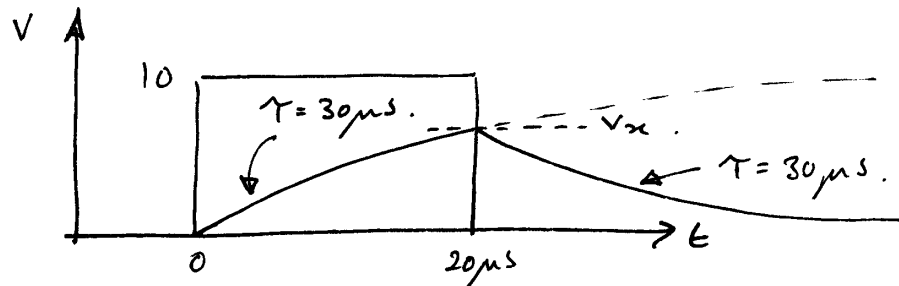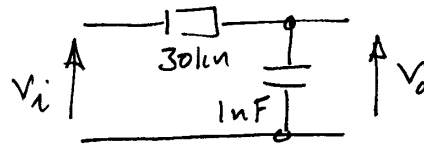

$$V_x = 10 \left(1 - e^{-20/30} \right) = 4.87 \text{ V.}$$

(ii).

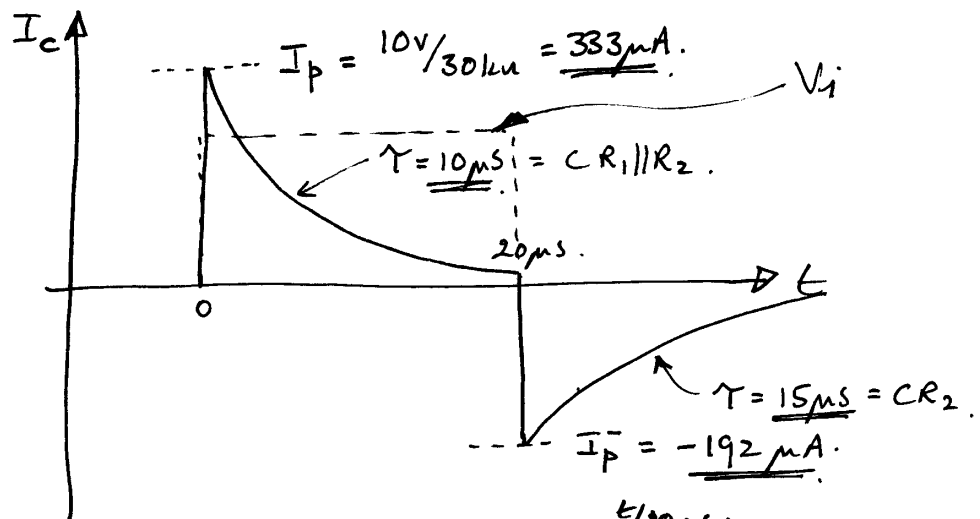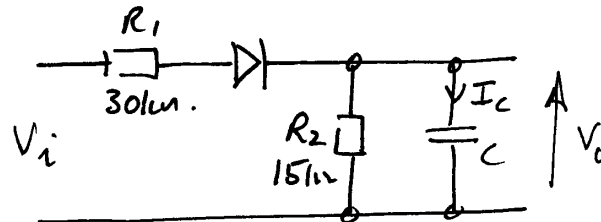

between $0 + 20\mu\text{s}$ $V(t) = 3.33(1 - e^{-t/10\mu\text{s}})$.

so at $20\mu\text{s}$ $V_o = 3.33(1 - e^{-2}) = 2.88 \text{ V.}$

$$I_p^- = -\frac{2.88}{15k\Omega} = -192 \mu\text{A.}$$


Q3 (a) (i) $I_{con} = \frac{24}{200} = \underline{\underline{120 \text{ mA}}}$ (ignores V_{CEsat}).

(ii) To support $I_{con} = 120 \text{ mA}$, $I_{B(on)}$ must be at least $\frac{I_{con}}{h_{FE}} = \frac{120 \text{ mA}}{35} = 3.43 \text{ mA}$.

If $V_i = 5 \text{ V}$ and $V_{BE} = 0.7 \text{ V}$,


R_B given by $R_B = \frac{5 - 0.7}{3.43 \text{ mA}} = \underline{\underline{1.25 \text{ k}\Omega}}$.

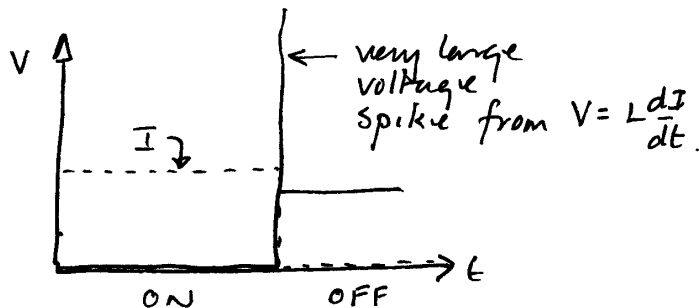(iii) L stores energy while T_1 is on. When T_1 tries to turn off, the stored energy in the inductor tries to keep the current flowing into what suddenly becomes a high impedance node. Hence, V_{CE} rises rapidly as the current seeks a circuit through which it can pass..... This high voltage can damage T_1 .



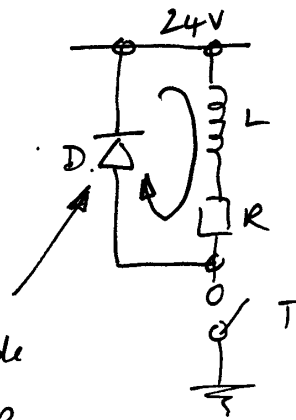Problem can be eased by providing a path for the inductor current by using an idling or freewheeling diode →

Current circulates as shown and stored energy is lost as heat in D and R .



Q3 b (i) V_B given by potential division of V_{CC} (18V)


$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = 18 \frac{68k\Omega}{188k\Omega} = \underline{6.5V}$$

$$\therefore V_E = V_B - 0.7 = 5.8V. \text{ so } I_E \approx I_C = \frac{5.8}{R_E} = \underline{1.93mA}$$

$$V_C = V_{CC} - I_C R_L = 18 - 1.93 \times 3k\Omega \\ = 18 - 5.8V \\ = \underline{12.2V}$$

$$g_m = \frac{e I_C}{kT} \text{ (given)} = \frac{1.93 \times 10^{-3}}{0.026} = \underline{0.074 A/V} \\ = \underline{74 mA/V}$$
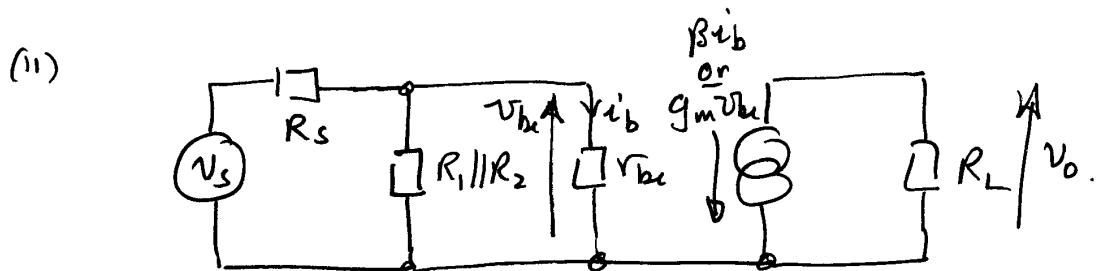
$$r_{be} = \beta / g_m \text{ (given)} = \frac{400}{0.074} = \underline{5.4k\Omega}$$




— 1 mark per error.

(iii) $\frac{v_o}{v_{be}} = -g_m R_L$ (from o/p side) $= -222$

$$\frac{v_{be}}{v_s} = \frac{r_{be} \parallel R_1 \parallel R_2}{R_s + r_{be} \parallel R_1 \parallel R_2} = \frac{4.81k\Omega}{2.21k\Omega + 4.81k\Omega} \\ = 0.69$$

$$\therefore \frac{v_o}{v_s} = 0.69 \times (-222) = \underline{-153 V/V}$$

Q4 (a)

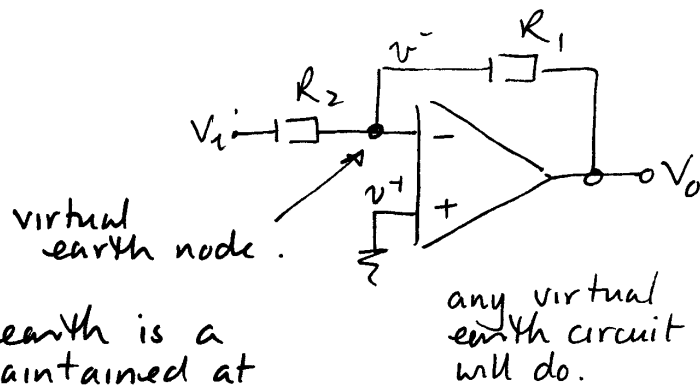


The virtual earth is a point that is maintained at earth (ground) potential, even though it isn't actually connected to ground.

It exists in the ckt above because of the very high gain of the op-amp.

$V_o = A_v (v^+ - v^-)$ where A_v is very large. If V_o is finite (say somewhere between +15V and -15V) and A_v is somewhere in the region of 10^6 V/V , then v^+ and v^- must be very close in potential (within 15 μV of each other in this example). Thus if v^+ is connected to ground, v^- will always be close to ground potential.

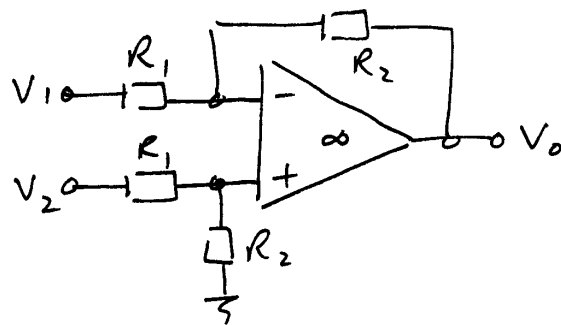(b) can either use superposition or work out v^+ & v^- and equate them.




superposition ...

$$\begin{aligned}
 V_o &= V_o|_{V_1} + V_o|_{V_2} \\
 &= -\frac{R_2}{R_1} V_1 + V_2 \frac{R_2}{R_1 + R_2} \cdot \frac{R_1 + R_2}{R_1} \\
 &= -\frac{R_2}{R_1} V_1 + \frac{R_2}{R_1} V_2
 \end{aligned}$$

$$\text{or } \frac{V_o}{V_2 - V_1} = \frac{R_2}{R_1}$$

non-inv. gain acting on v^+

(c)

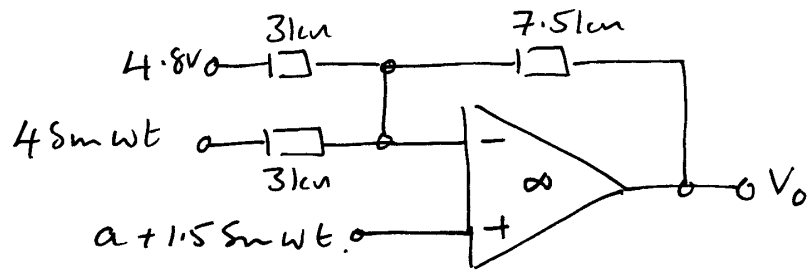

(i) considering ac

$$V_o \Big|_{4 \sin \omega t} = -2.5 \times 4 \sin \omega t = -10 \sin \omega t$$

$$\begin{aligned} V_o \Big|_{1.5 \sin \omega t} &= 1.5 \sin \omega t \times \frac{7.5 + 3 \parallel 3}{3 \parallel 3} \\ &= 1.5 \sin \omega t \times \frac{9}{1.5} = 9 \sin \omega t \end{aligned}$$

$$\begin{aligned} \therefore V_{oT} &= \sin \omega t (-10 + 9) = -\sin \omega t \\ &= \sin(\omega t + \pi) \end{aligned}$$

ie magnitude = 1, $\phi = \underline{\underline{\pm 180^\circ}}$.

(ii) considering d.c.

$$V_o \Big|_{4.8V} = -2.5 \times 4.8V$$

$$V_o \Big|_a = a \cdot \frac{7.5 + 3 \parallel 3}{3 \parallel 3} = 6a.$$

$$V_{oT} = -2.5 \times 4.8 + 6a = 0.$$

$$\text{or } a = \frac{2.5 \times 4.8}{6} = 2.5 \times 0.8 = \underline{\underline{2V}}$$