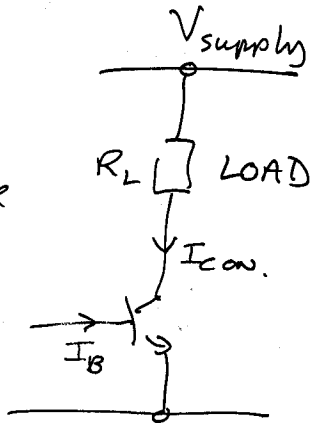


## Driving a Bipolar Transistor Switch.

To work out  $I_{CON}$  assume that switch has negligible on-state voltage across it.


$$I_{CON} = \frac{V_{supply}}{R_L}$$



$$\frac{I_C}{I_B} \approx \text{constant} \Rightarrow h_{FE} \text{ static current gain.}$$

$h_{FE}$  varies significantly from device to device  $\rightarrow$  manufacturers specify a MIN + MAX + sometimes typical value.

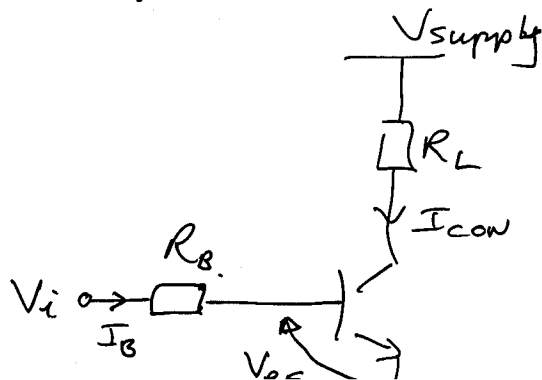We must use the  $h_{FE MIN}$  if we want all specimens of this transistor type to switch properly.



$$I_B = \frac{I_{CON}}{h_{FE MIN}}$$

I must use  $I_{B MAX}$  here —  $I_{B MAX}$  comes from using  $h_{FE MIN}$ .

$$I_{B MAX} = \frac{I_{CON}}{h_{FE MIN}}$$

$$\therefore \frac{I_{CON}}{h_{FE MIN}} = \frac{V_{i ON} - V_{BE ON}}{R_B}$$

$$\text{or } R_B = \frac{(V_{i ON} - V_{BE ON}) h_{FE MIN}}{I_{CON}}$$

What if the load is something a bit more complicated than a simple — eg a car head lamp.


eg 72W lamp from 12V

$$P = \frac{V^2}{R} \quad \frac{144}{72} = 2 \Omega$$

hot resistance.

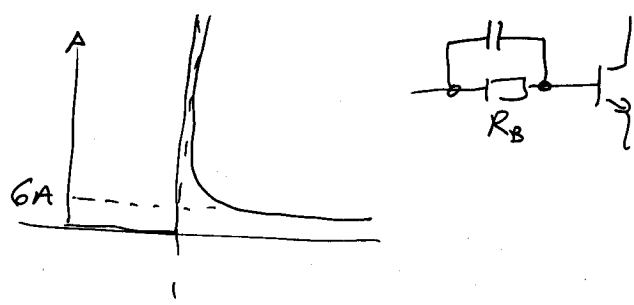The cold resistance of a lamp like this will typically be around an order of magnitude lower than the hot resistance.






Need to look for maximum ratings that are bigger than 1, 2 + 3.
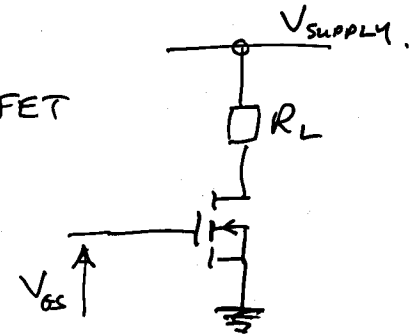
## MOSFET SWITCHES.


To switch the MOSFET "on" - a  $V_{GS}$  of between 10 + 15V is needed.



On state current  $\rightarrow \frac{V_{SUPPLY}}{R_L} = I_{DON}$

In the "on" state the MOSFET behaves like a resistance,  $r_{DS(on)}$

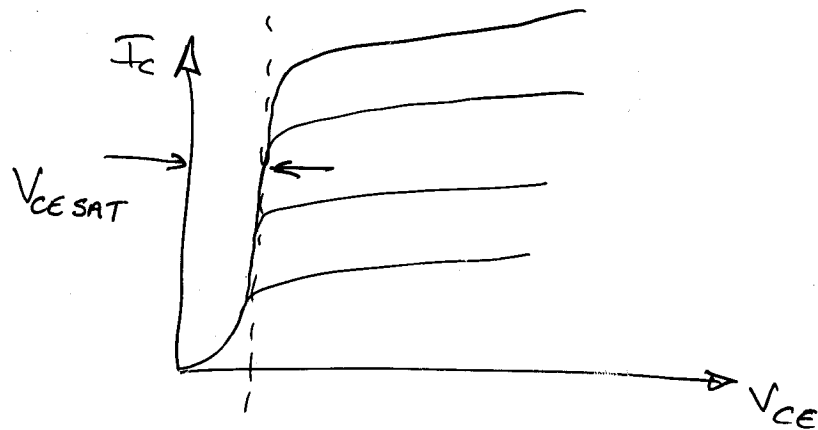So on-state power loss =  $I_{DON}^2 \cdot r_{DS(on)}$ .



Power dissipated in transistor

IS  $V_{CESAT} \times I_{CON} \equiv P_D$

How is the transistor chosen

Transistor must be able to



- 1) withstand the off-state voltage (which usually equals the  $V_{SUPPLY}$ )
- 2) withstand the on-state current (usually  $I_{CON} = \frac{V_{SUPPLY}}{R_L}$ )
- 3) dissipate sufficient thermal energy (ie,  $P_D$ )

## Switches with inductive loads

It's all about  $V = L \frac{dI}{dt}$ .


Driver for  $I_{OFF}$  is the inductor.

"idling" or "freewheeling" diode

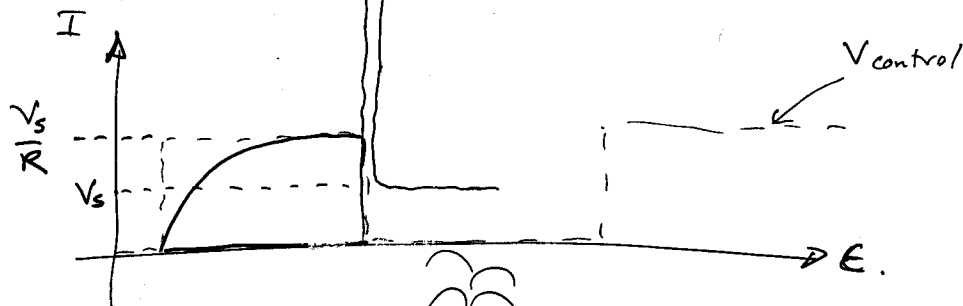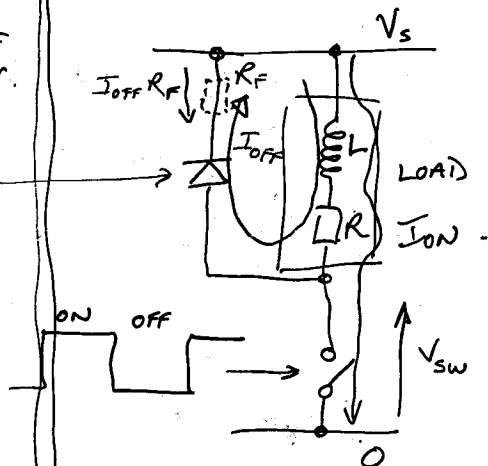


Energy entering C =  $\frac{1}{2} L I_p^2$  every switch off event.


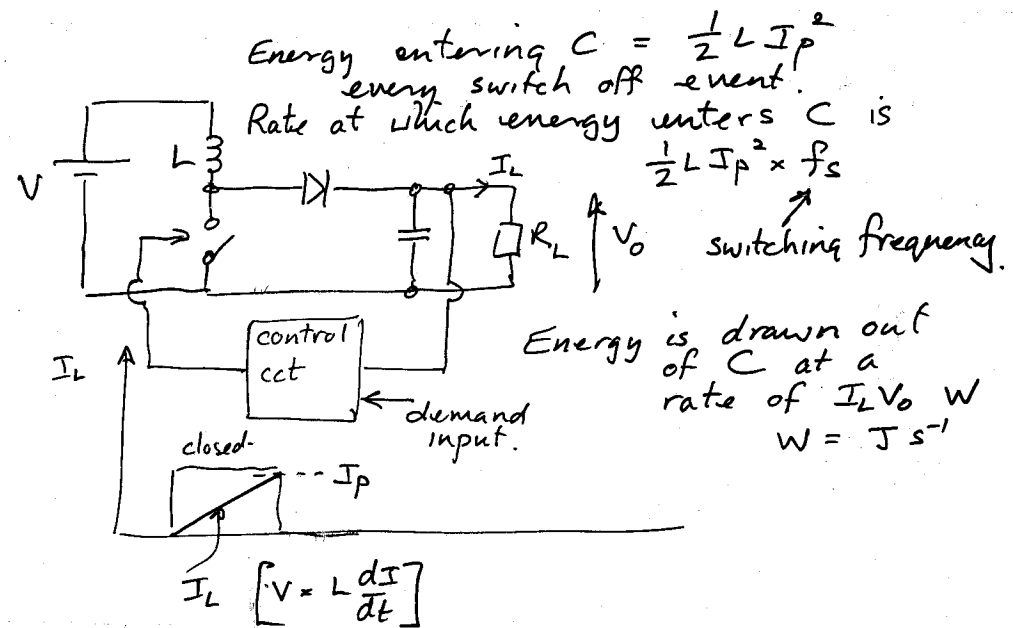
Rate at which energy enters C is  $\frac{1}{2} L I_p^2 \times f_s$



## Full Switch Bridge Circuit

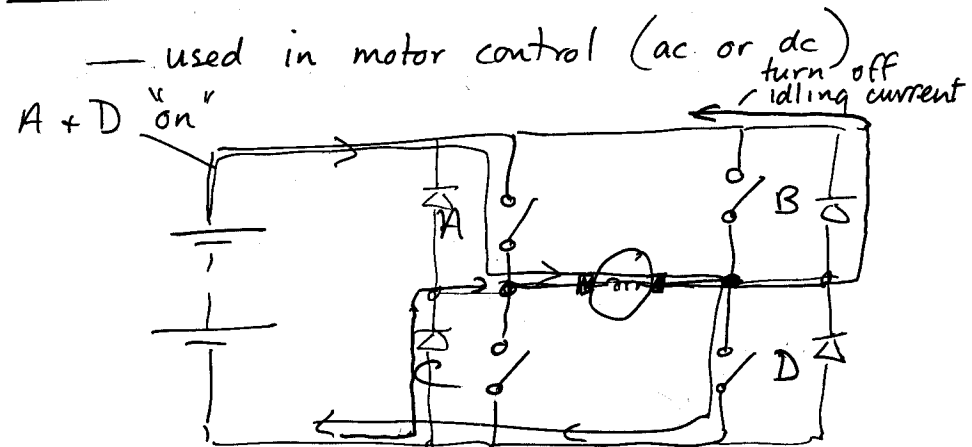

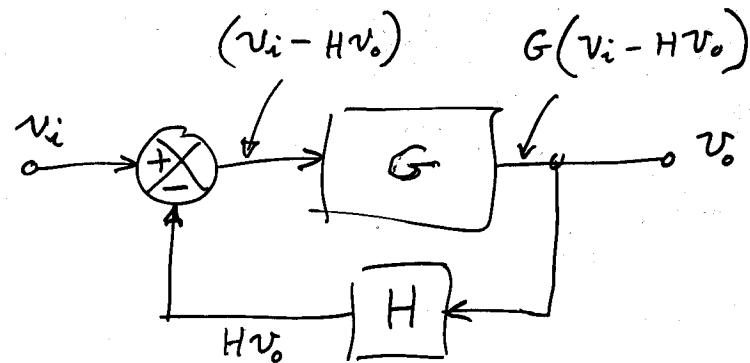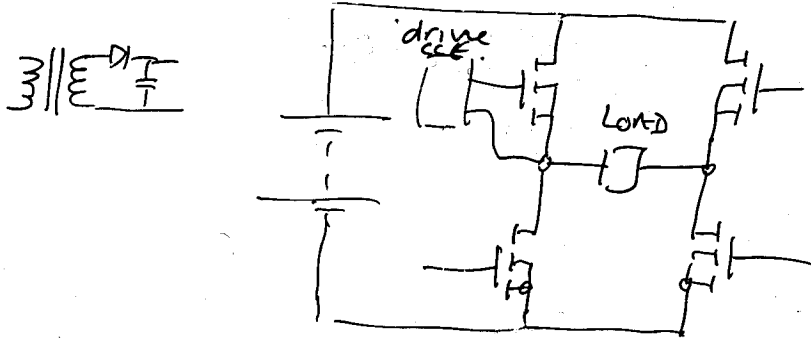if switch A & D are "on", current will flow from left to right  
 if switch C & B are "on", current will flow from right to left.




So  $G(v_i - Hv_o)$  must equal  $v_o$   
 rearranging to get  $\frac{v_o}{v_i} = \text{system gain}$   
 $= \frac{G}{1 + GH}$

if  $G$  can be made sufficiently big such that  $GH \gg 1$

$$\frac{v_o}{v_i} \approx \frac{G}{GH} = \frac{1}{H}$$

So what is inside a normal op-amp

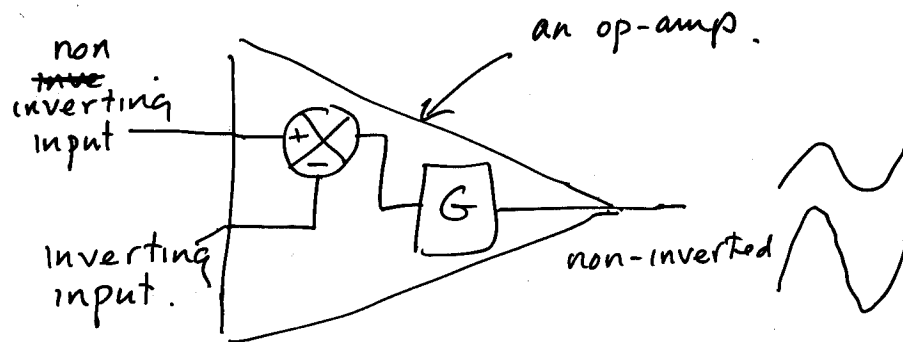

$\approx$  typically  $10^4$  to  $10^7$   $V/V$ .

## Bipolar v Mosfets.

low on-state voltage drop	higher on state voltage drop
medium speed	fast - will work up to MHz
relatively high control ckt power.	works up to $\sim 100$ kHz
	easy to control
	don't need much control power.

Insulated Gate Bipolar Transistor  
 — hybrid BJT/MOSFET

## Operational Amplifiers


$$\frac{(v_i - Hv_o)}{1} \rightarrow \frac{G(v_i - Hv_o)}{1}$$

$G$  typically  $10^4$  to  $10^6$  V/V.

wide frequency range  
— say 100s MHz

inverted

low frequency  
up to a couple  
of MHz.



The key equation for op-amps

$$v_o = A_v (v^+ - v^-)$$

non-inverting  
input voltage


inverting  
input voltage

open loop  
gain


( $G$  in the classic control system)

if  $A_v \Rightarrow \infty$  then for finite  $v_o$   
 $(v^+ - v^-) \Rightarrow 0$   
 so  $v^+ \approx v^-$


Two basic circuit shapes

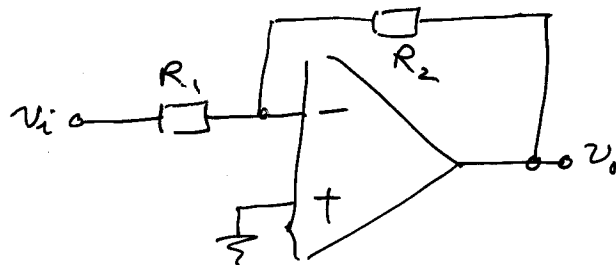

inverting  
amplifier

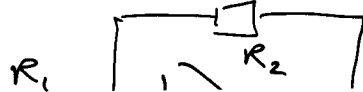


inverting  
amplifier.

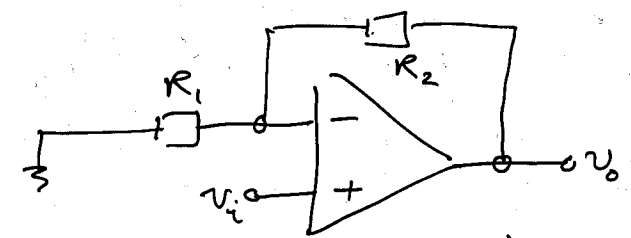


non-inverting amplifier

Note the similarities between these two  
circuits.

other common  
forms of non-  
inverting

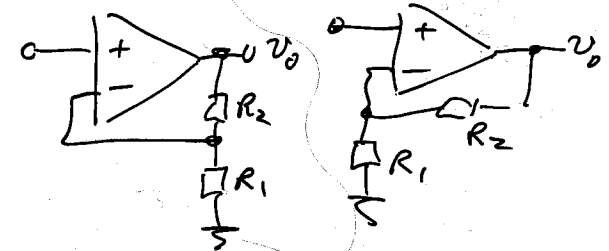

Designing an inverting amplifier.

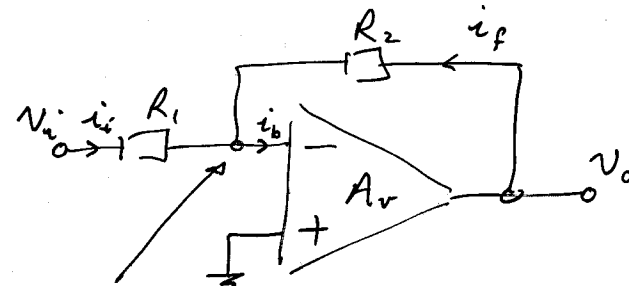

often  
called a  
"virtual  
ground"  
or  
"virtual  
earth"

$A_v \Rightarrow \infty$

$$v_o = A_v (v^+ - v^-)$$

$\therefore v^+ - v^- \Rightarrow 0$  for a finite  $v_o$

$i_b$  is usually negligibly small.

Summing currents at  $v^-$  node


$$i_i + i_f = 0$$

$$\frac{v_i - 0}{R_1} + \frac{v_o - 0}{R_2} = 0 \quad \text{or} \quad \frac{v_i}{R_1} = -\frac{v_o}{R_2}$$

$$\text{or } \frac{v_o}{v_i} = \text{gain} = -\frac{R_2}{R_1}$$

Non-inverting amplifier

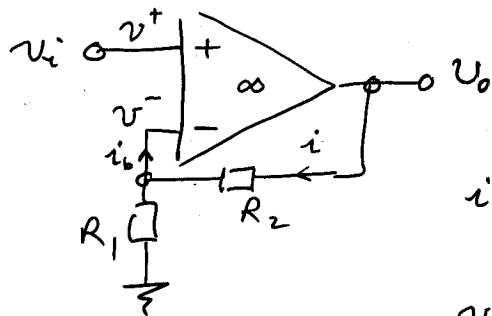- again assume  $A_v \Rightarrow \infty$   
so  $v^+ \approx v^-$



$$i = \frac{v_o}{R_1 + R_2} \quad \left\{ \begin{array}{l} i_b \text{ negligibly} \\ \text{small} \end{array} \right.$$

$$v^- = iR_1 = \frac{v_o R_1}{R_1 + R_2}$$


$$v^+ = v^-$$

$$v_i = \frac{v_o R_1}{R_1 + R_2}$$

$$\frac{v_o}{v_i} = \frac{R_1 + R_2}{R_1}$$

What is the effect of  $A$  being finite

Non inverting with finite  $A_v$

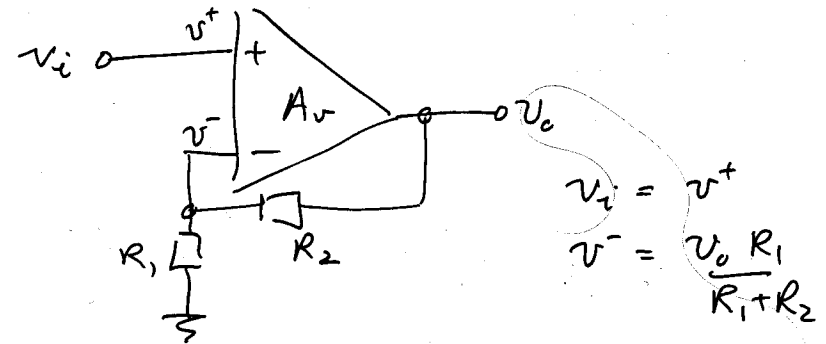

$$v_o = A_v (v^+ - v^-)$$

$$= A_v \left( v_i - \frac{v_o R_1}{R_1 + R_2} \right)$$


$$v_o \left[ \frac{1}{A_v} + \frac{R_1}{R_1 + R_2} \right] = v_i$$

$$\frac{v_o}{v_i} = \frac{1}{\frac{1}{A_v} + \frac{R_1}{R_1 + R_2}}$$

for  $A_v$  to have a negligible effect on  $\frac{v_o}{v_i}$

$$A_v \gg \frac{R_1 + R_2}{R_1}$$

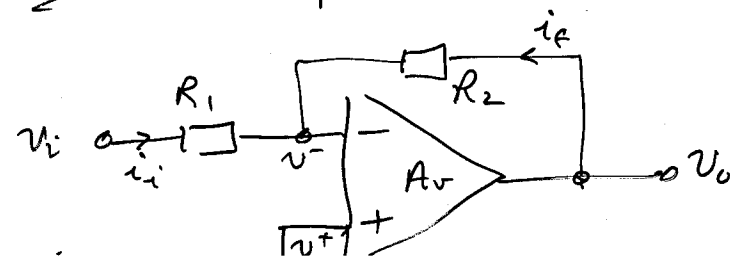~~to~~ Inverting Amplifier with finite  $A_v$ .



✓

sum currents at inverting input node

$$i_i + i_f = 0$$

$$\frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} = 0$$

$$\frac{v_i}{R_1} + \frac{v_o}{R_2} = v^- \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] = v^- \left[ \frac{R_1 + R_2}{R_1 R_2} \right]$$

$$\frac{v_i R_2 + v_o R_1}{R_1 + R_2} = v^-$$



using  $v_o = A_v (v^+ - v^-)$

$$\frac{v_o}{A_v} = 0 - \frac{v_i R_2}{R_1 + R_2} - \frac{v_o R_1}{R_1 + R_2}$$

$$v_o \left[ \frac{1}{A_v} + \frac{R_1}{R_1 + R_2} \right] = - \frac{v_i R_2}{R_1 + R_2}$$

$$\frac{v_o}{v_i} = \frac{- \frac{R_2}{R_1 + R_2}}{\frac{1}{A_v} + \frac{R_1}{R_1 + R_2}}$$

Unity gain buffer

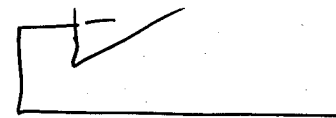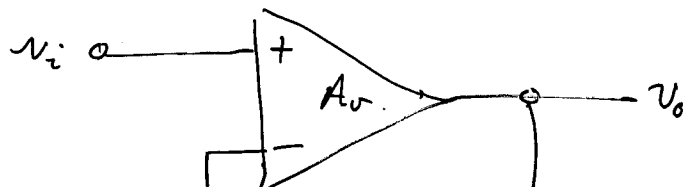


$$v_o = A_v (v^+ - v^-)$$

$\uparrow \quad \quad \uparrow$   
 $v_i \quad \quad v_o$

$$v_o = A_v (v_i - v_o)$$


$$v_o (1 + A_v) = A_v v_i$$

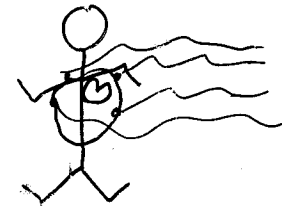
$$\frac{v_o}{v_i} = \frac{A_v}{1 + A_v} \approx 1$$



Op-amp circuits with multiple inputs.

i) A summing circuit ...

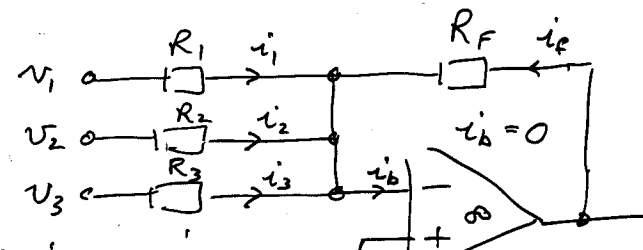

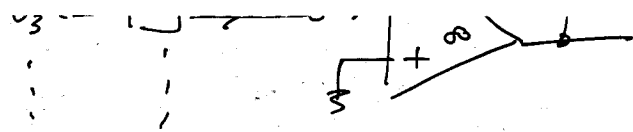

Sum currents at inverting input node


$$i_1 + i_2 + i_3 + i_f = 0$$

$$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$$

$$\frac{v_1 - 0}{R_1} + \frac{v_2 - 0}{R_2} + \frac{v_3 - 0}{R_3} + \frac{v_0 - 0}{R_F}$$

$$\text{or } v_0 = -v_1 \frac{R_F}{R_1} - v_2 \frac{R_F}{R_2} - v_3 \frac{R_F}{R_3} - \dots$$

A more general multiple input problem

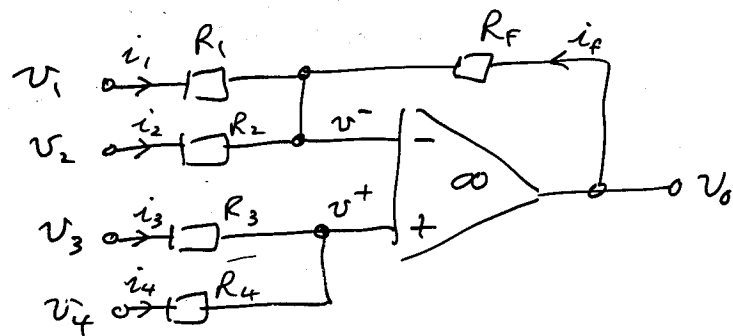

Two approaches are useful

- 1) superposition principle.
- 2) work out  $v^+$ , work out  $v^-$  and then equate them.

using method 2...

sum currents at  $v^-$  node

$$i_1 + i_2 + i_f = 0$$

$$i_1 + i_2 + i_f = 0$$

$$\downarrow \quad \downarrow \quad \downarrow$$

$$\frac{v_1 - v^-}{R_1} + \frac{v_2 - v^-}{R_2} + \frac{v_0 - v^-}{R_F}$$

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_0}{R_F} = v^- \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right]$$

$$\text{or } v^- = \frac{\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_0}{R_F}}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right)}$$

summing currents at  $v^+$  node.

$$i_3 + i_4 = 0$$

$$\downarrow \quad \downarrow$$

$$\frac{v_3 - v^+}{R_3} + \frac{v_4 - v^+}{R_4} = 0$$

$$\frac{v_3}{R_3} + \frac{v_4}{R_4} = v^+ \left[ \frac{1}{R_3} + \frac{1}{R_4} \right]$$

$$v^+ = \frac{\frac{v_3}{R_3} + \frac{v_4}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4}}$$

now equate  $v^+$  and  $v^-$

$$\frac{\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_0}{R_F}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F}} = \frac{\frac{v_3}{R_3} + \frac{v_4}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4}}$$

hence



$$\frac{v_0}{R_F} = \frac{\frac{v_3}{R_3} + \frac{v_4}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4}} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right] - \frac{v_1}{R_1} - \frac{v_2}{R_2}$$

$$= \frac{v_3}{R_3} + \frac{v_4}{R_4} \left[ \dots \right] - \dots - \dots$$



$$= \frac{\frac{V_3}{R_3} + \frac{V_4}{R_4}}{\frac{R_3+R_4}{R_3R_4}} \left[ \sim \right] - \sim - \sim$$
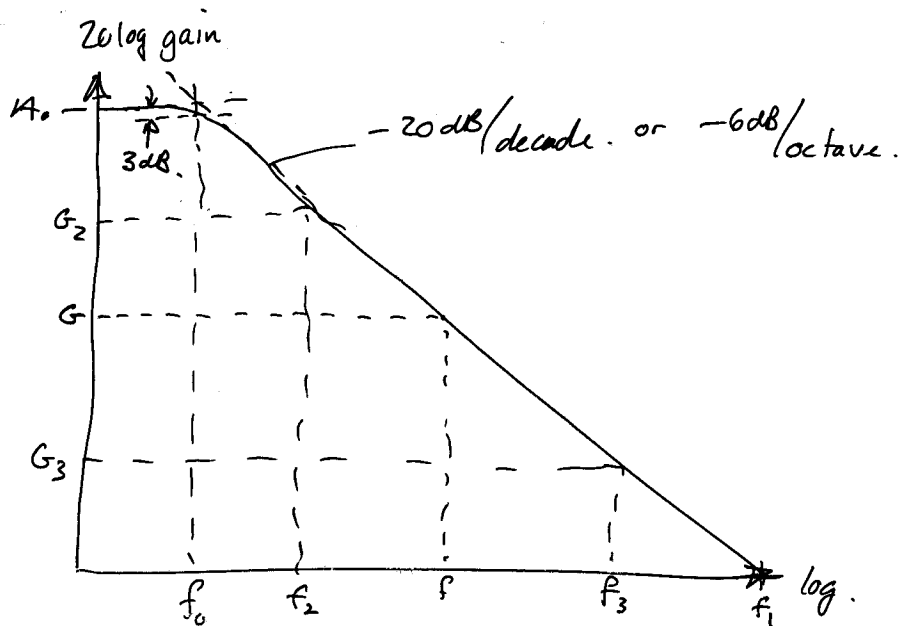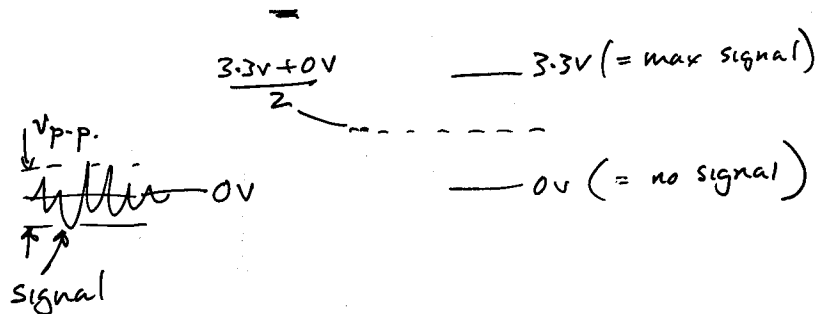
$$= \underbrace{\left( \frac{R_4}{R_3+R_4} V_3 + \frac{V_4 R_3}{R_3+R_4} \right)}_{V^+} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right] - \frac{V_1}{R_1} - \frac{V_2}{R_2}$$



$G \times f = \text{constant}$   
 called "gain-bandwidth" product.  
 $G_1 f = G_2 f_2 = G_3 f_3 = 1 \times f_1$   
 also called "unity gain frequency"