 


# EEE 331 – Tutorial Sheet 1


## Bookwork questions

These would normally form 40% of an examination paper.

- 1)
  - a) Sketch the Hybrid- $\pi$  s.s. model for a BJT.
  - b) Define the physical origins of each of the elements in the circuit.
  - c) Which elements can be ignored when the load impedance is small? (and for a bonus hard question, why?)
- 2) Sketch the s.s. model for a MOSFET
- 3) State the relationships between;
  - a) collector current and base-emitter voltage for a BJT
  - b) drain current and gate-source voltage for a MOSFET
- 4) Calculate the values of  $Z_1$  and  $Z_2$  in figure 2, given that the circuit in figure 2 is equivalent to that shown in figure 1. Show all of your analysis.



*Figure 1*

 


*Figure 2*

- 5) State the voltage gain in terms of BJT s.s. parameters and circuit elements for the following circuits.
  - a) Common-emitter
  - b) Common-base
  - c) Common-collector
- 6) What effect does emitter degeneration have on the output impedance of a common-emitter circuit?
- 7) Give one common application of a common-collector circuit, explaining why this circuit is particularly attractive for this application.

## Application questions

These questions would normally form 30% of an exam paper.


- 8) The BJT in the high-power, single-ended output stage below obeys the relationship  $I_C = 4 \times 10^{-31} \exp(100 \times V_{be})$ . Calculate the gain for the circuit, assuming that a quiescent current of 1A flows through the resistor  $R_e$  and that  $i_b \ll i_I$ .

 

**Figure 3**


For a bonus difficult question, why is a two stage topology with a voltage gain stage and a push-pull output stage preferable to the circuit given above?

- 9) Calculate the mid-frequency gain of the circuit below. You should assume that the capacitors  $C_1$  and  $C_2$  are short circuits at the frequencies of interest that the internal capacitances of the BJT are open circuits and that  $r_{bb}$ ,  $r_{ce}$ , and  $r_{cb}$  can be neglected. Also calculate the output impedance of the circuit from the small signal's point of view in the mid-frequency range.

 


**Figure 4**

- 10) The circuit shown below in figure 5a has a voltage gain of 100. The circuit comprises a BJT with  $C_{CB} = 10\text{pF}$  which has  $V_{be\text{ on}} = 0.7\text{V}$  and  $V_{ce\text{ on}} = 1\text{V}$ . The waveform generator is programmed to give an output of the type shown in figure 5b. Plot a graph of the rate of change of  $v_o$  as a function of  $t$ . How could one increase the slew rate of the following?

 

**Figure 5a**

 

**Figure 5b**

### Difficult questions

Usually constitute roughly 30% of the paper.

- 11) Explain why MOSFETs are rarely used as transistors in voltage gain stages if BJTs are available.
- 12) Explain (i.e. do not use equations) why including emitter degenerating resistors reduces the gain of a common-emitter amplifier.

Emitter degeneration is used commonly to better define the bias for a BJT. Sketch a circuit diagram showing how a common-emitter gain stage with emitter degeneration can be modified so that a s.s. does not incur this gain penalty.

- 13) Explain the difference between the Miller effect and slew rate limiting.
- 14) Why are additional capacitors sometimes included between base and collector in voltage gain sections of power amplifiers?