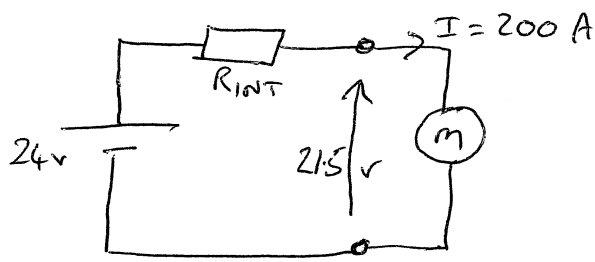


QUESTION: 1

1

(a) Initially the battery is connected to the starter motor:



The voltage drop across the internal resistance is:

$$V_{INT} = 24 - 21.5 = 2.5 \text{ V}$$

Hence the internal resistance of the battery is:

$$R_{INT} = \frac{V_{INT}}{I} = \frac{2.5}{200} = \underline{\underline{0.0125 \Omega}}$$

The power dissipated in the battery is then - $P_{INT} = I^2 R_{INT}$
 $= 200^2 \times 0.0125$
 $= \underline{\underline{500 \text{ W}}}$


The total power supplied by the battery is:

$$P_{TOT} = 24 \times 200 = 4800 \text{ W}$$

Hence the system efficiency is:

$$\text{Efficiency} = \frac{P_{TOT} - P_{LOSS}}{P_{TOT}} \times 100 = \frac{4800 - 500}{4800} = \underline{\underline{89.6\%}}$$

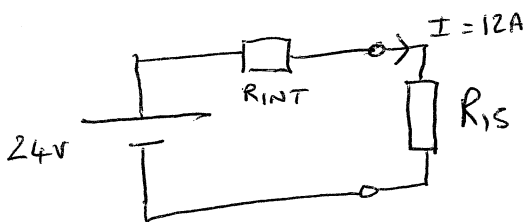(b) When the heater is first switched on it has a resistance of R_{IS} and at the final temperature it will be R_F .



$$\frac{V}{I} = R_{INT} + R_{IS} = \frac{24}{12} = 2 \Omega$$

$$\text{Hence } R_{IS} = 2 - 0.0125 = 1.9875 \Omega$$

QUESTION 1 (CONTINUED)

2

Similarly at the final temperature:

$$R_F \neq R_{INT} = \frac{V}{I} = \frac{24}{9} = 2.667 \Omega$$

$$\text{Hence } R_F = 2.667 - 0.0125 = 2.655 \Omega$$

$$\text{Now } \frac{R_F}{R_{20}} = \frac{R_0 (1 + \alpha_0 T_F)}{R_0 (1 + \alpha_0)}$$

$$\therefore \frac{2.655}{1.988} = \frac{(1 + 12.5 \times 10^{-3} T_F)}{(1 + 12.5 \times 10^{-3} \times 15)}$$


$$\therefore 1.336 = \frac{(1 + 12.5 \times 10^{-3} T_F)}{1.1875}$$

$$\therefore \underline{T_F = 46.9^\circ \text{C}}$$

(ii) At the final temperature the Power is $I^2 R_F = 9^2 \times 2.655$
 $= \underline{\underline{215 \text{ W}}}$

$$\text{Hence the efficiency} = \frac{215}{24 \times 9} \times 100\% = \underline{\underline{99.5\%}}$$

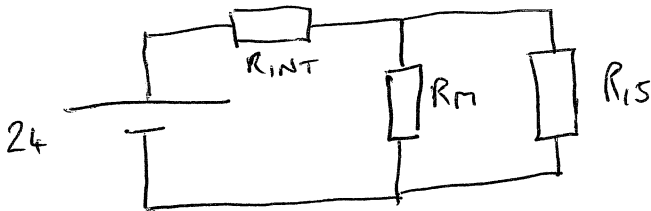(iii) When both the heater and starter are operated together:



$$\text{From part (a)} \quad R_M = \frac{21.5}{200} = 0.1075 \Omega$$

$$R_{15} = 1.988 \Omega$$


$$\therefore R_T = R_{INT} + \frac{1}{\frac{1}{R_M} + \frac{1}{R_{15}}} = 0.1145 \Omega$$

$$\text{Hence current is } \frac{24}{0.1145} = \underline{\underline{209.6 \text{ A}}}$$

QUESTION 1 (CONTINUED)

3

(c)(i)

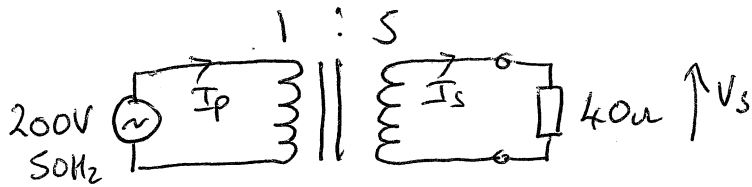

$$\text{Since } \frac{V_p}{V_s} = \frac{N_p}{N_s} \Rightarrow V_s = V_p \cdot \frac{N_s}{N_p} = \frac{200 \times 5}{1} = \underline{\underline{1000 V_{rms}}}$$

$$I_s = \frac{V_s}{R_s} = \frac{1000}{40} = 25 A_{rms}$$

$$\text{Now } \frac{I_p}{I_s} = \frac{N_s}{N_p} \Rightarrow I_p = \frac{N_s I_s}{N_p} = \frac{5 \times 25}{1} = \underline{\underline{125 A_{rms}}}$$

$$\text{Power dissipated} = I_s^2 R = 25^2 \times 40 = \underline{\underline{25 kW}}$$

(ii) The secondary impedance is now:

$$R + j2\pi fL = 40 + j2\pi \times 50 \times 0.15 = 40 + j47.1 \Omega \\ = 61.8 \angle 49.7^\circ \Omega$$

$$\therefore I_s = \frac{1000 \angle 0^\circ}{61.8 \angle 49.7^\circ} = 16.18 \angle -49.7^\circ A_{rms}$$

$$\therefore I_p = I_s \times 5 = \underline{\underline{80.9 \angle -49.7^\circ A_{rms}}}$$

$$\text{Power dissipated in load} = I_s^2 \times 40 = 16.18^2 \times 40 = \underline{\underline{10.47 kW}}$$

$$(\text{check } P = V_p I_p \cos \phi = 200 \times 80.9 \times \cos(-49.7) = 10.47 kW)$$

QUESTION 1 (CONTINUED)

4

(iii) The input power factor would be $\cos(-49.7^\circ) = \underline{\underline{0.647 \text{ lagging}}}$

The VA rating is $200 \times 80.9 = \underline{\underline{16.18 \text{ kVA}}}$

(iv) Since $V_{rms} = 4.44 f N \phi_{max}$


$$\text{then } N_p = \frac{V_{rms}}{4.44 f \cdot \phi_{max}} = \frac{200}{4.44 \times 50 \times 5 \times 10^{-3}} = \underline{\underline{180 \text{ TURNS}}}$$

(v) $V_{rms} = 4.44 \times 60 \times 180 \times 5 \times 10^{-3} = \underline{\underline{239.8 \text{ V}_{rms}}}$

QUESTION 2

5

(a)(i)

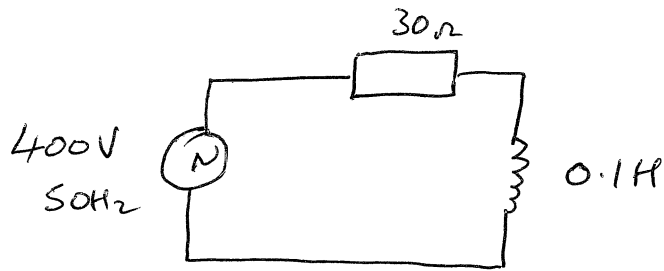

The impedance of the coil is given by:

$$Z = R + j2\pi fL = 30 + j \cdot 2\pi \cdot 50 \cdot 0.1$$
$$= 30 + j31.42 = \underline{\underline{43.44 \angle 46.3^\circ \Omega}}$$

(ii) The current flowing in the coil is:


$$I = \frac{V \angle 0^\circ}{Z \angle 46.3^\circ} = \frac{400 \angle 0^\circ}{43.44 \angle 46.3^\circ} = \underline{\underline{9.21 \angle -46.3^\circ \text{ A}}}$$

(iii) The real power is:

$$P = VI \cos \phi = 400 \times 9.21 \times \cos 46.3^\circ$$
$$= \underline{\underline{2545 \text{ W}}}$$

The power-factor is $\cos \phi = \cos(-46.3) = \underline{\underline{0.69 \text{ lagging}}}$

(b)

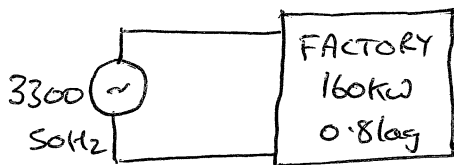

(i) VA rating = $\frac{P}{\cos \phi} = \frac{160}{0.8} = \underline{\underline{200 \text{ kVA}}}$

(ii) kVAR rating = $S \sin \phi = 200 \cdot 0.6 = \underline{\underline{120 \text{ kVAR}}}$

(iii) Magnitude of current = $\frac{S}{V} = \frac{200 \times 10^3}{3.3 \times 10^3} = 60.61 \text{ A}$

and the phase angle = $\cos^{-1} 0.8 = 36.87^\circ$ lagging

ie. $\underline{\underline{I = 60.61 \angle -36.87^\circ}}$

(c) For the heatingovens:

$$P_{L1} = 50 \text{ kW} \quad Q_{L1} = 0 \text{ kVAR}$$

QUESTION 2 (CONTINUED)

6

For the motor load:

$$P_{L2} = S \cos \phi = 100 \times 10^3 \times 0.75 = 75 \text{ kW}$$

$$Q_{L2} = S \sin \phi = 100 \times 10^3 \times \sin(\cos^{-1} 0.75) = 66.14 \text{ kVAR}$$

(i) Therefore the total factory load is:

$$P_T = P_F + P_{L1} + P_{L2} = 160 + 50 + 75 = 285 \text{ kW}$$


$$Q_T = Q_F + Q_{L1} + Q_{L2} = 120 + 0 + 66.14 = 186.14 \text{ kVAR}$$

$$\therefore \text{VA rating is } \sqrt{P_T^2 + Q_T^2} = \sqrt{285^2 + 186.14^2} = \underline{\underline{340.4 \text{ kVA}}}$$


(ii) Phase angle = $\tan^{-1} \frac{Q_T}{P_T} = \tan^{-1} \frac{186.14}{285} = 33.15^\circ \text{ lagging}$

$$\therefore \text{power factor} = \cos 33.15 = \underline{\underline{0.837 \text{ lagging}}}$$

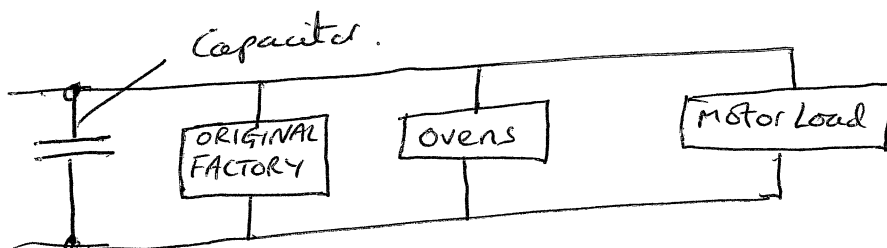(d) (i) Capacitor is connected across the total load in parallel:



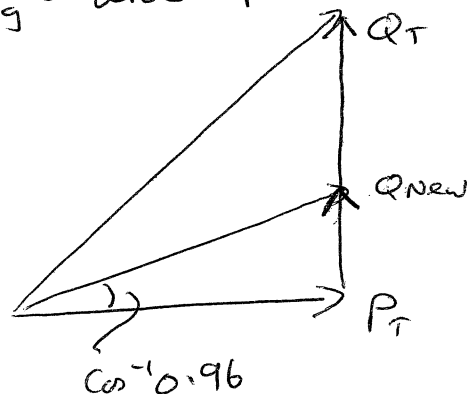(ii) Adding the capacitor does not change P_T . Since p.f. needs to be 0.96 lagging - draw power triangle.



QUESTION 2 (CONTINUED)

7

$$Q_{\text{New}} = P_T \tan(\cos^{-1} 0.96) = 285 \tan 16.26^\circ = 83.12 \text{ kVAR}$$

Here capacitor must provide:

$$\begin{aligned} Q_{\text{OLD}} - Q_{\text{NEW}} &= 186.14 - 83.12 \\ &= \underline{\underline{103.02 \text{ kVAR}}} \end{aligned}$$

Current drawn by the capacitor:

$$I_C = \frac{103.02 \times 10^3}{3300} = \underline{\underline{31.22 \text{ Arms}}}$$

$$\begin{aligned} \text{Since } Q_C &= \frac{V_C^2}{X_C} \Rightarrow X_C = \frac{V_C^2}{Q_C} = \frac{3300^2}{103.02 \times 10^3} \\ &= 105.7 \Omega \end{aligned}$$

$$\text{and } C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \cdot 50 \times 105.7} = \underline{\underline{30.1 \mu\text{F}}}$$


(d)(iii) The peak voltage the capacitor must withstand is

$$V_{\text{PK}} = 3300 \times \sqrt{2} = \underline{\underline{4667 \text{ V}}}$$

QUESTION 3

8

(a) First consider the 10V source:

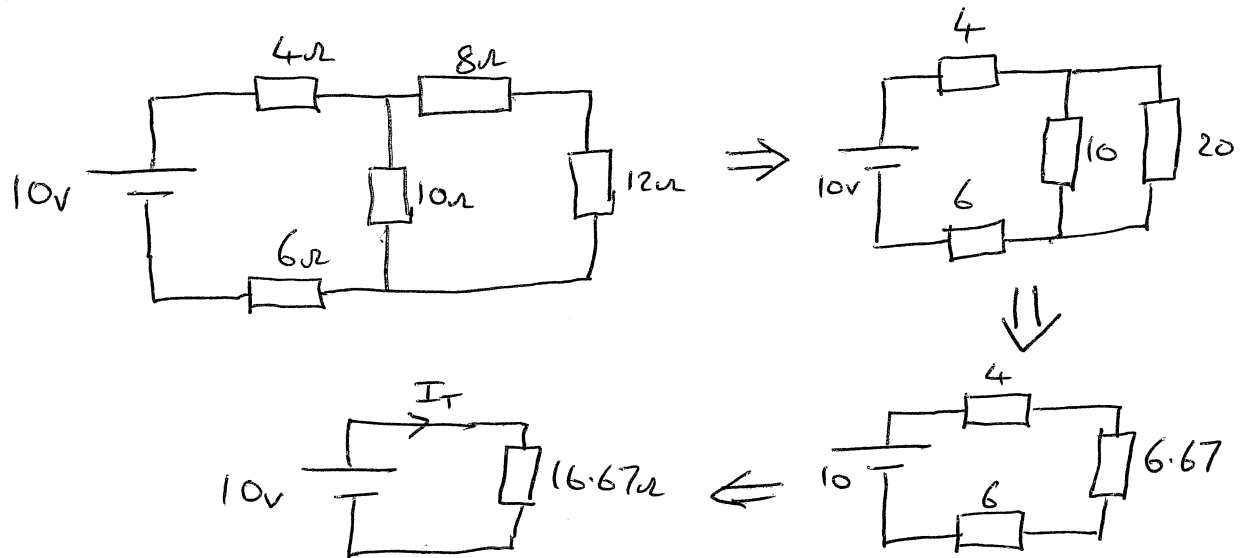


$$\therefore I_T = \frac{10}{16.67} = 0.6A$$

\therefore Current through the 10Ω resistor is:

$$I_{10\Omega} = I_T \cdot \frac{20}{(10+20)} = 0.6 \times \frac{2}{3} = 0.4A \downarrow$$

Now consider the 40V Supply:

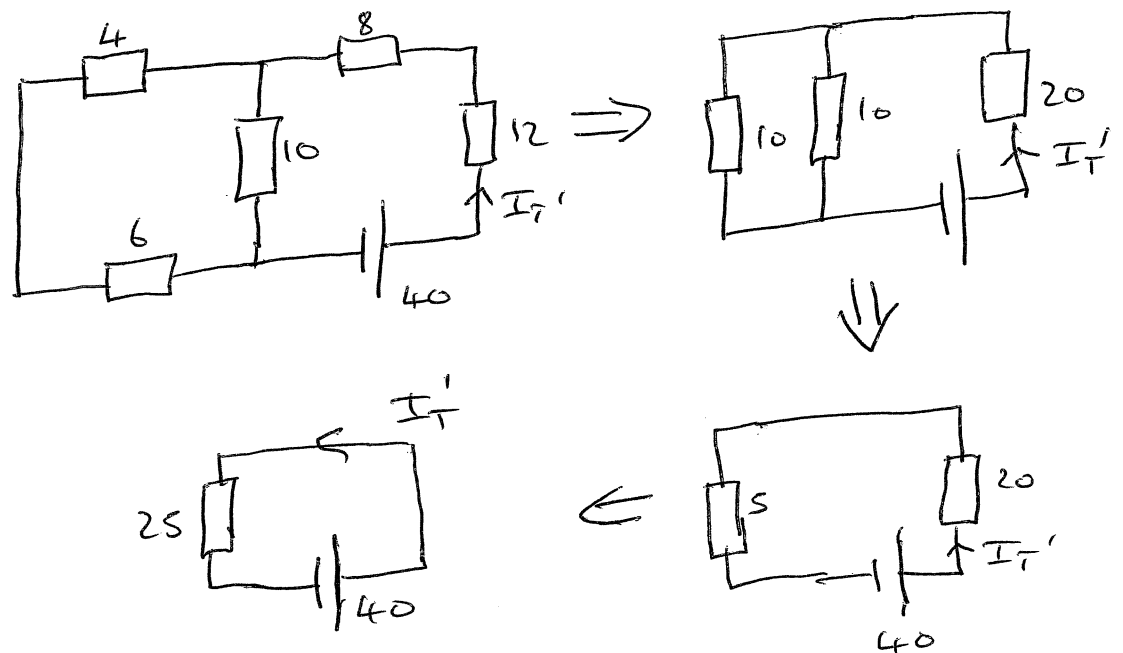

$$I_T' = \frac{40}{25} = 1.6A$$

$$\therefore \text{Current through the } 10\Omega \text{ resistor} = 1.6 \times \frac{10}{20} = 0.8A \downarrow$$

QUESTION 3 (CONTINUED)

9

∴ Total current through the 10Ω resistor is:

$$I_{10\text{TOTAL}} = 0.4\downarrow + 0.8\downarrow = \underline{\underline{1.2A\downarrow}}$$

(b) For the Thevenin circuit we need the open circuit voltage. This is effectively the voltage across the 12Ω resistor. Using working from part (a).

For the $10V$ source the current through the 12Ω resistor is

$$I_{12a} = I_T \times \frac{10}{30} = 0.2A\downarrow$$


For the $40V$ source the current through the 12Ω resistor is equal to $I_T' = 1.6A\uparrow$

Hence the total current through the 12Ω resistor is:

$$I_{12\text{TOTAL}} = 0.2\downarrow + 1.6\uparrow = 1.4\uparrow$$

Hence the Thevenin voltage is $1.4 \times 12 = 16.8V\downarrow$


The resistance network is:

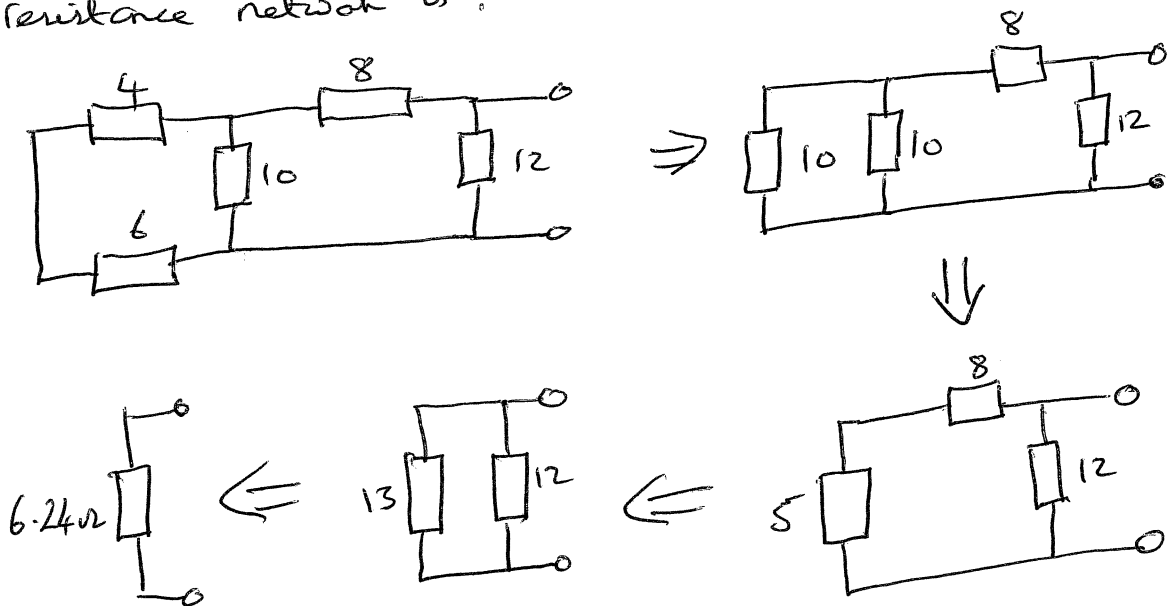

QUESTION 3 (CONTINUED)

10

Hence the Thevenin circuit is:

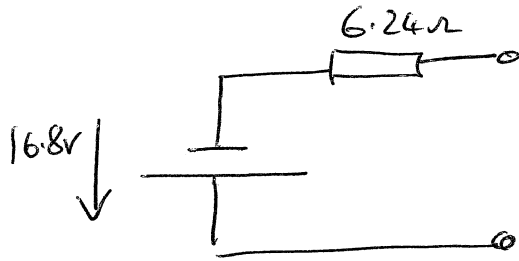

When the load is connected the current is:


$$I_L = \frac{16.8}{(6.24 + 20)} = 0.64 \text{ A}$$

Hence the power dissipated in the load is:

$$P_L = 0.64^2 \times 20 = \underline{\underline{8.19 \text{ W}}}$$

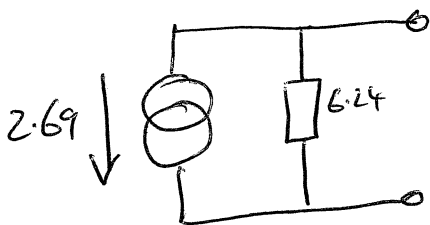(c) The Norton circuit can be found directly from the Thevenin circuit.

$$I_N = \frac{E_T}{R_T} = \frac{16.8}{6.24} = 2.69 \text{ A}$$



(d) At steady state $\frac{dI}{dt} = 0$ hence $V_L = 0$ and C_1 is fully charged. The current is therefore governed by the 2 resistors.

(i) Applying Kirchhoff's law (use defined direction of I_s)

$$60 + 20I_s + 10I_s = 0$$

$$\underline{\underline{I_s = -2 \text{ A}}}$$

QUESTION 3 (CONTINUED)

11

$$(ii) \text{ Energy stored in } L_1 = \frac{1}{2} L_1 I_S^2 = \frac{1}{2} \times 100 \times 10^{-3} \times 2^2 \\ = \underline{\underline{0.2 \text{ J}}}$$

The voltage across the capacitor is equal to the voltage across $R_2 = 20 \times 2 = 40 \text{ V}$

$$\therefore \text{ Energy stored in the capacitor, } C_1 \\ = \frac{1}{2} C V^2 = \frac{1}{2} \times 1 \times 10^{-3} \times 40^2 = 0.8 \text{ J}$$

(iii) Total power dissipated in the circuit is:

$$P_T = I_S^2 (R_1 + R_2) = 2^2 \cdot 30 = \underline{\underline{120 \text{ W}}}$$

EEE123 Solutions to Q4 to Q6 – 2014/15

4.

a) Load current is simply given by:

$$I_L = \frac{V_{DC}}{R_L} = \frac{150}{60} = 2.5A$$

The load power is given by:

$$P_L = \frac{V_{DC}^2}{R_L} = \frac{150^2}{60} = 375W$$

Or alternatively,

$$P_L = I_L^2 R_L = 2.5^2 \times 60 = 375W$$

b) The minimum base current required to support this load is:

$$I_{B(min)} = \frac{I_L}{h_{FE}} = \frac{2.5}{125} = 20mA$$

This minimum value of base current is also given by:

$$I_{B(min)} = \frac{V_i - V_{BE}}{R_{B(max)}}$$

Rearranging yields:

$$R_{B(max)} = \frac{V_i - V_{BE}}{I_{B(min)}} = \frac{5 - 0.7}{0.02} = 215\Omega$$

c) In practice, it would be wise to adopt value some 2-3 time smaller to allow for device variation, different operating conditions, including for example, temperature rise of the device.

d) When the BJT transistor is fully turned on, (V_{ce}) is 1.15V. Hence the power loss in the transistor is simply:

$$P_{loss} = V_{ce} I_C = 1.15 \times 2.5 = 2.87W$$

e) For a MOSFET, the power loss is given by:

$$P_{loss} = I_L^2 R_{DS\ on}$$

Equating this to the loss for the BJT yields:

$$R_{DS\ on} < \frac{2.87}{2.5^2}$$

Hence


$$R_{DS\ on} < 0.46\Omega$$

f) Other advantages:

- Eliminates need for a base resistor
- Easier to drive in terms of current rating of control side electronics (notwithstanding transient)
- Lower loss on control side

5.

a)

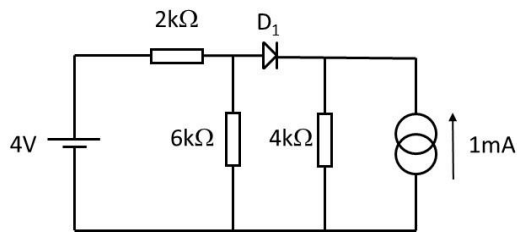

Assume the diode is conducting and replace the diode with a +0.7V voltage supply with is positive at the anode. Replace the current source and its parallel resistance by a Thevenin equivalent and apply a Thevenin simplification to the voltage source and the 2kΩ and 6kΩ resistors.

For the voltage source and 2kΩ and 6kΩ resistors:

$$\text{Open - circuit voltage} = \left(\frac{6}{6+2} \right) \times 4 = 3V$$

$$\text{Short - circuit current} = \frac{4}{2 \times 10^3} = 2mA$$


$$\text{Hence } R_{TH} = 1.5k\Omega$$

For the current source and shunt resistor:

$$\text{Open - circuit voltage} = 1 \times 10^{-3} \times 4 \times 10^3 = 4V$$

$$\text{Short - circuit current} = 1mA$$

$$\text{Hence } R_{TH} = 4k\Omega$$

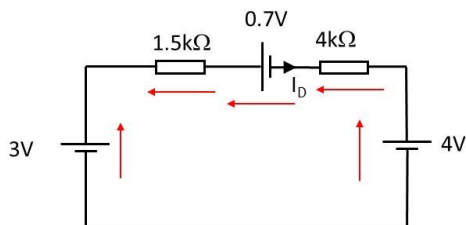

$$3 - 1500I_D - 0.7 - 4000I_D - 4 = 0$$

Hence, I_D is given by:

$$I_D = \frac{-1.7}{5500} = -0.31mA$$

Since this current is negative, then the original assumption was incorrect, and hence the diode is non-conducting in this circuit.

This can also be solved by nodal analysis.

b) The peak AC voltage is 162.6V

Including the two on-state diode voltage drop reduces this to 161V – neglecting these diode drops does not result in any meaningful difference in this case.

$$V_{ave} = \frac{2V_p}{\pi} = \frac{2 \times 161}{\pi} = 102.5V$$

c) It is necessary to calculate V_{rms} applied to the load (and not use V_{ave}):

$$V_{rms} = \frac{V_p}{\sqrt{2}} = \frac{161}{\sqrt{2}} = 113.8V$$

(slightly lower than supply due to the on-state voltage drop)

Hence, average power delivered to load:

$$P_L = \frac{V_{rms}^2}{R_L} = \frac{113.8^2}{40} = 324W$$


d) With a smoothed output (nominally around 161V), a slight overestimate of the load current is given by:

$$I_L = \frac{161}{40} = 4.02A$$

Assuming that the current falls linearly during the discharge period, then a slight overestimate of the capacitance is given by:

$$C_{min} = \frac{I}{dV/dt} \approx \frac{I}{\Delta V/\Delta t} \approx \frac{4.02 \times 0.00125}{6} = 0.839mF$$


e)

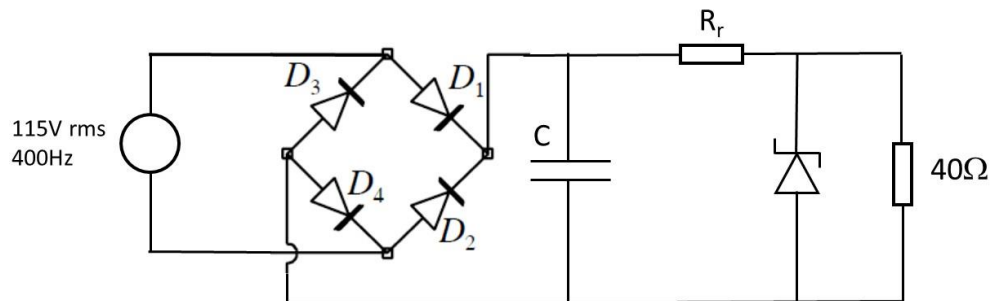

The regulator resistor R_r drops the appropriate voltage between the capacitor voltage and the load which is determined by the total current flowing.

6.

a)

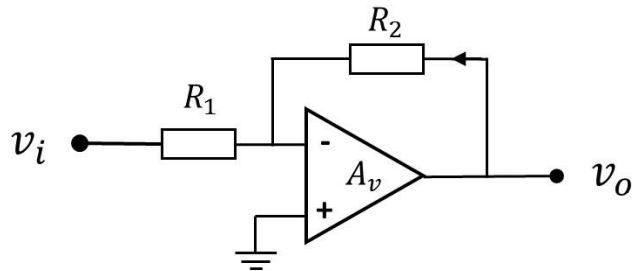

Assumptions:

- The op-amp gain $A_v \rightarrow \infty$
- The op-amp has infinite input resistance

In order to determine the effective gain of this circuit, we start by summing the currents into the v^- node:

$$i_i + i_f = 0$$

(since an op-amp has close to infinite input impedance, i.e. no current flows into the op-amp input)

This can be written as:

$$\frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} = 0$$

But from the discussion above $v^- = 0$ (because it is a virtual earth) and so:

$$\frac{v_i}{R_1} + \frac{v_o}{R_2} = 0$$

Hence, the effective gain is given by:

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

b) To get an input resistance of $10k\Omega$, then $R_1 = 10k\Omega$ and hence:

$$R_2 = -\text{gain} \times R_1 = 100 \times 10,000 = 1M\Omega$$


c) With a source impedance of $2k\Omega$, there is a potential divider action at play in setting v_i at the input stage. Specifically:

$$v_i = \frac{10,000}{10,000 + 2,000} v_s$$

Where v_s is the

Hence the actual voltage present at v_i is only 83.3% of the source voltage, i.e. a 16.7% error.

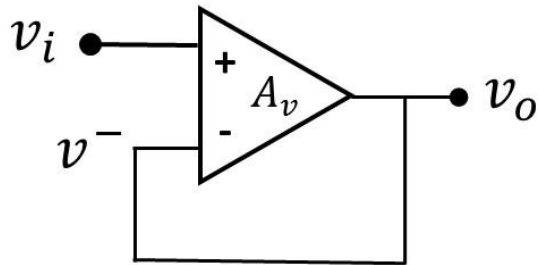d) This can be remedied by including a unity buffer which has an input impedance close to that of the op-amp itself and a low output impedance (10s of Ω). The circuit diagram is:




[Important to get correct polarity of input terminals]

e) With the finite op-amp gain:

$$\frac{v_o}{v_i} = -\frac{\frac{R_2}{R_1 + R_2}}{\frac{1}{A_v} + \frac{R_1}{R_1 + R_2}} = 99.8$$

i.e. 0.2% change in effective gain.

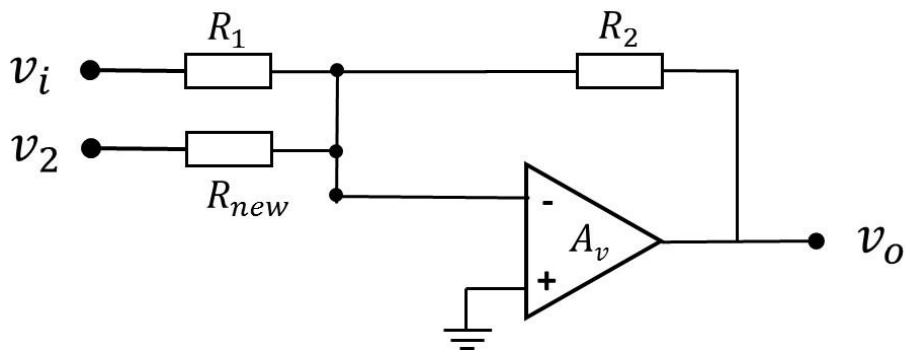f) The modified circuit (which is in effect a summer) is:



Assuming R_2 remains fixed at $1\text{M}\Omega$, then the new resistor is $20\text{k}\Omega$ to give a gain of -50.