

Solutions

Q1a

The fraction of the incident power that is absorbed by the load, is missing from the signal returned to the generator. This “loss” is called the return loss (RL) (1 mark)

$$RL = -10 \log \left(\frac{P_{in}^-}{P_{in}^+} \right) = -10 \log |\Gamma_{in}|^2 = -20 \log |\Gamma_{in}| \quad (1 \text{ mark})$$

Q1b

$$\lambda = \frac{c}{f} = 10 \text{ cm}$$

Therefore

$$\beta \ell = \frac{2\pi}{\lambda} \times 1 = 0.628 \quad (1 \text{ mark})$$

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan(\beta \ell)}{Z_o + jZ_L \tan(\beta \ell)} = (62 - j35) \Omega \quad (1 \text{ mark})$$

$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = 0.19 - j0.25 = 0.31 \angle -52.7^\circ \quad (1 \text{ mark})$$

$$VSWR = \frac{1 + |\Gamma_{in}|}{1 - |\Gamma_{in}|} = 1.9 \quad (1 \text{ mark})$$

$$IL = 10 \log \left(1 - |\Gamma_{in}|^2 \right) = -0.45 \text{ dB} \quad (1 \text{ mark})$$

Q1c

For a lossless line

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan(\beta \ell)}{Z_o + jZ_L \tan(\beta \ell)}$$

When the line is terminated by a load impedance of $Z_L = 0$, i.e. short circuited line, the input impedance is given by

$$Z_{inSC} = jZ_o \tan(\beta \ell) \quad (1 \text{ mark})$$

which is a reactive impedance that can be made equivalent to a lumped capacitor or inductor by adjusting the length ℓ . An inductive reactance can be obtained using $0 \leq \ell \leq 0.25\lambda$, while for $0.25\lambda \leq \ell \leq 0.5\lambda$ a capacitive reactance can be achieved. (2 marks)

When the line is terminated by a load impedance of $Z_L = \infty$, i.e. open circuited line, the input impedance is given by

$$Z_{inOC} = -jZ_o \cot(\beta \ell) \quad (1 \text{ mark})$$

Again, this is a reactive impedance that can be made equivalent to a lumped capacitor or inductor by adjusting the length ℓ . A capacitive reactance can be obtained using $0 \leq \ell \leq 0.25\lambda$ while for $0.25\lambda \leq \ell \leq 0.5\lambda$ an inductive reactance can be achieved. (2 marks)

Q1d

The voltage at any point along the line is a superposition of the incident and reflected voltage components, i.e.

$$V = V_{inc} + V_{ref} \quad (1 \text{ mark})$$

Therefore the voltage at a distance d from the load is given by

$$V = V_{inc} (1 + \Gamma e^{-2j\beta d}) \quad (1 \text{ mark})$$

$$|V| = |V_{inc}| \left| 1 + \rho e^{-2j(\beta d - \frac{\theta}{2})} \right|$$

In which ρ and θ represent the magnitude and phase of the reflection coefficient at the load, (1 mark)
which means

$$|V_{max}| = |V_{inc}| (1 + \rho) \quad \text{when} \quad (\beta d - \frac{\theta}{2}) = n\pi \quad (1 \text{ mark})$$

and

$$|V_{min}| = |V_{inc}| (1 - \rho) \quad \text{when} \quad (\beta d - \frac{\theta}{2}) = n\pi + \frac{\pi}{2} \quad (1 \text{ mark})$$

Since the voltage standing wave ratio is defined as


$$VSWR = \frac{|V_{max}|}{|V_{min}|} \quad (1 \text{ mark})$$

Therefore

$$VSWR = \frac{1 + |\rho|}{1 - |\rho|} \quad (1 \text{ mark})$$

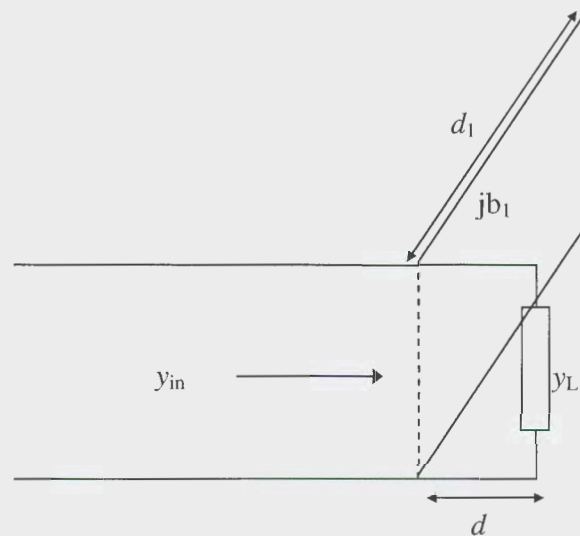Q2a

A single open, or short, circuited transmission line stub whose length d_1 may be varied between 0 and 0.25λ , and whose position along a transmission line, d , is adjustable over a range of 0.5λ will match Z_L to the main line. (1 mark)



(1 mark)

The main problem is to choose d_1 and d such that $y_{in}=1$, i.e. matched to the line. The distance d is chosen such that y_L is transformed to some point lying on the unit conductance circle, i.e. in the absence of stub $y_{in}=1 \pm jb$. (2 marks)

Q2b

For a VSWR of 5, the VSWR circle can be plotted on the Smith chart. (1 mark)

Since the angle of input reflection coefficient is 40° , point A represents the normalized input

impedance, i.e. $z_{in} = 1.3 + j2$ (1 mark)

which means $Z_{in} = (65 + j100)\Omega$ (1 mark)

To find the load impedance, move a distance of 0.1λ , towards load, from point A to B. (1 mark)


The impedance at B $z_L = 0.3 + j0.63$ (1 mark)

which means $Z_L = 15 + j31.5$ (1 mark)


The Complete Smith Chart

Black Magic Design

0.12

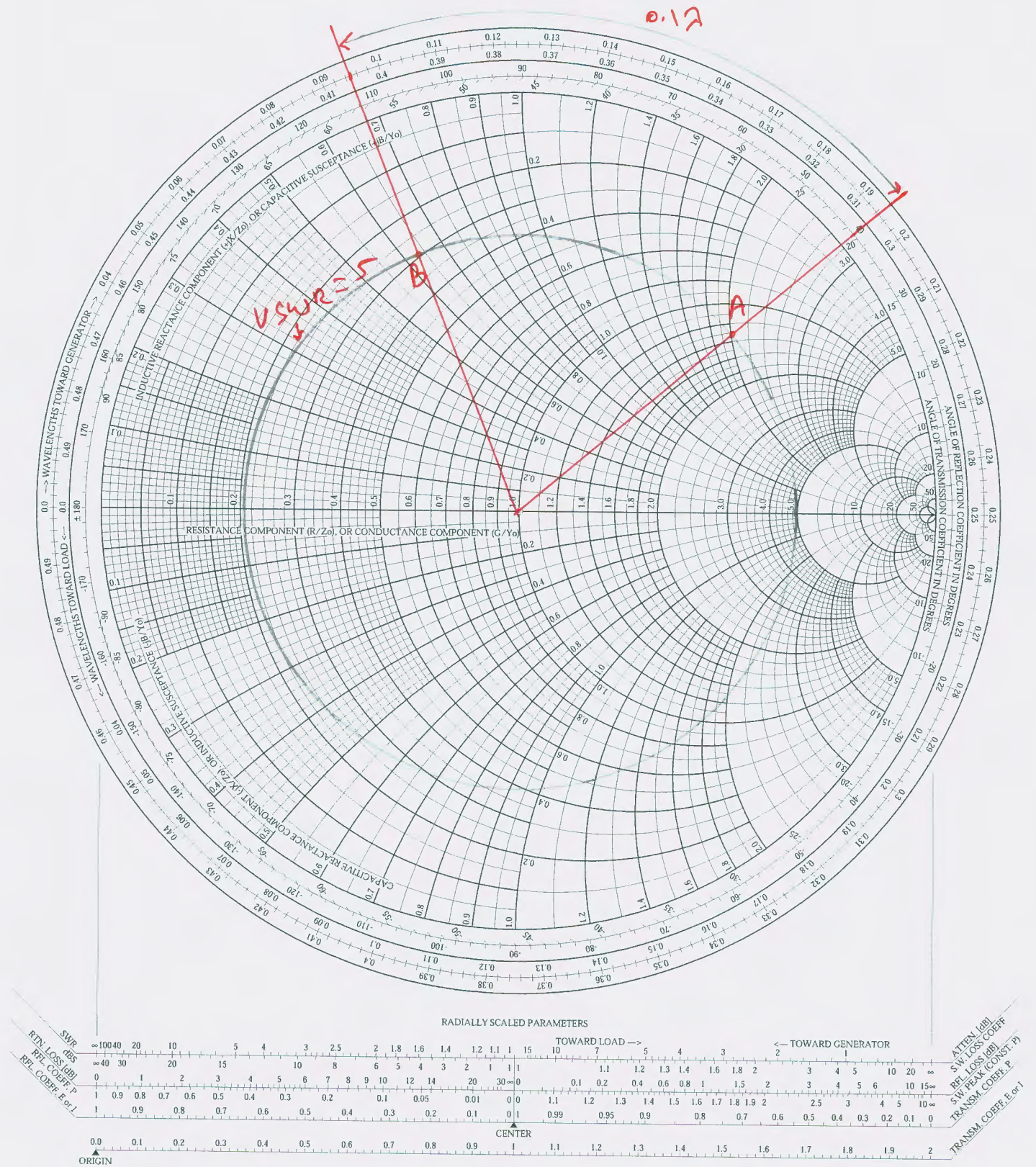

Q2c

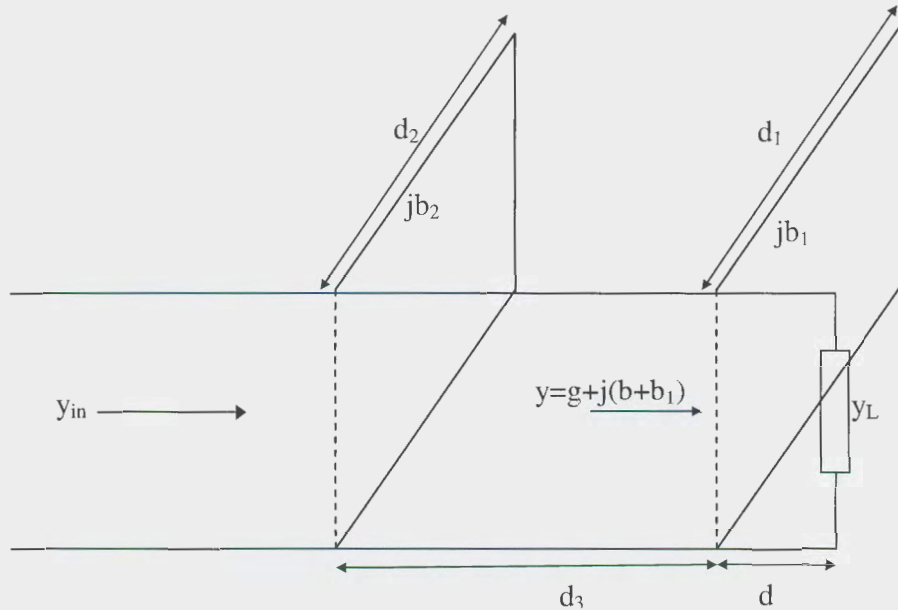

$$z_L = \frac{(100 + j40)}{50} = 2 + j0.8$$

(point A)

(1 mark)

$$\text{i.e. } y_L = 0.43 - j0.17$$

(point B)

(1 mark)

Step 1

Rotate the unit *g* circle *Towards Load*, by a distance of $d_3 = 0.125\lambda$.

(1 mark)

Step 2

Move from point B to intersect the new, rotated, unit circle at point C. The movement should be on the corresponding conductance circle, since the stub does not alter the real part of the admittance.

(1 mark)

Step 3

The admittance at point C is

$$y_C = 0.43 + j0.18$$

(1 mark)

compare it with that at B

$$y_L = 0.43 - j0.17$$

shows that stub 1 has provided $j0.35$, i.e. $b_1 = 0.35$

(1 mark)

Step 4

For an o.c. stub, this means $d_1 = 0.054\lambda$, i.e. the distance from D to E on the chart.

(1 mark)

Step 5

Move a distance $d_3 = 0.125\lambda$ along the line from the 1st stub position to the 2nd stub position (from point C to F).

(1 mark)

Step 6

At point F, the admittance is $y_F = 1 + j0.9$, i.e. stub 2 must provide $-j0.9$ ($b_2 = -0.9$) to reach the matched condition.

(1 mark)

Step 7


For an o.c. stub, this means $d_2 = 0.133\lambda$, i.e. the distance from G to H on the chart.

(1 mark)

D2C

The Complete Smith Chart

Black Magic Design

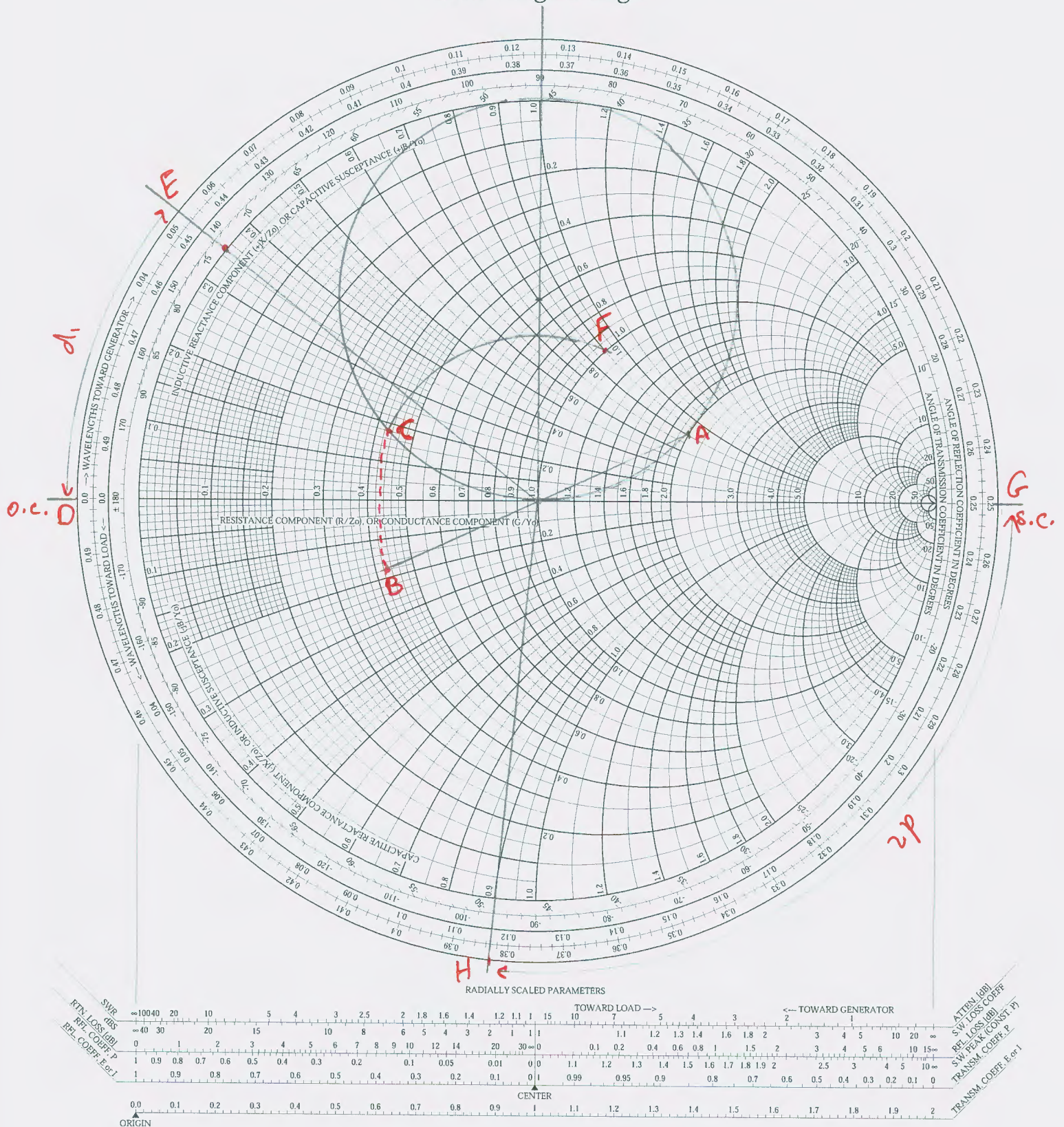

Q3a



SFD can be used for a graphical representation of the interaction between the incident and scattered waves in a microwave network. (1 mark)

There are two basic components of any SFD:

Nodes; each port in the network has two nodes a_n and b_n . The node a_n represents a wave entering port n , while node b_n represents a wave reflected from port n .

Branches; each branch represents a direct path between a-node and b-node. For each branch there is an associated S parameter or reflection coefficient. (1 mark)

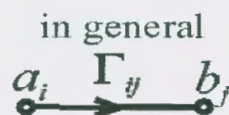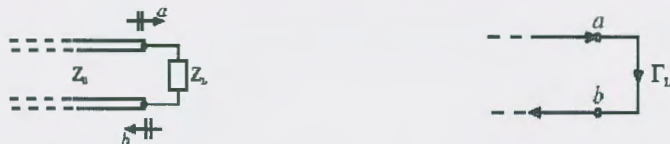An example of the SFD of a one-port network is shown below



(2 marks)

Q3b

Available Power Gain

$$G_A = \frac{P_{avn}}{P_{avs}} \quad (1 \text{ mark})$$

It is the ratio between power available from the network and the power available from the source. In most of the cases this gain is independent of Z_L . Gain of some active circuits is a function of Z_L .

(1 mark)

Transducer Power Gain

$$G_T = \frac{P_L}{P_{avs}} \quad (1 \text{ mark})$$

It is the ratio between power available at the load and the power available from the source. This gain depends on both Z_g and Z_L . (1 mark)

Q3c

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

(1 mark)

For the given network

$$V_1 = V_2 - 75 I_2$$

(1 mark)

$$I_1 = -I_2$$

(1 mark)

which gives

$$A=1, B=75, C=0, D=1$$

(1 mark)

Q3d

To calculate S_{11} , the impedance Z_{in1} is required when the network is terminated with Z_0 , where $Z_0 = Z_{o1} = Z_{o2}$

$$Z_{in1} = \frac{Z_1(Z_2 + Z_o)}{Z_1 + Z_2 + Z_o} \quad (1 \text{ mark})$$

$$S_{11} = \Gamma_{in} = \frac{Z_{in1} - Z_o}{Z_{in1} + Z_o}$$

i.e.

$$S_{11} = \frac{Z_1 Z_2 - Z_o(Z_2 + Z_o)}{Z_1 Z_2 + Z_o(Z_2 + Z_o) + 2Z_o Z_1} \quad (1 \text{ mark})$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

For the 1st port

$$V_1 = \sqrt{Z_o}(a_1 + b_1)$$

$$V_2 = \sqrt{Z_o}b_2 \quad (1 \text{ mark})$$

Therefore

$$\frac{V_1}{V_2} = \frac{(a_1 + b_1)}{b_2} = \frac{(1 + \frac{b_1}{a_1})}{\frac{b_2}{a_1}} = \frac{1 + S_{11}}{S_{21}}$$

i.e.

$$S_{21} = \frac{V_2}{V_1}(1 + S_{11}) \quad (1 \text{ mark})$$

Since

$$V_2 = V_1 \frac{Z_o}{(Z_o + Z_2)}$$

then

$$\frac{V_2}{V_1} = \frac{Z_o}{(Z_o + Z_2)} \quad (1 \text{ mark})$$

$$1 + S_{11} = \frac{2Z_1(Z_o + Z_2)}{Z_1 Z_2 + Z_o(Z_2 + Z_o) + 2Z_o Z_1}$$

Therefore

$$S_{21} = \frac{2Z_o Z_1}{Z_1 Z_2 + Z_o(Z_2 + Z_o) + 2Z_o Z_1} \quad (1 \text{ mark})$$

Similarly

$$Z_{in2} = Z_2 + \left(\frac{Z_1 Z_o}{Z_1 + Z_o} \right)$$

then

$$S_{22} = \frac{Z_{in2} - Z_o}{Z_{in2} + Z_o} = \frac{Z_1 Z_2 + Z_o(Z_2 - Z_o)}{(Z_1 Z_2 + Z_o(Z_o + Z_2)) + 2Z_1 Z_o} \quad (1 \text{ mark})$$

and

$$S_{12} = \frac{2Z_o Z_1}{Z_1 Z_2 + Z_o(Z_2 + Z_o) + 2Z_o Z_1} \quad (1 \text{ mark})$$

Q4a

Generally transistors presents a significant impedance mismatch, so matching will be achieved over a narrow frequency bandwidth. When bandwidth is an issue, then we design for a gain less than the maximum, imperfect matching, to improve bandwidth. (2 marks)

Sometimes it is required to design an amplifier with a specific gain, other than the maximum.

Constant gain circles will be used to facilitate design for a specific gain. (2 marks)

Q4b

The reflections coefficients can be calculated as

$$\Gamma_s = \frac{Z_g - Z_o}{Z_g + Z_o} = \frac{20 - 50}{20 + 50} = -0.429 \quad (0.5 \text{ mark})$$

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{30 - 50}{30 + 50} = -0.25 \quad (0.5 \text{ mark})$$

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = 0.455 \angle 150^\circ \quad (1 \text{ mark})$$

$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} = 0.408 \angle -151^\circ \quad (1 \text{ mark})$$

Therefore the required gains are

$$G = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 (1 - |\Gamma_{in}|^2)} = 5.94 \quad (1 \text{ mark})$$

$$G_A = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11}\Gamma_s|^2 (1 - |\Gamma_{out}|^2)} = 5.85 \quad (1 \text{ mark})$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2) (1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 |1 - \Gamma_s \Gamma_{in}|^2} = 5.49 \quad (1 \text{ mark})$$

Q4c

$$N = \frac{NF - NF_{\min}}{4R_N / Z_o} |1 + \Gamma_{\text{opt}}|^2 = \frac{1.778 - 1.58}{80 / 50} |1 + 0.62 \angle 100^\circ|^2 = 0.145 \quad (1 \text{ mark})$$

$$C_{NF} = \frac{\Gamma_{\text{opt}}}{(N + 1)} = 0.541 \angle 100^\circ \quad (1 \text{ mark})$$

$$r_{NF} = \frac{\sqrt{N(N + 1 - |\Gamma_{\text{opt}}|^2)}}{(N + 1)} = 0.29 \quad (1 \text{ mark})$$

Next we calculate data for several input section constant gain circles

G_s	g_s	C_s	R_s
1.5dB	0.905	$0.56 \angle 60^\circ$	0.204
1.7dB	0.948	$0.58 \angle 60^\circ$	0.149
1.8dB	0.970	$0.59 \angle 60^\circ$	0.112

The noise figure and constant gain circles are plotted on the Smith chart (4 marks, 1 for each circle)

and the $G_S = 1.8\text{dB}$ circle just intersects the noise figure circle, and any higher gain will result in a worse noise figure. (1 mark)

From the Smith chart the optimum solution is then $\Gamma_S = 0.55 \angle 70^\circ$ when $NF = 2.5\text{dB}$. (2 marks)

