

WEEK 1 - worked Example

Given a function $F = \bar{A}B + \bar{B}C$, produce a logic gate diagram and a truth table.

Solution The order of precedence is NOT, AND, OR. This means that when we evaluate the function, we evaluate NOT first then AND then OR. There are 3 variables A, B, C so the truth table will have $2^3 = 8$ rows covering all possible combinations of A, B, C. (2 because this is a binary system)

ABC	\bar{A}	$\bar{A} \cdot B$	\bar{B}	$\bar{B} \cdot C$	F
000	1	0	1	0	0
001	1	0	1	1	1
010	1	1	0	0	1
011	1	1	0	0	1
100	0	0	1	0	0
101	0	0	1	1	1
110	0	0	0	0	0
111	0	0	0	0	0

calculate \bar{A} and \bar{B} before 'AND'ing

$F = \bar{A}B + \bar{B}C$ order of precedence is telling us that this is the same as


$$F = (\bar{A}B) + (\bar{B}C)$$

calculate these terms before 'OR'ing


To construct a logic diagram:

The inputs (generally taken from the left) are A, B, C

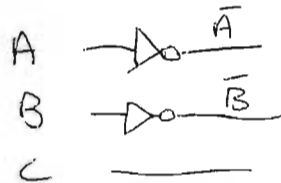- ① form the NOT of A and B as NOT has the highest order of precedence.



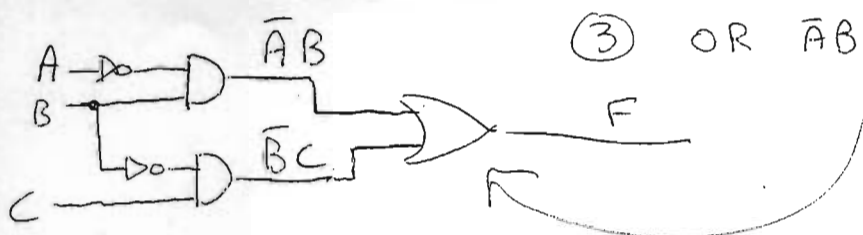- ② Form the AND terms $\bar{A}B$ and $\bar{B}C$



- ③ OR $\bar{A}B$ with $\bar{B}C$

