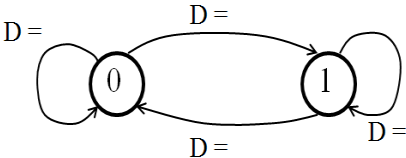
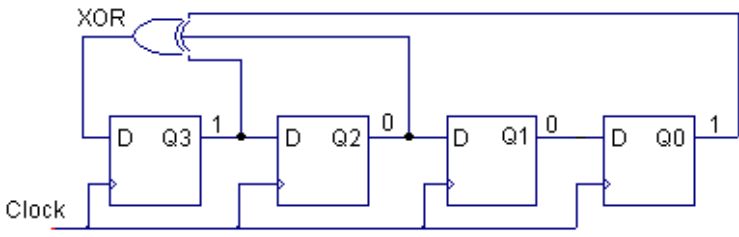


EEE104 – Digital Systems - Interim Test 2009

Answer All questions by writing the answer in the appropriate box provided

<p>1 Write down the value for A B C D that will satisfy the Boolean expression below.</p> $\overline{A.B.C.D} = 0$	<table border="1" style="width: 100%; text-align: center;"> <tr> <th style="padding: 5px;">A</th> <th style="padding: 5px;">B</th> <th style="padding: 5px;">C</th> <th style="padding: 5px;">D</th> </tr> <tr> <td style="height: 30px;"></td> <td></td> <td></td> <td></td> </tr> </table>	A	B	C	D																				
A	B	C	D																						
<p>2 Complete the following Boolean expressions: (where A' represents NOT A)</p>	<p>i. $A + 1 =$ ii. $A + A' =$ iii. $A + A =$ iv. $A + 0 =$</p>																								
<p>3 Express the decimal number -39 as an eight bit binary 2's complement number.</p>	<div style="border: 1px solid black; height: 40px; width: 100%;"></div>																								
<p>4 Complete the truth table for the circuit below.</p> <div style="text-align: center; margin: 20px;"> </div>	<table border="1" style="width: 100%; text-align: center;"> <tr> <th style="padding: 5px;">A B</th> <th style="padding: 5px;">F</th> </tr> <tr><td style="padding: 5px;">0 0</td><td style="height: 30px;"></td></tr> <tr><td style="padding: 5px;">0 1</td><td></td></tr> <tr><td style="padding: 5px;">1 0</td><td></td></tr> <tr><td style="padding: 5px;">1 1</td><td></td></tr> </table>	A B	F	0 0		0 1		1 0		1 1															
A B	F																								
0 0																									
0 1																									
1 0																									
1 1																									
<p>5 Write down the dual of the expression $X.0 = 0$ (duality principle)</p>	<div style="border: 1px solid black; height: 40px; width: 100%;"></div>																								
<p>6 Complete the truth table for the 2-to-1 multiplexer given by:</p> <table style="margin: 20px auto; border-collapse: collapse;"> <tr> <td style="border-right: 1px solid black; padding: 5px 10px; text-align: center;">S</td> <td style="padding: 5px 10px; text-align: center;">Y</td> </tr> <tr> <td style="border-right: 1px solid black; padding: 5px 10px; text-align: center;">0</td> <td style="padding: 5px 10px; text-align: center;">A</td> </tr> <tr> <td style="border-right: 1px solid black; padding: 5px 10px; text-align: center;">1</td> <td style="padding: 5px 10px; text-align: center;">B</td> </tr> </table> <p>where S is the select line, A,B are the data inputs Y is the output</p>	S	Y	0	A	1	B	<table border="1" style="width: 100%; text-align: center;"> <tr> <th style="padding: 5px;">S A B</th> <th style="padding: 5px;">Y</th> </tr> <tr><td style="padding: 5px;">0 0 0</td><td style="height: 30px;"></td></tr> <tr><td style="padding: 5px;">0 0 1</td><td></td></tr> <tr><td style="padding: 5px;">0 1 0</td><td></td></tr> <tr><td style="padding: 5px;">0 1 1</td><td></td></tr> <tr><td style="padding: 5px;">1 0 0</td><td></td></tr> <tr><td style="padding: 5px;">1 0 1</td><td></td></tr> <tr><td style="padding: 5px;">1 1 0</td><td></td></tr> <tr><td style="padding: 5px;">1 1 1</td><td></td></tr> </table>	S A B	Y	0 0 0		0 0 1		0 1 0		0 1 1		1 0 0		1 0 1		1 1 0		1 1 1	
S	Y																								
0	A																								
1	B																								
S A B	Y																								
0 0 0																									
0 0 1																									
0 1 0																									
0 1 1																									
1 0 0																									
1 0 1																									
1 1 0																									
1 1 1																									

Please Turn Over

7	What binary number is represented by the hexadecimal number DA																
8	Express the function $F(A,B) = A \text{ XNOR } B$ as a fundamental product of sums.																
9	Complete the truth table for a half adder with inputs A and B	<table> <tr> <th>A B</th><th>SUM</th><th>CARRY</th></tr> <tr> <td>0 0</td><td></td><td></td></tr> <tr> <td>0 1</td><td></td><td></td></tr> <tr> <td>1 0</td><td></td><td></td></tr> <tr> <td>1 1</td><td></td><td></td></tr> </table>	A B	SUM	CARRY	0 0			0 1			1 0			1 1		
A B	SUM	CARRY															
0 0																	
0 1																	
1 0																	
1 1																	
10	Complete the state diagram for a D-Type flip-flop, by filling in the D input values on the directed lines.																
11	What is the frequency in MHz of a clock waveform that has a pulse width of 10ns and a duty cycle of 20%																
12	<p>The linear feedback shift register shown below is in the state 1001. What will the new stable state be after the next two clock pulses have been applied?</p> 	<p>Q3 =</p> <p>Q2 =</p> <p>Q1 =</p> <p>Q0 =</p>															

Examiner Use Only: