

Q1(ii) at h.f. $X_c \ll R_1$ and $X_c \ll R_2 \therefore \frac{v_o}{v_i} \approx 1$

at l.f. $X_c \gg R_1$ and $X_c \gg R_2 \therefore \frac{v_o}{v_i} \approx \frac{R_1 + R_2}{R_1}$

$$\begin{aligned}
 \text{(ii)} \quad \frac{v_o}{v_i} &= \frac{R_1 + \frac{R_2/s}{R_2 + 1/s}}{R_1} = \frac{R_1 + \frac{R_2}{1 + sCR_2}}{R_1} \\
 &= \frac{R_1 + sCR_1R_2 + R_2}{R_1(1 + sCR_2)} = \frac{R_1 + R_2}{R_1} \cdot \frac{1 + sC \frac{R_1R_2}{R_1 + R_2}}{1 + sCR_2} \\
 &\equiv k \cdot \frac{1 + jf/f_1}{1 + jf/f_0} \quad \text{where } k = \frac{R_1 + R_2}{R_1}, \quad f_1 = \frac{R_1 + R_2}{2\pi C R_1 R_2} \\
 &\quad \text{and } f_0 = \frac{1}{2\pi C R_2}
 \end{aligned}$$


(iii). immediately before the step, l.f. gain dominates

$$\text{so } v_o|_{t=0^-} = -2 \times \text{l.f. gain} = -12 \text{ V}$$

$$v_o|_{t=0^+} = -12 + \Delta v_o \text{ due to step.}$$

$$= -12 + 4 \times \text{h.f. gain} = -12 + 4 = -8 \text{ V.}$$

$$v_o|_{t \rightarrow \infty} = +2 \times \text{l.f. gain} = +12 \text{ V.}$$

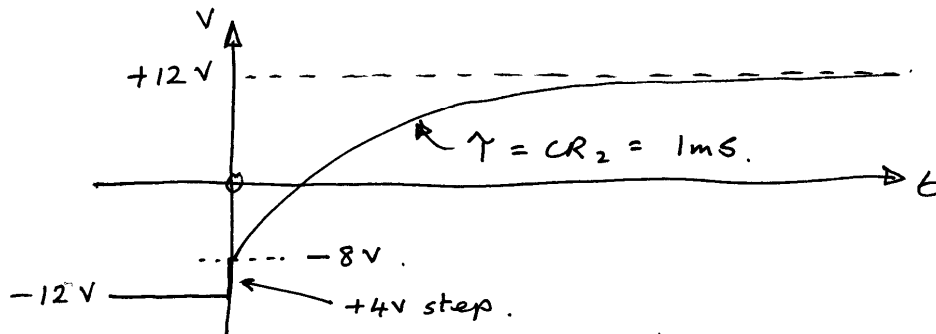

$$\text{(iv)} \quad \frac{v_o}{v_i} = 6 \cdot \frac{1 + j \frac{400}{955}}{1 + j \frac{400}{159}}$$

$$\left| \frac{v_o}{v_i} \right| = 6 \left[\frac{1 + \left(\frac{400}{955} \right)^2}{1 + \left(\frac{400}{159} \right)^2} \right]^{1/2} = 6 \left[\frac{1 + 0.175}{1 + 6.329} \right]^{1/2} = \underline{\underline{2.40}}$$

$$\begin{aligned}\angle\left(\frac{v_o}{v_i}\right) &= \tan^{-1} \frac{400}{955} - \tan^{-1} \frac{400}{159} \\ &= 22.7^\circ - 68.3^\circ = \underline{\underline{-45.6^\circ}}\end{aligned}$$

(v) With two identical circuits in series

$$\text{overall } |gain| = gain(1) \times gain(2) = 2.4^2 = \underline{\underline{5.76}}$$

$$\begin{aligned}\text{overall phase} &= \text{phase}(1) + \text{phase}(2) = 2 \times (-45.6) \\ &= \underline{\underline{-91.2^\circ}}\end{aligned}$$

(vi) The pole frequency is 159 Hz, the zero frequency is 995 Hz. At 100 kHz neither will be having a significant effect and so design gain ≈ 1 .

$$\begin{aligned}\text{The required GBP is therefore } &1 \times 100 \text{ kHz} \\ &= \underline{\underline{100 \text{ kHz}}}\end{aligned}$$

Q2 (i) parasitic second order behaviour arises when unwanted component reactances interact to form an underdamped second order behaviour.

note that the question asks only about transient responses. No marks are available for frequency domain comments

The commonest indicator of parasitic second order responses is ringing in response to transient signal changes. In the frequency domain one would observe gain peaking at particular frequencies and phase shifts that approached -180° .

(ii) Sum currents at v^- node

$$i_m - i_p + i_f = 0$$

$$v^- = -v_o / A_v$$

$$\therefore i_p = v^- s C_p = -\frac{v_o s C_p}{A_v}$$

$$i_f = \frac{v_o - v^-}{Z_f} = \frac{v_o}{Z_f} \left(1 + \frac{1}{A_v}\right)$$

$$= v_o \left(1 + \frac{1}{A_v}\right) \left(\frac{1 + s C_f R_f}{R_f}\right)$$

$$\therefore i_m = -v_o \left[\frac{s C_p}{A_v} + \frac{1 + s C_f R_f}{R_f} + \frac{1 + s C_f R_f}{A_v R_f} \right]$$

$$= -\frac{v_o}{R_f} \left[\frac{s C_p R_f}{A_v} + 1 + s C_f R_f + \frac{1}{A_v} + \frac{s C_f R_f}{A_v} \right]$$

$$= -\frac{v_o}{R_f} \left[1 + \frac{1}{A_v} + s R_f \left(C_f \left(1 + \frac{1}{A_v}\right) + \frac{C_p}{A_v} \right) \right]$$

$$\text{or } \frac{v_o}{i_m} = - \frac{R_f}{1 + \frac{1}{A_v} + s R_f \left[C_f \left(1 + \frac{1}{A_v}\right) + \frac{C_p}{A_v} \right]}$$

$$(iii) \frac{v_o}{i_m} \approx - \frac{R_f}{1 + s \left[\frac{1}{GBP} + C_f R_f \right] + s^2 \frac{C_p R_f}{GBP}}$$

This is a low pass transfer function.

ω_n , the undamped natural frequency is


$$\omega_n = \sqrt{\frac{GBP}{C_p R_f}} \text{ by comparison with standard form.}$$

$$\frac{1}{\omega_n q} = \frac{1}{GBP} + C_f R_f = \text{coefficient of "s" in the denominator.}$$

$$\begin{aligned} \therefore \frac{1}{q} &= \omega_n \left[\frac{1}{GBP} + C_f R_f \right] = \sqrt{\frac{GBP}{C_p R_f}} \left[\frac{1}{GBP} + C_f R_f \right] \\ &= \frac{1}{\sqrt{GBP C_p R_f}} + \frac{\sqrt{GBP R_f}}{\sqrt{C_p}} \cdot C_f \\ &= \frac{1 + \sqrt{GBP R_f} \cdot C_f \cdot \sqrt{GBP R_f}}{\sqrt{GBP C_p R_f}} \end{aligned}$$

$$\text{or } q = \frac{\sqrt{GBP \cdot C_p \cdot R_f}}{1 + GBP \cdot R_f \cdot C_f}$$

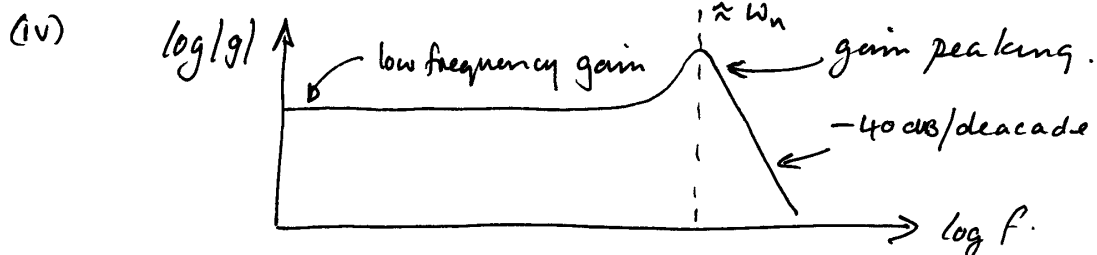note that the labels are not required by the question so are not necessary in order to get the 2 marks for part (iv)



$$\begin{aligned} \text{(v)(a) When } C_f = 0, \quad q &= \sqrt{GBP \cdot C_p \cdot R_f} \\ &= \sqrt{2 \cdot \pi \cdot 4 \cdot 10^6 \cdot 50 \cdot 10^{-12} \cdot 10^4} \\ &= \underline{\underline{3.54}} \end{aligned}$$

(b) For a q of 0.707 ...

$$\begin{aligned} 0.707 &= \frac{3.54}{1 + GBP \cdot R_f \cdot C_f} \quad \text{or } C_f = \frac{3.54}{0.707} - 1 \\ &\quad \frac{1}{GBP \cdot R_f} \\ &= \frac{4}{2 \cdot \pi \cdot 4 \cdot 10^6 \cdot 10^4} = \underline{\underline{15.9 \text{ pF}}} \approx 16 \text{ pF} \end{aligned}$$

Q3a) $R_{Th} = 2k\Omega // 1k\Omega = \underline{\underline{667\Omega}}$ by inspection

$$\overline{V_{on}^2} / \text{due to } R_1 = 4kTR_1 \left(\frac{R_2}{R_1 + R_2} \right)^2 = 33.1 \times 10^{-18} \times \frac{1}{9} = 3.68 \times 10^{-18}$$

$$\overline{V_{on}^2} / \text{due to } I_{pA} = (I_{pA})^2 \times R_{Th}^2 = 10^{-24} \times 445 \times 10^3 = 0.44 \times 10^{-18}$$

$$\overline{V_{on}^2} / \text{due to } S_{nV} = (S_{nV})^2 \times \left(\frac{R_2}{R_1 + R_2} \right)^2 = 25 \times 10^{-18} \times \frac{1}{9} = 2.78 \times 10^{-18}$$

$$\overline{V_{on}^2} / \text{due to } S_{pA} = (S_{pA})^2 \times R_{Th}^2 = 25 \times 10^{-24} \times 445 \times 10^3 = 11.13 \times 10^{-18}$$

$$\overline{V_{on}^2} / \text{due to } R_2 = 4kTR_2 \left(\frac{R_1}{R_1 + R_2} \right) = 16.56 \times 10^{-18} \times \frac{4}{9} = 7.36 \times 10^{-18}$$


$$\overline{V_{onT}^2} = [3.68 + 0.44 + 2.78 + 11.13 + 7.36] \times 10^{-18} = 25.39 \times 10^{-18}$$

$$\therefore V_{nTh} = \sqrt{25.39 \times 10^{-18}} = \underline{\underline{5.04 \mu V \text{ Hz}^{-1/2}}}$$

(i) $\overline{V_{onT}^2} = 4kT_e R_{Th}$

or $T_e = \frac{\overline{V_{onT}^2}}{4k R_{Th}} = \underline{\underline{690 \text{ K}}}$

(b)(i).

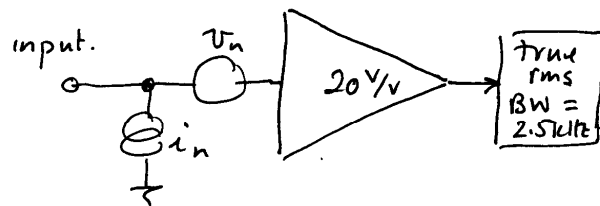

when input is shorted to ground, i_n has no effect so meter reading is...

$$8 \times 10^{-6} = \sqrt{V_n^2 (20)^2 2500}$$

$$\text{or } V_n = \frac{8 \times 10^{-6}}{20 \sqrt{2500}} = \underline{\underline{8 \mu V \text{ Hz}^{-1/2}}}$$

(ii) when input grounded by $3.9 \text{ k}\Omega$, meter reading is

$$13 \mu\text{V} = \sqrt{(v_n^2 + i_n^2 3.9 \text{ k}\Omega^2 + 4kT 3.9 \text{ k}\Omega)(20)^2 2500.}$$

$$= \sqrt{(64 \times 10^{-18} + i_n^2 \cdot 3.9 \text{ k}\Omega^2 + 64.6 \times 10^{-18}) \times 10^6.}$$

$$13 \text{ nV} = \sqrt{128.6 \times 10^{-18} + (i_n \cdot 3.9 \text{ k}\Omega)^2.}$$

$$(169 - 128.6) \times 10^{-18} = (i_n \cdot 3.9 \text{ k}\Omega)^2.$$

$$40.4 \times 10^{-18} = i_n^2 \times 3.9 \text{ k}\Omega^2$$

$$i_n = \sqrt{\frac{40.4 \times 10^{-18}}{15.21 \times 10^6}} = \underline{\underline{1.63 \text{ pA Hz}^{-1/2}}}.$$

(iii) Optimum R_s from an F point of view ...

$$F = \frac{v_n^2 + i_n^2 R_s^2 + 4kT R_s}{4kT R_s.}$$

$$= \frac{v_n^2}{4kT R_s} + \frac{i_n^2 R_s}{4kT} + 1.$$

$$\frac{dF}{dR_s} = -\frac{v_n^2}{4kT R_s^2} + \frac{i_n^2}{4kT} = 0 \text{ for min.}$$

$$\therefore \frac{i_n^2}{4kT} = \frac{v_n^2}{4kT R_s^2} \quad \text{or} \quad R_s = \frac{v_n}{i_n}$$

$$\therefore R_{s \text{ opt}} = \frac{8 \times 10^{-9}}{1.63 \times 10^{-12}} = \underline{\underline{4.9 \text{ k}\Omega}}.$$

(If they remember the result & use it correctly they'll get the marks but if their memory is faulty they will get no marks.)

Q4 (i) Class A In a class A amplifier, the output devices both conduct throughout the signal cycle.

Class B In a class B amplifier, the output devices are never on together and never off together. One device deals with the half cycles and the other with the other half cycles.

(ii) Power Supplied = Power Dissipated + Load Power

$$V_s I_{\text{SAVE/supply}} = P_D + \frac{V_p^2}{2R_L}$$

$$2 V_s \frac{I_p}{\pi} = P_D + \frac{V_p^2}{2R_L}$$

$$2 V_s \frac{V_p}{\pi R_L} = P_D + \frac{V_p^2}{2R_L}$$

$$\text{or } P_D = 2 \frac{V_s V_p}{\pi R_L} - \frac{V_p^2}{2R_L}$$

$$\frac{dP_D}{dV_p} = \frac{2V_s}{\pi R_L} - \frac{2V_p}{2R_L} = 0 \text{ for maximum}$$

$$\text{ie max } P_D \text{ when } \frac{2V_s}{\pi R_L} = \frac{2V_p}{2R_L} \text{ or } \underline{V_p = \frac{2V_s}{\pi}}$$

When $V_p = \frac{2V_s}{\pi}$, total dissipation is.

$$P_D = \frac{2V_s \left(\frac{2V_s}{\pi}\right)}{\pi R_L} - \frac{\left(\frac{2V_s}{\pi}\right)^2}{2R_L} = \frac{4V_s^2}{\pi^2 R_L} - \frac{2V_s^2}{\pi^2 R_L}$$

$$= \frac{2V_s^2}{\pi^2 R_L} \text{ for both output devices.}$$

$$\therefore \text{for one device, } \underline{P_D = \frac{V_s^2}{\pi^2 R_L}}$$

$$(iii) P = \frac{V_p^2}{2R_L} \quad 1000 = \frac{V_p^2}{2 \cdot 4}$$

$$\text{or } V_p^2 = 8000 \text{ so } V_p = V_s \approx \underline{\underline{90V.}}$$

$$(iv) \quad I_{pm} = V_{pm}/R_L = 90/4 = \underline{\underline{22.5 \text{ A}}}$$

$$I_{AVE} = \frac{I_p}{\pi} \quad \text{since each supply provides energy for alternative half cycles only}$$

$$= \frac{22.5}{\pi} = \underline{\underline{7.16 \text{ A}}}$$

$$(v) \quad \text{peak output device current} = \underline{\underline{22.5 \text{ A}}}$$

$$\text{peak output device voltage} = 2V_s = \underline{\underline{180 \text{ V}}}$$

$$\text{maximum average power dissipation is } \frac{V_s^2}{\pi^2 R_L} = \frac{90^2}{\pi^2 R_L} = \underline{\underline{202 \text{ W}}}$$

(vi)

$$T_s = T_j - \frac{P_D}{3} (\theta_{jc} + \theta_{cs})$$

$$= 150^\circ - 67.3 (1.1^\circ \text{C/W})$$


$$= 150^\circ - 74^\circ$$

$$= 76^\circ$$

$$T_s - T_A = P_D \theta_{SA}$$

$$76 - 35 = 202 \theta_{SA}$$
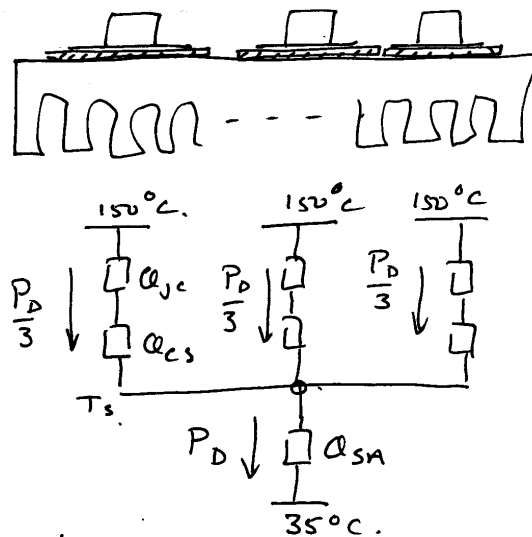
$$\frac{41}{202} = \theta_{SA} = \underline{\underline{0.2^\circ \text{C/W}}}$$



the comment is not required by the question and full marks can be gained without it

This would be a large heatsink and in most amplifiers would have fan assisted cooling to allow the heat to be removed from a much smaller dissipating area.