

1. Describe an equivalent circuit of the MOS cascode circuit in Figure 1 and find the trans-conductance, i.e. the ratio between the output current and input voltage.

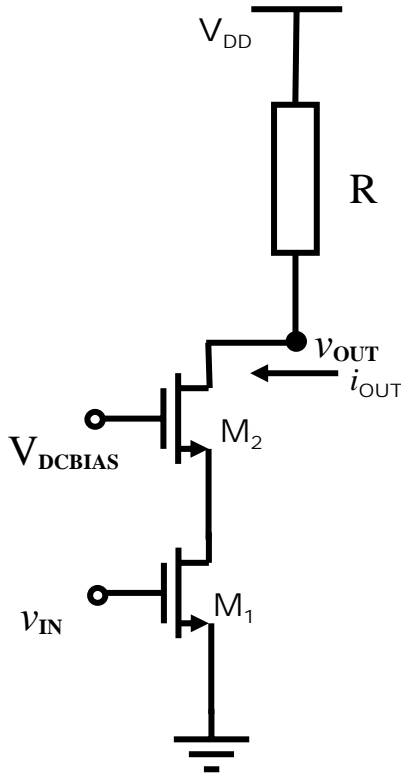


Figure 1a.

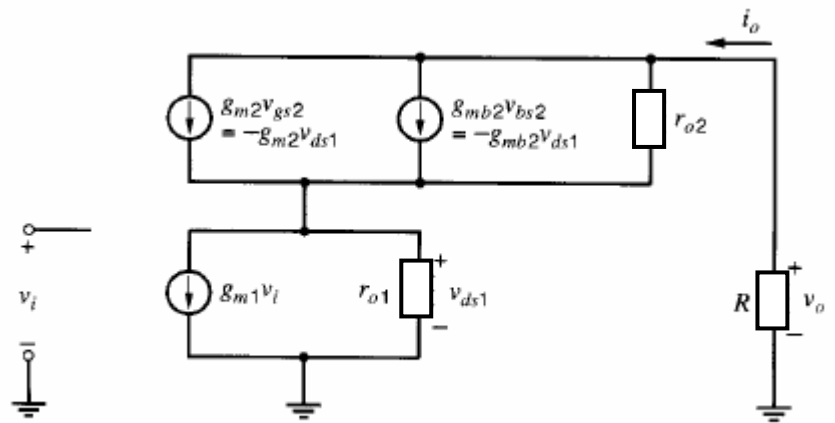


Figure 1b.

The small-signal equivalent circuit is shown in Figure 1b. Since the input is connected to the gate of M1, the input impedance is

$$R_i \rightarrow \infty$$

To find the transconductance, set $R=0$ to short the output and calculate the current i_o . From KCL at the output,

$$i_o + g_{m2}v_{ds1} + g_{mb2}v_{ds1} + \frac{v_{ds1}}{r_{o2}} = 0 \quad (1.1)$$

From KCL at the source of M2,

$$g_{m1}v_i + g_{m2}v_{ds1} + g_{mb2}v_{ds1} + \frac{v_{ds1}}{r_{o1}} + \frac{v_{ds1}}{r_{o2}} = 0 \quad (1.2)$$

Solving (1.2) for v_{ds1} , substituting into (1.1), and rearranging gives

$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0} = g_{m1} \left(1 - \frac{1}{1 + (g_{m2} + g_{mb2}) r_{o1} + \frac{r_{o1}}{r_{o2}}} \right) \approx g_{m1}$$

2. State a voltage gain of common source amplifier with an active load as in Figure 2, with a representation of a small signal equivalent circuit.

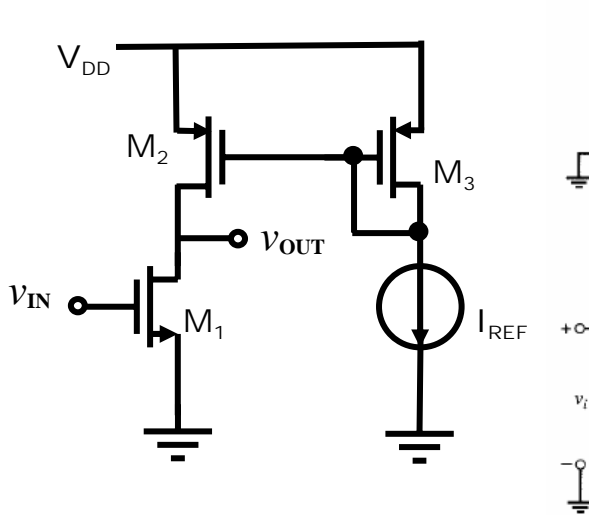


Figure 2.1

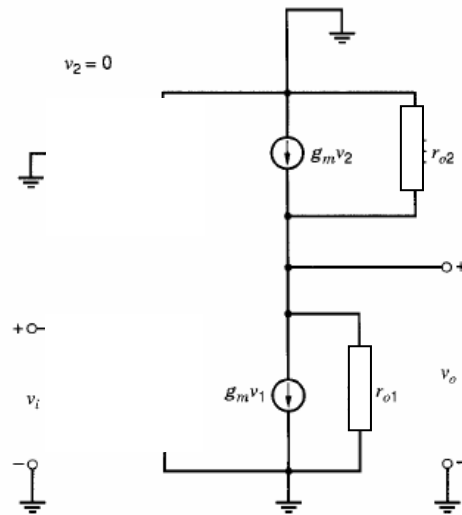


Figure 2.2

The primary characteristics of interest in the small signal analysis are the voltage-gain and output resistance when both devices operated in the active region. The small signal circuit is shown in Figure 2.2. Since I_{REF} in Figure 2.1 is assumed constant, the large-signal gate-source voltage of load transistor M2 is constant. Therefore, the small-signal voltage-controlled current $g_{m2}v_2=0$. To find the output resistance, we set the input to zero. Therefore $v_i=0$ and $g_{m1}v_i=0$, and the output resistance is

$$R_o = r_{o1} || r_{o2} \quad (2.1)$$

Since $v_2=0$, $g_{m1}v_i$ flows in $r_{o1} || r_{o2}$ and

$$A_v = - g_{m1}(r_{o1} || r_{o2}) \quad (2.2)$$

3. A CMOS differential pair with the current mirror load is shown in Figure 3.

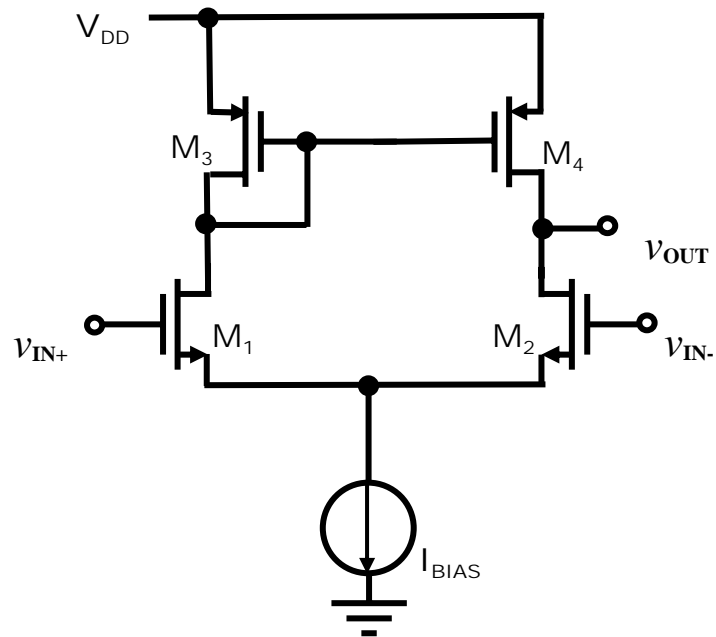


Figure 3.

3-1. Describe the circuit operation as a differential amplifier by representing an equivalent circuit.

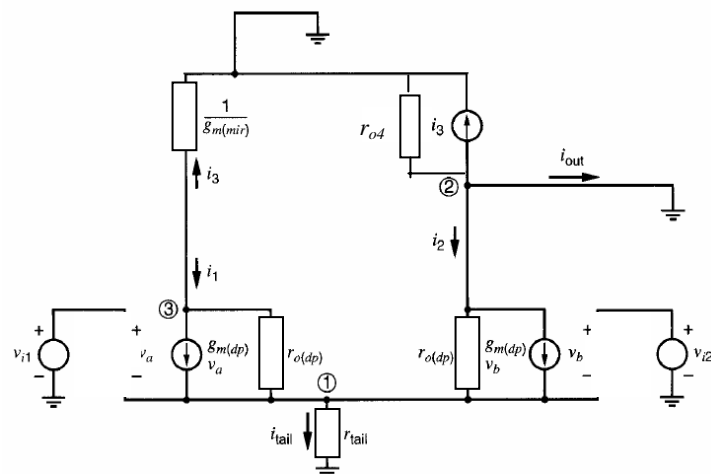


Figure 3.1

Assume $r_{tail} \rightarrow \infty$, $r_{o(dp)} \rightarrow \infty$, and $r_{o4} \rightarrow \infty$. The voltage v_1 at node 1 becomes the common-mode component v_{ic} , where $v_{ic} = (v_{i1} + v_{i2})/2$.

Let $v_{id} = v_{i1} - v_{i2}$ represent the differential mode of the input signal. Then $v_{i1} = v_{ic} + (v_{id}/2)$ and $v_{i2} = v_{ic} - (v_{id}/2)$. Therefore,

$$i_1 = g_{m(dp)}(v_{i1} - v_1) = g_{m(dp)} v_{id}/2$$

and

$$i_2 = g_{m(dp)}(v_{i2} - v_1) = -g_{m(dp)} v_{id}/2$$

(Please remember $v_1 = v_{ic}$.)

If with a resistive load and a single-ended output, only i_2 will flow in the output. Due to the active loads (also acting current mirror) of M3 and M4, not only i_2 but also most of i_3 flows in the output.

Therefore transconductance $G_m(dm)$ of a differential input transistor pair is

$$\begin{aligned} G_{m(dm)} &= i_{out} / v_{id} \\ &= g_{m(dp)} \end{aligned}$$

where $i_{out} = -i_3 - i_2$ (with active loads - current mirror as a pair of load).

3-2. State the output resistance.

The output resistance R_o is the resistance looking back into the node 2 with both inputs connected to small-signal ground:

$$R_o = r_{o4} || r_{o(dp)}$$

where r_{o4} , $r_{o(dp)}$ are output resistance of M4 and M2 (one of dp, differential pair), respectively.

4. Find the output resistance of a MOSFET. Assume the transistor operates in the active region with $I_D=5\mu\text{A}$ and $V_A=50\text{V}$. Neglect the body effect.

The output resistance of transistor is

$$r_o = \frac{V_A}{I_D} = \frac{50 \text{ V}}{5 \mu\text{A}} = 10\text{M}\Omega$$