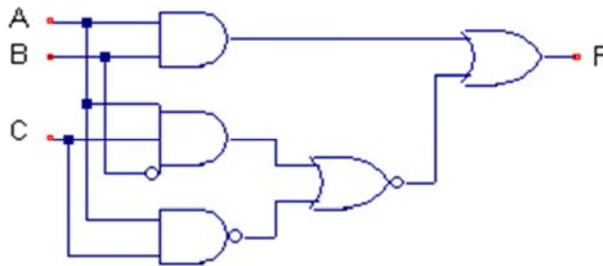



1. Complete the following equations:

$$X + 1 = \quad X + X = \quad X.0 = \quad X.1 = \quad X + 0 = \quad X + \overline{X} =$$

2. Use a truth table to prove that  $X.Y + \overline{X}.Z + Y.Z = X.Y + \overline{X}.Z$
3. Simplify the Boolean expression  $F = (X + Y)(X + Z)$
4. Find the truth table for the function  $F = X.Y + X.\overline{Y} + Y.\overline{Z}$  and use it to express F as a sum of minterms and a product of maxterms.
5. Describe the circuit below using a maxterm list.



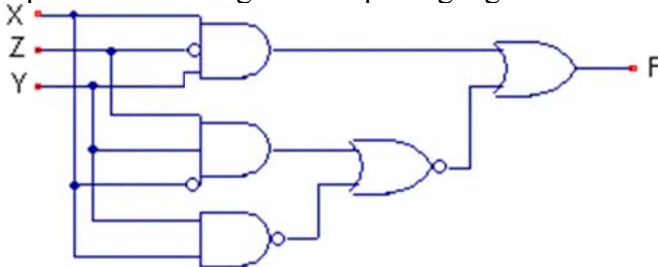6. Apply De Morgan's Theorem to  $F = A.\overline{B}.(C + \overline{D})$
7. Find an expression for the logic circuit below. Simplify this to show that the circuit is equivalent to a single two input logic gate.



8. An aircraft safety system accepts three binary signals X, Y, Z. The output warning light comes on ( $W = '1'$ ) when:

$$X = Y \text{ and } X \neq Z \text{ or } \\ X = Z \text{ and } X \neq Y$$

Find the truth table for this system and express it as a canonical product-of-sums.

9. Write down the truth table for the exclusive OR function and hence obtain a logic expression for it.
10. Express the exclusive NOR function as a Product of Sums.