

## Worked Solutions - Tutorial Sheet 1

1. No information on  $M$  Use circ data  
to calculate  $M$ .

On d.c

$$\begin{vmatrix} V_F \\ V_q \end{vmatrix} = \begin{vmatrix} R_F \\ \omega_r M \end{vmatrix} \quad \begin{vmatrix} 0 \\ R_q \end{vmatrix} \quad \begin{vmatrix} I_F \\ I_q \end{vmatrix}$$

But  $V = V_F + V_q$  &  $I = I_F = I_q$  since  
mk is a series m/c.

$$V = (R_F + R_q + \omega_r M) I$$

$$\omega_r M = \frac{V}{I} - R_F + R_q$$

$$M = \frac{V - IR}{\omega_r} = 1.66 \text{ H}$$

$$P_{\text{dep}} = VI = (R + \omega_r M) I^2$$

$$= \underbrace{I^2 R}_{P_{\text{loss}}} + \underbrace{I^2 \omega_r M}_{P_{\text{mech}}}$$

$$= P_{\text{loss}} + P_{\text{mech}}$$

$$P_{\text{mech}} = I^2 \omega_r M = T \omega_r$$

$$\therefore T = M I^2 = 0.597 \text{ N}$$

On a.c

$$\begin{bmatrix} V_F \\ V_q \end{bmatrix} = \begin{bmatrix} R_F + L_F p & 0 \\ \omega_r M & R_A + L_A p \end{bmatrix} \begin{bmatrix} \tilde{I}_F \\ \tilde{I}_A \end{bmatrix}$$

But again  $V = V_F + V_q$        $\tilde{I} = \tilde{I}_F + \tilde{I}_A$

$$V = R\tilde{I} + Lp\tilde{I} + \omega_r M\tilde{I}$$

On sinusoidal supply  $p = j\omega$

$$V = R\tilde{I} + j\omega_s L\tilde{I} + \omega_r M\tilde{I}$$

let  $N = \frac{\text{actual speed}}{\text{synchronous speed}} = \frac{\omega_r}{\omega_s}$

$$\begin{aligned} V &= R\tilde{I} + j\omega_s L\tilde{I} + \omega_r \frac{\omega_s}{\omega_s} M\tilde{I} \\ &= R\tilde{I} + j\omega_s L\tilde{I} + N\omega_s M\tilde{I} \quad [X_m = \omega_s M] \\ &= R\tilde{I} + j\omega_s L\tilde{I} + NX_m\tilde{I} \\ &= (R + NX_m + j\omega_s L)\tilde{I} \end{aligned}$$

$$\text{Power } \alpha p = \text{Re}\{V\tilde{I}\}$$

$$= (R + NX_m)\tilde{I}^2$$

$$= P_{\text{ain}} + P_{\text{mech}}$$

$$P_{mech} = N X_m \tilde{I}^2 = T \omega_r$$

$$T \omega_r = \frac{\omega_r}{\omega_s} \omega_s M \tilde{I}^2$$

$$T = M \tilde{I}^2$$

Since  $T$  is the same as for d.c case then

$$I = \sqrt{\frac{T}{M}} = \underline{0.6A}$$

[Same as d.c case since in both cases  $T = M I^2$  &  $M$  is same for both a.c + d.c]

From earlier

$$V = \tilde{I} (R + N X_m + j \omega_s L)$$

$$\left| \frac{V}{\tilde{I}} \right| = \left( (R + N X_m)^2 + (\omega_s L)^2 \right)^{1/2}$$

$$(R + N X_m)^2 = \frac{V^2}{\tilde{I}^2} - (\omega_s L)^2$$

$$N = \frac{1}{X_m} \left( \frac{V^2}{\tilde{I}^2} - (\omega_s L)^2 \right)^{1/2} - \frac{R}{X_m} \leftarrow N_B$$

$$= \frac{1}{\omega_s M} \left( \frac{V^2}{\tilde{I}^2} - (\omega_s L)^2 \right)^{1/2} - \frac{R}{X_m}$$

$\downarrow$   
 $N_B$

$$= \frac{N_B}{2\pi f M} \left( \frac{V^2}{\tilde{I}^2} - (2\pi f L)^2 \right)^{1/2} - \frac{R}{2\pi f M}$$

$$= 0.460$$

$$\frac{\omega_r}{\omega_s} = 0.460$$

$$\omega_r = 144.47 \text{ rad s}^{-1}$$

$$= \underline{1380} \text{ rpm.}$$

$$\text{P.F.} = \frac{R + N X_m}{\sqrt{(R + N X_m)^2 + (\omega_s L)^2}}$$

$\omega_s M \equiv \omega_s L$

$$\frac{274.89}{\sqrt{274.89^2 + 188.5^2}}$$

$$= 0.825 \text{ lag (since } j \text{ term is rise)}$$

P.F. is a function of speed, since  $N$  is a function of speed.

Starting torque is the torque produced when  $\omega_r = 0$ .

For d.c. case.

$$I = \frac{V}{R} = 6.57 \text{ A}$$

$$T = M I^2 = 71.68 \text{ Nm}$$

For a.c case,

$$|I| = \frac{|V|}{|Z|}$$

$\omega = 0$

$$= \frac{200}{\sqrt{R^2 + (\omega L)^2}}$$

$$= \frac{200}{\sqrt{R^2 + (2\pi f L)^2}}$$

$$= 1.04 \text{ A}$$

$$\therefore T = MI^2 = 1.8 \text{ Nm}$$

Starting torque ratio

$$\frac{\text{a.c starting torque}}{\text{d.c starting torque}} = \frac{1.8}{71.68} = \frac{1}{39.8}$$

$$\begin{aligned}
 2. \quad R &= 50 \Omega \\
 L &= 0.7 \text{ H} \\
 240 \text{ V} \\
 50 \text{ Hz.}
 \end{aligned}$$

For both a.c + d.c operation of a universal motor:

$$T = M_{af} I^2$$

$\therefore$  Since in both cases in question, the load torque remains constant, the as the mutual inductance is the same then the current is the same

$$\therefore \underline{I = 0.6 \text{ A}}$$

For d.c + a.c operation

$$\begin{vmatrix} V_a \\ V_f \end{vmatrix} = \begin{vmatrix} R_a + L_a p & \omega_r M_{af} \\ 0 & R_f + L_f p \end{vmatrix} \begin{vmatrix} I_a \\ I_f \end{vmatrix}$$

for d.c + a.c operation constraining equations are:

$$V = V_a + V_f \quad I = I_a = I_f$$

For d.c  $p = 0$

$$V = [R_a + R_f + \omega_r M_{af}] I \quad \therefore \omega_r = \frac{V}{I} \cdot \frac{(R_a + R_f)}{M_{af}}$$

Have got  $V, I, R$  &  $L$   $\therefore$  need  $M_{qt}$   
get this from a.c conditions  $\downarrow$

on a.c  $p = j\omega_s$

$$V = [R_q + R_f + \omega_r M_{qt} + j\omega_s(L_q + L_f)] I$$

$$\therefore \frac{V}{I} = R_q + R_f + \omega_r M_{qt} + j\omega_s(L_q + L_f)$$

$$\therefore \left| \frac{V}{I} \right| = \left( (R_q + R_f + \omega_r M_{qt})^2 + (\omega_s(L_q + L_f))^2 \right)^{\frac{1}{2}}$$

$$\text{But } R_q + R_f = R \quad L_q + L_f = L$$

$$\therefore \frac{V^2}{I^2} = (R + \omega_r M_{qt})^2 + (\omega_s L)^2$$

$$\therefore \frac{V^2}{I^2} - (\omega_s L)^2 = (R + \omega_r M_{qt})^2$$

$$\therefore R + \omega_r M_{qt} = \left( \frac{V^2}{I^2} - (\omega_s L)^2 \right)^{\frac{1}{2}}$$

$$\therefore M_{qt} = \frac{1}{\omega_r} \left( \frac{V^2}{I^2} - (\omega_s L)^2 \right)^{\frac{1}{2}} - \frac{R}{\omega_r}$$

Substitute in values given

$$M_{qt} = \frac{284 \cdot 12}{1500 \times \frac{2\pi}{60}} - 1.81 \text{ H.}$$

For d.c case of operation

$$\omega_r = \frac{280}{0.6} - 50 = 184.16 \text{ rad s}^{-1}$$

$$= \underline{\underline{1760 \text{ r.p.m}}}$$

Case not mix up a.c + d.c data  
Such as applied volts.

Similar to question ①

Find M from initial operation data &  
use in other cases.




3. Torque =  $p M I^2$  where  $p$  = pole pairs.

At 40 Nm gross torque

$$I^2 = \frac{T}{p M}$$
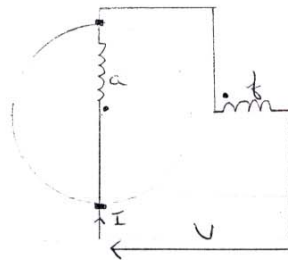
$$I = \sqrt{\frac{T}{p M}} = \sqrt{\frac{40}{2 \times 0.009}} = 47.14 \text{ A.}$$



$$\begin{bmatrix} V_a \\ V_f \end{bmatrix} = \begin{bmatrix} R_a + L_a p & p \omega_r M_{fa} \\ 0 & R_f + L_f p \end{bmatrix} \begin{bmatrix} I_a \\ I_f \end{bmatrix}$$

N.B.  $\nearrow$  since flux axis leads voltage axis.

But  $V = V_a + V_f$   
 $I = I_a = I_f$

$$V = [(R_a + R_f + p \omega_r M_{fa}) + p (L_a + L_f)] I$$

But in steady state a.c  $p = j \omega_s$

$$V = [R_a + R_f + j \omega_s M_{fa} + j \omega_s (L_a + L_f)] I$$

$$\frac{|V|^2}{|I|^2} = (R_a + R_f + P_p \omega_r M_{fa})^2 + (L_a + L_f)^2 \omega_s^2$$

$$\omega_r = \frac{\sqrt{\frac{V^2}{I^2} - \omega_s^2 (L_a + L_f)^2} - R_a - R_f}{P_p M_{fa}}$$

$$= \frac{205.70 \text{ rads}^{-1}}{2}$$

$$= 102.85 \text{ rads}^{-1}$$

$$\omega_r = \frac{102.85}{2\pi} \times 60 = 983 \text{ rpm.}$$

[Note importance of pole pairs]

$$\text{From } V = [(R_a + R_f + P_p \omega_r M_{fa}) + (L_a + L_f)^2 j \omega_s^2] I$$

$$\text{Then } P = \text{Re} \{VI\}$$

$$= (R_a + R_f + P_p \omega_r M_{fa}) I^2$$

$$= P_{\text{dis}} + P_{\text{elec}_{ap}}$$

$$P_{\text{elec}_{ap}} = P_p \omega_r M_{fa} I^2$$

$$= 4.114 \text{ kW}$$

$$= \frac{4.114}{743} \text{ h.p.} = 5.53 \text{ hp.}$$

Take care to distinguish between  $\omega_s$  &  $\omega_r$ .

$$\text{Power factor} = \cos \left[ \tan^{-1} \left( \frac{\omega_s (L_a + L_f)}{R_a + R_f + P_p \omega_r M_{fa}} \right) \right]$$

$$= 0.672 \text{ lagging}$$

Important to include lagging!

Note importance of pole pair.  
Must be included in matrix with rotational emfs.

Alternative way to do problem would have been to work through theory

$$\text{to get } P_{elec} = P_p \omega_r M_{fa} I^2$$

$$T = \frac{P_{elec}}{\omega_r} = P_p M_{fa} I^2$$

i.e. prove  $T = P_p M_{fa} I^2$  and not assume at start