

EEE117 Problem Sheet

Capacitors and Inductors

- Q1** (i) The capacitor in figure 1 is initially contains zero charge. Sketch a graph to show how the capacitor voltage varies as a function of time if the current generator has the waveform shown.
- (ii) How much charge is in the capacitor at $t = 8\text{ms}$? ($1\mu\text{C}$)

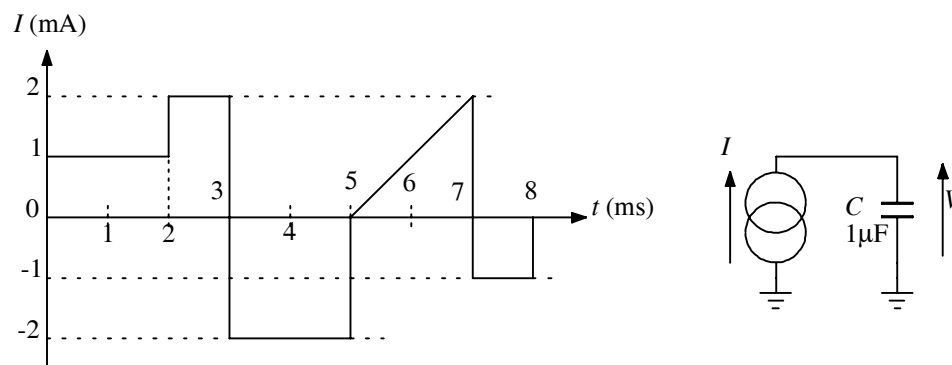


Figure 1

- Q2** Draw a graph to show how capacitor current I in figure 2 varies with time. Work out the area and polarity of any impulsive currents. ($-3\mu\text{C}$ @ 2ms , $+2\mu\text{C}$ @ 6ms , $-2\mu\text{C}$ @ 7ms)

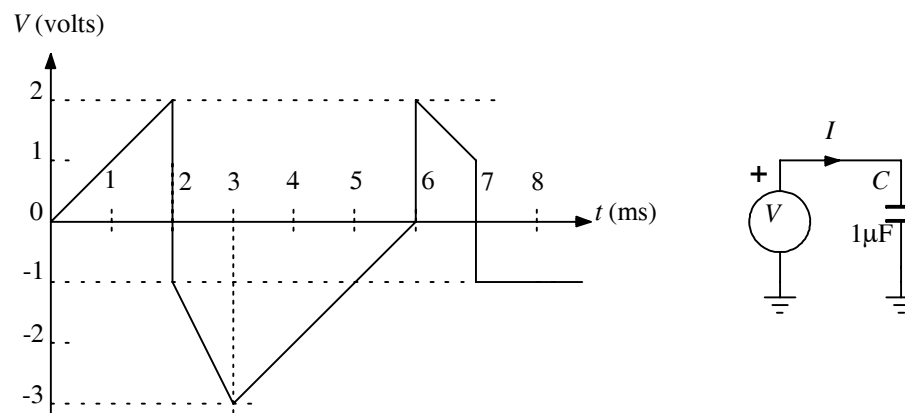


Figure 2



- Q4** (i) Find I_S in the circuit of figure 4. [1.25 A]
(ii) Find the energy stored in all the L s and C s in the circuit. [330 pF, 0 J; 0.1 μ F, 9.45 μ J; 1 μ F, 12.5 μ J; 10 μ F, 281 μ J; 10 mH, 7.82 mJ; 0.1 H, 0 J; 0.15 H, 117 mJ]



- (iv) What is the maximum voltage that occurs across L and C after switch off for $C = 1$ nF, $C = 10$ nF and $C = 100$ nF? [2 kV, 632 V, 200 V]

Note: Capacitors are often used in this way to limit the peak voltage across an inductor that occurs when current is suddenly switched off. Furthermore the idea of charging an inductor with energy and then dumping that energy into a capacitor is the basis of many modern power supplies.