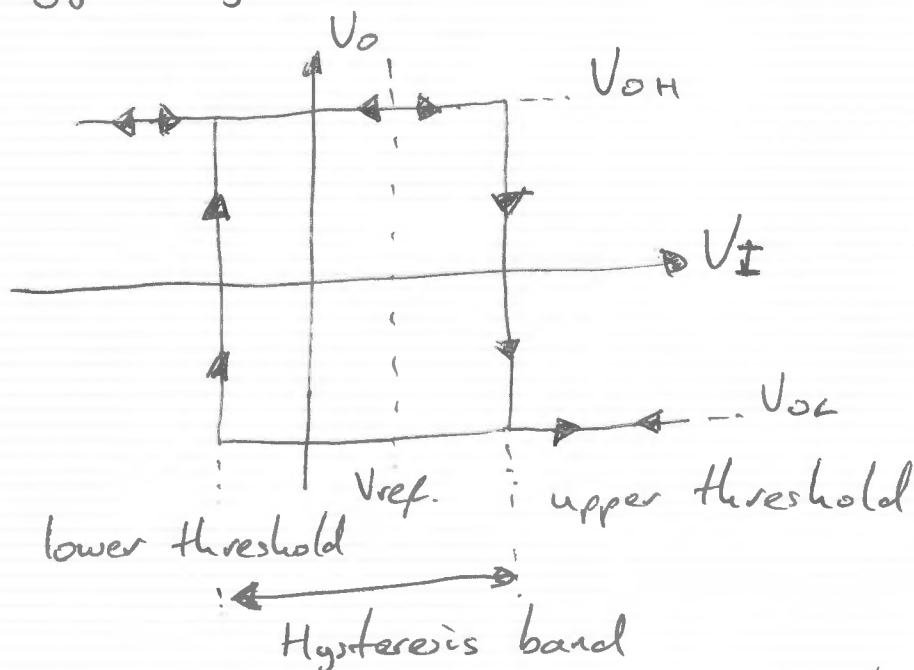


Q1

(1)

a) Hysteresis improves a comparator circuit's immunity to noise by placing a deadband around the switching boundary.

b) Schmitt trigger hysteresis characteristic



Inverting Schmitt trigger  $V_I > V^+_H$   $V_O$  goes low ( $V_{OL}$ )  
 $V_I < V^+_L$   $V_O$  goes high ( $V_{OH}$ )

Need to find value of  $V_I$  that causes  $V_O$  to change state

$$V^+ = V_{ref} - (V_{ref} - V_O) \frac{R_1}{R_1 + R_2}$$


If  $V_O = V_{OH}$  then  $V^+_H = V_{ref} - (V_{ref} - V_{OH}) \frac{R_1}{R_1 + R_2}$  - upper threshold

If  $V_O = V_{OL}$  then  $V^+_L = V_{ref} - (V_{ref} - V_{OL}) \frac{R_1}{R_1 + R_2}$  - lower threshold

$$\text{Hysteresis} = V^+_H - V^+_L = (V_{OH} - V_{OL}) \frac{R_1}{R_1 + R_2}$$

Q1 c).

(2)

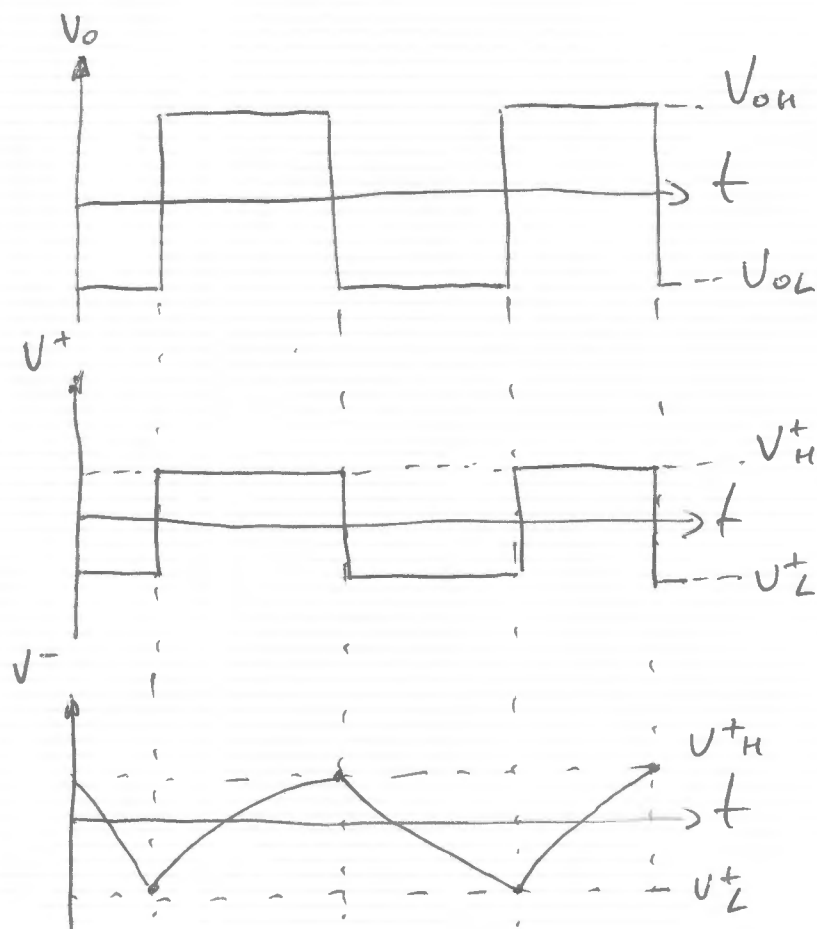

d) When  $V_o = V_{oh}$ ,  $V_c(t) = V^-(t) = (V_{oh} - V_L^+)(1 - e^{-\frac{t}{\tau}}) + V_L^+$ .

Since  $V_{oh} = -V_{ol}$ ,  $V_H^+ = -V_L^+ = \frac{R_1}{R_1 + R_2} V_{oh}$

One complete half-period is the time taken for  $V^-$  to travel from  $V_L^+$  to  $V_H^+$ . So,

$$\frac{R_1}{R_1 + R_2} V_{oh} = (V_{oh} + \frac{R_1}{R_1 + R_2} V_{oh})(1 - e^{-\frac{t}{\tau}}) - V_{oh} \frac{R_1}{R_1 + R_2}$$

Simplifying and solving for  $t$  gives

$$t = \tau \ln \left( \frac{2R_1 + R_2}{R_2} \right)$$



so the whole oscillation period is.

$$T_{osc} = 2t = 2\tau \ln \left( \frac{2R_1 + R_2}{R_2} \right) = 2RC \ln \left( \frac{2R_1 + R_2}{R_2} \right)$$

e).  $RC = \frac{T_{osc}}{2 \ln \left( \frac{2R_1 + R_2}{R_2} \right)} = 1.28 \times 10^{-4} \text{ s.}$

Q 2

a)

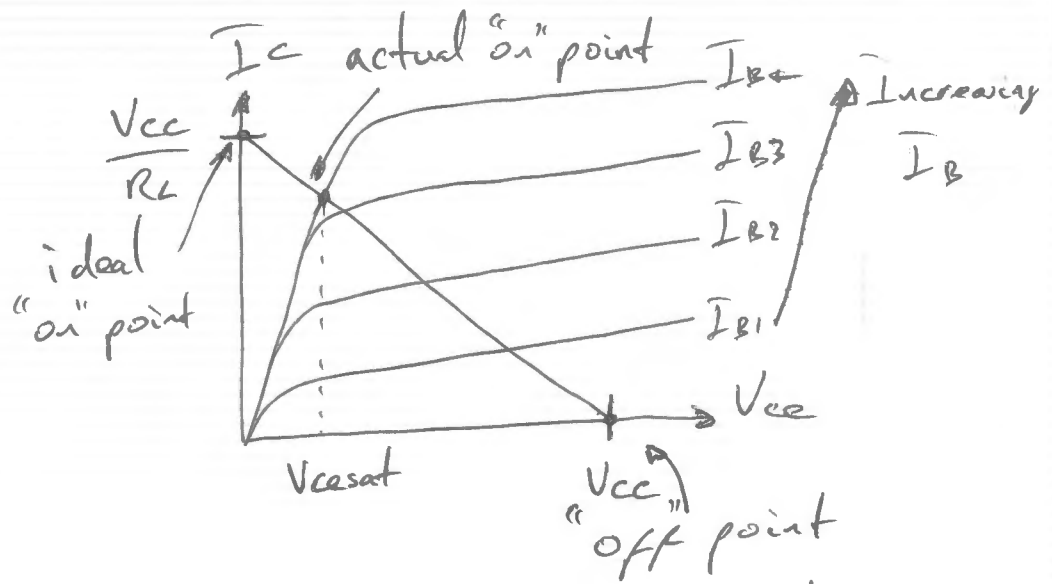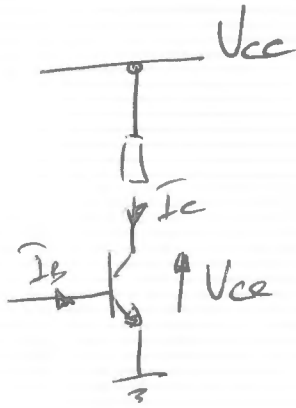

b) Overdriving is necessary to compensate for the difficulty associated with specifying a suitable value for  $h_{FE}$  which varies with temperature, collector current and device-to-device.

Advantage - improves turn-on time

Disadvantage - degrades turn-off time due to reverse recovery of transistor.

c) Assuming  $V_{cesat} \approx 0V$ ,  $I_C \approx \frac{V_{CC}}{R_L} = \frac{300}{15} = 20A$ .

$$I_{BS} = \frac{I_C}{h_{FE}} = \frac{20}{50} = 0.4A$$

$$I_B = M \cdot I_{BS} = 6 \times 0.4 = 2.4A$$

$$R_B = \frac{V_{IOn} - V_{beOn}}{I_B} = \frac{9 - 1}{2.4} = 3.33\Omega$$

d) If  $I_B = 2.4A$  then  $Q_s = I_B \times t_s = 2.4 \times 450 \times 10^{-9} = 1.08 \times 10^{-6}C$


$$Q_s = C_b \Delta V \quad \Delta V = (V_{IOn} - V_{beOn}) - (V_{Ioff} - V_{beoff}) = 8 - (-3) = 11.$$

$$C_b = \frac{Q_s}{\Delta V} = \frac{1.08 \times 10^{-6}}{11} = 98nF \quad (100nF)$$

Q3

e)

Schottky  
diode

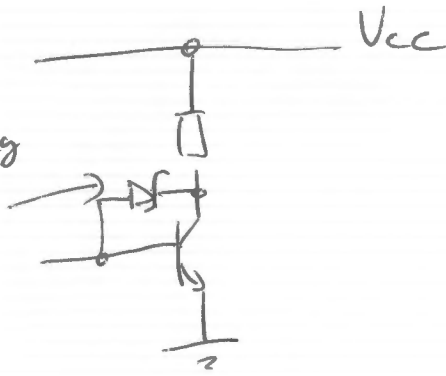

Q3

a) Barkhausen criterion.

Self-sustained oscillations occur when the loop gain = 1 and phase difference  $\angle = 0^\circ$

There are two ways to achieve this.

$$\begin{aligned} \text{loop gain} &= 1 \\ \text{phase} &= 0^\circ \end{aligned}$$

$$\begin{aligned} \text{loop gain} &= -1 \\ \text{phase} &= 180^\circ \end{aligned}$$

b) Transfer function.

$$Z_1 = R + \frac{1}{sC} = \frac{sCR + 1}{sC}$$

$$Z_2 = \frac{1}{\frac{1}{R} + sC} = \frac{R}{1 + sCR}$$

$$\frac{V_2}{V_1} = \frac{Z_2}{Z_1 + Z_2} = \frac{sCR}{s^2 C^2 R^2 + 3sCR + 1}$$

$$c) \frac{V_2}{V_1} = \frac{j\omega CR}{1 - \omega^2 C^2 R^2 + 3j\omega CR}$$

purely real when  $1 - \omega^2 C^2 R^2 = 0$ .

$$\omega_{osc} = \frac{1}{CR} \quad f_{osc} = \frac{1}{2\pi CR}$$


$$\text{at } f_{osc} \quad \left| \frac{V_2}{V_1} \right| = \frac{1}{3}$$

d)

$$\frac{V_0}{V_2} = 1 + \frac{R_1}{R_2} = 3$$

$$\therefore \frac{R_1}{R_2} = 2$$

$$R_1 = 1k\Omega, R_2 = 2k\Omega$$

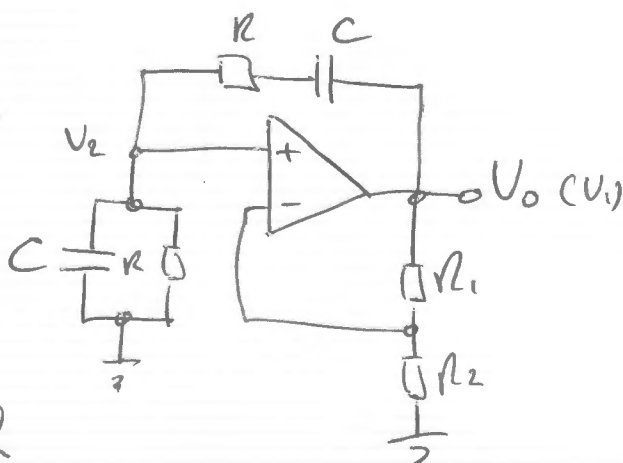

$$f_{osc} = \frac{1}{2\pi CR}$$

$$R = \frac{1}{2\pi f_{osc} C}$$

$$C = 10nF$$


$$R = 15,915k\Omega$$

Q327. Non-linear gain is required to ensure sustained oscillation are achieved as the circuit component values vary due to temperature and ageing.

As  $V_o$  increase the loop gain needs to decrease to maintain stability.


$$\frac{V_o}{V_i} = 1 + \frac{R_1}{R_2}$$

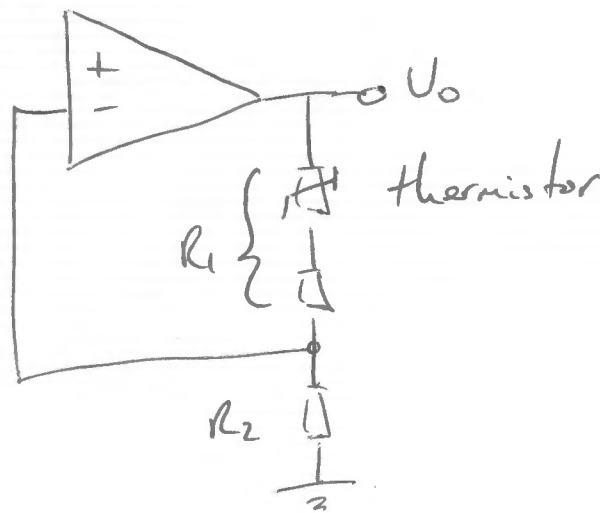the above expression will decrease if  $R_1$  decreases so  $R_1$  would need to be the thermistor




4.

a)  $T_1$  on,  $D$  off

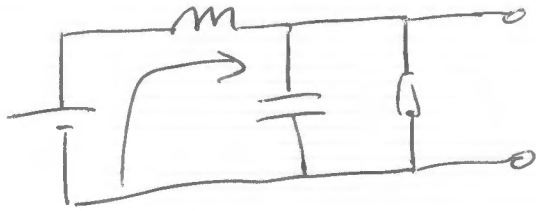


$T_1$  off,  $D$  on

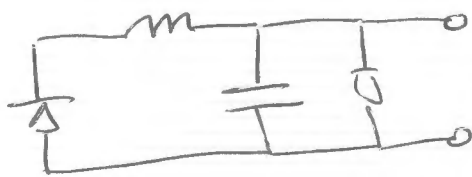

when  $T_1$  is on energy is stored in the inductor  
when  $T_1$  is off energy is transferred from the inductor to the capacitor.

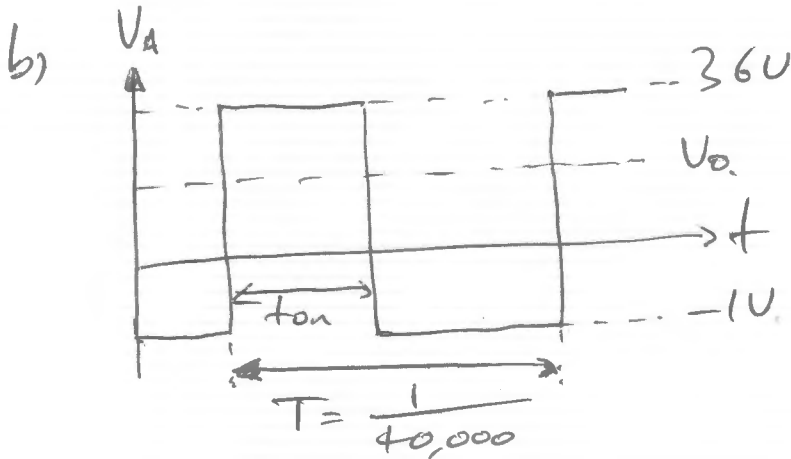The inductor is the main energy storage element and the capacitor controls the ripple voltage



$$V_o = \frac{1}{T} \int_0^T V_A(t) dt = \frac{1}{T} [V_{dc} t_{on} - (T - t_{on})]$$

$$t_{on} = \frac{T(V_o + 1)}{V_{dc} + 1} = \frac{6}{37} T = 4.05 \times 10^{-6} \text{ s}$$

c) Resistor  $R_L$  is used to control the minimum value of inductor current to ensure current continuously flows in the inductor

$$I_{o \min} = \frac{V_o}{R_L} = \frac{5}{330} = 0.015 \text{ A}$$

Need to ensure  $I_{\text{omin}} - \frac{\Delta I}{2} > 0$

$$V_{dc} - V_o = L \frac{\Delta I}{t_{\text{on}}} \quad \therefore \frac{\Delta I}{2} = (V_{dc} - V_o) \frac{t_{\text{on}}}{2L}$$

$$L > \frac{(V_{dc} - V_o) t_{\text{on}}}{2 I_{\text{omin}}}$$

$$> 4.18 \text{ mH.}$$

2) Value of  $C$  to limit  $V_r < 50 \text{ mV}$ .



$$Q = \int (I_L - I_o) dt. = \frac{1}{2} \frac{T}{2} \frac{\Delta I}{2} = \frac{T \Delta I}{8}$$

$$Q = C \Delta V.$$

ensure that  $\Delta V < V_r$ .

$$\Delta V = \frac{Q}{C} \quad \text{so} \quad \frac{Q}{C} < V_r.$$

$$\text{or } C > \frac{Q}{V_r} > \frac{T \Delta I}{8 V_r}.$$

$$\text{Assume } I_{\text{omin}} = \frac{\Delta I}{2}.$$

$$C > \frac{T I_{\text{omin}}}{4 V_r}$$

$$> 1.87 \mu\text{F}.$$



e) Synchronous buck converter deadtime

Dead time is required to be inserted into the MOSFET control signals to ensure that both MOSFETs do not conduct simultaneously.

Should both MOSFETs conduct at the same time large pulsating currents would flow and in all likelihood they would become damaged.