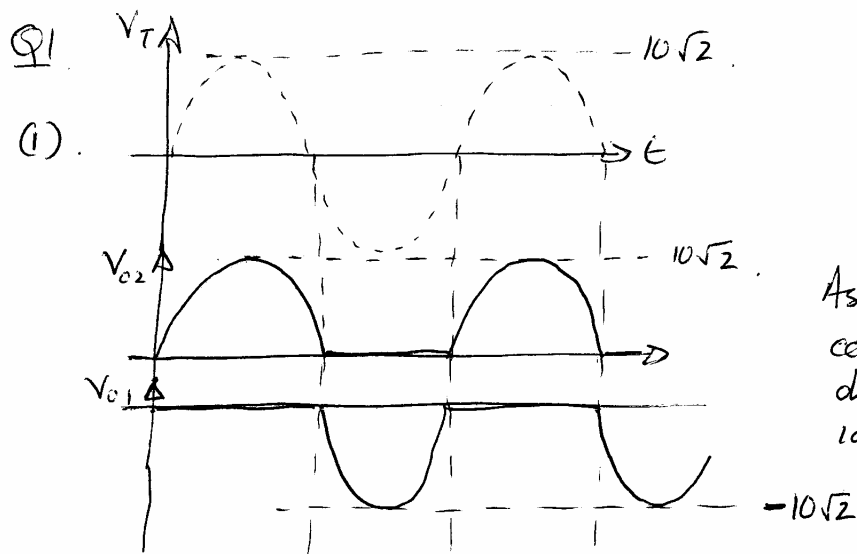


(1)



Assumption is
components (inc
diodes) are
ideal.

(ii). $V_{T AVE} = 0$.

$$V_{o1 AVE} = -\frac{V_p}{\pi} = \frac{-10\sqrt{2}}{\pi} = \underline{\underline{-4.5V}}$$

$$V_{o2 AVE} = \frac{V_p}{\pi} = \frac{10\sqrt{2}}{\pi} = \underline{\underline{4.5V}}$$


(iii) A ripple no larger than 1V pk-pk with $I_L = 100\text{mA}$ is needed. Assume instantaneous charging...

$$I = C \frac{dv}{dt} = C \frac{V_R}{1/50\text{Hz}}$$

$$= 100\text{mA}$$


$$\therefore C = \frac{10^{-1}}{50 \times 1}$$
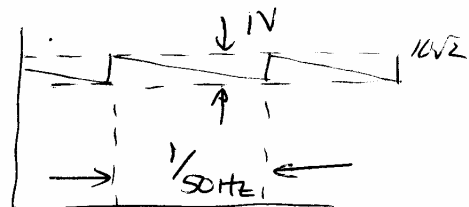
$$= \underline{\underline{2000\mu\text{F}}}$$




(2)

(iv)

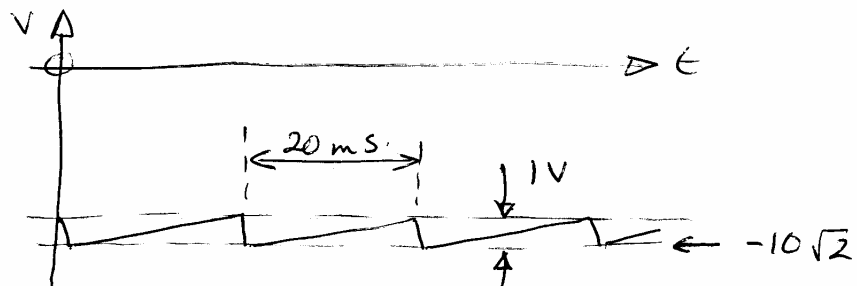

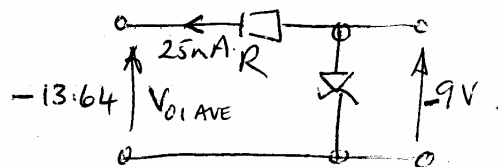(v) current through zener diode ckt is
 $\frac{100 \text{ mA}}{4} = 25 \text{ mA}.$

$$V_{O1 \text{ AVE}} = 10\sqrt{2} - 0.5 \\ = 13.64 \text{ V}.$$




$$\therefore R = \frac{-9 - (-13.64)}{25 \text{ mA}} \\ = \underline{\underline{185 \Omega}}$$

For the ripple, R forms a potential divider with r_z

$$V_{\text{ripple}} = V_{\text{in ripple}} \cdot \frac{r_z}{R + r_z} \\ = 1 \times \frac{6}{191} = \underline{\underline{31.4 \text{ mV}_{\text{pk-pk}}}}$$


(3)

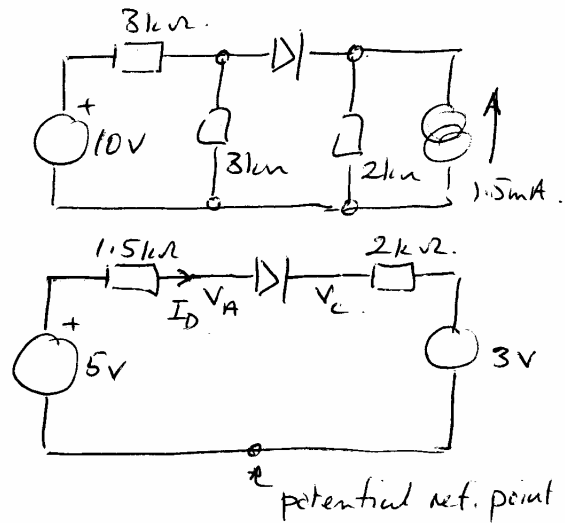Q2(a)(i) The easiest way to approach this Q is to form Thevenin equivalents of both sources If one assumes no current flows, $V_A = 5V$ and $V_C = 3V$ so $V_A - V_C = 2V$ so current must be flowing.



$$I_D = \frac{5V - 3V - 0.7V}{1.5k\Omega + 2k\Omega} = \frac{1.3V}{3.5k\Omega} = \underline{\underline{371\mu A}}$$

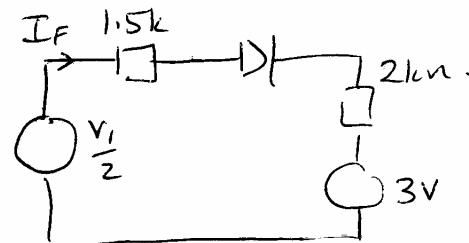(ii) The critical value of V_i is $3.7 \times 2 = 7.4V$. (This is when diode is on the point of conduction.)




For voltages above this


value, $\frac{\Delta V_i / 2}{\Delta I_F} = (1.5 + 2)k\Omega$; for voltages below, $I_F = 0$

(4)


(iii) cont.

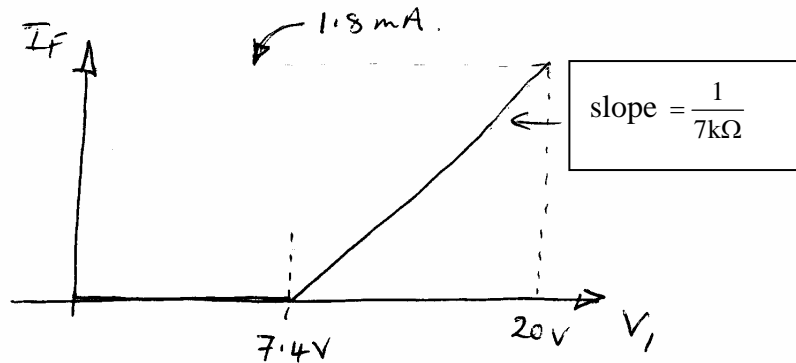

(b)(i)

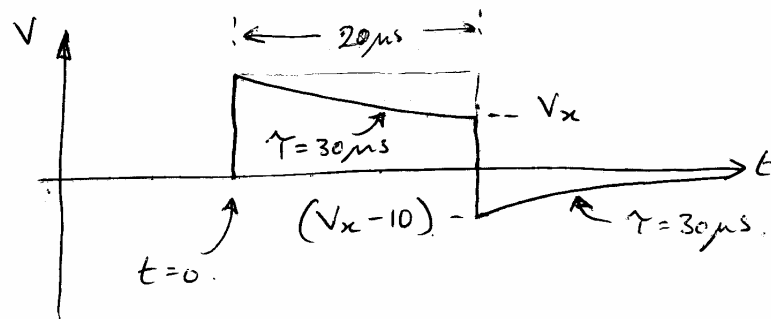

(ii)

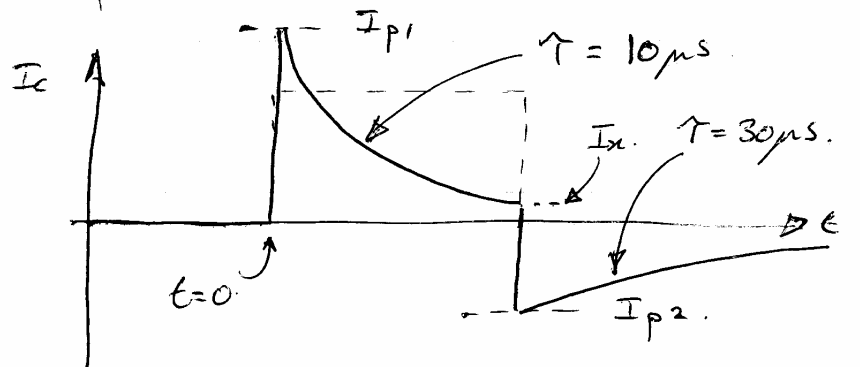

$$I_{p1} = \frac{10V}{R_1 \parallel R_2} = \frac{10V}{1k\Omega} = \underline{10mA}$$

$$I_x = 10mA e^{-20\mu s / 10\mu s} = 1.35mA$$

$$\text{and } V_x = 1.35V$$

$$\therefore V_x - 10 = -8.65$$

$$\text{So } I_{p2} = \frac{-8.65V}{3k\Omega} = \underline{-2.88mA}$$

(5)

Q3. (a)(i). D provides a path for the inductor current when the switch switches off and thereby limits the maximum voltage that appears across the switch at switch-off.

(ii) If T_1 has been "on" for a long time, all transient effects due to L will have settled down so

$$I_{D(on)} = \frac{42}{R_L + r_{D(on)}} = \frac{42}{84 \Omega} = \underline{\underline{0.5 A}}.$$

(neglecting $r_{D(on)}$ is permissible providing its neglect is stated as an approximation).

$$\begin{aligned} \text{(iii) Power loss in } T_1 &= I_{D(on)}^2 r_{D(on)} \\ &= 0.5^2 \times 4 \\ &= \underline{\underline{1 W}}. \end{aligned}$$

(iv) At turn-off, the 0.5A through $L + R_L$ is diverted through $D + R_S$. At the instant of turn off $I_F = 0.5A$ so 20V is dropped across R_S , and 0.7 across D , giving a max V_{DS} of

$$42 + 20 + 0.7 = \underline{\underline{62.7 V}}$$

(b)(i). For figure 3b ...

$$18 = (I_C + I_1)R_L + I_1(R_F + R_B)$$

$$\text{and } 0.7 = I_1 R_B.$$

where I_1 is the current through $R_F + R_B$.

(6)

eliminating $I_1 \dots$

$$18 = I_C R_L + \frac{0.7}{R_B} [R_L + R_F + R_B]$$

$$\text{or } I_C = \frac{1}{R_L} \left[18 - \frac{0.7}{R_B} (R_L + R_F + R_B) \right]$$

$$= \underline{\underline{1.02 \text{ mA}}}$$

$$\text{and } I_1 = \frac{0.7}{R_B} = 70 \mu\text{A}$$

$$\therefore V_C = 18 - (I_1 + I_C) R_L = 18 - 1.09 \text{ mA} \times 8.2 \text{ k}\Omega$$


$$= 18 - 8.9 \text{ V}$$

$$= \underline{\underline{9.1 \text{ V}}}$$


$$g_m = \frac{e I_C}{k T} \quad (\text{from given useful relationships})$$

$$= \frac{1.02 \times 10^{-3}}{0.026} = \underline{\underline{39 \text{ mA/V}}} \quad \text{or} \quad \underline{\underline{0.039 \text{ A V}^{-1}}}$$

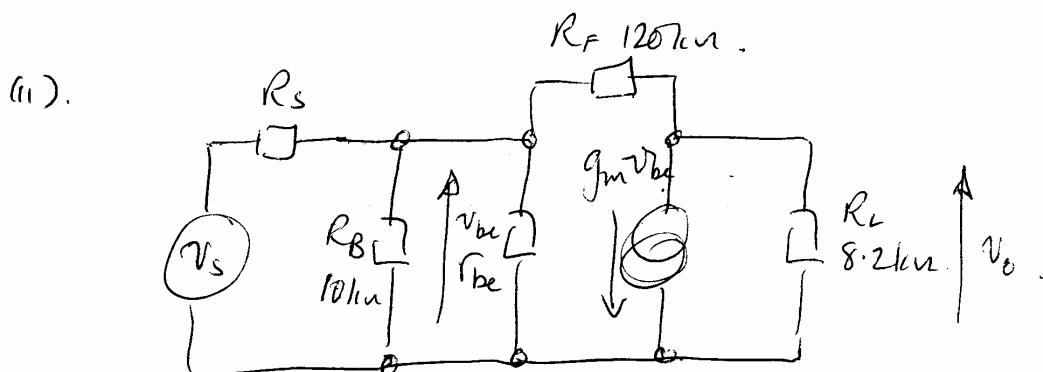
$$r_{be} = \beta / g_m \quad (\text{given}) = \frac{400}{0.039} = \underline{\underline{10.2 \text{ k}\Omega}}$$



(7)

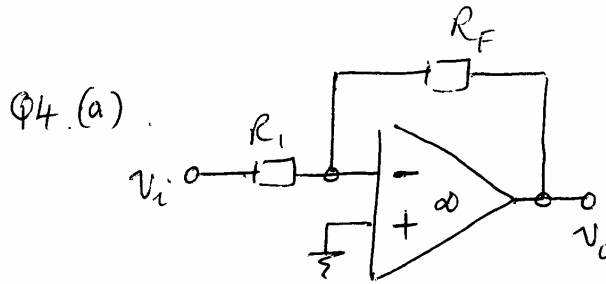


inverting amplifier
gain = $-R_F/R_1$

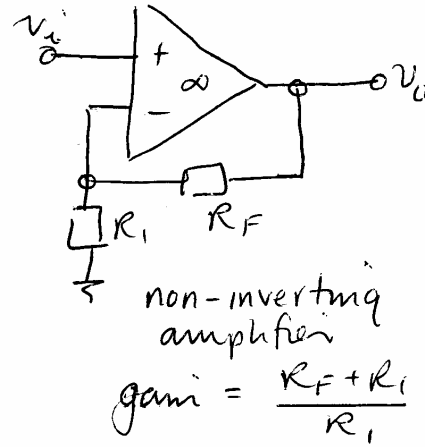

non-inverting amplifier
gain = $\frac{R_F + R_1}{R_1}$

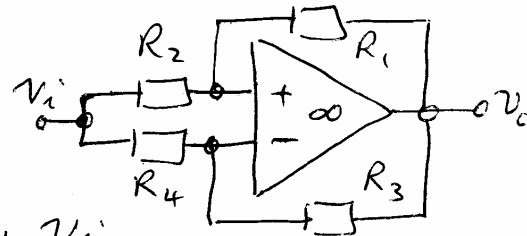(b) (i) since $A_v \Rightarrow \infty$
 $v^+ = v^-$



$$\therefore v^+ = (v_o - v_i) \frac{R_2}{R_2 + R_1} + v_i$$


$$v^- = (v_o - v_i) \frac{R_4}{R_3 + R_4} + v_i$$

$$\text{so } (v_o - v_i) \frac{R_2}{R_1 + R_2} + v_i = (v_o - v_i) \frac{R_4}{R_3 + R_4} + v_i$$

$$v_o \left[\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right] = v_i \left[\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right]$$


$$\text{or } \underline{\underline{\frac{v_o}{v_i} = 1}}$$

(ii) Simpler circuit is

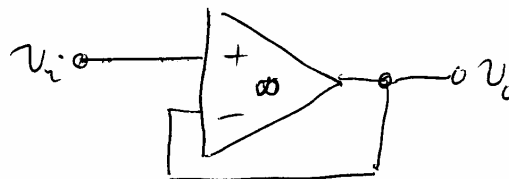

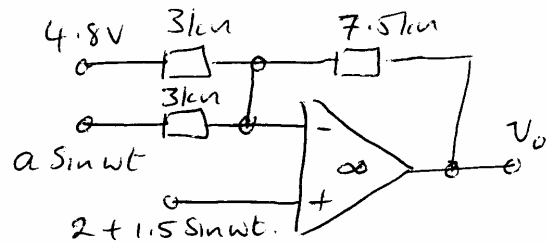(8)

(c). Since we are only interested in the ac component of the output, the d.c terms can be considered as grounds.



$$v_o \Big|_{\text{due to } a \sin \omega t} = a \sin \omega t \times \left(-\frac{7.5}{3} \right)$$

$$\begin{aligned} v_o \Big|_{\text{due to } 1.5 \sin \omega t} &= 1.5 \sin \omega t \times \frac{7.5k\Omega + 3k\Omega / 3k}{3k\Omega / 3k} \\ &= 1.5 \sin \omega t \times \frac{9k\Omega}{1.5k\Omega} \end{aligned}$$

and the sum of these two components should be zero ...

$$-\frac{5}{2} a \sin \omega t + 1.5 \times 6 \times \sin \omega t = 0.$$

$$a = \frac{9 \times 2}{5} = \underline{\underline{3.6}}$$