

# EEE225: Analogue and Digital Electronics

## Lecture IX

James E. Green

Department of Electronic Engineering  
University of Sheffield  
`j.e.green@sheffield.ac.uk`

# This Lecture

## 1 Opamps with Frequency Dependent Feedback



- Pole-Zero Circuits
- Passive and Active First Order Circuits: Standard Forms
- Passive and Active First Order Circuits: Low Pass with 'k'
- Low Pass with 'k': Time and Frequency Domain Response
- Passive and Active First Order Circuits: High Pass with 'k'
- High Pass with 'k': Time and Frequency Domain Response
- Pole-Zero Response
- Passive PZ example: Getting the Standard Form...
- Active PZ example: Getting the Standard Form...

## 2 Review

## 3 Bear
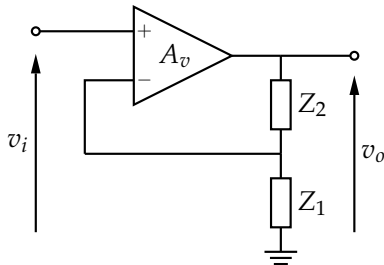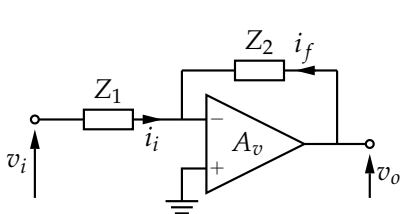
## Pole-Zero Circuits

Pole-zero circuits aim to adjust the magnitude and phase response of an analogue system. They are constructed from the standard amplifier blocks but with  $Z_1$  or  $Z_2$  having some frequency dependent components - almost always capacitors. Inductors are too imperfect<sup>1</sup>




---

<sup>1</sup>If an inductance is required, it may be manufactured with a capacitance and an opamp or two forming a gyrator, a kind of impedance transformer. See <http://sound.westhost.com/articles/gyrator-filters.htm> for examples.

## Standard Forms

First order transfer functions fall into one of three standard forms,  
low pass,

$$\frac{v_o}{v_i} = k \frac{1}{1 + s\tau} = k \frac{1}{1 + j \frac{\omega}{\omega_0}} = k \frac{1}{1 + j \frac{f}{f_0}} \quad (1)$$


high pass,

$$\frac{v_o}{v_i} = k \frac{s\tau}{1 + s\tau} = k \frac{j \frac{\omega}{\omega_0}}{1 + j \frac{\omega}{\omega_0}} = k \frac{j \frac{f}{f_0}}{1 + j \frac{f}{f_0}} \quad (2)$$

and pole zero,


$$\frac{v_o}{v_i} = k \frac{1 + s\tau_1}{1 + s\tau_0} = k \frac{1 + j \frac{\omega}{\omega_1}}{1 + j \frac{\omega}{\omega_0}} = k \frac{1 + j \frac{f}{f_1}}{1 + j \frac{f}{f_0}} \quad (3)$$
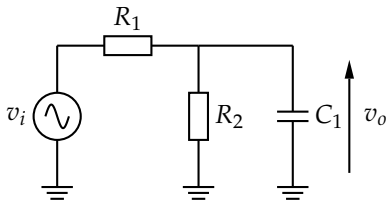
## Passive and Active First Order: Low Pass with 'k'



For the passive circuit:
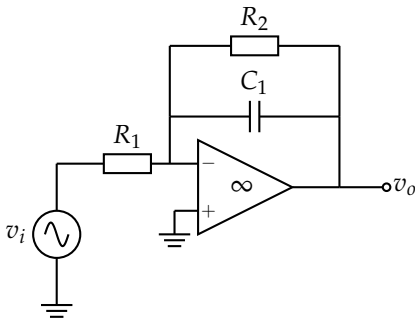
$$\frac{R_2}{R_1 + R_2} \cdot \frac{1}{s C_1 (R_1 // R_2) + 1} \quad (4)$$





For the active circuit:


$$-\frac{R_2}{R_1} \cdot \frac{1}{s C_1 R_2 + 1} \quad (5)$$

*They are not identical!* but they are similar in the shape of the frequency response.
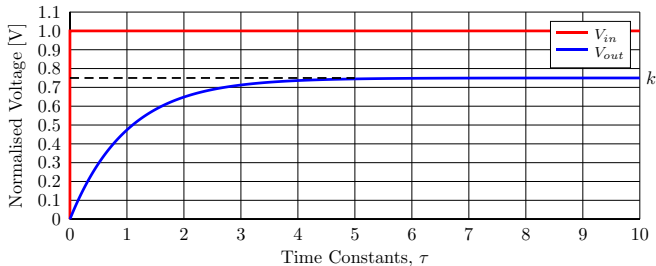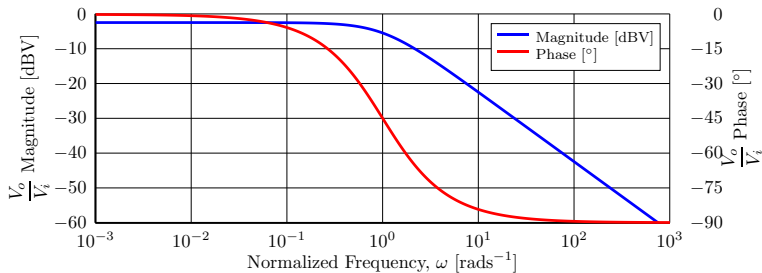
# Time and Frequency Domain Response (Passive Version)


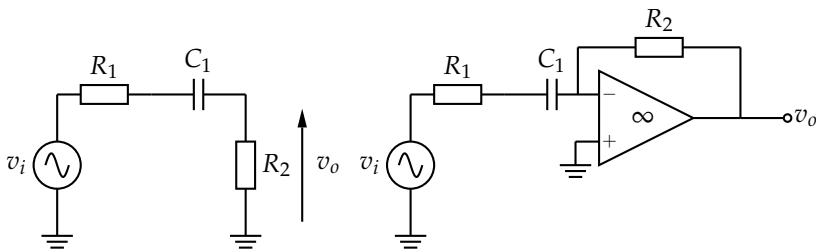
## Passive and Active First Order: High Pass with 'k'



For the passive circuit:



$$\frac{R_2}{R_1 + R_2} \cdot \frac{s C_1 (R_1 + R_2)}{s C_1 (R_1 + R_2) + 1} \quad (6)$$

For the active circuit:

$$-\frac{R_2}{R_1} \cdot \frac{s C_1 R_1}{s C_1 R_1 + 1} \quad (7)$$

*They are not identical!* but they are similar in the shape of the frequency response.

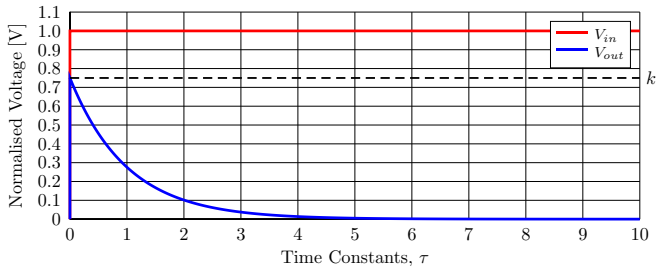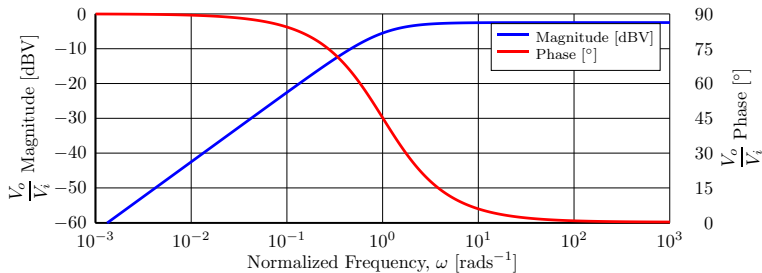
# Time and Frequency Domain Response (Passive Version)




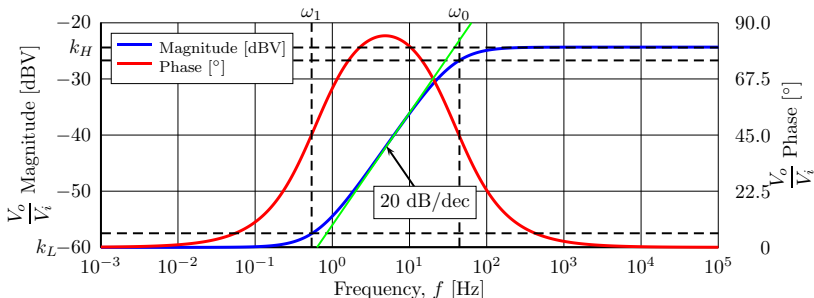
## Passive and Active First Order: Pole-Zero (or Zero-Pole)

- The PZ system is the linear sum of HP and LP
- There is one pole and one zero.
- The pole may appear at a lower or higher frequency than the zero. The circuit is called pole-zero regardless!
- The pole determines the time constant,  $\tau$
- Occasionally may be called lead or lag compensator in control systems discussion.



- There are two “gains” a low frequency (or DC,  $f \rightarrow 0$ ) gain and a high frequency ( $f \rightarrow \infty$ ) gain,  $k_L$  and  $k_H$  respectively.
- If zero frequency ( $\omega_1$ ) < pole frequency ( $\omega_0$ ) then  $k_L < k_H$  and phase “leads” (+ ve) between the pole and zero. This is the case in the last slide.
- If the zero frequency ( $\omega_1$ ) > pole frequency ( $\omega_0$ ) then  $k_L > k_H$  and phase “lags” (- ve) between the pole and zero.
- Magnitude slope tends to  $\pm 20$  dB/dec as the system is first order. Phase tends to  $+90$  or  $-90$  depending on PZ or ZP but often does not make it all the way.

Standard Forms:

frequency domain:


$$k \frac{1 + s \tau_1}{1 + s \tau_0} \quad (8)$$

Alternatively:

$$k \cdot \frac{1}{1 + s \tau_0} + k \cdot \frac{\tau_1}{\tau_0} \cdot \frac{s \tau_0}{1 + s \tau_0} \quad (9)$$


- The high frequency gain,  $k_H = k \cdot \frac{\tau_1}{\tau_0}$  and  $k = k_L$ .

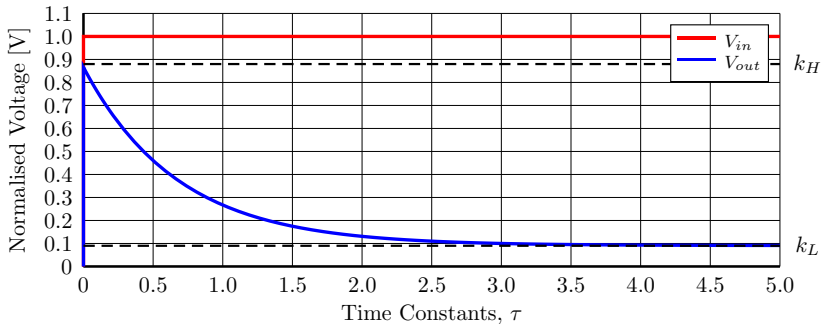The step response depends on which of the pole or zero are at the lower frequency but for zero frequency  $<$  pole frequency we have something that is broadly HP looking but  $v_{out}$  does not fall to zero, it tends towards  $k_L$ . For zero frequency  $>$  pole frequency we have something broadly LP but also having a finite  $k_H$ .


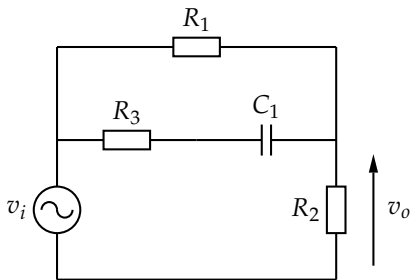
## Passive Pole-Zero Example

Find the transfer function of the following PZ circuit.



- Notice  $k$  is at the front and has no  $\omega$  dependence.
- The  $s^0$  (unity) coefficient is 1 in the numerator and denominator.
- The highest power of  $s$  is one.
- Always ask yourself, what is HF gain? what is LF gain? (good sanity check)...

$$k \cdot \frac{s \tau_1 + 1}{s \tau_0 + 1} = \frac{R_2}{R_1 + R_2} \cdot \frac{s C_1 (R_1 + R_3) + 1}{s C_1 \left( \frac{R_2 R_1 + R_2 R_3 + R_1 R_3}{R_1 + R_2} \right) + 1} \quad (10)$$

It's a potential divider with  $R_2$  developing the output voltage,

$$v_o = \frac{R_2 v_i}{R_2 + R_1 // \left(R_3 + \frac{1}{sC_1}\right)} \quad (11)$$

Expanding,

$$\frac{v_o}{v_i} = \frac{R_2}{R_2 + \frac{R_1 \left(R_3 + \frac{1}{sC_1}\right)}{R_1 + R_3 + \frac{1}{sC_1}}} \quad (12)$$

Need to head towards  $1 + s\tau$  on the bottom. Multiply top (numerator) and bottom (denominator) by  $R_1 + R_3 + \frac{1}{sC_1}$

$$\frac{R_2 \left(R_1 + R_3 + \frac{1}{sC_1}\right)}{R_2 \left(R_1 + R_3 + \frac{1}{sC_1}\right) + R_1 \left(R_3 + \frac{1}{sC_1}\right)} \quad (13)$$

Multiplying out the brackets (expanding),

$$\frac{R_2 R_1 + R_3 R_2 + \frac{R_2}{s C_1}}{R_2 R_1 + R_3 R_2 + \frac{R_2}{s C_1} + R_1 R_3 + \frac{R_1}{s C_1}} \quad (14)$$

Multiplying top and bottom by  $s C_1$ ,

$$\frac{(R_2 R_1 + R_3 R_2) s C_1 + R_2}{s C_1 R_2 (R_1 + R_3) + R_2 + R_1 R_3 s C_1 + R_1} \quad (15)$$

The unity term (coefficient of  $s^0$ ) in the denominator is  $R_1 + R_2$ .  
So lets divide top and bottom by  $R_1 + R_2$  to get  $s\tau + 1$  on the bottom.


$$\frac{s C_1 \frac{R_2(R_1+R_3)}{R_1+R_2} + \frac{R_2}{R_1+R_2}}{s C_1 \frac{(R_2 R_1 + R_2 R_3 + R_1 R_3)}{R_1+R_2} + 1} \quad (16)$$

Having found the desired form of the denominator we know the pole has a time-constant,  $\tau_0 = C_1 \frac{(R_2 R_1 + R_2 R_3 + R_1 R_3)}{R_1 + R_2}$ . The numerator is still not in the right form though as it must be  $1 + s \tau_1$ . We need to divide the numerator by the numerator's present coefficients of  $s^0$ , which are  $\frac{R_2}{R_1 + R_2}$ . We can't change the denominator though, it is already in the desired form, so we are unbalancing our expression.  $k$ , the frequency independent gain, will restore balance by becoming the unity coefficients of the numerator,  $\frac{R_2}{R_1 + R_2}$ .

$$\frac{\frac{R_2}{R_1 + R_2} \cdot \left( s C_1 \cdot \frac{\cancel{R_2} (R_1 + R_3)}{\frac{\cancel{R_1} + \cancel{R_2}}{\cancel{R_1} + \cancel{R_2}}} + \frac{\cancel{R_2}}{\frac{\cancel{R_1} + \cancel{R_2}}{\cancel{R_1} + \cancel{R_2}}} \right)}{s C_1 \frac{(R_2 R_1 + R_2 R_3 + R_1 R_3)}{R_1 + R_2} + 1} \quad (17)$$

Performing the cancellations in (17) and bringing  $k$  outside of the fraction yields (10).

## Active Pole-Zero Example

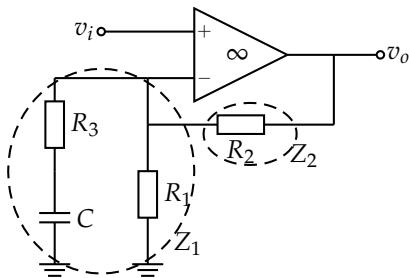

HF gain: (at HF,  $C \rightarrow 0 \Omega$ )

$$\frac{v_o}{v_i} = \frac{R_2 + (R_1 // R_3)}{R_1 // R_3} \quad (18)$$

LF gain: (at LF,  $C \rightarrow \infty \Omega$ )

$$\frac{v_o}{v_i} = \frac{R_2 + R_1}{R_1} \quad (19)$$

This is a standard non-inverting amplifier which has the gain expression:

$$\frac{v_o}{v_i} = \frac{Z_2 + Z_1}{Z_1} = \frac{R_2 + R_1 // \left(R_3 + \frac{1}{j\omega C}\right)}{R_1 // \left(R_3 + \frac{1}{j\omega C}\right)} \quad (20)$$



$$\frac{R_2 + \frac{R_1 \left( R_3 + \frac{1}{j\omega C} \right)}{R_1 + R_3 + \frac{1}{j\omega C}}}{\frac{R_1 \left( R_3 + \frac{1}{j\omega C} \right)}{R_1 + R_3 + \frac{1}{j\omega C}}} \quad (21)$$

Multiply top and bottom by  $j\omega C$ ,

$$\frac{R_2 + \frac{R_1 (R_3 j\omega C + 1)}{1 + j\omega C (R_1 + R_3)}}{\frac{R_1 (R_3 j\omega C + 1)}{1 + j\omega C (R_1 + R_3)}} \quad (22)$$

Multiply top and bottom by  $1 + j\omega C (R_1 + R_3)$ ,

$$\frac{R_2 (1 + j\omega C (R_1 + R_3)) + R_1 (1 + j\omega C R_3)}{R_1 (1 + j\omega C R_3)} \quad (23)$$

Collecting terms,

$$\frac{R_1 + R_2 + j\omega (R_2 R_1 + R_2 R_3 + R_1 R_3) C}{R_1 (1 + j\omega C R_3)} \quad (24)$$

Taking  $k$  outside, and comparing terms with the standard form,

$$\frac{R_1 + R_2}{R_1} \cdot \frac{1 + j\omega C \left( \frac{R_2 R_1 + R_2 R_3 + R_1 R_3}{R_1 + R_2} \right)}{1 + j\omega C R_3} \equiv k \frac{1 + j\omega \tau_1}{1 + j\omega \tau_0} \equiv k \frac{1 + j \frac{f}{f_1}}{1 + j \frac{f}{f_0}} \quad (25)$$

$$f_1 = \frac{R_1 + R_2}{2\pi C (R_1 R_2 + R_2 R_3 + R_1 R_3)} \quad (26)$$

$$f_0 = \frac{1}{2\pi C R_3} \quad (27)$$

$$k = \frac{R_1 + R_2}{R_1} \quad (28)$$

when  $\omega \gg 2\pi f_1$  and  $2\pi f_0$  (i.e. at high frequencies), the 1s are negligible compared to the  $f$  terms,

$$\left| \frac{v_o}{v_i} \right| = k \left| \frac{\cancel{1}^2 + \left( \frac{f}{f_1} \right)^2}{\cancel{1}^2 + \left( \frac{f}{f_0} \right)^2} \right|^{\frac{1}{2}} = k \frac{\frac{f}{f_1}}{\frac{f}{f_0}} = k \frac{f_0}{f_1} \quad (29)$$

$$k \frac{f_0}{f_1} = \frac{\cancel{R_1 + R_2}}{R_1} \cdot \frac{\frac{1}{2\pi C R_3}}{\frac{\cancel{R_1 + R_2}}{2\pi C (R_1 R_2 + R_2 R_3 + R_3 + R_1 R_3)}} \quad (30)$$

$$\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1 R_3} = \frac{R_1 R_2 + R_2 R_3}{R_1 R_3} + 1 \quad (31)$$

$$R_2 \left( \frac{R_1 + R_2}{R_1 R_3} \right) + 1 = \frac{R_2}{R_1 // R_3} + 1 = \frac{R_2 + R_1 // R_3}{R_1 // R_3} \quad (32)$$

Compare (32) with (18). At low frequencies,

$\omega \ll 2\pi f_1$  and  $2\pi f_0$ , the 1s dominate the  $f$  terms, and gain  $\rightarrow k$ .

## Review

- Revisited some EEE117 material on frequency and time domain response of first order LP and HP systems.
- Noted that the Pole-Zero circuit is a summation of the LP and HP first order circuits.
- Enumerated some key points about the pole zero circuit/system including:
  - There is one pole and one zero
  - The pole can be found at a lower frequency than the zero or *vice versa*.
  - The pole determines the time constant,  $\tau$ .
  - sometimes called “lead/lag compensation circuits”.
- Examined a passive network pole zero circuit similar to EEE117
- Examined an active, opamp based, pole zero circuit.

