
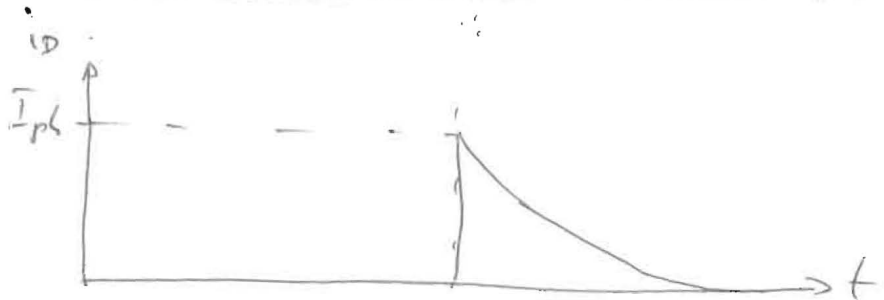
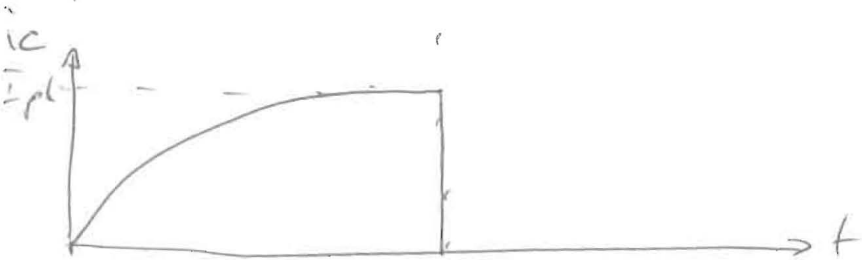


Q1

a) Waveforms for i_L , i_C and i_D .

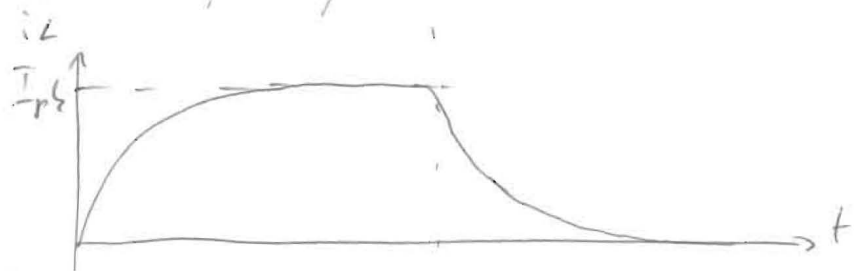

2 marks for each waveform.
1 mark lost for each error.

b) Turn-on delay.

$$i_L \geq 0.4A = I_{LON}$$

$$i_L(t) = \frac{V_s}{R} (1 - e^{-\frac{t}{\tau}}) \quad \tau = \frac{L}{R} = 2\mu s$$

$$t_{don} = -\tau \ln\left(1 - \frac{I_{LON} R}{V_s}\right)$$

$$= \underline{\underline{810\mu s}}$$

c) Turn-off delay

$$i_L \leq 0.15A$$

$$i_L(t) = \frac{V_s}{R} e^{-\frac{t}{\tau}} = i_{LOFF}$$

$$t_{doff} = -\tau \ln\left(\frac{i_{LOFF} R}{V_s}\right)$$

$$= \underline{\underline{4.15\mu s}}$$

Q1

d) Value of R_s to make $t_{\text{doff}} = 2\text{ms}$.

$$\tau = \frac{L}{R+R_s}$$

$$t_{\text{doff}} = -\frac{L}{R+R_s} \ln\left(\frac{i_{L\text{off}} R}{V_s}\right)$$

$$R_s = \frac{-L}{t_{\text{doff}}} \ln\left(\frac{i_{L\text{off}} R}{V_s}\right) - R$$


$$= \underline{\underline{43.2\Omega}}$$

e) Waveform of V_{CE} and V_{CE} rating.

At instant when diode conducts a voltage of V_{ds} is dropped across R_s so $V_{CE} = V_C = V_s + V_{ds}$

$$= V_s + \frac{V_s R_s}{R}$$
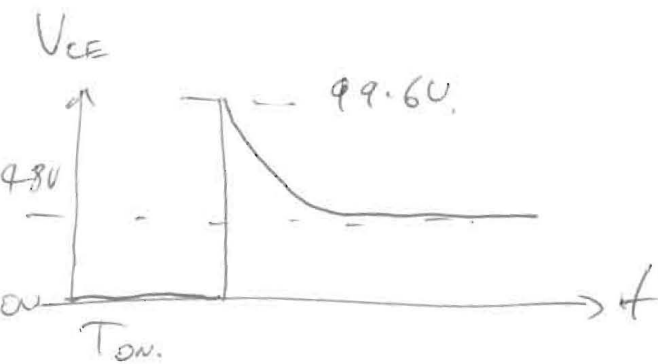
$$= V_s \left(1 + \frac{R_s}{R}\right) = \underline{\underline{99.6V}}$$



Q2

b) cont

Transistor turns on when $V_{BEON} = 0.7V$.

$$I_{lim} = \frac{V_{BEON}}{R_s}$$

$$R_s = \frac{V_{BEON}}{I_{lim}} = \underline{\underline{0.0875\Omega}}$$

Under a short ckt condition all of the supply voltage is dropped across T. Thus,

$$V_{CE} = 48V, I_C = 8A$$

$$P = VI = 384W.$$

c) Efficiency.


$$P_{out} = \frac{V_{out}^2}{R_L} = \frac{12^2}{6} = \underline{\underline{24W}}$$

$$\begin{aligned} P_{loss \text{ in } T} = P_T &= V_{CE} I_{out} = (V_{CE} - V_{out}) I_{out} \\ &= (36 - 12) \times 2 = \underline{\underline{48W}} \end{aligned}$$

$$P_{loss \text{ in } R_s} = P_{Rs} = I_{out}^2 R_s = 4 \times 0.0875 = 0.35W.$$

$$\begin{aligned} \text{Efficiency } \eta &= \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss}} = \frac{P_{out}}{P_{out} + P_T + P_{Rs} + P_R} \\ &= \frac{24}{24 + 48 + 0.35} = 33\% \end{aligned}$$

Q2 Series voltage regulator

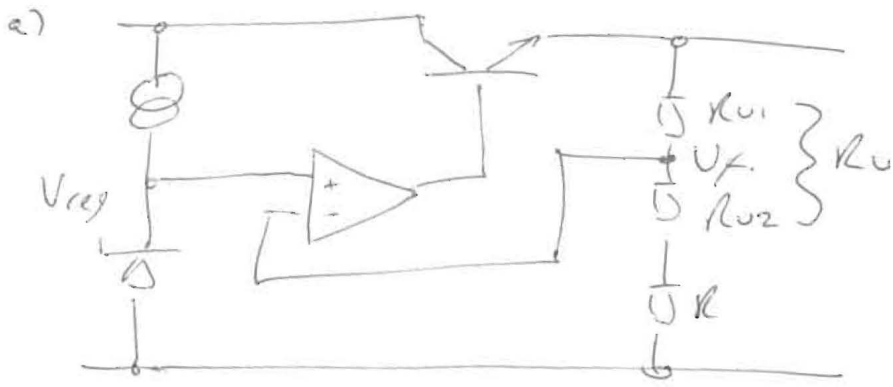

$$A_o = \infty, V_{ref} = V^+, V_f = V^-, V^+ = V^-, V_{ref} = 4V.$$

$$V_f = \frac{R_{u2} + R}{R_{u1} + R_{u2} + R} \times V_{out}$$

$$V_{out} = \frac{R_{u1} + R_{u2} + R}{R_{u2} + R} \times V_{ref}$$

If $0 \leq x \leq 1$ is the position of R_u 's wiper.

$$R_{u1} = R_u x$$


$$R_{u2} = R_u (1 - x).$$

$$x = 0, R_{u1} = 0$$

$$V_{out} = V_{out(min)} = \underline{4V}$$

$$x = 1, V_{out} = V_{out(max)} = \underline{16.12V}$$

b) Current limiting.

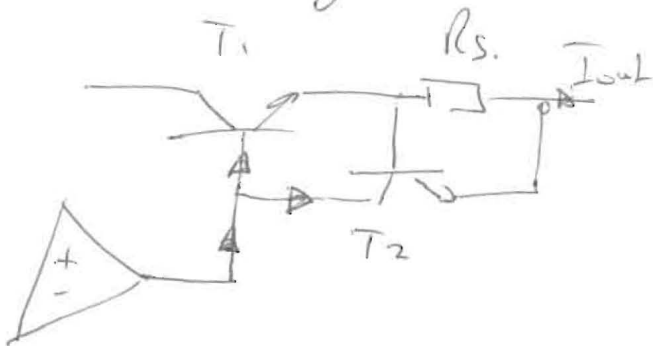


A current sensing resistor R_s is added in series with the output to measure the current. When the voltage drop across R_s exceeds $0.7V$, T_2 turns on reducing

the bias on T_1 . As the output current increases further T_2 is driven harder providing a natural limit to I_{out} .

e) Non-ideal op-amp

$$A_v = 100$$

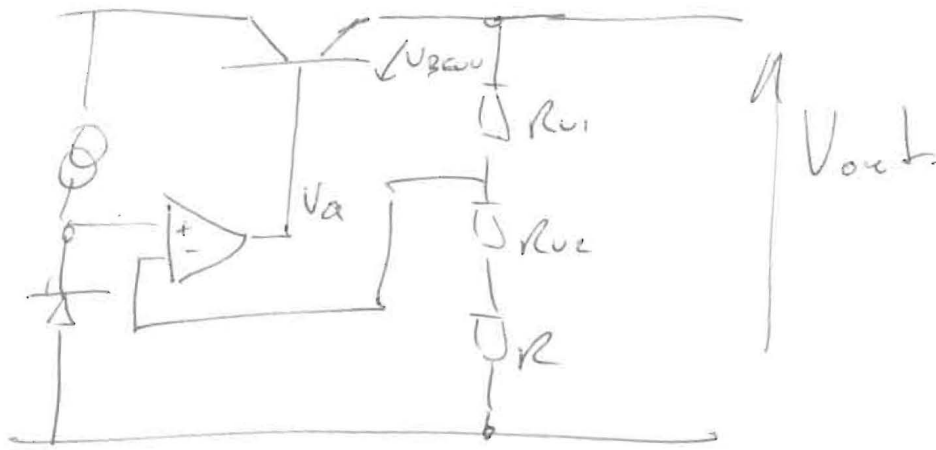

$$V_a = A_v (V^+ - V^-)$$

$$V_{out} = V_a - V_{BEON}$$

$$= A_v (V^+ - V^-) - V_{BEON}$$

$$= A_v \left(V_{ref} - \frac{R_{o2} + R}{R_{i1} + R_{o2} + R} \times V_{out} \right) - V_{BEON}$$

$$V_{out} + A_v \frac{R_{o2} + R}{R_{i1} + R_{o2} + R} V_{out} = A_v V_{ref} - V_{BEON}$$

$$V_{out} (1 + A_v k) = A_v V_{ref} - V_{BEON}$$

$$V_{out} = \frac{A_v V_{ref} - V_{BEON}}{1 + A_v k}$$

Using similar terminology as in part a),

$$x=0 \quad V_{out} = V_{outmin} = \frac{100 \times 4 - 0.7}{101} = \underline{\underline{3.95V}}$$

$$x=1 \quad V_{out} = V_{outmax} = \frac{100 \times 4 - 0.7}{1 + 100 \times 0.2481} = \underline{\underline{15.47}}$$


Q3c) cont.

$$\text{Now } I_{C1} = \frac{V_i}{R_1} \quad \& \quad I_{C2} = \frac{V_{ref}}{R_2}$$

$$V_o = -\alpha V_T \ln \left(\frac{V_i}{V_{ref}} \cdot \frac{R_2}{R_1} \right)$$

α is gain of A_2 .

d) Bolometric RMS converter

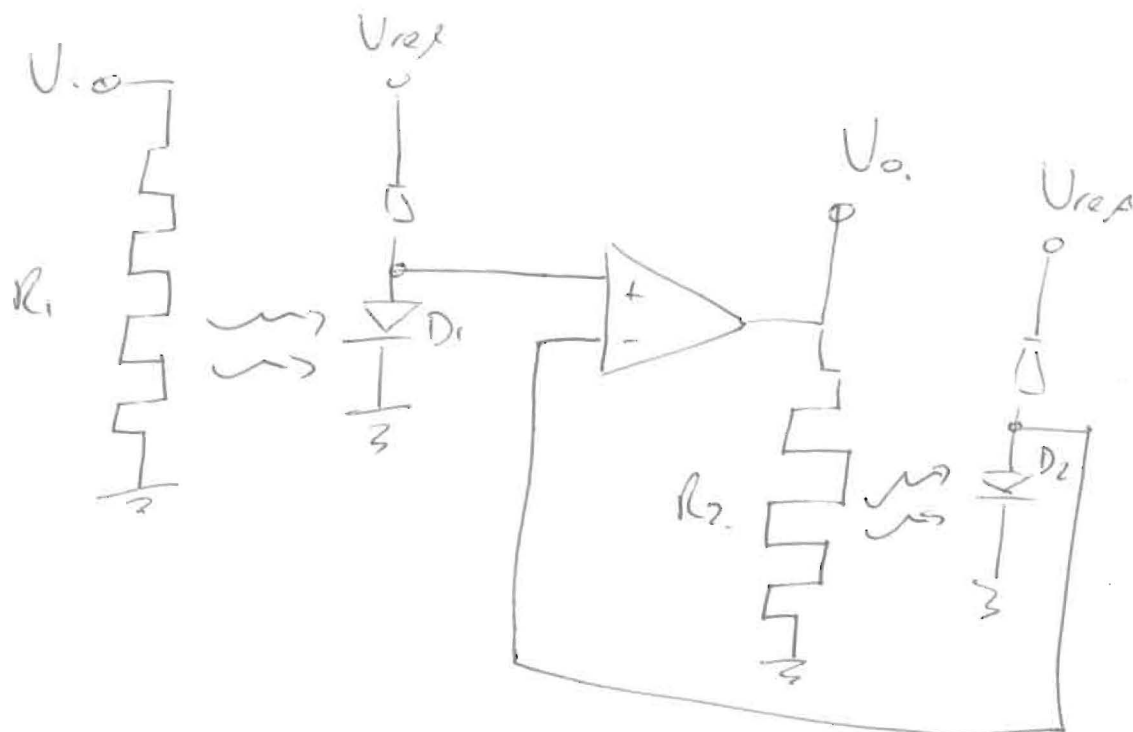


V_i is converted into heat using R_1 .

Temperature of R_1 is measured by D_1 and compared to the temp. of R_2 by the error amp.

Negative feedback cause V_o to vary in accordance to the RMS value of V_i .


Q33 Log amp.

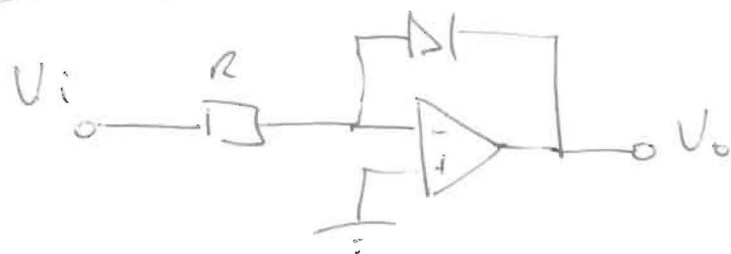

$$\frac{V_i}{R} = I_s e^{-\frac{V_o}{0.026}}$$

$$\therefore V_o = -0.026 \ln\left(\frac{V_i}{I_s R}\right)$$

c).

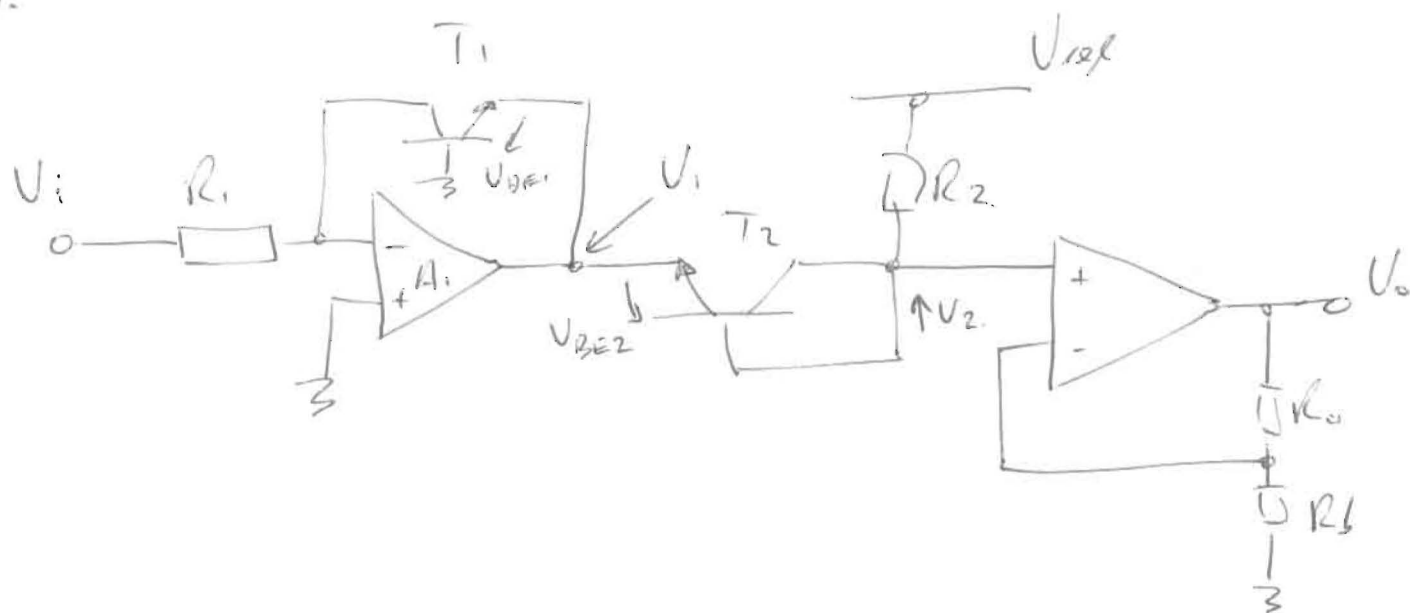

$$V_2 = V_1 + V_{BE2} = V_{BE2} - V_{BE1}$$

Assume that $I_{C1} \approx I_s e^{\left(\frac{V_{BE1}}{V_T}\right)}$

or $V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_s}\right)$

$$\therefore V_2 = V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right) - V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$$

Since T_1 & T_2 are matched


$$I_{S1} = I_{S2} = I_s \quad V_{T1} = V_{T2} = V_T$$

$$V_2 = V_T \ln\left(\frac{I_{C2}}{I_s}\right) - V_T \ln\left(\frac{I_{C1}}{I_s}\right) = V_T \ln\left(\frac{I_{C2}}{I_{C1}}\right)$$

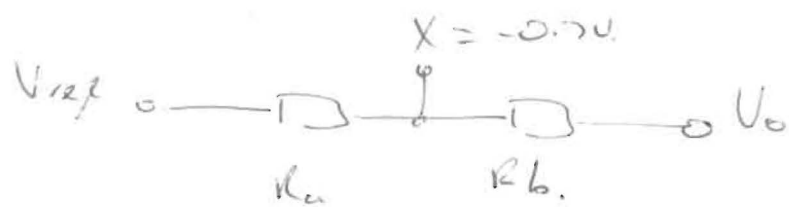Q3a) Shaping ckt.

The circuit has an incremental gain of $-\frac{R_f}{R}$ until D_1 or D_2 conduct.


Assuming that V_i is +ve, D_1 will conduct when $X = -0.7V$.



$$\frac{V_{ref} + 0.7}{R_a} = \frac{-0.7 - V_o}{R_b}$$


$$V_o = - \left[\frac{R_b}{R_a} V_{ref} + \frac{0.7(R_a + R_b)}{R_a} \right]$$

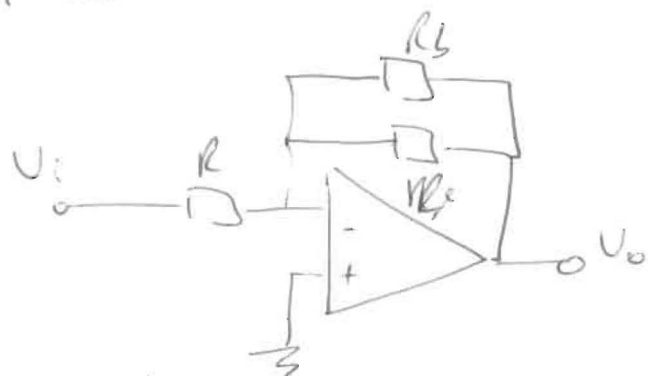After D_1 has switched on the ckt becomes



$$\frac{V_o}{V_i} = - \frac{R_f || R_b}{R}$$


V_o/V_i characteristic is

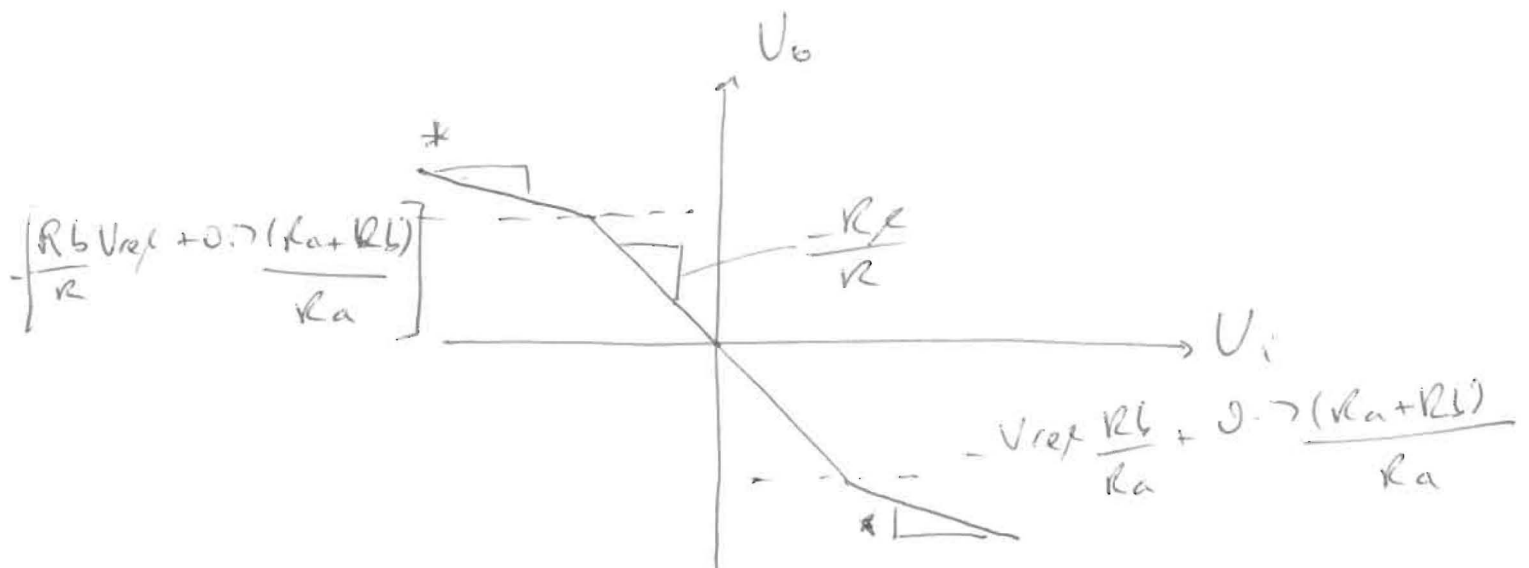


* gradient / incremental gain = $-\frac{R_f || R_b}{R}$

4a) Sub-circuits


i) Soft Diode.

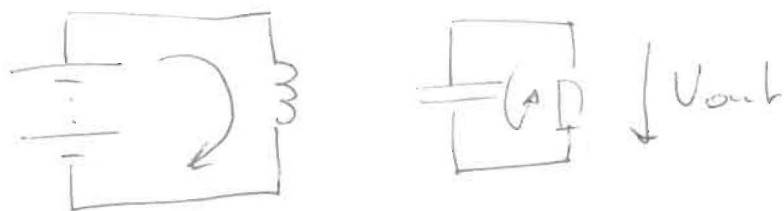




ii) Soft Diode.

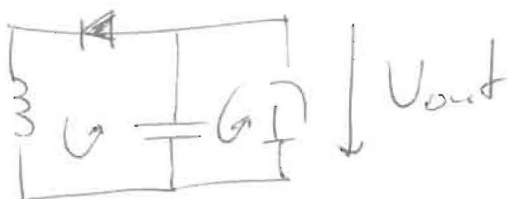

iii) Soft Diode.

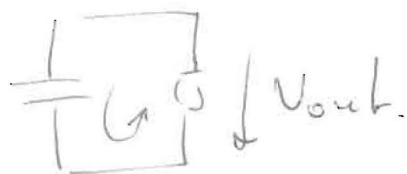

b) Waveforms.

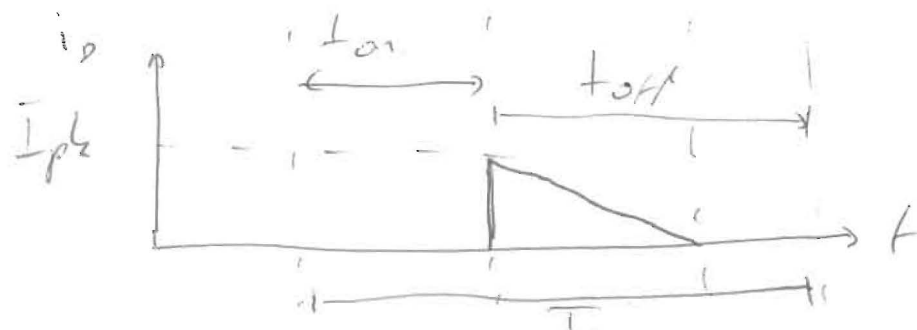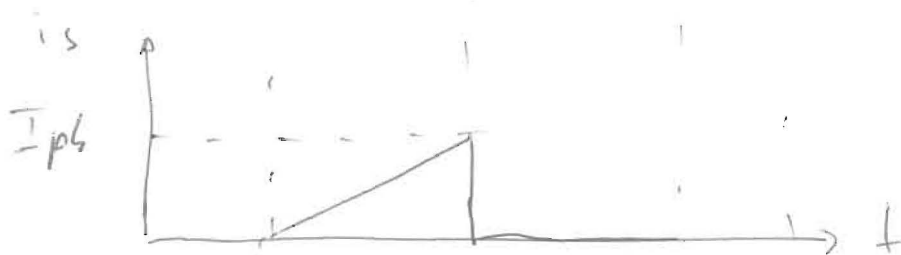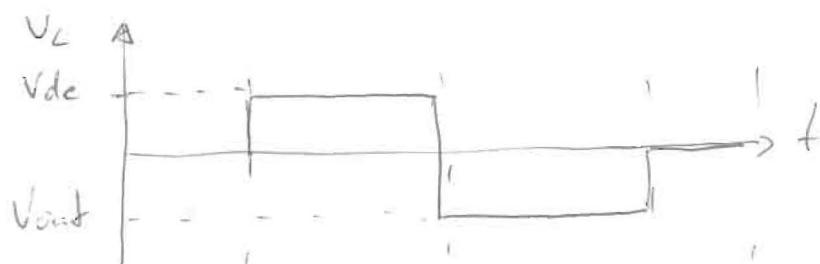

c) Output voltage

Peak energy stored in L $E = \frac{1}{2} L I_{pk}^2$

when S is on $V_{dc} = L \frac{I_{pk}}{t_{on}}$

$$I_{pk} = \frac{V_{dc} t_{on}}{L} = \frac{V_{dc} T}{2L}$$

$$E = \frac{1}{2} L \left(\frac{V_{dc} t_{on}}{L} \right)^2$$

Energy consumed by the load is $E = \frac{V_{out}^2}{R_L} \times T$

Equating the two energies and rearranging gives

$$V_{out} = \sqrt{\frac{R_L}{2L}} \frac{V_{dc}}{2} \quad \text{where } t_{on} = \frac{T}{2} = \frac{1}{f_s}$$

substituting values gives

$$\underline{V_{out} = 400V}$$

d) Peak-to-peak ripple voltage

Assume V_{out} is fairly constant

$$I_{pk} = \frac{V_{dc} T}{2L}$$

$$\Delta I = \frac{I_{pk} L}{V_{out}} = \frac{V_{dc} T}{2L} \times \frac{L}{V_{out}} = \frac{V_{dc} T}{2V_{out}}$$

$$Q = I \Delta t = \frac{1}{2} \times \Delta I \times I_{pk}$$

$$= \frac{1}{2} \times \frac{V_{dc} T}{2V_{out}} \times \frac{V_{dc} T}{2L} = \frac{V_{dc}^2 T^2}{8L V_{out}}$$

$$C \Delta V = Q$$

$$\Delta V = \frac{Q}{C} = \frac{1}{8LC} \frac{V_{dc}^2}{V_{out}} T^2$$

$$= \frac{1}{8LC f_s^2} \frac{V_{dc}^2}{V_{out}}$$

$$= \underline{\underline{5.67V}}$$