

Data Provided: You may need to use the following physical constants:

Charge on electron:	$q = -1.602 \times 10^{-19} \text{ C}$
Free electron rest mass:	$m_0 = 9.110 \times 10^{-31} \text{ kg}$
Speed of light in vacuum:	$c = 2.998 \times 10^8 \text{ m s}^{-1}$
Planck's constant:	$h = 6.626 \times 10^{-34} \text{ Js}$
Boltzmann's constant:	$k = 1.381 \times 10^{-23} \text{ JK}^{-1}$
Melting point of ice:	$0^\circ\text{C} = 273.2 \text{ K}$
Permittivity of free space:	$\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$
Permeability of free space:	$\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$

**The University of Sheffield****DEPARTMENT OF ELECTRONIC AND ELECTRICAL
ENGINEERING****EEE225 Analogue and Digital Electronics**

Answer **ALL** questions.

Part A: State whether each of the following statements is TRUE or FALSE and justify your answer with a brief (2 lines maximum) justification.

- 1) The conductivity of n-type silicon varies significantly as the room temperature changes.

(2)

- 2) High doping in semiconductors can enable higher temperature device operation.

(2)

- 3) The built-in voltage (or contact potential) in a p-n junction is approximately equal to the band-gap of the semiconductor.

(2)

- 4) Metal-semiconductor schottky junctions are usually used when high speed switching is required.

(2)

- 5) You can differentiate between an LED and a laser by the amount of optical power they emit.

(2)

- 6) Any semiconductor material that can be used to make a solar-cell can also be used to make a photodiode.

(2)


- 7) When a silicon p-n junction diode is exposed to sunlight, you can obtain a voltage at the terminals that is approximately equal to the built-in voltage.

(2)

- 8) In a perfectly compensation doped semiconductor, the concentration of acceptors and donors falls to below the intrinsic carrier concentration.


(2)

 - 9) Most Blu-Ray DVD players use the semiconductor material InGaAs ($E_g = 0.7 \text{ eV}$) to make the blue lasers.



(2)

 - 10) In an enhancement mode MOST, the drain current can vary linearly with drain voltage.



(2)

Part B: Question 11

- a) Sketch, label and discuss briefly the conduction mechanisms in an induced channel Metal Oxide Semiconductor Transistor (MOST). Identify all the significant parts of the device.



(10)

- b) The unsaturated drain characteristic of such a device as in (a) can be represented by:

$$I_d = \frac{\mu_e C_g}{l^2} \left[V_g - V_T - \frac{V_d}{2} \right] V_d$$


where the symbols have their usual meaning.

- i) Under what voltage conditions does saturation of the drain current happen?



(2)

 - ii) What is the transconductance in the saturation region?




(4)

- iii) Show that the transconductance is simply given by twice the ratio of the saturated drain current to drain voltage.



(4)

 - c) Sketch the schematic band diagram of a rectifying (schottky) metal-semiconductor junction in equilibrium when the semiconductor is n-type, identifying clearly the built-in (contact) potential and the Fermi-level. State clearly the relative work functions for the metal and semiconductor.



(10)

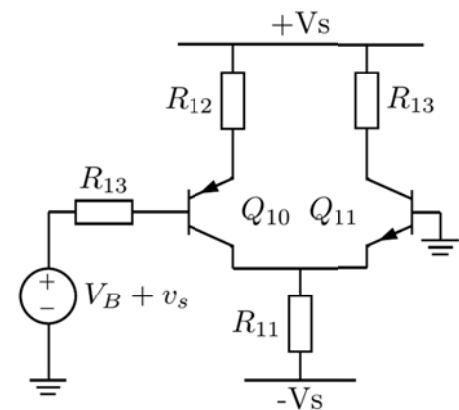
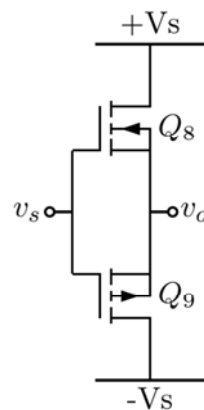
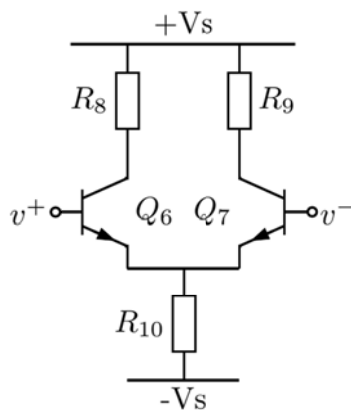
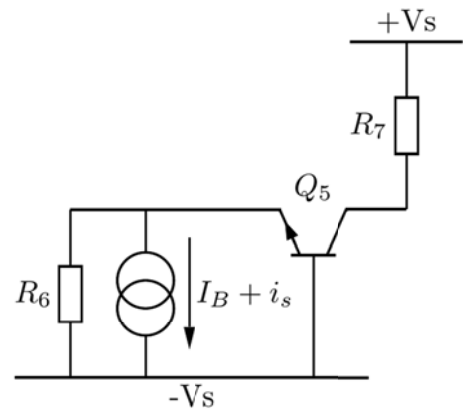
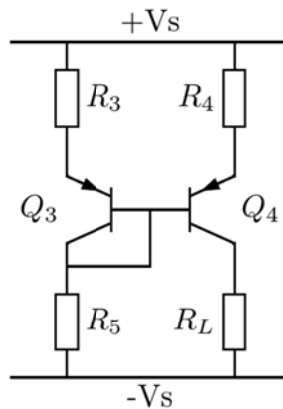
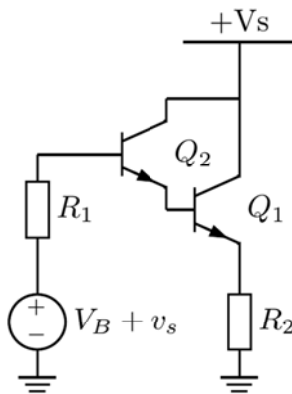


Figure 1: Some Common Analogue Transistor Circuit Blocks

- 12 Identify the circuits in Figure 1 by writing the letters A to F next to the names below. *Some Letters may fall into two categories.* **{1 mark for each correct assignment}**

Emitter follower	Differential amplifier	Cascode
Common base	Push pull	Current Mirror
Common collector	Darlington	Common Emitter

- 13 Using the column headings below list the transistors in Figure 1 according to type.
{1 mark for each correct}


NPN and N Channel		PNP and P Channel	

- 14 In Figure 1d, $+V_s = 15 \text{ V}$, $-V_s = -15 \text{ V}$, $v^+ = v^- = -1 \text{ V}$ and $R_{10} = 10 \text{ k}\Omega$. Find $I_{R_{10}}$. State two assumptions you made. **{3 marks}**

- 15 Is the input described in Question 14 *common mode* or *differential mode*? **{1 mark}**


- 16 In Figure 1f, $+V_s = 15 \text{ V}$, $-V_s = -15 \text{ V}$, $V_B = 4.3 \text{ V}$ and the collector currents of both transistors are $100 \text{ }\mu\text{A}$. Find values of R_{11} and R_{12} that would satisfy these DC conditions. State one assumption you have made. **{6 marks}**

- 17 Draw the small signal equivalent circuit of Figure 1c and label all components. **{3 marks}**



- 18 Derive an expression for the transimpedance (collector voltage/input current, v_c/i_{in}) of Fig. 1c. **{7 marks}**

 Hint: Start by summing currents at the emitter.



- 19 Why is R_6 is often neglected in the calculation of transimpedance for this circuit. **{2 marks}**



- 20 Derive an expression for the output impedance of the circuit in Fig 1a. hint: remove R2 and use a current source to drive the emitter of Q1. **{7 marks}**

- 21 Hence or otherwise describe the impedance transforming nature of the transistor in a few sentences. **{3 marks}**