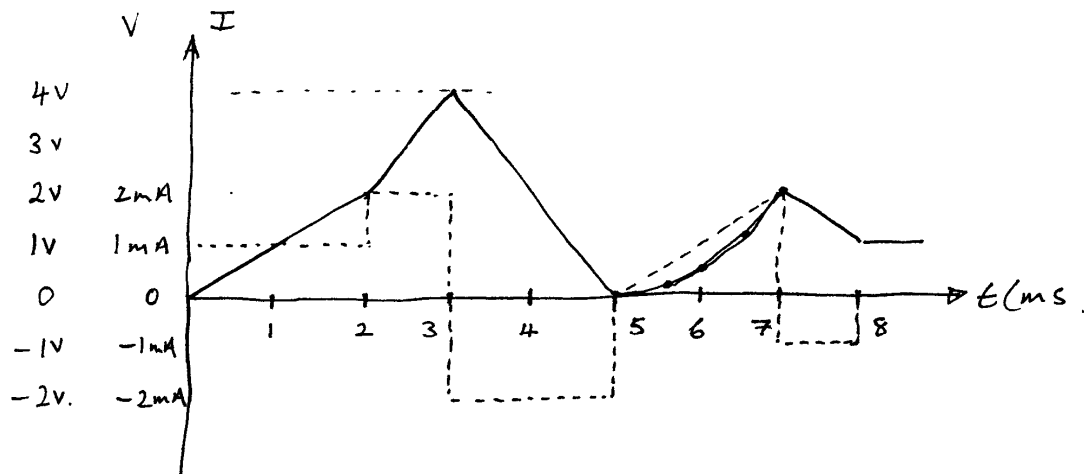


Q1 (i)





In this question, the evolution of charge in the capacitor is the area exposed under the current time graph as  $t$  increases. When  $I$  is constant, area increases at a constant rate with respect to time.  $\therefore$  Charge in and voltage across the capacitor are related by  $Q = CV$   
or  $\Delta Q = C \Delta V$ .

The only slightly tricky bit is between  $t = 5\text{ms}$  +  $t = 7\text{ms}$ . Here the area does not change linearly with time; instead it follows a quadratic relationship. The waveform can be sketched by working out the area between  $5\text{ms}$  +  $5.5\text{ms}$  ( $= 0.125\mu\text{C}$ ), between  $5\text{ms}$  +  $6\text{ms}$  ( $0.5\mu\text{C}$ ), between  $5\text{ms}$  +  $6.5\text{ms}$  ( $= 1.125\mu\text{C}$ ) and between  $5\text{ms}$  and  $7\text{ms}$  ( $= 2\mu\text{C}$ ). Alternatively, if you are good at maths, you can say that between  $5\text{ms}$  +  $7\text{ms}$   $I(t) = t$  (taking  $5\text{ms}$  as the time origin).

$$\begin{aligned} \text{so } V_C \Big|_{5\text{ms}-7\text{ms}} &= \frac{1}{C} \int_0^{2\text{ms}} t \, dt + V_{\text{initial}} \\ &= \frac{1}{C} \left[ \frac{t^2}{2} \right]_0^{2\text{ms}} + V_{\text{initial}}. \end{aligned}$$

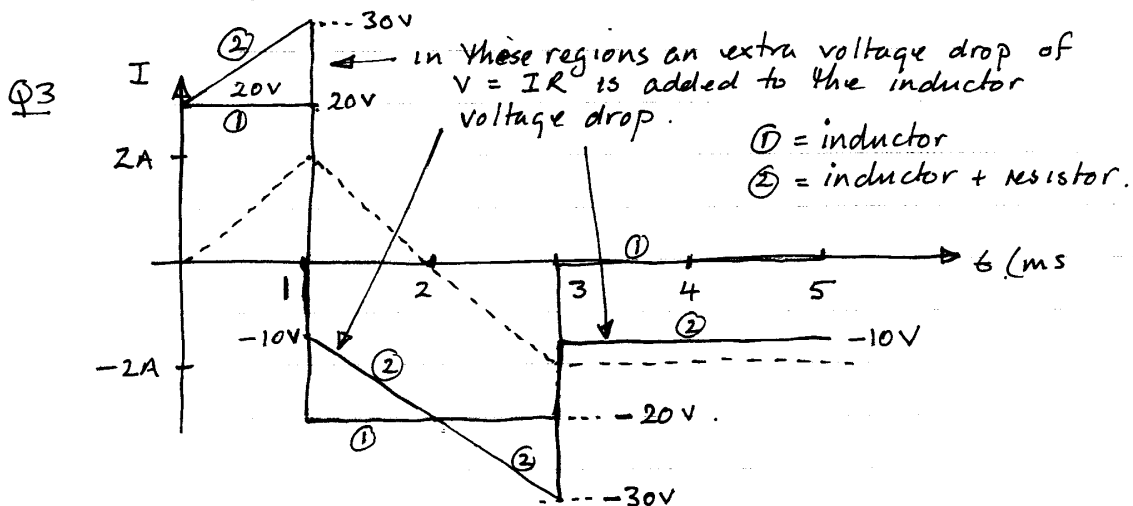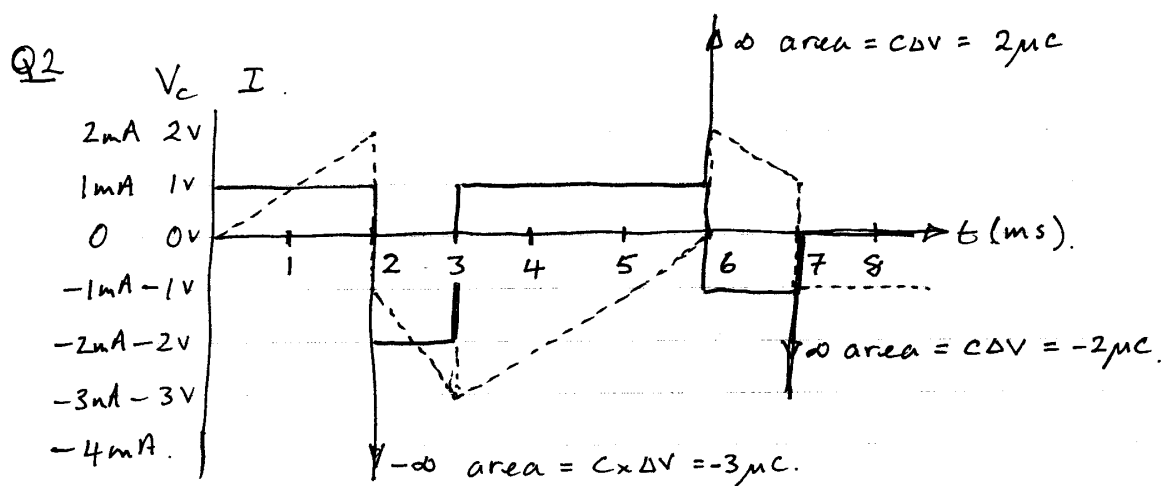(ii) The total +ve area =  $6\mu\text{C}$ ; total -ve area =  $5\mu\text{C}$ .


$$\text{net area @ } 8\text{ms} = 6\mu\text{C} - 5\mu\text{C} = \underline{\underline{1\mu\text{C}}}.$$



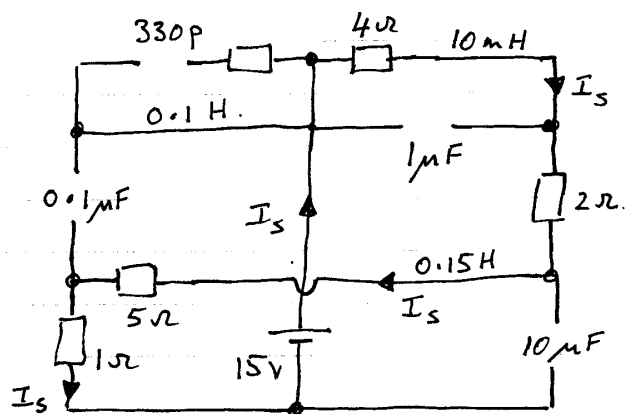Q4 The path of  $I_s$  is indicated on the diagram. The total resistance of that path is

$$4 + 2 + 5 + 1 = 12\Omega$$

$$\therefore I_s = \frac{15V}{12\Omega} = 1.25A$$



To find the stored energies, the voltage across each  $C$  must be worked out and the current through each  $L$  must be worked out.....

Consider the inductors ....

10mH and 0.15H carry  $I_s$  so their stored energies are ....

$$E_{10\text{mH}} = \frac{1}{2} \cdot 0.01 \times 1.25^2 = \underline{7.8\text{mJ}}.$$

$$E_{0.15\text{H}} = \frac{1}{2} \cdot 0.15 \times 1.25^2 = \underline{117\text{mJ}}.$$

The 0.1H inductor carries a current of zero so ...

$$E_{0.10\text{H}} = \underline{0\text{J}}.$$

Consider the capacitors ....

The 330pF capacitor has zero volts across it

$$E_{330\text{pF}} = \underline{0\text{J}}$$

The 1 $\mu$ F capacitor has a voltage drop across it of  $I_s \times 4\Omega$ , ie 5V

$$E_{1\mu\text{F}} = \frac{1}{2} \cdot 10^{-6} \cdot 5^2 = \underline{12.5\mu\text{J}}$$

The 0.1 $\mu$ F capacitor has 15V on its top terminal and  $I_s \times 1\Omega$  on its bottom terminal giving a voltage difference of  $15 - 1.25 = 13.75\text{V}$ .

$$E_{0.1\mu\text{F}} = \frac{1}{2} \cdot 0.1\mu\text{F} \times 13.75^2 = \underline{9.45\mu\text{J}}.$$


The 10 $\mu$ F capacitor has across it the voltage generated by  $I_s$  flowing through the  $5\Omega + 1\Omega$  resistors

$$E_{10\mu\text{F}} = \frac{1}{2} \cdot 10^{-5} \cdot 7.5^2 = \underline{281\mu\text{J}}.$$

Note that in this circuit the inductors are storing much more energy than the capacitors. If the resistors were all changed to k $\Omega$  instead of  $\Omega$ , the capacitor energy storage would remain the same but the inductor stored energies would be a factor of  $10^6$  times smaller than they are here — ie nJ instead of mJ. Inductors make very effective energy stores in low voltage high(ish) current applications.

Q5

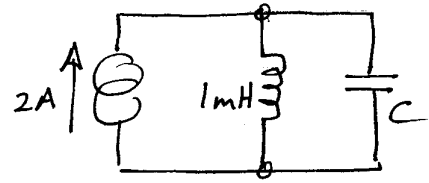(i) Since the 2A is steady and  
 $V_L = L \frac{dI}{dt}$ ,  $\frac{dI}{dt} = 0$  and  $V_L = 0$



(ii) Energy stored in the inductor  
 is  $E_{1mH} = \frac{1}{2} \cdot 10^{-3} \cdot 2^2$   
 $= 2mJ$

(iii) There is no voltage across the capacitor so  
 $E_C = 0 J$ .

(iv)  $E_C = \frac{1}{2} C V^2 = 2mJ$

$$\text{so for } 1nF \quad V^2 = \frac{2 \times 2mJ}{1nF} = 4 \times 10^6$$

$$\therefore V_{Cmax} = \sqrt{4 \times 10^6} = \underline{2kV}$$

$$\text{for } 10nF \quad V^2 = \frac{2 \times 2mJ}{10nF} = 400 \times 10^3$$

$$V_{Cmax} = \sqrt{400 \times 10^3} = \underline{632 V}$$

$$\text{for } 100nF \quad V^2 = \frac{2 \times 2mJ}{100nF} = 40 \times 10^3$$

$$V_{Cmax} = \sqrt{40 \times 10^3} = \underline{200 V}$$