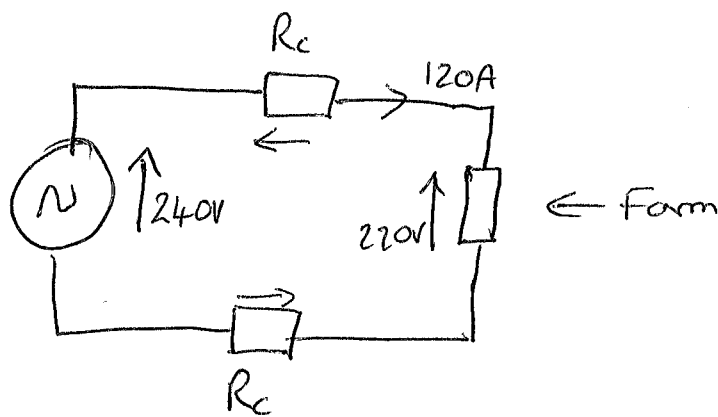


Q1

1



R_c is the resistance of the cable.

Applying Kirchhoff's law around the loop.

$$240 - 120R_c - 220 - 120R_c = 0$$

$$\therefore 20 = 240R_c$$

$$\therefore R_c = 0.0833 \Omega$$

Since $R_c = \frac{\rho L}{A}$ then $A = \frac{\rho L}{R_c}$

$$\therefore A_{\min} = \frac{1.8 \times 10^{-8} \times 800}{0.0833} = 1.728 \times 10^{-4} \text{ m}^2 = \underline{\underline{17.3 \text{ mm}^2}}$$

If $A < 17.3 \text{ mm}^2$ R_c will be $> 0.0833 \Omega$ and there will be a greater voltage drop.

(ii) Power consumed by the farm = $220 \times 120 = \underline{\underline{26.4 \text{ kW}}}$

Power provided by the generator = $240 \times 120 = \underline{\underline{28.8 \text{ kW}}}$

Hence the efficiency is $\frac{26.4 \times 10^3}{28.8 \times 10^3} \times 100 = \underline{\underline{91.7\%}}$

(Check: losses in cables = $2I^2 R_c = 2 \cdot 120^2 \cdot 0.0833 = 2.4 \text{ kW}$)
 $26.4 + 2.4 = 28.8 \text{ kW}$

QUESTION 1 (CONTINUED)

2

(b)(i) The factory draws a power of 100kW at 0.85 p.f. lag.

$$P = S \cos \phi \Rightarrow S = \frac{P}{\cos \phi} = \frac{100 \times 10^3}{0.85} = \underline{\underline{117.65 \text{ KVA}}}$$

(ii) Reactive power is given by:

$$Q = S \sin \phi = 117.65 \times \sin(\cos^{-1} 0.85) = \underline{\underline{61.98 \text{ kVAR}}}$$

(iii) Current drawn from the supply:-

$$S = VI \Rightarrow I = \frac{S}{V} = \frac{117.65 \times 10^3}{800} = \underline{\underline{147 \text{ A}_{\text{rms}}}}$$

(c)(i) After the factory is enlarged the total load is as follows:

	P	Q
Original	100000	61980
Heaters	20000	0
Motors	<u>84000</u>	<u>112000</u>
	204000W	173980VAR

$$\therefore \text{New KVA rating of the site is } \sqrt{P^2 + Q^2} = \sqrt{204^2 + 173.98^2} \\ = \underline{\underline{268 \text{ KVA}}}$$

(ii) The new power factor is $\frac{204}{268} = \underline{\underline{0.761 \text{ lagging}}}$

$$\left(\text{or } \tan^{-1} \left(\frac{173.98}{204} \right) = 40.46^\circ \Rightarrow \cos 40.46 = 0.761 \right)$$

(iii) To correct the power factor to unity the capacitors must supply 173.98 kVAR leading.

The current drawn by the capacitors:

$$I_c = \frac{173.98 \times 10^3}{800} = 217.5 \text{ Arms.}$$

QUESTION 1 (CONTINUED)

3

$$X_c = \frac{V_c}{I_c} = \frac{800}{217.5} = 3.68 \Omega.$$

$$\text{Now } X_c = \frac{1}{2\pi f C} \Rightarrow C = \frac{1}{2\pi f X_c} = \frac{1}{100\pi \cdot 3.68}$$

$$= 8.65 \times 10^{-4} \text{ F}$$

$$\underline{\underline{\text{or } 865 \mu\text{F}}}$$


(iv) The peak voltage the capacitor must withstand is:

$$V_{pk} = \sqrt{2} V_{rms} = \sqrt{2} \times 800 = \underline{\underline{1131 \text{ Volts}}}$$

QUESTION 2

4

(a)

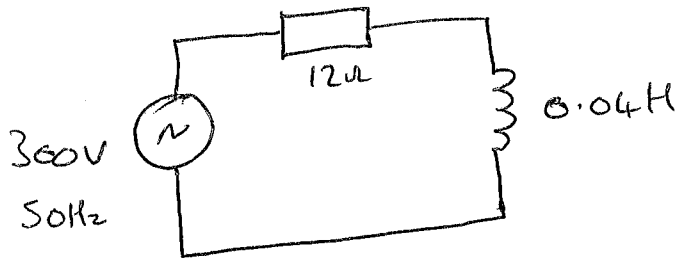

(i) Impedance of the circuit:

$$\begin{aligned} Z &= R + j\omega L = R + j2\pi fL = 12 + j2\pi \cdot 50 \cdot 0.04 \\ &= 12 + j12.57 \\ &= \underline{\underline{17.4 \angle 46.3^\circ \Omega}} \end{aligned}$$

(ii) The current flowing in the coil is given by:

$$I = \frac{V}{Z} = \frac{300 \angle 0^\circ}{17.4 \angle 46.3^\circ} = \underline{\underline{17.24 \angle -46.3^\circ \text{ Arms}}}$$


(iii)

The real power drawn from the supply is:

$$P = I^2 R = 17.24^2 \times 12 = \underline{\underline{3566.6 \text{ W}}}$$

(or alternatively $P = VI \cos \phi = 300 \times 17.24 \times \cos 46.3^\circ \approx 3570 \text{ W}$)

(b) (i)

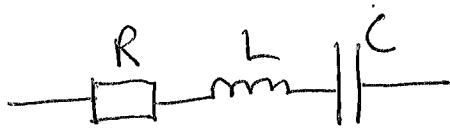

$$Z = R + j\omega L - \frac{j}{\omega C} = \underline{\underline{R + j(\omega L - \frac{1}{\omega C})}}$$




Circuit is resonant when the imaginary term is zero.

$$\therefore Z = R \text{ and } \omega L = \frac{1}{\omega C}$$

$$\text{Hence } \omega_r^2 = \frac{1}{LC} \Rightarrow \omega_r = \frac{1}{\sqrt{LC}} \text{ or } f_r = \underline{\underline{\frac{1}{2\pi\sqrt{LC}}}}$$

QUESTION 2 (CONTINUED)

5

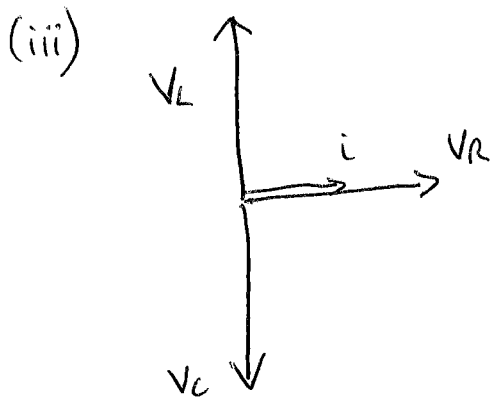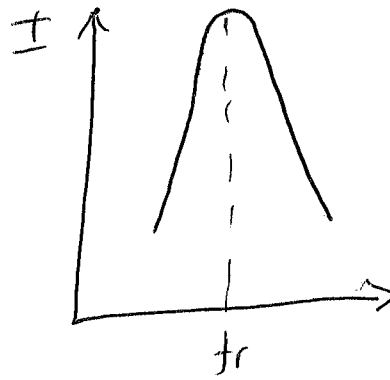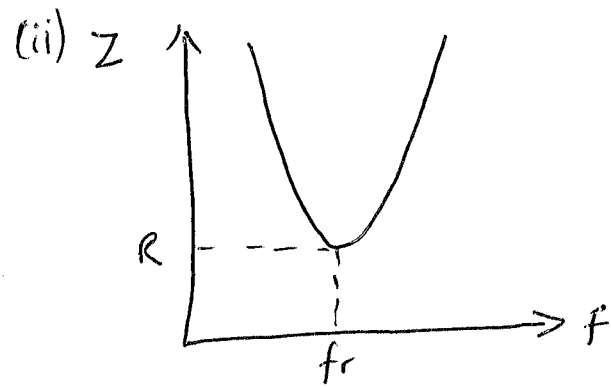

- (iv) For maximum current the circuit must be at resonance
i.e. $f_r = 50 \text{ Hz}$.

$$\text{Since } f_r = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = \frac{1}{4\pi^2 f_r^2 L}$$

$$\therefore C = \frac{1}{4 \cdot \pi^2 \cdot 50^2 \cdot 0.04} = \underline{\underline{253 \mu\text{F}}}$$

Since at resonance $Z = R$ then the current will be

$$I = \frac{300}{12} = 25 \text{ A}$$

and the power dissipated will be $I^2 R = 25^2 \times 12 = \underline{\underline{7500 \text{ W}}}$

QUESTION 2 (CONTINUED)

6

(c) If the frequency increases to 60Hz

$$\text{then } jX_L = j2\pi \cdot 60 \cdot 0.04 = j15.08 \Omega$$

$$\text{and } -jX_C = \frac{-j}{2\pi \cdot 60 \cdot 253 \times 10^{-6}} = -j10.48 \Omega$$

$$\therefore Z = 12 + j15.08 - j10.48 = 12 + j4.6 \Omega \\ = \underline{\underline{12.85 \angle 20.97^\circ \Omega}}$$

$$I = \frac{300 \angle 0^\circ}{12.85 \angle 20.97^\circ} = \underline{\underline{23.35 \angle -20.97^\circ \text{ Arms}}}$$

$$|V_R| = I \cdot R = 23.35 \times 12 = 280.2 \text{ Vrms.}$$


$$|V_L| = I \cdot X_L = 23.35 \times 15.08 = 352.1 \text{ Vrms}$$

$$\therefore \text{Voltage across the electromagnet} = \sqrt{V_R^2 + V_L^2} \\ = \sqrt{280.2^2 + 352.1^2} = \underline{\underline{450 \text{ Vrms.}}}$$

QUESTION 3

7

(a)

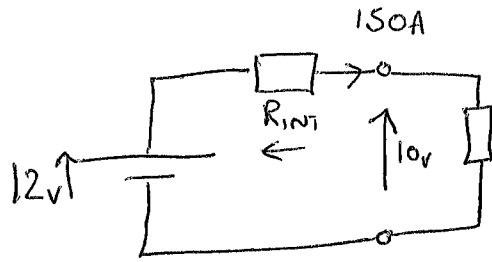

Applying Kirchhoff's law:

$$12 - 150R_{INT} - 10 = 0$$

$$\therefore R_{INT} = \frac{2}{150} = \underline{\underline{0.0133\Omega}}$$

$$\text{Power dissipated within the battery} = I^2 \times R_{INT} = 150^2 \times 0.0133 = \underline{\underline{2999.25W}}$$


$$P_{\text{output}} = V_{\text{out}} \times I = 10 \times 150 = 1500W$$

$$P_{\text{BATT}} = V_{\text{BATT}} \times I = 12 \times 150 = 1800W$$

$$\text{Hence efficiency} = \frac{P_{\text{out}}}{P_{\text{BATT}}} = \frac{1500}{1800} \times 100\% = \underline{\underline{83.3\%}}$$

$$(\text{Check } P_{\text{out}} + P_{\text{loss}} = 1500 + 299.9 \approx 1800W)$$

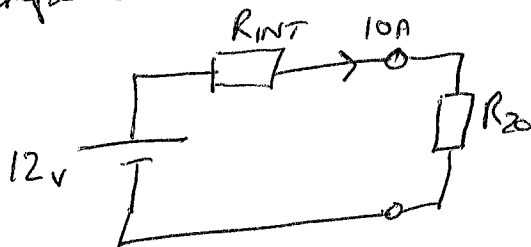(b) First calculate the resistance at 20°C and at the final temperature:



$$R_{INT} + R_{20} = \frac{V}{I} = \frac{12}{10} = 1.2\Omega$$

$$\text{Since } R_{INT} = 0.0133$$

$$\text{then } R_{20} = 1.1867\Omega$$

Similarly at the final temperature

$$R_{INT} + R_F = \frac{12}{7} = 1.714\Omega$$

$$\text{Hence } R_F = 1.714 - 0.0133 = 1.7007\Omega$$

QUESTION 3 (CONTINUED)

8

$$\text{Now } \frac{R_F}{R_{20}} = \frac{R_0}{R_0} \frac{(1 + \alpha_0 \cdot T_F)}{(1 + \alpha_0 \cdot 20)}$$

$$\therefore \frac{1.7007}{1.1867} = \frac{(1 + 12.5 \times 10^{-3} \cdot T_F)}{(1 + 12.5 \times 10^{-3} \cdot 20)}$$


$$\therefore 1.433 = \frac{(1 + 12.5 \times 10^{-3} T_F)}{1.25}$$

$$\therefore T_F = \underline{\underline{63.3^\circ \text{C}}}$$

(ii) At the final temperature $\text{Power} = I^2 \cdot R_F = 7^2 \times 1.7007 = \underline{\underline{83.33 \text{ W}}}$

Hence the efficiency = $\frac{83.33}{12 \times 7} \times 100\% = \underline{\underline{99.2\%}}$

(c)

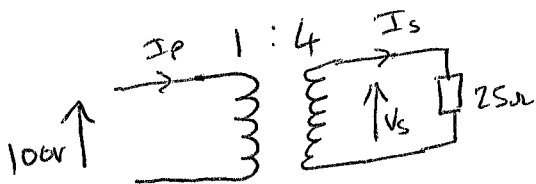

$$\text{Since } \frac{V_P}{V_S} = \frac{N_P}{N_S} \Rightarrow V_S = \frac{N_S \cdot V_P}{N_P} = \frac{4 \times 100}{1} = \underline{\underline{400 \text{ V}}}$$

$$I_S = \frac{400}{25} = 16 \text{ Arms.}$$

$$\text{Now } \frac{I_P}{I_S} = \frac{N_S}{N_P} \Rightarrow I_P = \frac{I_S \cdot N_S}{N_P} = \frac{16 \times 4}{1} = \underline{\underline{64 \text{ Arms}}}$$

$$\text{Power dissipated} = I^2 R = 16^2 \cdot 25 = \underline{\underline{6.4 \text{ kW}}}$$

QUESTION 3 (CONTINUED)

9

(ii) The secondary impedance is now:

$$Z_s = R + j \cdot 2\pi f L = 30 + j \cdot 2\pi \cdot 50 \cdot 0.1 \\ = 30 + j31.4 = 43.4 \angle 46.3^\circ \Omega$$

$$I_s = \frac{400 \angle 0^\circ}{43.4 \angle 46.3^\circ} = 9.217 \angle -46.3^\circ \text{ Arms}$$

$$\therefore I_p = 4 \times 9.217 \angle -46.3^\circ = \underline{\underline{36.87 \angle -46.3^\circ}}$$

$$\text{Power dissipated in load} = I_s^2 \cdot R_s = 9.217^2 \cdot 30 = \underline{\underline{2.55 \text{ kW}}}$$

$$(\text{check } P = V_p I_p \cos \phi = 100 \times 36.87 \times \cos 46.3 = 2.55 \text{ kW})$$

(iii) The input power factor would be $\cos 46.3^\circ = \underline{\underline{0.69 \text{ lag}}}$

$$\text{The VA rating} = 100 \times 36.87 = \underline{\underline{3678 \text{ VA}}}$$

(iv) Since $V_{rms} = 4.44 f N \phi_{max}$

$$\text{then } N_p = \frac{V_{rms}}{4.44 f \cdot \phi_{max}} = \frac{100}{4.44 \times 50 \times 4 \times 10^{-3}}$$


$$= \underline{\underline{113 \text{ TURNS}}}$$

(v) If the frequency is 60 Hz



$$V_{rmsmax} = 4.44 \times 60 \times 113 \times 4 \times 10^{-3} = \underline{\underline{120 \text{ V}_{rms}}}$$

QUESTION 4

10

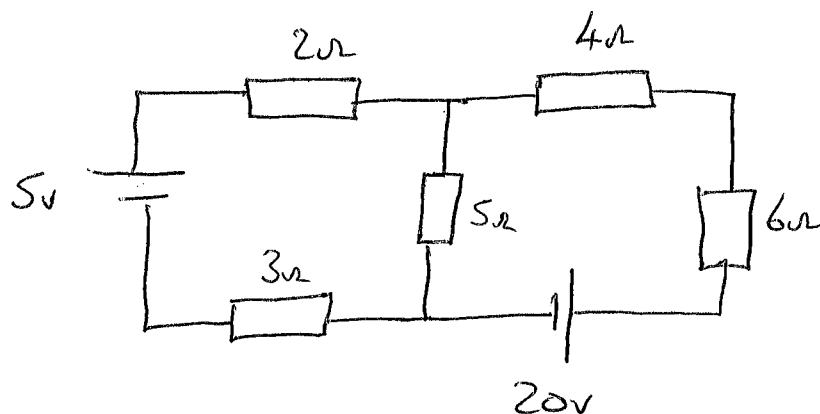

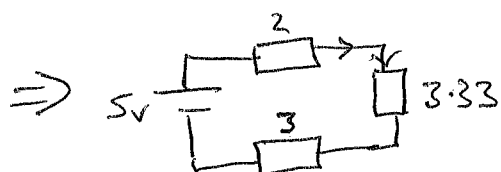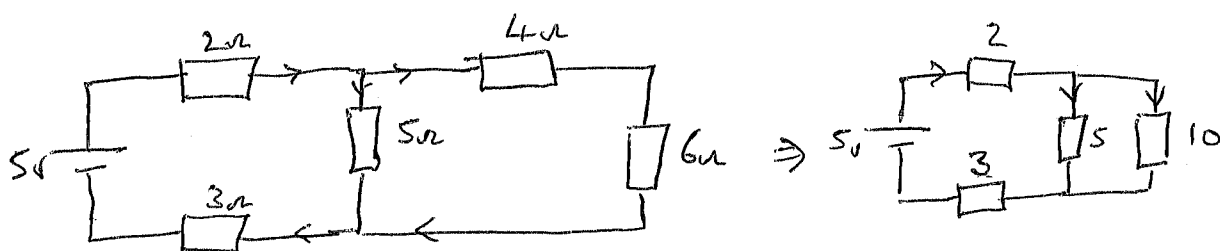Consider the 5V supply - short out the 20V battery.




$$\therefore I_T = \frac{5}{2+3+3.33} = 0.600 \text{ A}$$

And hence current through 5Ω resistor is:

$$I_S = I_T \cdot \frac{10}{5+10} = 0.6 \times \frac{10}{15} = 0.4 \text{ A} \quad \downarrow$$

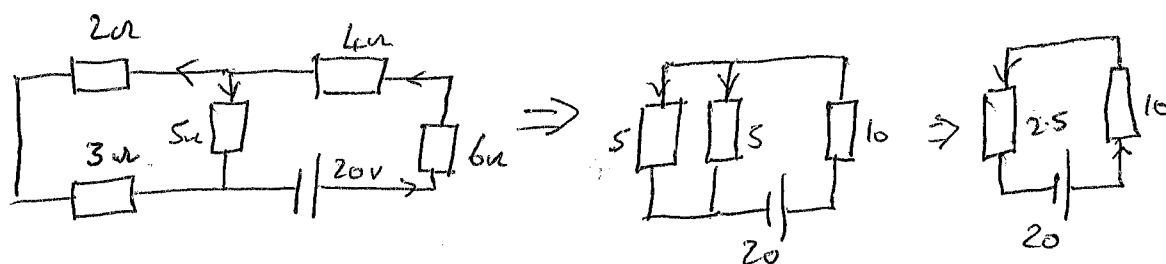Now Consider the 20V supply short the 5V supply:



$$I_{T'} = \frac{20}{12.5} = 1.6 \text{ A}$$

QUESTION 4 (CONTINUED)

11


Current through the 5Ω resistor:

$$I_{S'} = I_T' = \frac{5}{5+5} \times 1.6 = 0.8A \downarrow$$

By superposition the total current through the 5Ω resistor is:

$$I_{STOT} = 0.4A \downarrow + 0.8A \downarrow = \underline{\underline{1.2A \downarrow}}$$

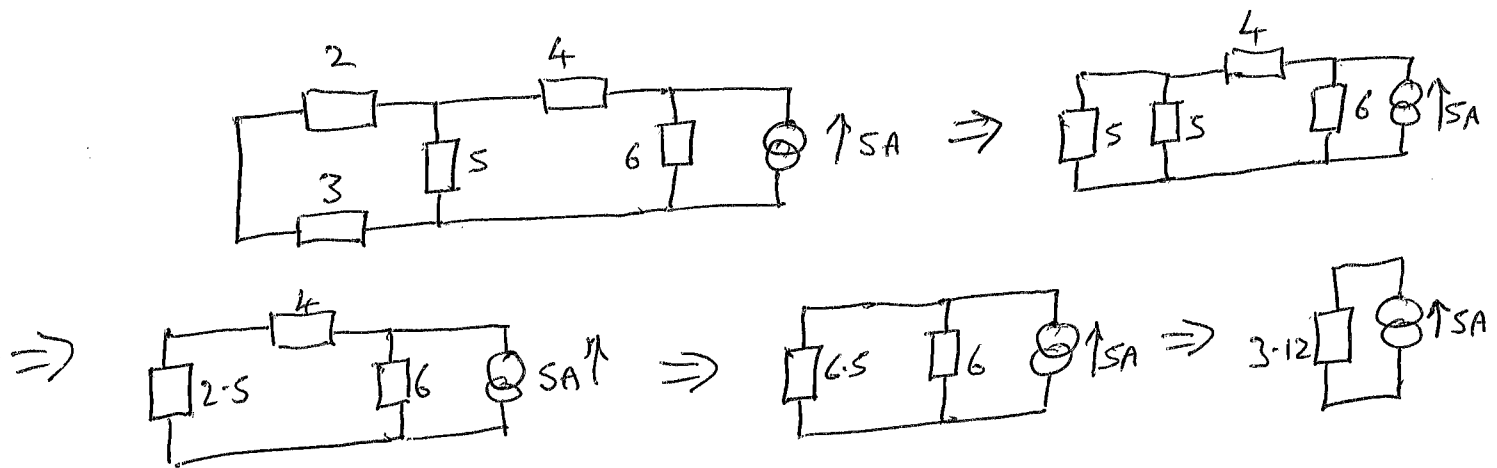(b) We can use the analysis of part (a) and now need to consider the effect of the $5A$ current source alone:



\therefore Voltage across $3.12\Omega = I \cdot R = 15.6V$. Hence current through the 6.5Ω resistor is $15.6/6.5 = 2.4A$. This is the same current flowing through the 2.5Ω . Hence the current flowing through the 5Ω resistor is half this $= 1.2A \downarrow$

By superposition the total current flowing through the 5Ω resistor is now:

$$I_{STOT} = 1.2A \downarrow + 1.2A \downarrow = \underline{\underline{2.4A \downarrow}}$$

(from (a))

QUESTION 4 (CONTINUED)

12

(c) For Thevenin we need the open-circuit voltage, i.e. the voltage across the 6Ω resistor:

Using the working from part (a).

For $5V$ source the current through the 6Ω resistor (load branch in network)


$$I_{61} = I_T \times \frac{5}{5+10} = 0.6 \times \frac{5}{15} = 0.2A \downarrow$$

For the $20V$ source the current through the 6Ω resistor is equal to $I_T = 1.6A \uparrow$.


\therefore Total current through the 6Ω resistor is $1.4A \uparrow$.

Hence the Thevenin voltage is $1.4 \times 6 = 8.4V \downarrow$

Resistance network is:

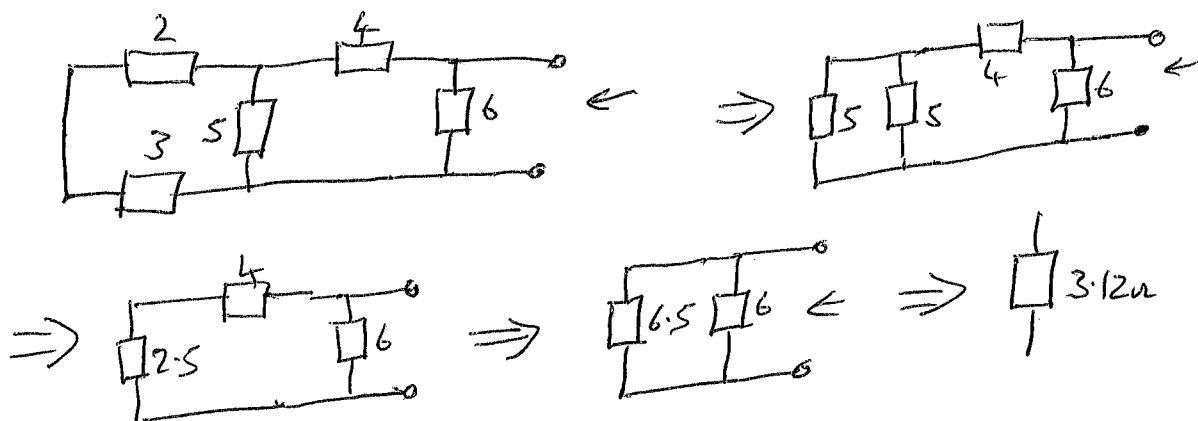

Hence Thevenin circuit is:

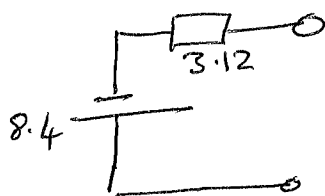

When load is connected $I = \frac{8.4}{(10+3.12)} = 0.64A \uparrow$

QUESTION 4 (CONTINUED)

13

Hence power in the load is $I^2 R_L = 0.64^2 \cdot 10 = \underline{\underline{4.096W}}$

(d) The Norton current can be found directly from the Thevenin current.

$$I_N = \frac{E_T}{R_T} = \frac{8.4}{3.12} = \underline{\underline{2.69A}}$$

Hence Norton current is:

