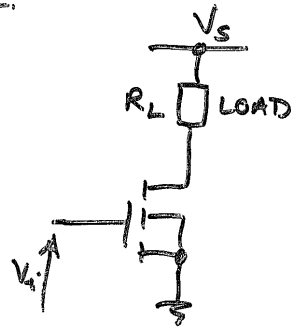


MOSFET SWITCHES

to switch device on
apply $> 10V$ to gate
with respect to source

[absolute maximum
 $V_{GS} = 20V$ for
most MOSFET
switches]



When "on" MOSFET behaves like
a resistor

- symbolically ... $r_{DS(on)}$
- specified by manufacturers.

On state equivalent
cct



usually $R_L \gg r_{DS(on)}$

$$I_{ON} \approx V_S / R_L$$

$$I_{ON} = \frac{V_S}{R_L + r_{DS(on)}}$$

perfectly acceptable

Power lost in switch during on


$$P_{sw} = I_{ON} r_{DS(on)}$$


Loads that contain inductance.

- any device that converts electrical to mechanical energy will contain inductance via magnetic fields.
- The inductance stores energy
- This causes problems for switches.


$$I_{ON} = \frac{V_S}{R}$$

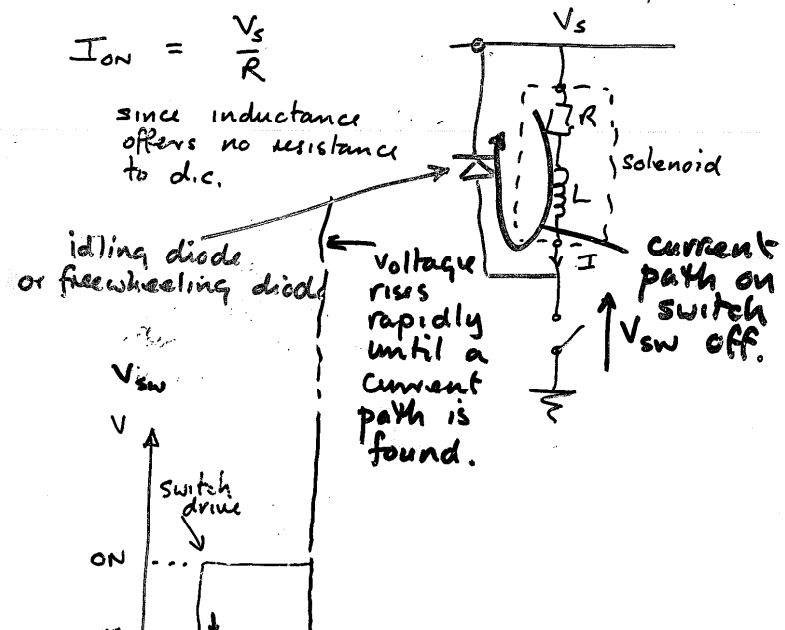since inductance
offers no resistance
to d.c.



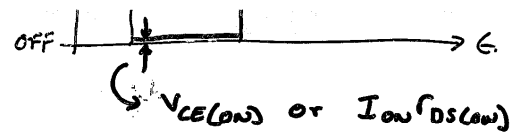

Getting energy out more quickly

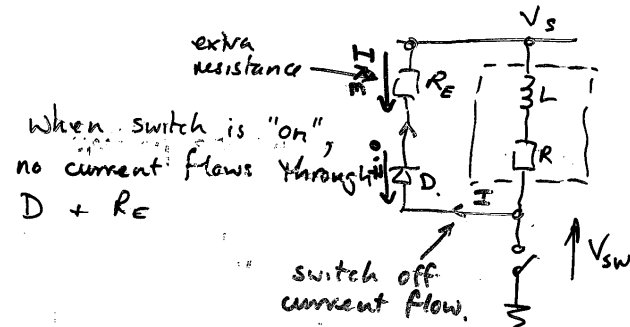


$$I_{ON} = \frac{V_s}{R} \text{ immediately before switch off}$$

so $I = \frac{V_s}{R}$ immediately after switching
because L tries to keep
the same current flowing.

$$V_{sw\ pl} = V_s + I R_E + 0.7$$

$$I = \frac{V_s}{R}$$

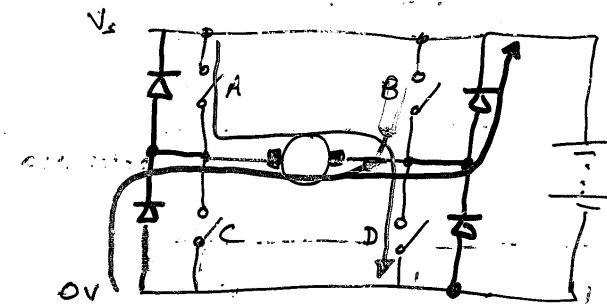
To drive electric motors ... H bridges
are used --



if $A + D$ on \rightarrow green current

if $A + D$ now switch off \rightarrow blue current.

Transistors as Amplifiers

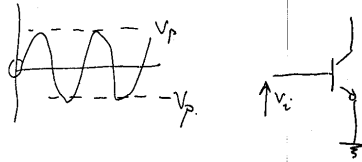


— All amplifying devices work by treating the signal as a small perturbation to a set of d.c. operating conditions — ie, a bias circuit must be designed that defines I_C (for a bipolar) or I_D (for a FET)

— I'll talk about BJT ccts

Bias problem is how to put a cct around the transistor that will control I_C

The objective of the bias cct is to control I_{BQ} .

Two sensible bias ccts...

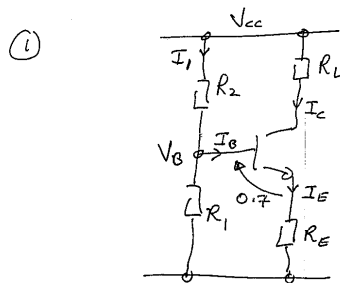

$R_1, R_2 + R_E$ are involved in control of I_C

Static Current gain = $\frac{I_C}{I_B}$
= large
 $\approx 200 - 300$


$$\begin{aligned} \text{So } I_E &= I_C + I_B \\ &\approx I_C \text{ since } I_C \gg I_B. \end{aligned}$$

$$I_1 \approx \frac{V_{CC}}{R_1 + R_2}$$

$$V_B = \frac{V_{CC} \cdot R_1}{R_1 + R_2} \quad (\text{assuming } I_B \text{ negligible})$$

$$V_B = 0.7 + I_E R_E \approx 0.7 + I_C R_E \quad (\text{since } I_C \approx I_E)$$

(2)
Assume I_B negligible

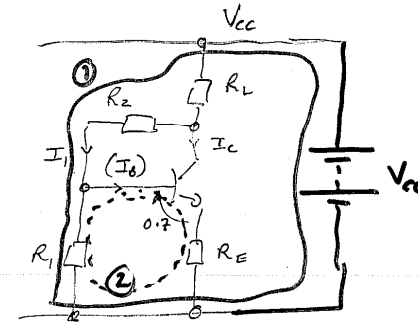

loop ①

$$I_1 R_1 + I_1 R_2 + (I_1 + I_C) R_L = V_{CC}$$


$$\text{or } I_1 (R_1 + R_2 + R_L) + I_C R_L = V_{CC}$$

loop ②


$$I_1 R_1 = 0.7 + I_C R_E \quad (\text{assumes } I_C \approx I_E)$$

Can't solve for I_1 yet



Getting Signals in + Out.

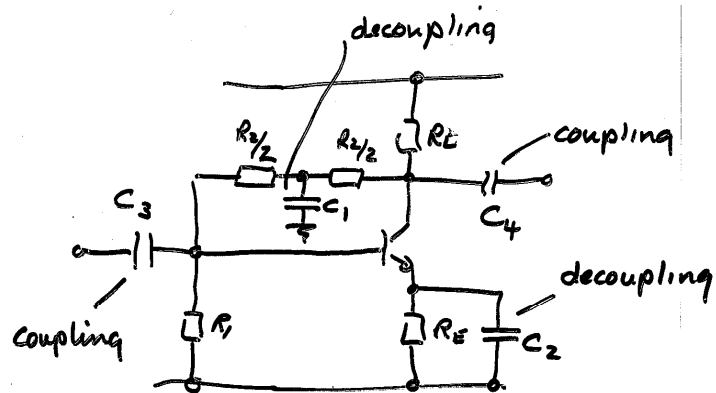


Small signal transistor model

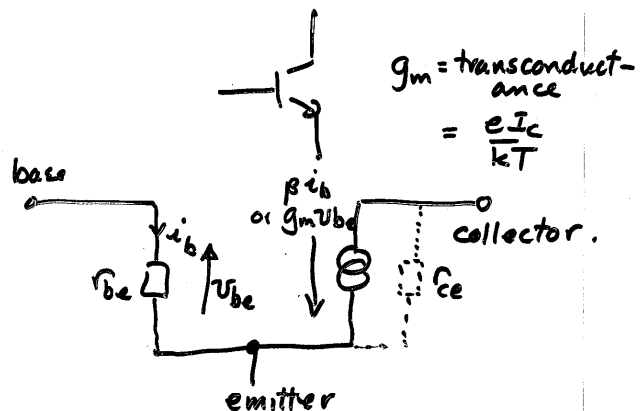

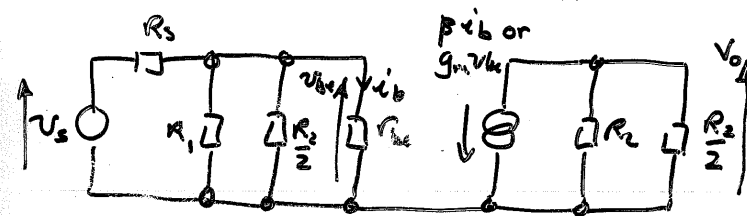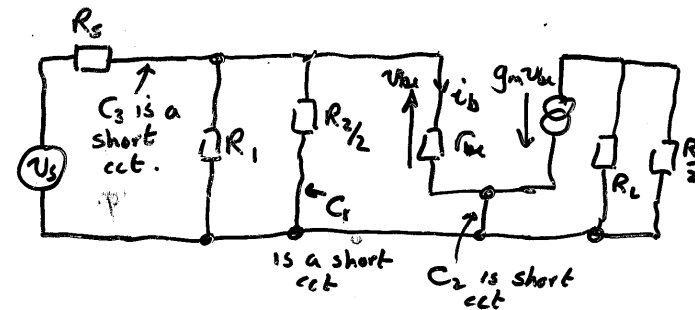Small signal version of whole cct
— put yourself in the position of
the signal



What is circuit gain?

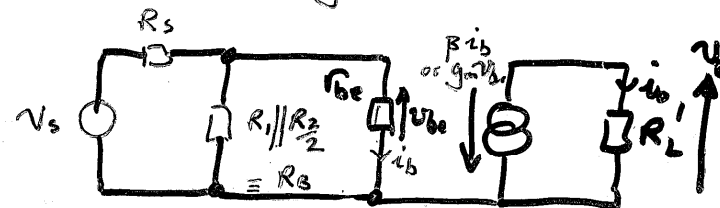

$$i_o R_L' = v_o \quad R_L' = R_L \parallel \frac{R_2}{2}$$

$$\text{and } i_o = -g_m v_{be}$$


$$\text{so } v_o = -g_m v_{be} R_L'$$

$$\text{For input ckt, } v_{be} = v_s \times \frac{r_{be} \parallel R_1 \parallel R_2}{R_s + r_{be} \parallel R_1 \parallel R_2}$$

$$\text{so } v_o = -g_m R_L' \cdot v_s \cdot \frac{r_{be} \parallel R_2}{R_s + r_{be} \parallel R_2}$$

$$\frac{v_o}{v_s} = -g_m R_L' \cdot \frac{r_{be} \parallel R_2}{R_s + r_{be} \parallel R_2}$$

means that if input is
output is

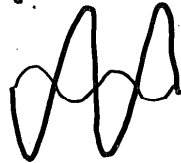


180° phase shift
between input +
output.

or signal shape is
inverted.

Operational Amplifiers

Two basic circuits.....

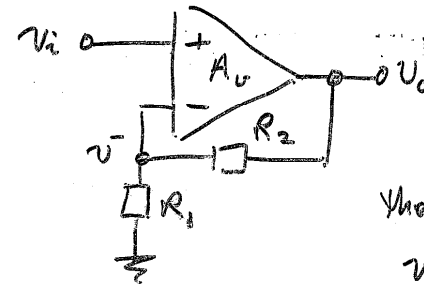

Let $A_v \Rightarrow \infty$

Then since $v_o = A_v(v^+ - v^-)$

$$v^+ - v^- = \frac{v_o}{A_v} \approx 0$$


since $A_v \approx \infty$

$$v^- = v_o \frac{R_1}{R_1 + R_2} \quad (\text{since negligible current flows into inverting input})$$

Since $v^+ \approx v^-$

$$v_i \approx v_o \frac{R_1}{R_1 + R_2} \quad \text{or} \quad \underline{\underline{\frac{v_o}{v_i} = \frac{R_1 + R_2}{R_1}}}$$

Inverting Amplifier

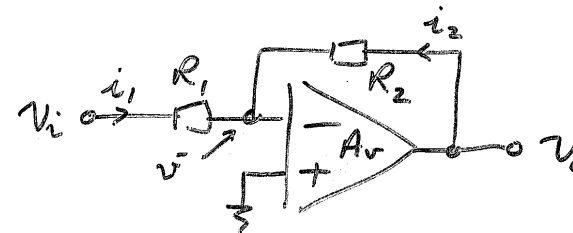

if $A_v \Rightarrow \infty$, $v^+ \approx v^-$

but $v^+ = 0$ so $v^- \approx 0$
 v^- often called a "virtual earth"

$$i_1 + i_2 = 0 \quad \text{since op-amp input current is negligible}$$

$$\downarrow \quad \downarrow$$

$$\frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} \quad \text{but } v^- \approx 0$$


$$\therefore \frac{v_i}{R_1} \approx -\frac{v_o}{R_2} \quad \text{so } \frac{v_o}{v_i} \approx -\frac{R_2}{R_1}$$

What about circuit input resistance?

- very high for non-inverting; governed by input resistance of op-amp itself. (and made even larger by the effects of the feedback.)
- quite low for inverting where v_{in} for the ckt = R_1 .

If one wants to explore the effects of a finite A_v , a slightly more involved approach is needed...

$v^+ \downarrow$

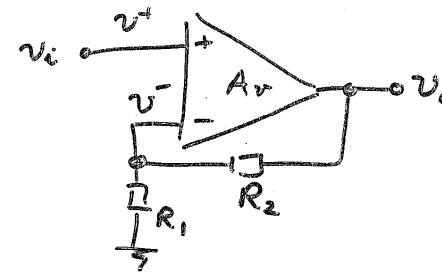

$$v^+ = v_i$$

$$v^- = v_o \frac{R_1}{R_1 + R_2}$$

now use op-amp equation

$$v_o = A_v (v^+ - v^-)$$

$$= A_v \left(v_i - \frac{v_o R_1}{R_1 + R_2} \right)$$


$$\frac{v_o}{A_v} + \frac{v_o R_1}{R_1 + R_2} = v_i$$

$$\frac{v_o}{v_i} = \frac{1}{\frac{1}{A_v} + \frac{R_1}{R_1 + R_2}}$$


— Always use ideal approximation for initial design

Op-amps with multiple inputs

$$v_i \frac{R_1}{1}$$

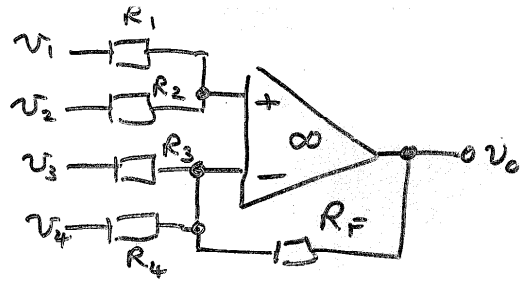

(1) using superposition

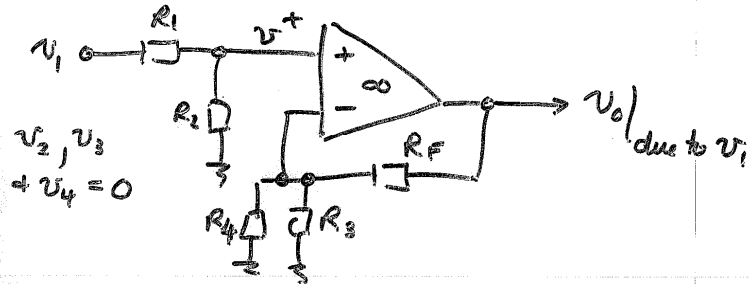

$$v_0|_{v_1} = v^+ \cdot \frac{R_F + R_3 || R_4}{R_3 || R_4}$$


$$\text{and } v^+ = v_1 \frac{R_2}{R_1 + R_2}$$

$$v_0|_{v_1} = v_1 \frac{R_2}{R_1 + R_2} \cdot \frac{R_F + R_3 || R_4}{R_3 || R_4}$$

$v_0|_{\text{due to } v_2}$ is very similar to $v_0|_{v_1}$

$v_0|_{\text{due to } v_2}$ is very similar to $v_0|_{v_1}$ since only $R_1 + R_2$ are changed

$$v_0|_{v_2} = v_2 \frac{R_1}{R_1 + R_2} \cdot \frac{R_F + R_3 || R_4}{R_3 || R_4}$$

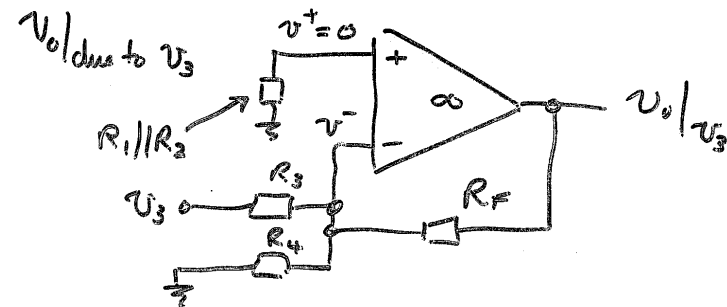

$$v_0|_{\text{due to } v_3} = v_3 \left(-\frac{R_F}{R_3} \right)$$

(R_4 plays no part because $v^+ = 0$ so $v^- = 0$ so 0V across R_4 at all times)

$$v_0|_{\text{due to } v_4} = v_4 \left(-\frac{R_F}{R_4} \right) \text{ using a similar argument.}$$

$$v_{0T} = v_0|_{v_1} + v_0|_{v_2} + v_0|_{v_3} + v_0|_{v_4}$$