

## EEE331 Analogue Electronics


### 2<sup>nd</sup> lecture:

- Miller transformation
- single transistor circuit elements:
  - common emitter
  - common base
  - emitter follower

## EEE331 Analogue Electronics

### Miller transformation: definition

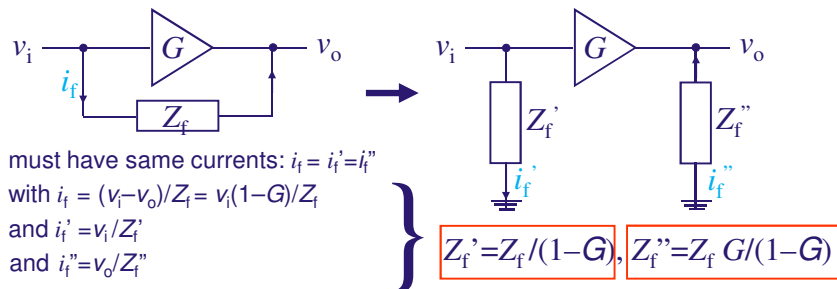
- problem: amplifier circuits with feedback elements are quite difficult to solve
- solution: **convert feedback circuit into separate input and output circuits** that are easier to solve & give better understanding of high-frequency behaviour
- example: amplifier with **gain  $G = v_o/v_i$**  and **feedback impedance  $Z_f = (v_i - v_o)/i_f$** :



## EEE331 Analogue Electronics

### Miller transformation: example

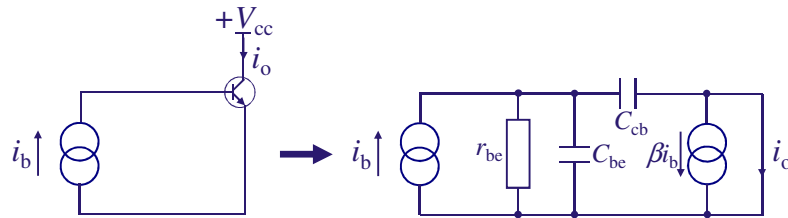- problem: small signal frequency response of BJT




- use hybrid  $\pi$  model (sometimes also called Giaccolleto model)
- driven by an ideal current source, hence  $r_{bb}=0$  has no effect
- load impedance on collector is zero, hence  $r_{cb}$  and  $r_{ce}$  can be omitted
- without load, any voltage change at input will cause no change in output voltage, hence  **$G=0$  without load**

## EEE331 Analogue Electronics

### Miller transformation: example

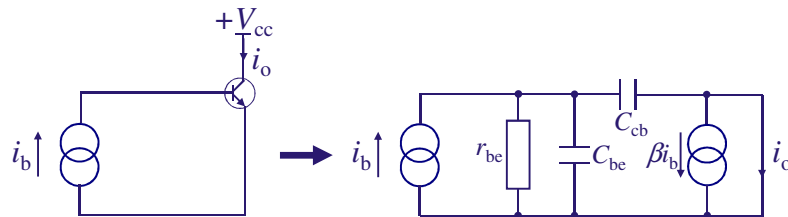- problem: small signal frequency response of BJT




- identify feedback elements between input and output:  $C_{cb}$
- remember: we derived **Miller transformation for impedance  $Z$** , hence for a capacitor this means we have to use  $1/(j\omega C)$ , which e.g. on the input side becomes  $1/[j\omega C(1-G)]$ .
- so, for input side:  $C_{cb}' = C_{cb}(1-G)$
- and for output side:  $C_{cb}'' = C_{cb}(G-1)/G$

## EEE331 Analogue Electronics

### Miller transformation: example

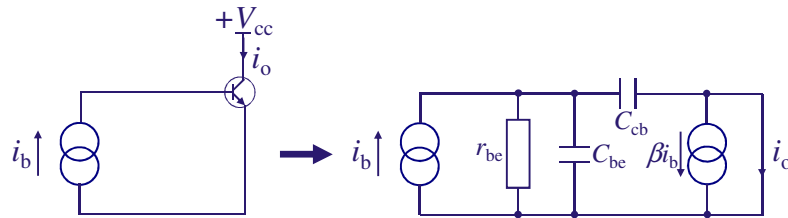
- problem: small signal frequency response of BJT



distinguish between 2 cases:

without load ( $G=0$ ) or with load ( $|G| \gg 1$ )

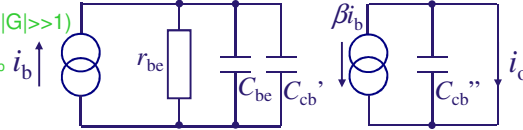- at input:  $C_{cb}' = C_{cb}$   $C_{cb}' \approx -GC_{cb}$
- at output:  $C_{cb}'' = \infty$   $C_{cb}'' \approx C_{cb}$



## EEE331 Analogue Electronics

### Miller transformation: explains small-signal frequency response of BJT

- for low frequencies  $f \approx 0$ , the base current flows as  $i_{br}$  ( $i_{bx}=0$ ), hence we have  $\beta_0 = \beta(f=0) = -i_o(0)/i_b(0) = -i_o/i_{br}$
- for high frequencies:

consider voltage across parallel combination of resistor and capacitors:

$$i_{br}r_{be} = v_{be} = i_{bx}Z_{cap} = i_{bx}/[j\omega(C_{be} + C_{cb})]$$

use Kirchhoff's Law for currents:


$$i_b = i_{br} + i_{bx} = i_{br} [1 + r_{be}j\omega(C_{be} + C_{cb})], \text{ thus}$$

get frequency-dependent gain

$$\beta(f) = -i_o(f)/i_b(f) = \frac{-i_o/i_{br}}{[1 + j\omega r_{be}(C_{be} + C_{cb})]}$$

with transition frequency  $\omega_{cut-off}$
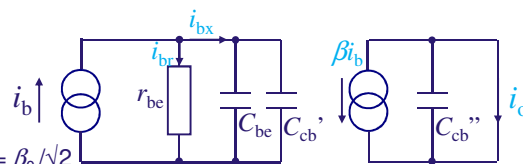
$$f_t = \frac{\beta_0/\omega_{cut-off}}{2\pi} \text{ so that } \beta(f_t) = \beta_0/\sqrt{2}$$



## EEE331 Analogue Electronics

### Miller transformation: explains small-signal frequency response of BJT

- for low frequencies  $f \approx 0$ , the base current flows as  $i_{br}$  ( $i_{bx}=0$ ), hence we have

$$\beta_0 = \beta(f=0) = -i_o(0)/i_b(0) = -i_o/i_{br}$$

- for high frequencies:

consider voltage across parallel combination of resistor and capacitors:

$$i_{br}r_{be} = v_{be} = i_{bx}Z_{cap} = i_{bx}/[j\omega(C_{be}+C_{cb})]$$

use Kirchhoff's Law for currents:


$$i_b = i_{br} + i_{bx} = i_{br}[1 + r_{be}j\omega(C_{be}+C_{cb})], \text{ thus}$$

get frequency-dependent gain

$$\beta(f) = -i_o(f)/i_b(f) = \frac{-i_o/i_{br}}{[1 + j\omega r_{be}(C_{be}+C_{cb})]}$$

with **transition frequency**  $\omega_{cut-off}$

$$f_t = \frac{|\beta_0|\omega_{cut-off}}{2\pi} \text{ so that } |\beta(f_t)| = 1/\sqrt{2} \approx 1$$

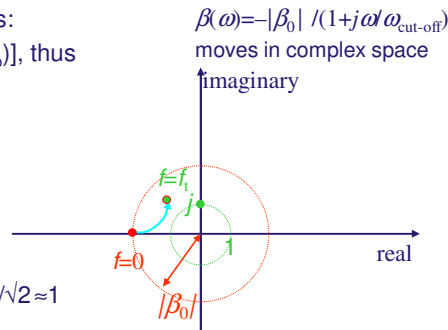


## EEE331 Analogue Electronics


### Single transistor circuits: common emitter, common base, emitter follower

#### 1. common emitter (BJT)


#### [common source (MOSFET)]

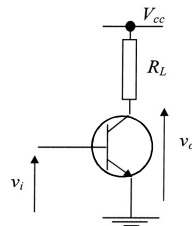

Common emitter

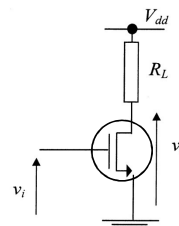

Common source

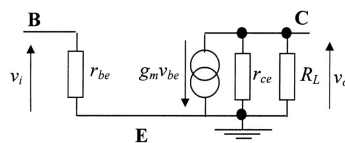


general method to determine input (output) impedance  $r_i$  ( $r_o$ ):

- draw small signal circuit for  $r_{bb} \rightarrow 0$ ,  $r_{cb} \rightarrow \infty$
- shorten other side to ground
- apply voltage or current to input (output)
- calculate resulting current or voltage

## EEE331 Analogue Electronics

### 1. common emitter (BJT)

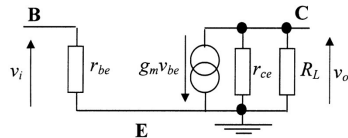

basic impedances here:

$$r_i = r_{be}$$

$$r_o = [1/r_{ce} + 1/R_L]^{-1} = r_{ce} R_L / (r_{ce} + R_L) \text{ (in parallel)}$$

$$\approx R_L \text{ for small load resistor } R_L$$

(not for current source!)

**calculation of voltage gain:**

consider output voltage:

voltage gain:

$$v_o = -g_m v_{be} r_{ce} R_L / (r_{ce} + R_L), \text{ thus}$$

$$v_o / v_i = v_o / v_{be} = -g_m r_{ce} R_L / (r_{ce} + R_L) \approx -g_m R_L$$

for small loads  $R_L$ , i.e. the voltage gain is high and controlled by the load  $R_L$ . This is relevant for voltage gain stages in OpAmps.

**common source (MOSFET)**


$r_i \rightarrow \infty$  (gate capacitance is open circuit at dc)  
High input resistance makes MOSFET particularly attractive as input stages of OpAmps!

$$r_o = r_{ds} R_L / (r_{ds} + R_L) \approx R_L \text{ (as above)}$$

## EEE331 Analogue Electronics
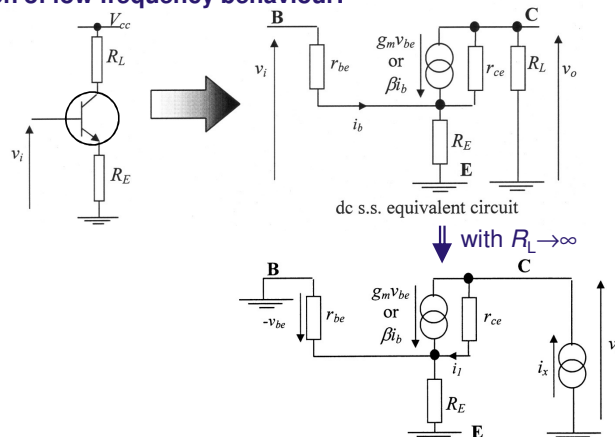
### 1. common emitter (BJT)

**emitter degeneration:** additional impedance between emitter and ground  
**calculation of low frequency behaviour:**



## EEE331 Analogue Electronics

### 1. common emitter (BJT)

**emitter degeneration:** additional impedance between emitter and ground

**calculation of low frequency impedance:**

consider current:  $i_1 = i_x - g_m v_{be}$  with voltage  $-v_{be} = i_x r_{be} R_E / (r_{be} + R_E)$   
 $= i_x + g_m i_x r_{be} R_E / (r_{be} + R_E)$

output voltage:  $v_x = -v_{be} + i_1 r_{ce}$   
 $= i_x r_{be} R_E / (r_{be} + R_E) + [i_x + g_m i_x r_{be} R_E / (r_{be} + R_E)] r_{ce}$   
 $= i_x \{ r_{be} R_E / (r_{be} + R_E) + r_{ce} [1 + g_m r_{be} R_E / (r_{be} + R_E)] \}$


**impedance:**  $v_x / i_x = r_{be} R_E / (r_{be} + R_E) + r_{ce} [1 + g_m r_{be} R_E / (r_{be} + R_E)]$

$\approx r_{ce} [1 + g_m r_{be} R_E / (r_{be} + R_E)]$  (for large  $g_m$ )

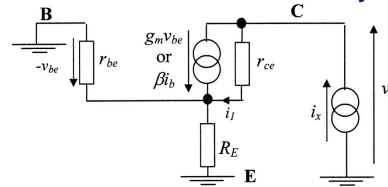**output impedance has increased drastically!**

note:

voltage across  $R_E$  limits  $v_{be}$ ,  
hence also  $i_b$  and  $i_c$ : emitter  
degenerated circuits are  
important for design of high  
impedance loads!



## EEE331 Analogue Electronics

### 1. common emitter (BJT)

**emitter degeneration:** additional impedance between emitter and ground

**calculation of low frequency transconductance:**


input voltage:  $v_i = i_b r_{be} + (i_b + \beta i_b) R_E$  with  $r_{be} = v_{be} / i_b = g_m v_{be} / g_m i_b = \beta / g_m$   
 $= i_c [1 / g_m + R_E (1 + 1 / \beta)]$

**transconductance:**

$i_c / v_i = 1 / [1 / g_m + R_E (1 + 1 / \beta)]$

$\approx g_m / (1 + g_m R_E)$  (since  $\beta \gg 1$ )

**transconductance  $dI_c / dV_{be} |_{V_{ce}=\text{const.}}$  is reduced by a factor  $(1 + g_m R_E)$ , i.e. for the CE circuit with  $R_E$  it is lower than for the BJT alone**

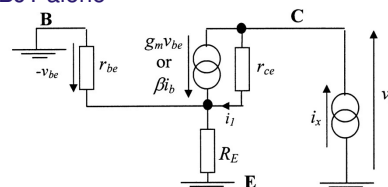

## EEE331 Analogue Electronics

### *note for common source (MOSFET):*


*source degeneration is less common than emitter generation because*

- $g_m$  is low anyway, and further reduction is undesirable
- rising input impedance would be pointless as  $R_i \rightarrow \infty$  anyway
- rising output impedance generally is beneficial for creating high impedance load but adverse if we are trying to build an output stage (which would require a low output impedance).

## EEE331 Analogue Electronics

### 1. common emitter (BJT)
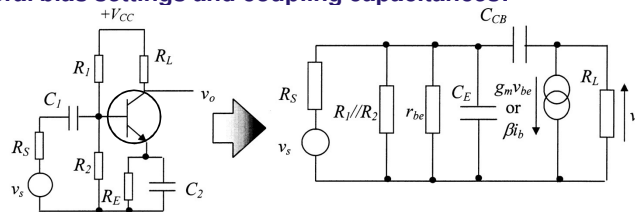
#### general bias settings and coupling capacitances:




- resistors  $R_1$ ,  $R_2$  and  $R_E$  define bias conditions of the BJT
- $R_1$  and  $R_2$  are connected to a constant voltage and so, from a small signal point of view, appear to be in parallel
- $r_{be} \ll R_S$  (in series) and  $r_{ce} \gg R_L$  (in parallel) can both be ignored
- capacitor  $C_1$  is a bypass capacitor that transmits the time-varying  $v_s$  to the base of the BJT without disturbing the dc bias conditions
- capacitor  $C_2$  is another bypass capacitor; it effectively compensates the negative feedback provided by  $R_E$ , thereby increasing gain
- at high frequencies,  $C_{CB}$  and  $C_E$  cannot be ignored.
- with voltage gain  $G = v_o/v_{be}$ ,  $C_{CB}$  becomes the target for the Miller transformation

## EEE331 Analogue Electronics
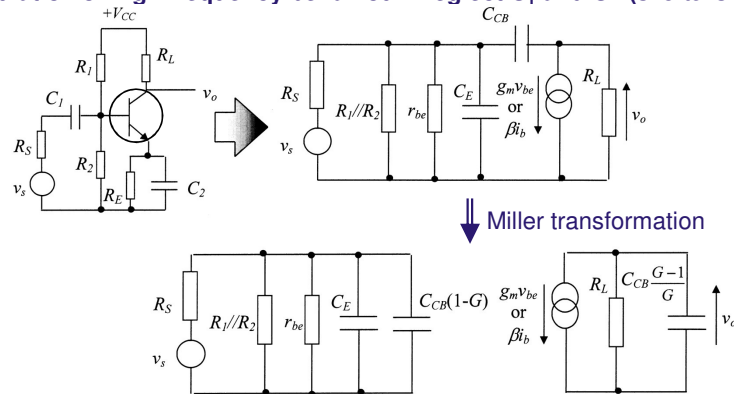
### 1. common emitter (BJT)

calculation of high frequency behaviour: neglect  $C_1$  and  $C_2$  (shortens  $R_E$ )



problem: circuit is 2<sup>nd</sup> order, with poles both on input and on output side:  
which limits the high frequency behaviour?

## EEE331 Analogue Electronics

### 1. common emitter (BJT)

calculation of high frequency behaviour:

assumption: input circuit is frequency limiting, i.e.  $f_i \ll f_o$  assumed

then:  $C_{CB} (G-1)/G$  negligible


output voltage:  $v_o \approx -g_m v_{be} R_L$

high- $f$  voltage gain:  $G_m = v_o/v_{be} = -g_m R_L$  is large and negative

corner frequencies:  $f_i = [2\pi (R_S // R_1 // R_2 // r_{be}) (C_E + C_{CB} (1-G))]^{-1}$

$f_o = [2\pi R_L C_{CB} (G-1)/G]^{-1}$

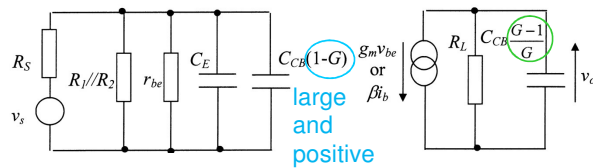where  $//$  means parallel connection and  $\omega = 1/R_{eff} C_{eff}$   
close to 1



NBs: impedance of capacitor is  $Z_c = 1/(j\omega C)$ , hence  $\omega = 1/RC$  and  $f = 1/(2\pi RC)$   
Always check assumption that  $f_i \ll f_o$  after calculation!



## EEE331 Analogue Electronics

### 1. common emitter (BJT)

#### calculation of mid frequency behaviour:

assumption:  $C_1$  and  $C_2$  are still short circuits, but  $C_{CB}$  and  $C_E$  open

then:  $C_{CB} (G-1)/G$  negligible

output voltage:  $v_o \approx -g_m v_{be} R_L$

mid- $f$  voltage gain:  $G_{mf} = v_o/v_i = -g_m R_L (R_1 // R_2 // r_{be}) / (R_S + R_1 // R_2 // r_{be})$


NBs: Miller effect describes the apparent increase of  $C_{CB}$  by factor  $(1-G)$ , which reduces the corner frequency. **Dominant pole compensation** means that in practice extra capacitance is often added between base and collector of BJTs of multi-transistor amplifier stages such as OpAmps to separate the pole frequencies due to the different stages, thereby avoiding instabilities and ensuring stable operation.

## EEE331 Analogue Electronics

### 1. common emitter (BJT) / [common source (MOSFET)]
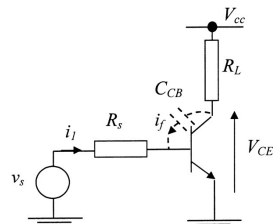
#### slew rate limiting:

For **large** input signals, the rate of change of  $V_{CE}$  is dominated by the availability of the base drive current. Consider  $I = dQ/dt = d(CV)/dt = C dV/dt$  [in analogy, for a power MOSFET the rate of change of drain voltage is governed by the availability of gate drive current].



consider BJT drive on process:

$v_s = 0$  for  $t < 0$ ,  $V_1$  for  $t \geq 0$

current to base for  $t \geq 0$ :  $I_1 = (V_1 - V_{BE})/R_S$

current to collector for  $t \geq 0$ :  $I_c = C_{CB} dV_{CE}/dt$

Rate of change at output is maximum when all the base current available is utilised by capacitor, i.e.  $I_t + I_B = 0$ , thus


$$\frac{dV_{CE}}{dt} \Big|_{\text{max-on}} = I_1 / C_{CB} = -I_B / C_{CB} = -(V_1 - V_{BE}) / (R_S C_{CB}) \text{ lags behind}$$

and correspondingly

$$\frac{dV_{CE}}{dt} \Big|_{\text{max-off}} = V_{BE} / (R_S C_{CB}) \text{ leads}$$

## EEE331 Analogue Electronics

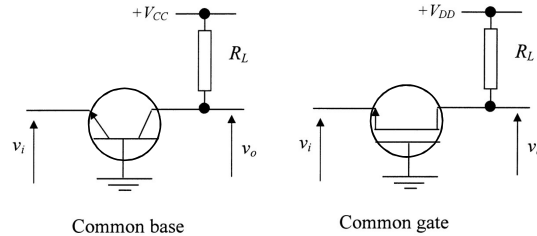
### 2. common base (BJT) / [common gate (MOSFET)]



voltage gain:  $G = g_m R_L$   
 current gain:  $i_o/i_i = 1/(1+1/G)$  (i.e.  $<1$ : **no current gain**, as  $I_C \leq I_E$ )  
 advantages: 1.  $C_{CB}$  does not cause high frequency feedback: ideal for **fast switches** (no Miller effect as  $I_C \approx I_E$ )  
 2. for large  $R_L$ , output impedance is higher than in CE mode, i.e. use as current source  
 derivation: cf section 3.3.3 in Gray's textbook

## EEE331 Analogue Electronics
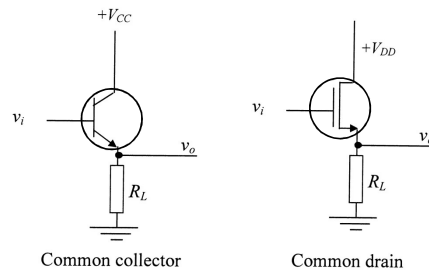
### 3. common collector = emitter follower (BJT) / [common drain (MOSFET)]



use Kirchoff's law at output node:  $(v_i - v_o)/r_{be} + \beta(v_i - v_o)/r_{be} - v_o/R_L = 0$ , thus  
 voltage gain:  $G = v_o/v_i = R_L(1+\beta)/[r_{be} + R_L(1+\beta)] = 1/[1 + r_{be}/(\beta+1)R_L] \approx g_m R_L/(1+g_m R_L) \cong 1$   
 Note: The gain is usually just less than unity, so the emitter follows the input voltage (hence the name emitter follower). These circuits have high input impedance and low output impedance and are useful for **buffers**.